



# Sardar Vallabhbhai National Institute of Technology, Surat

ECED Department

Subject: Digital Electronics & Logic Design (EC-207)  
B.Tech Computer, Sem-III, Div – (A&B)

Date: 15-09-2020

## Tutorial – 3 Hints/Solutions

1. Buffer Circuit. Hence  $V_o = V_i$  (Voltage at output of Opamp) = 6V. Then use voltage division to determine voltage across 4K resistor. Finally use any of the formulas ( $P = V^2/R$  or  $I^2 \cdot R$ ) to determine the required power across 4K. **Ans: 4 mW**
2. Ideal Opamp  $\rightarrow$  Voltage at  $V_+ =$  Voltage at  $V_-$ .  $V_s = 0$  makes voltage at  $V_{++} = 0$  volts. Apply KCL at inverting terminal or use the formula of inverting amplifier ( $V_o = -R_f/R_1 \cdot V_{in}$ ) to determine voltage at output node of opamp. The current then will be by ohms law,  $V_o/2K\Omega$ . **Ans: -10 mA**
3. Use the formula  $V_o = -R_f/R_1 \cdot V_{in}$  for all the three cases.
  - a. -2.4
  - b. -16
  - c. -400
4. Voltage division at input side gives  $v_1 = 4.5$  volts. Because of buffer configuration,  $v_2 = v_1 = 4.5$  volts. Once again employ voltage division at output to obtain the required answer. **Ans: 2.7 Volts.**
5.  $R_f = \infty$  makes 1<sup>st</sup> stage work as an inverting amplifier with a gain of -3. Voltage at output of 1<sup>st</sup> stage = -45 mV. 2<sup>nd</sup> stage is a non-inverting amplifier having a gain of  $(1 + R_f/R_1) = 4$ . **Ans: -180 mV**
6. Opamp as a Summer Configuration. Apply Equation and determine  $v_2$  value.  $V_o = -16.5 = [(-15/10 \cdot 2) + (-50/20 \cdot v_2) + (-50/50 \cdot -1)]$ . Solve for  $v_2$ . **Ans: 3 V**