



Expt. No:

7

Date:

24/09/2020**Diode Clipper Circuits (Shunt – Configuration)**

AIM: To study, design and plot the various shunt diode clipper circuits.

SOFTWARE TOOLS / OTHER REQUIREMENTS:

1. Multisim Simulator/Circuit Simulator

THEORY:


We know that when a diode is forward biased it allows current to pass through itself clamping the voltage across it to 0.7 volts (Practical Silicon Diode). While, when it is reverse biased, no current flows through it and the voltage across its terminals is unaffected, and this is the basic operation of the diode clipping circuit.


Clippers are networks that employ diodes to “clip” away a portion of an input signal without distorting the remaining part of the applied waveform.

There are two general categories of clippers: *Series* and *Parallel*. The series configuration is defined as the one where the diode is in series with the load, whereas the parallel variety has the diode in a branch parallel to the load.

SHUNT CONFIGURATIONS

SHUNT POSITIVE CLIPPER

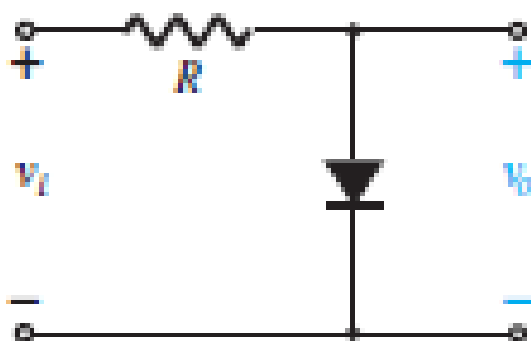

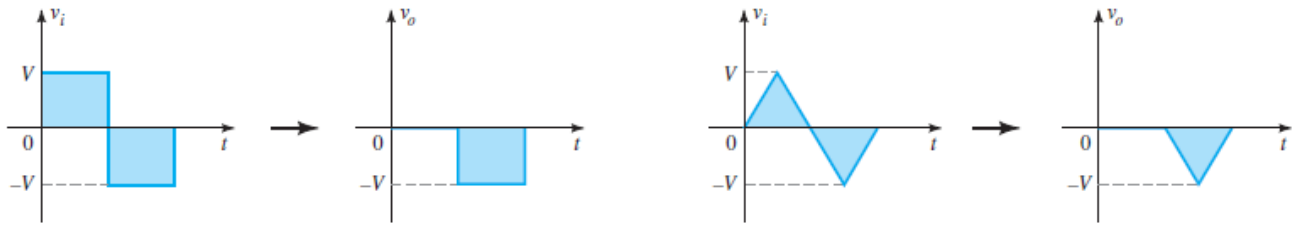


As shown above, when the positive half cycle appears, the diode being forward biased, acts as short circuit and thus the output voltage remains at zero level. During the negative half cycle, the diode is reverse biased, acts as open circuit and hence we see that the output node comes into direct contact with the input node, thereby the output follows the input. Since the positive cycle of the input is getting clipped-off, the configuration in the above circuit is known as shunt positive clipper.

Likewise if the polarity of the diode is reversed; we can clip-off the negative half of the input cycle. In this case, during the positive half cycle, the diode remains reverse biased thereby connecting the output node with input node and the output voltage follows the input. But when the negative half cycle appears, the diode gets forward biased creating a short across the output nodes resulting into a zero voltage at the output. The level will be 0.7 if a silicon diode is considered instead of an non-ideal diode.


FEW SHUNT DIODE CLIPPER CONFIGURATIONS

POSITIVE

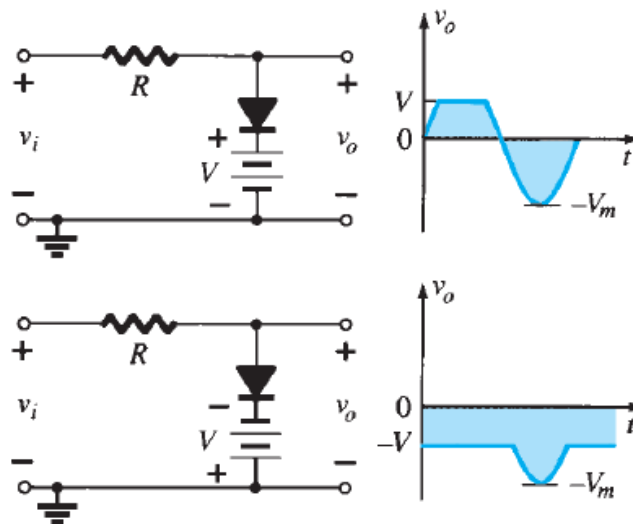




NEGATIVE

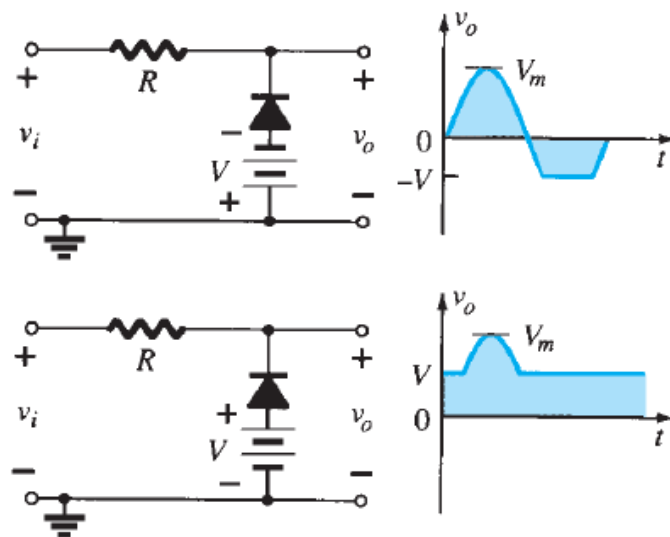

TWO LEVEL CLIPPERS

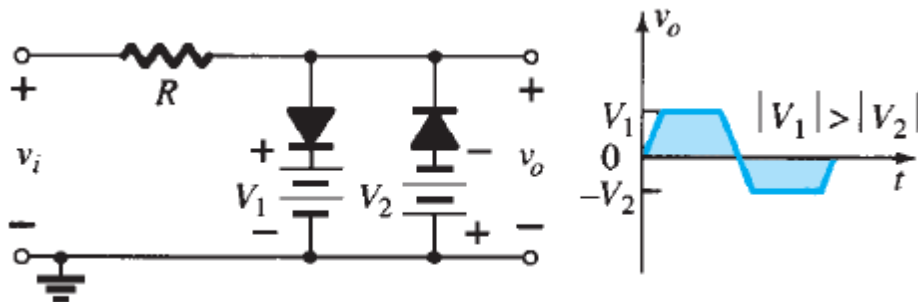
These circuits employ clipping in both the directions (Positive as well as Negative Half Cycles) as shown in figure below:






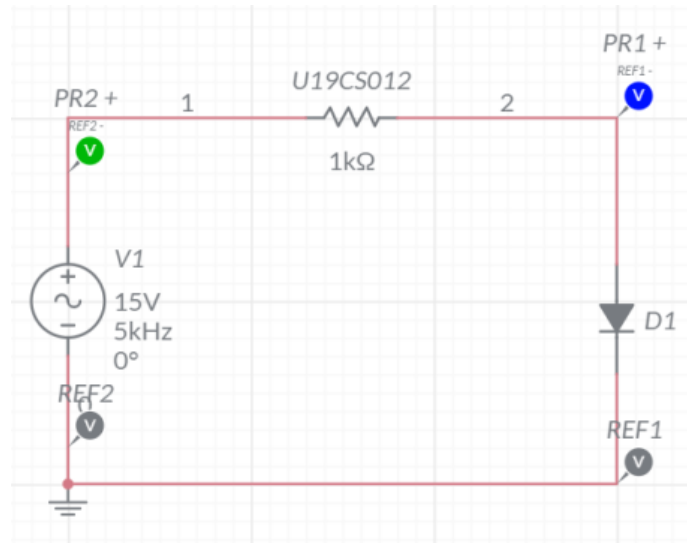1.) SHUNT POSITIVE CLIPPER

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)




WAVEFORMS (FROM MULTISIM)

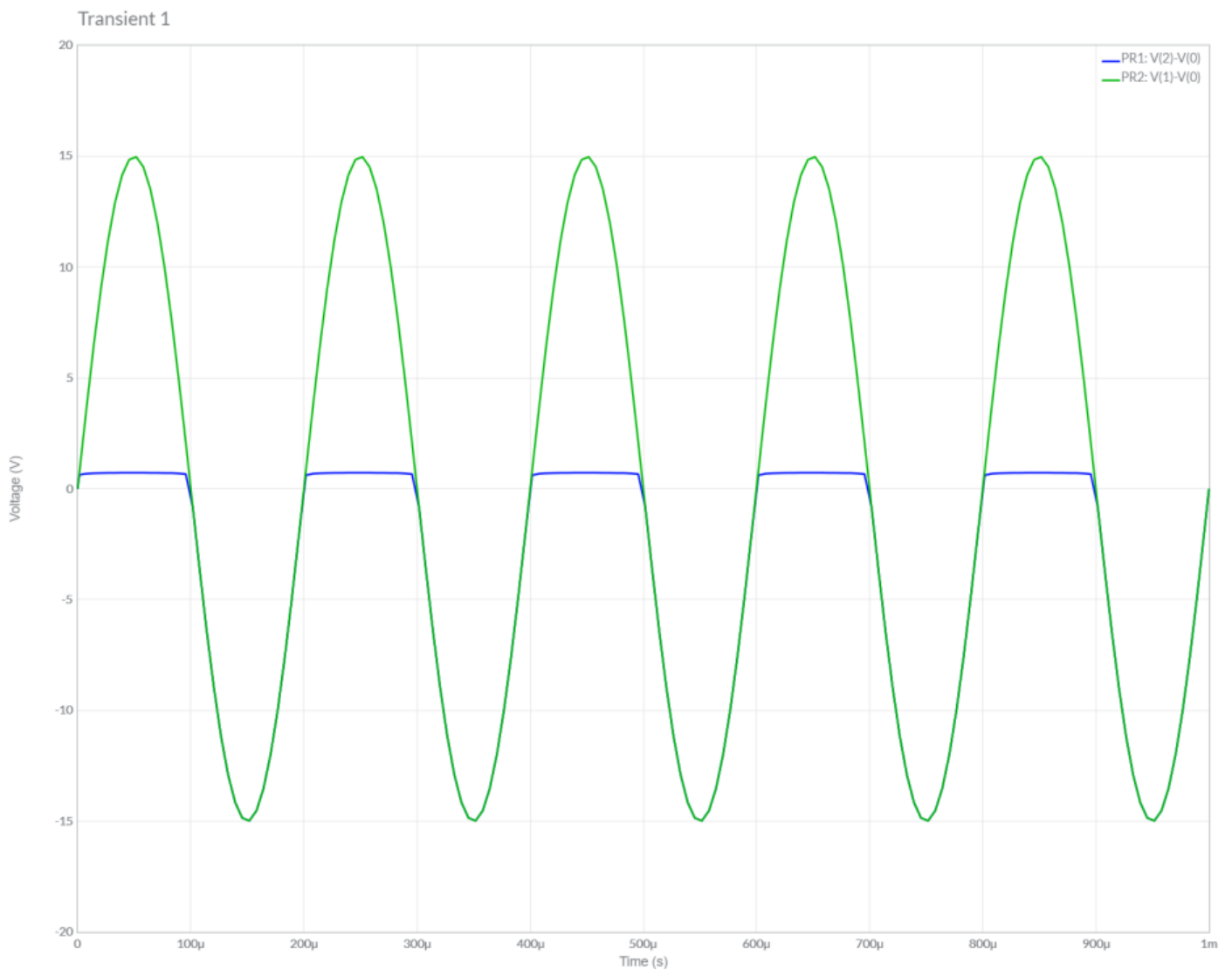




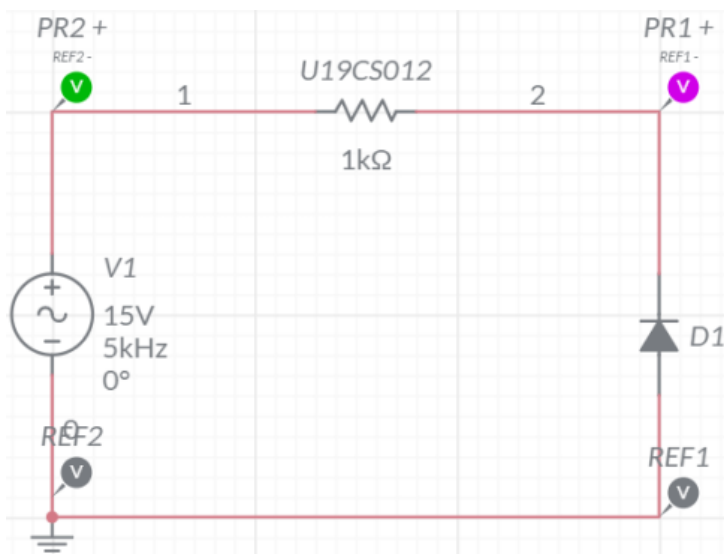2.) SHUNT NEGATIVE CLIPPER

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)




WAVEFORMS (FROM MULTISIM)

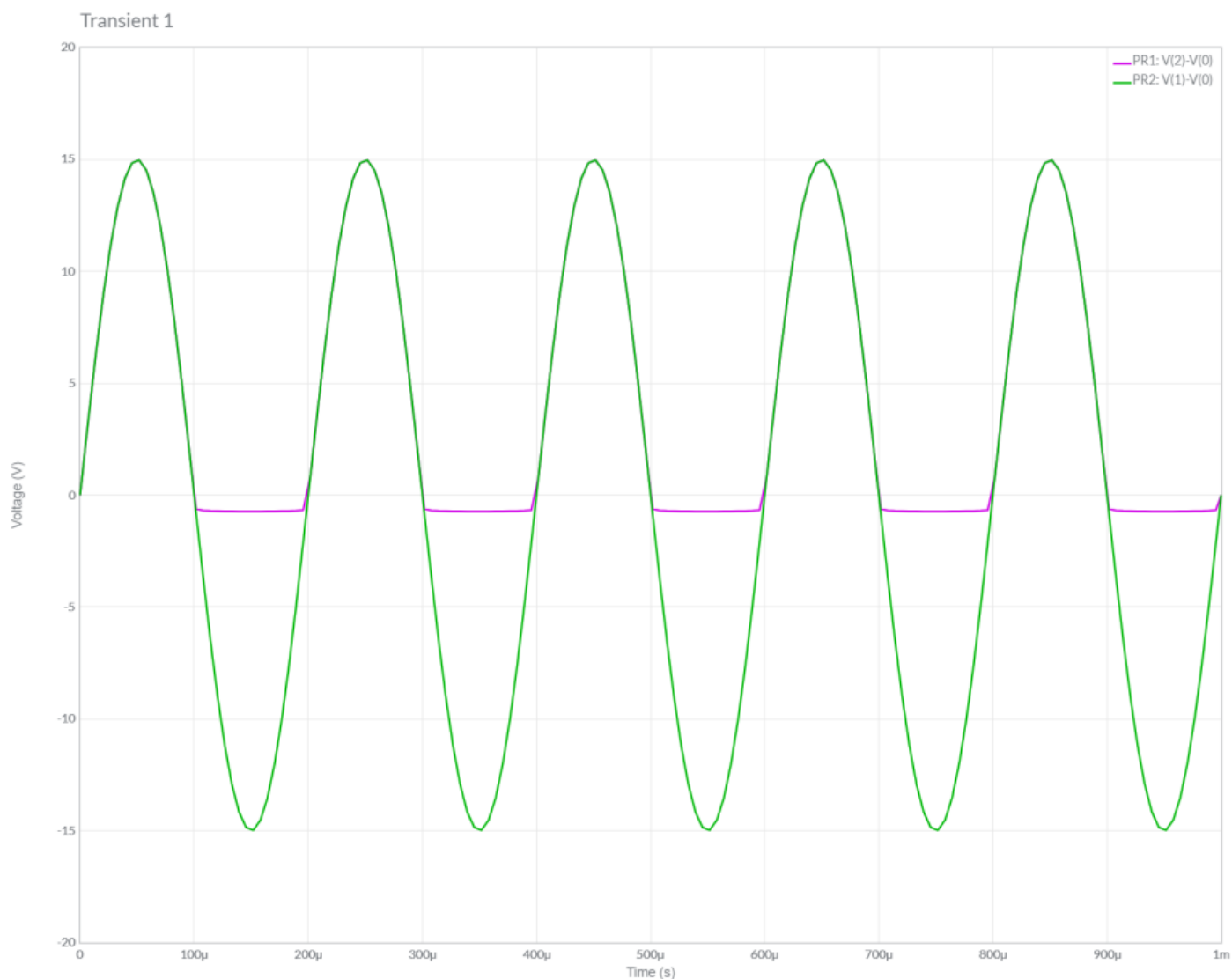




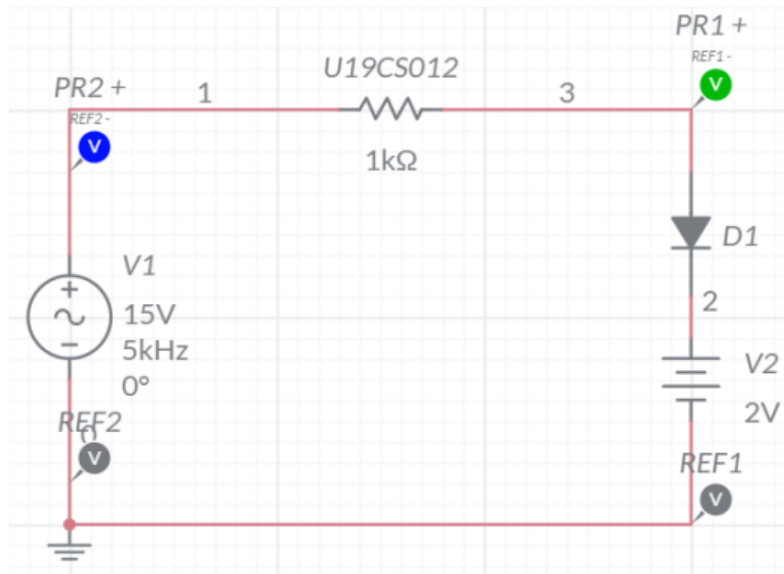3.) SHUNT POSITIVE CLIPPER WITH BIAS-I

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)




WAVEFORMS (FROM MULTISIM)

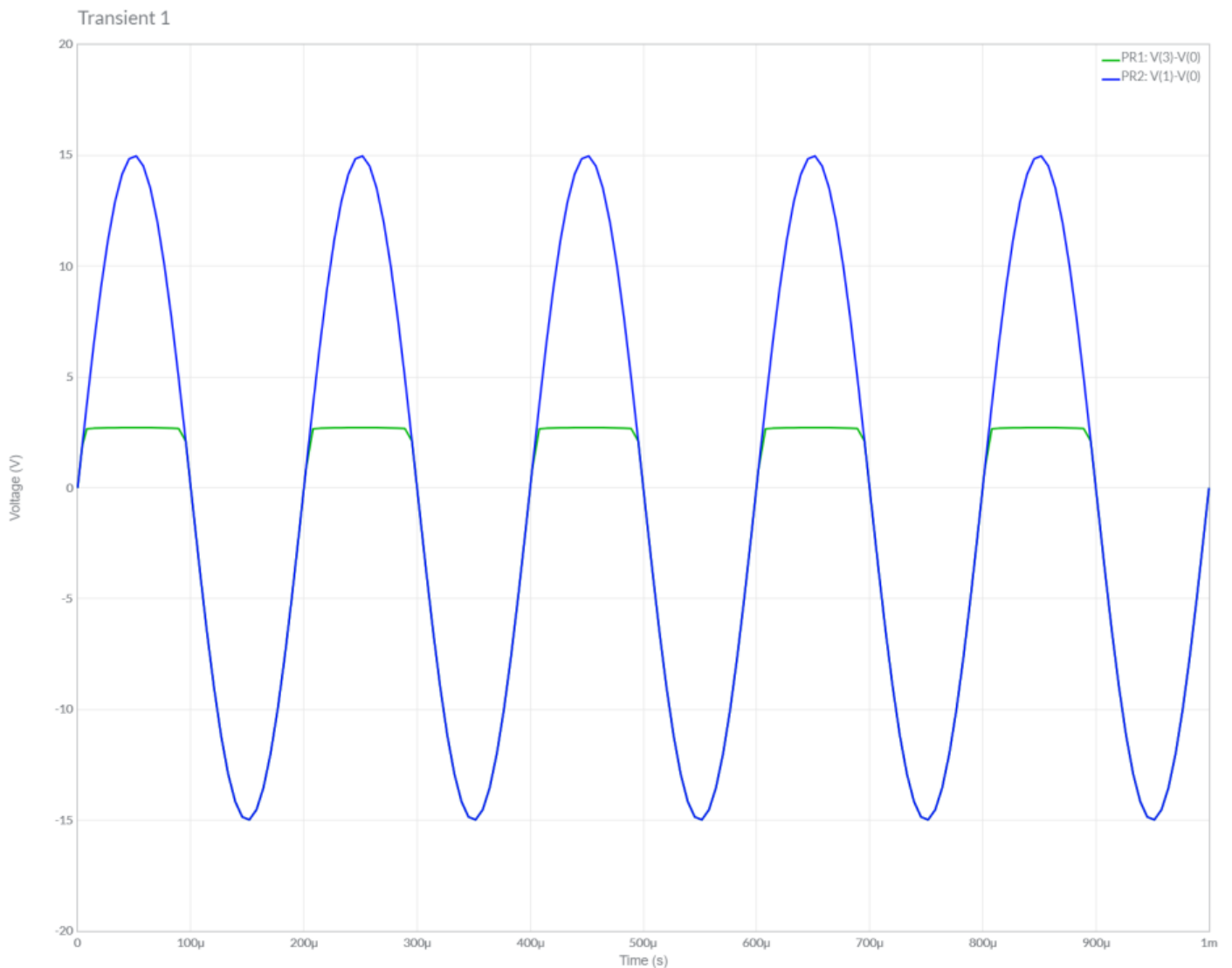




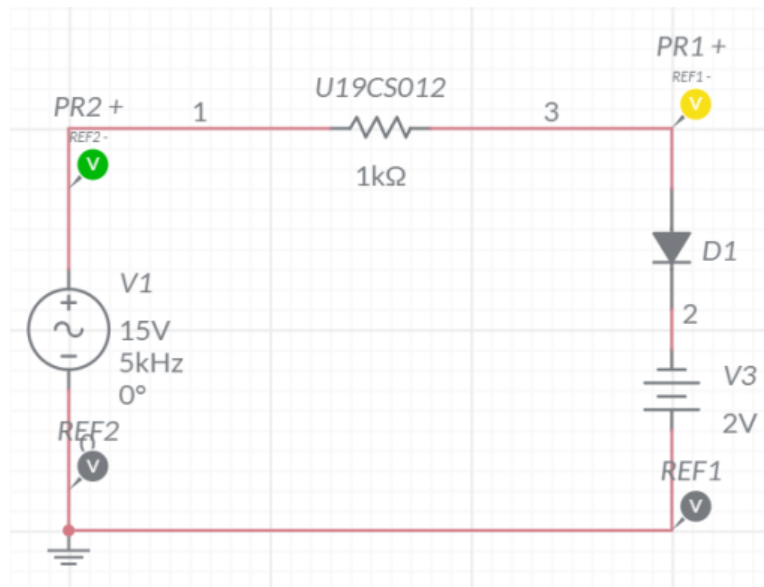4.) SHUNT POSITIVE CLIPPER WITH BIAS-II

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)




WAVEFORMS (FROM MULTISIM)

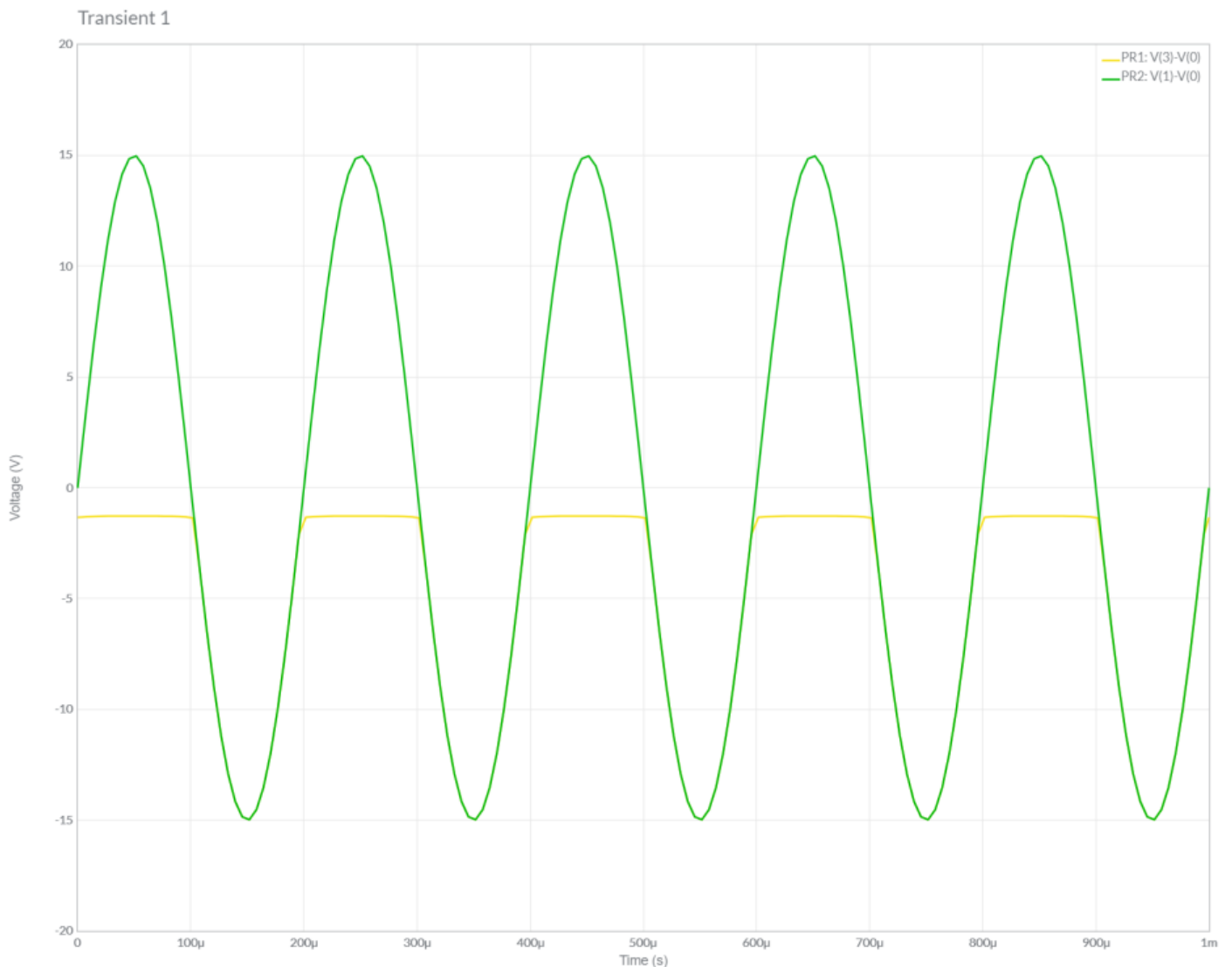




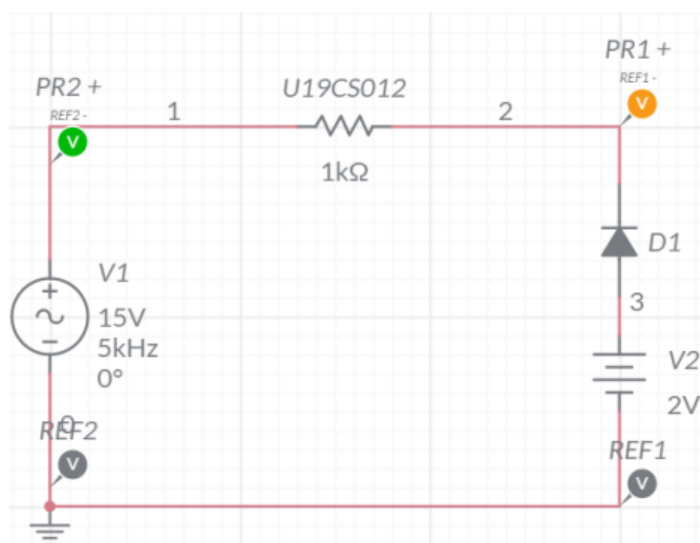5.) SHUNT NEGATIVE CLIPPER WITH BIAS-I

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)




WAVEFORMS (FROM MULTISIM)

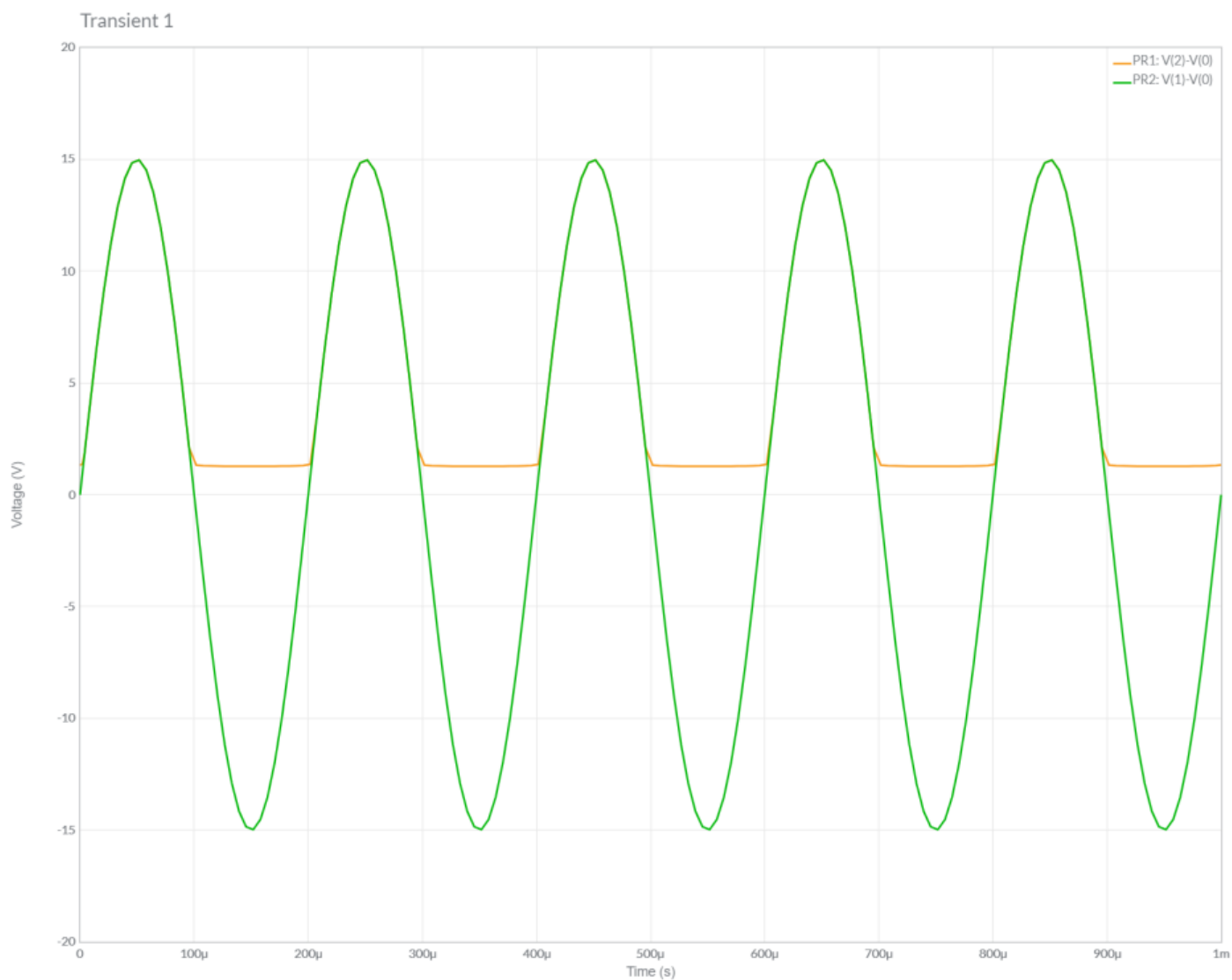




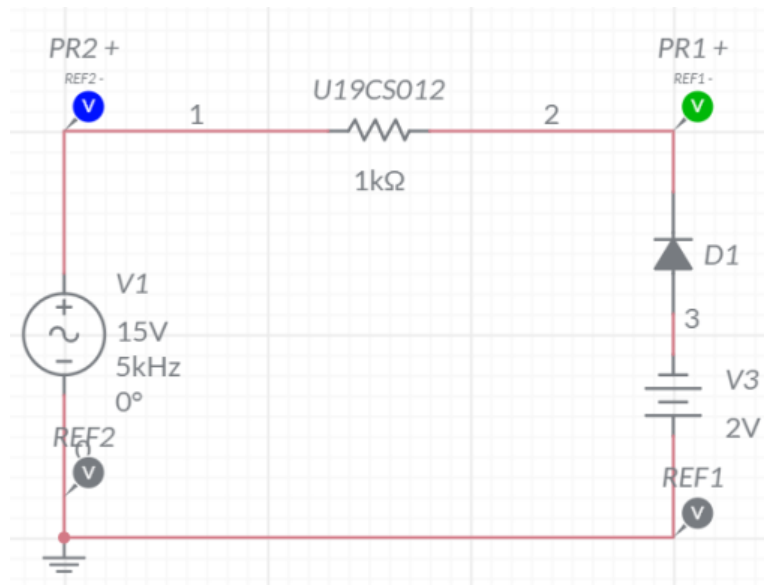6.) SHUNT NEGATIVE CLIPPER WITH BIAS-II

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)




WAVEFORMS (FROM MULTISIM)

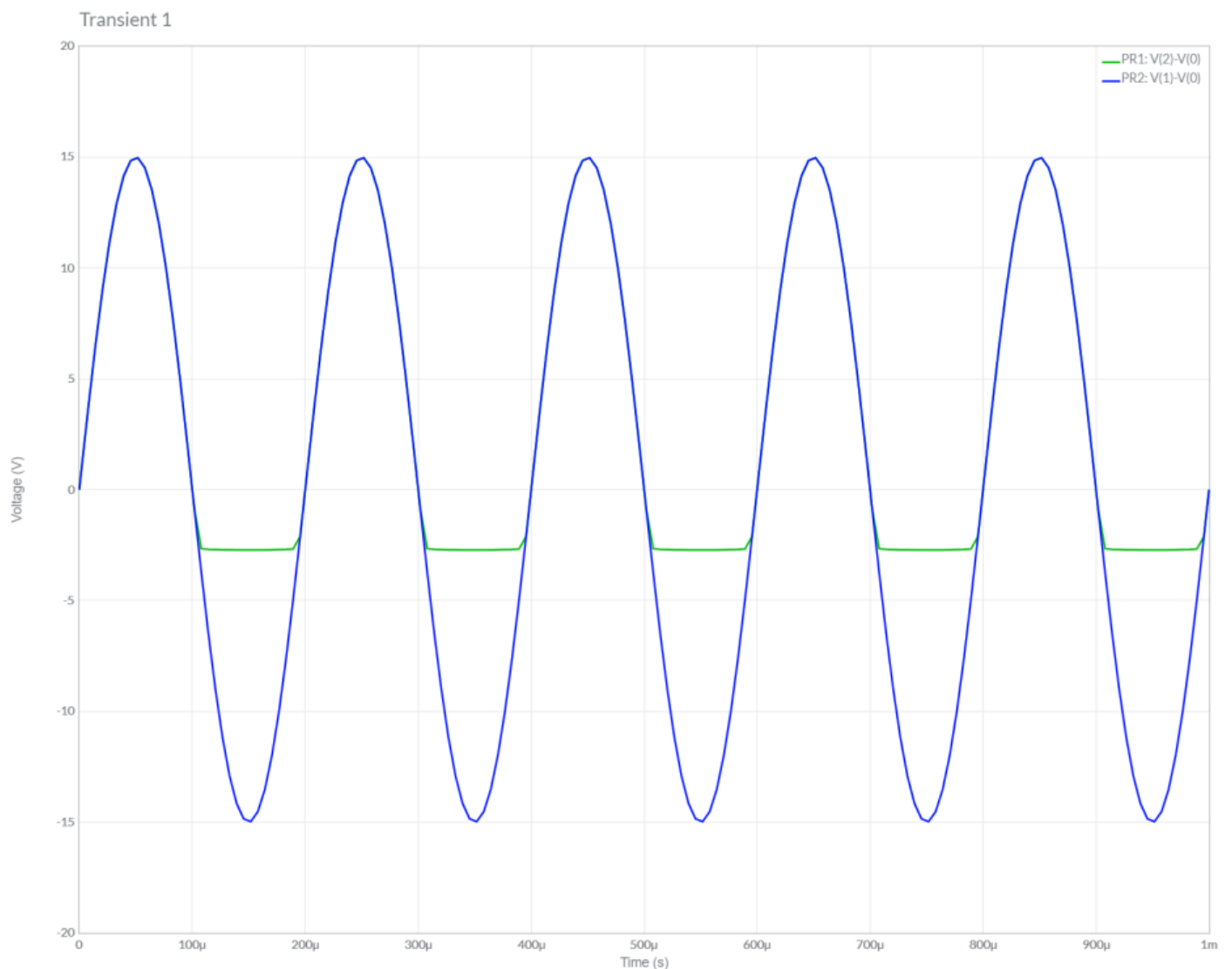




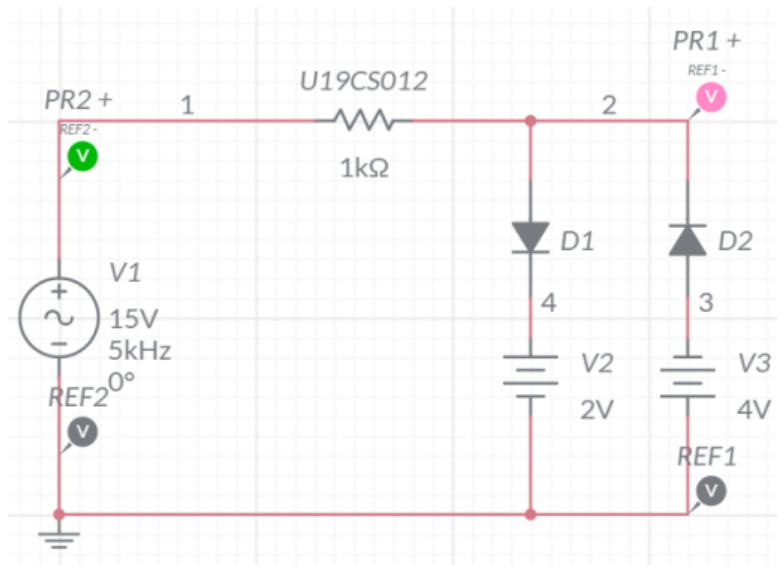7.) DUAL CLIPPER

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)



WAVEFORMS (FROM MULTISIM)

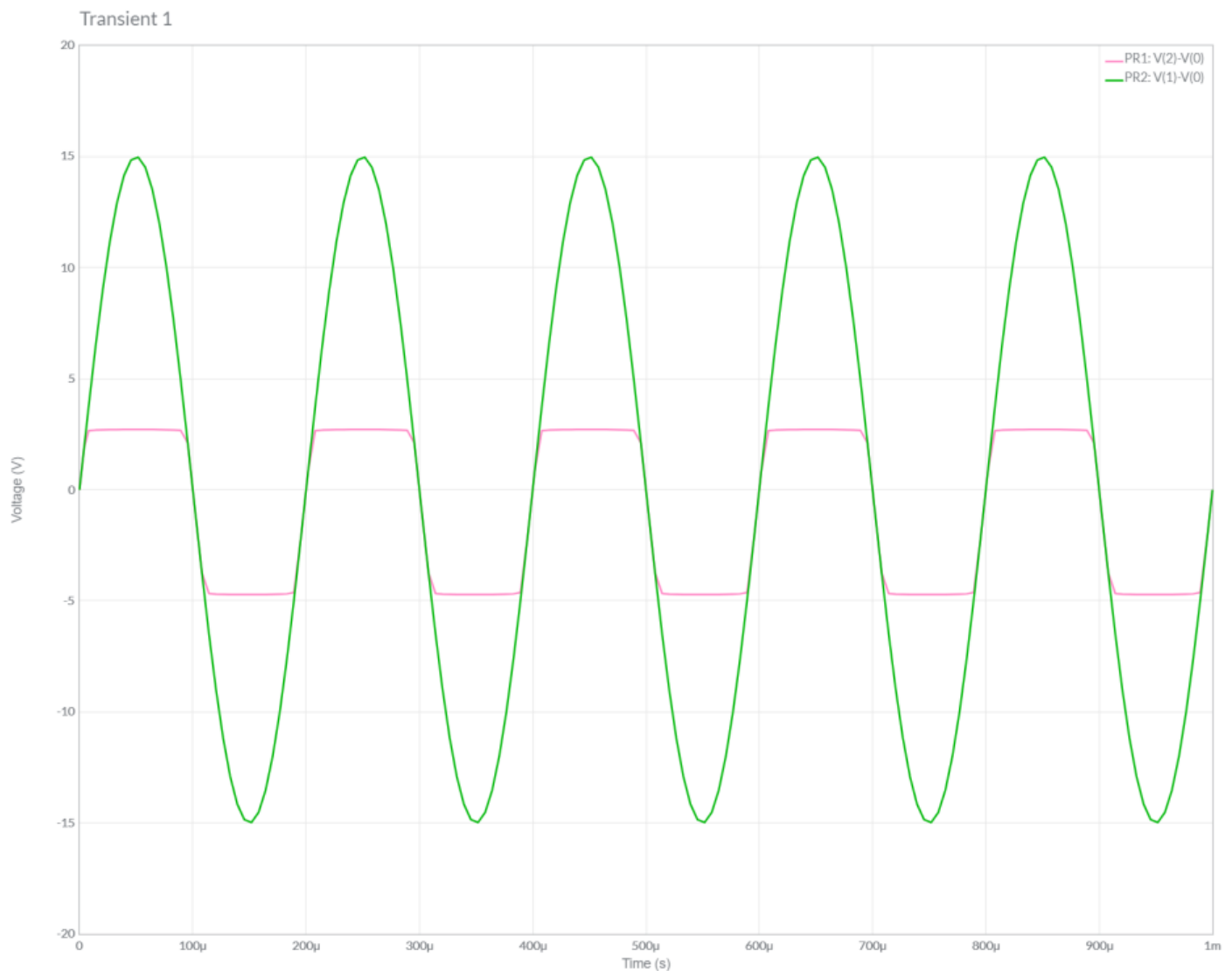



CONCLUSIONS

- 1.) In this Experiment, We have studied about Shunt Clipper Circuits [Both Positive and Negative] along with Different Biasing Applied.
- 2.) We Verified the Theoretical Knowledge of Shunt Clippers by Performing Simulations of 7 Cases of Shunt Clippers in Multisim.
- 3.) Hence, we have Successfully Designed, Plotted and Verified Various Shunt Diode Clipper Circuits.




ASSIGNMENT-7

U19CS012

1. Determine and plot the output voltage waveform for the given circuits. Also verify the same using Multisim.


Circuit a.)

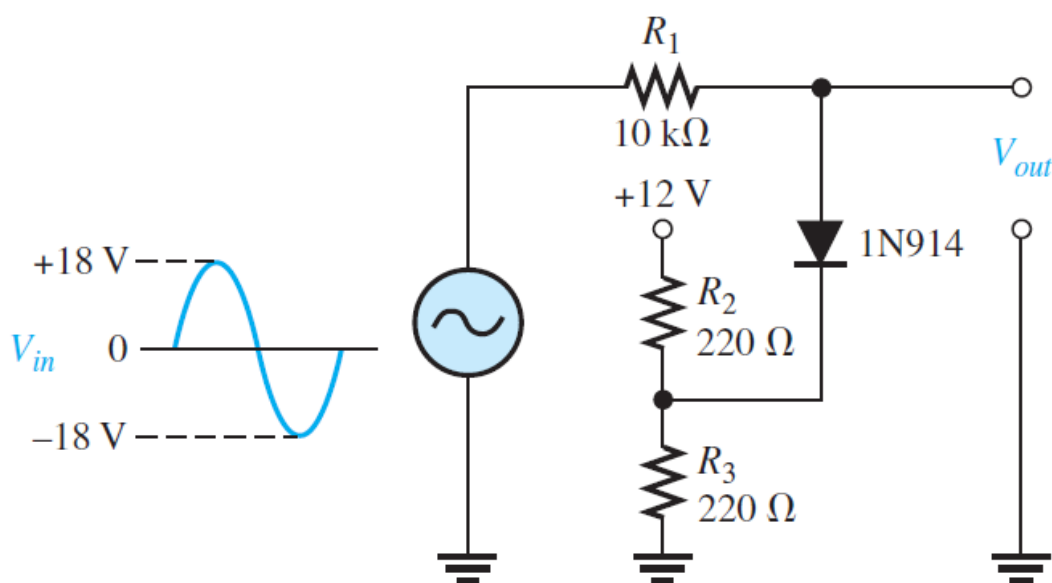




A.) Multisim Calculations:

1.) Circuit Image:

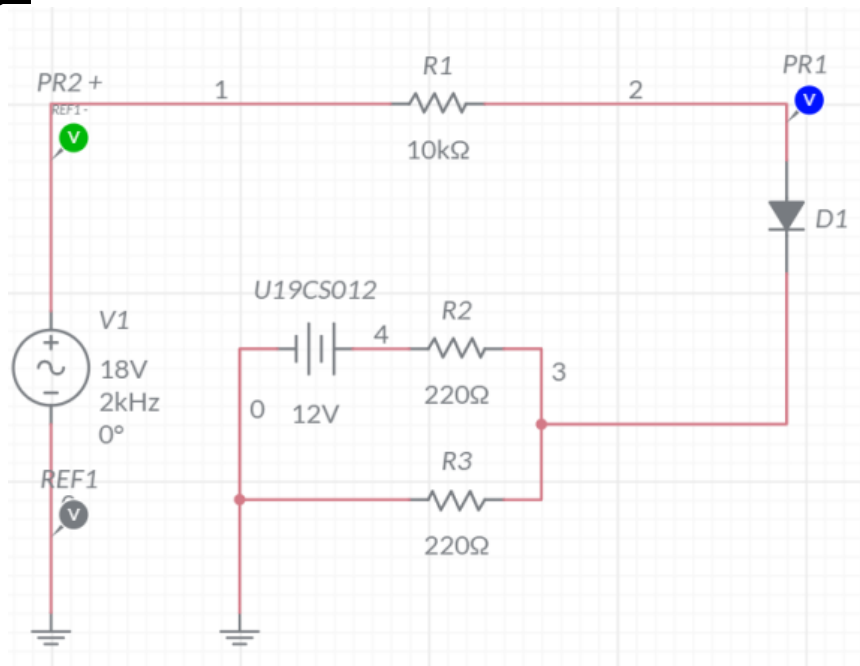

2.) Grapher Image:

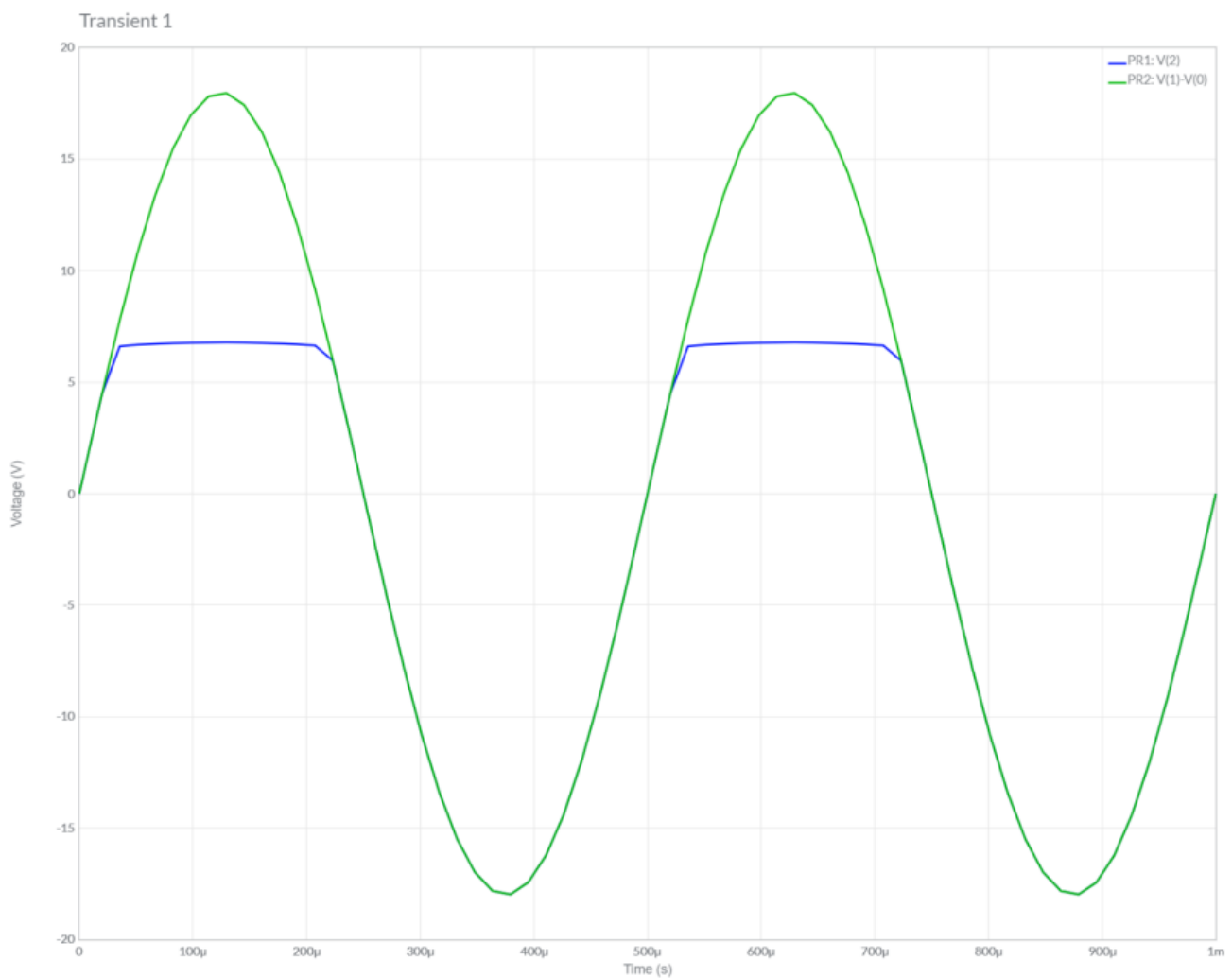




B.) Theoretical Calculations:

Practical-7 Assignment
(UI9CS012)

Q.1.7 Determine and Plot Output Voltage waveform

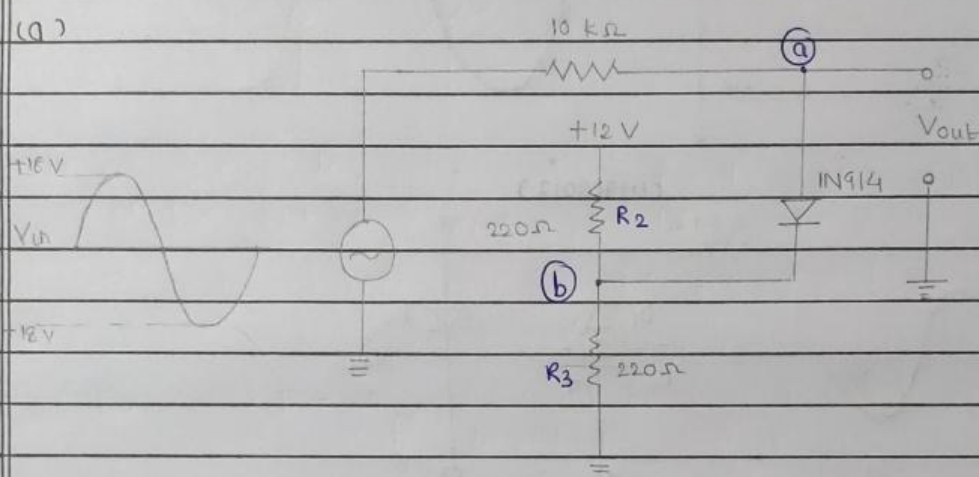→ Current through 12 V battery and passing through R_2 and R_3 .

$$I = \frac{12}{R_2 + R_3} = \frac{12}{220 + 220} = \frac{12}{440}$$

$$\text{Voltage at } b, V_b = I \times R_3 = \frac{12}{440} \times 220 = 6\text{ V}$$

∴ Voltage at Cathode of Diode = 6 V ∴ $V_i(t) < (6 + 0.7)\text{ V}$ diode will be reverse biased,∴ Diode $\xrightarrow{\text{act}}$ Open circuit


$$\therefore V_o = V_i(t) \quad \text{for } [V_i(t) < (6.7)\text{ V}] \quad \text{--- (1)}$$

→ For $V_i(t) > 6.7\text{ V}$, diode will be forward biased and will act asShort circuit for voltage drop of 0.7 V


$$\therefore V_o = V_b + 0.7 = (6 + 0.7)\text{ V}$$

$$\therefore V_o = 6.7\text{ V}$$
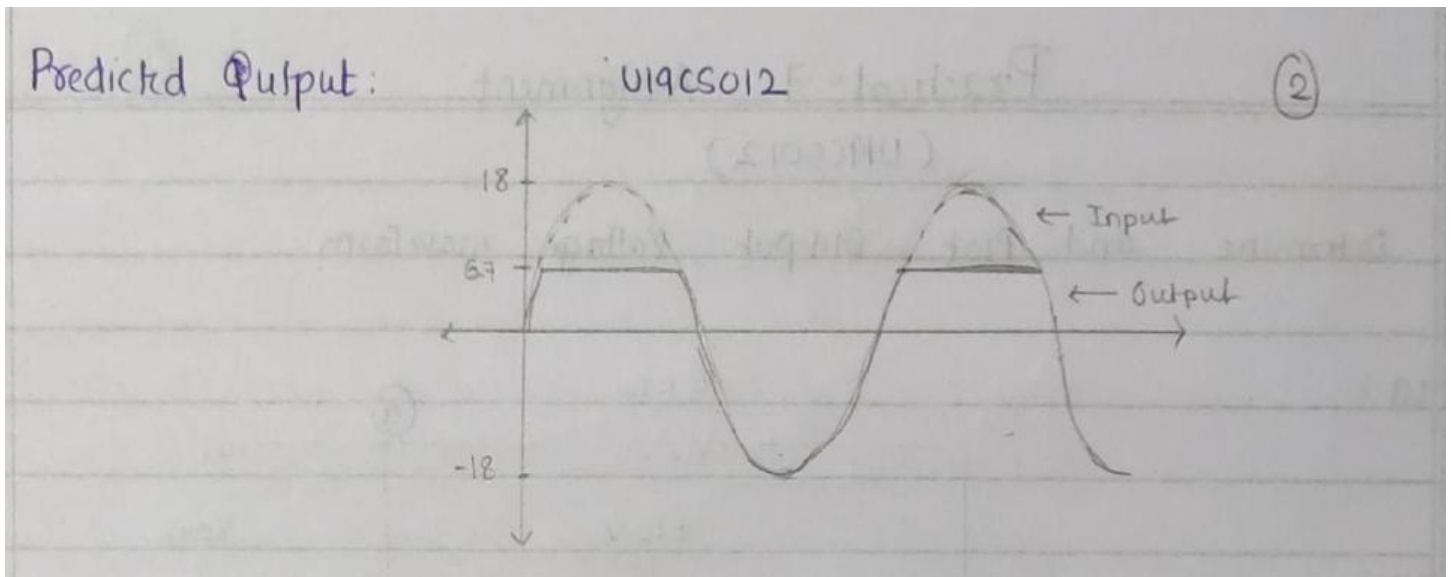
$$\therefore V_o = 6.7\text{ V} \quad \text{for } [V_i > 6.7\text{ V}] \quad \text{--- (2)}$$




Circuit b.)

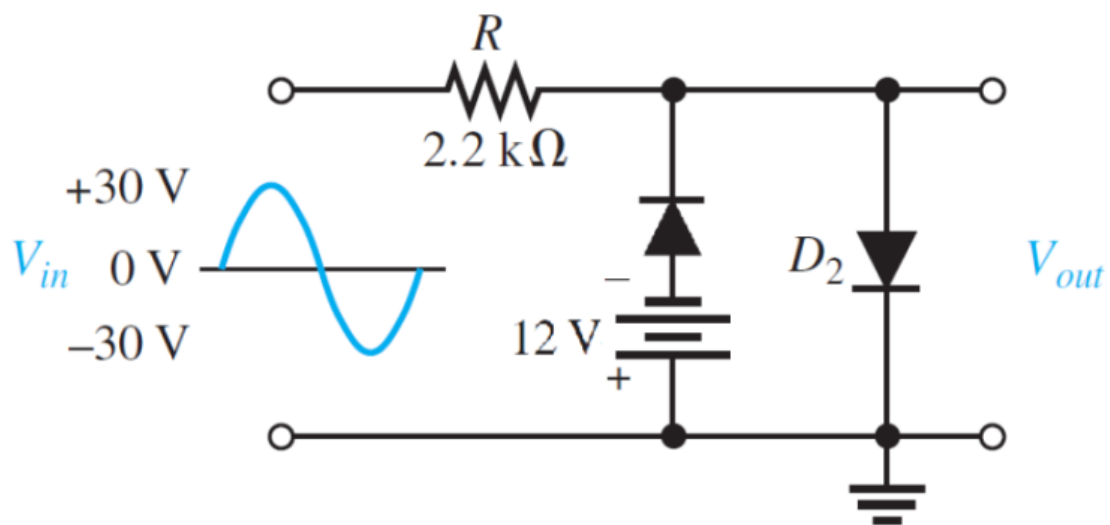





A.) Multisim Calculations:


1.) Circuit Image:

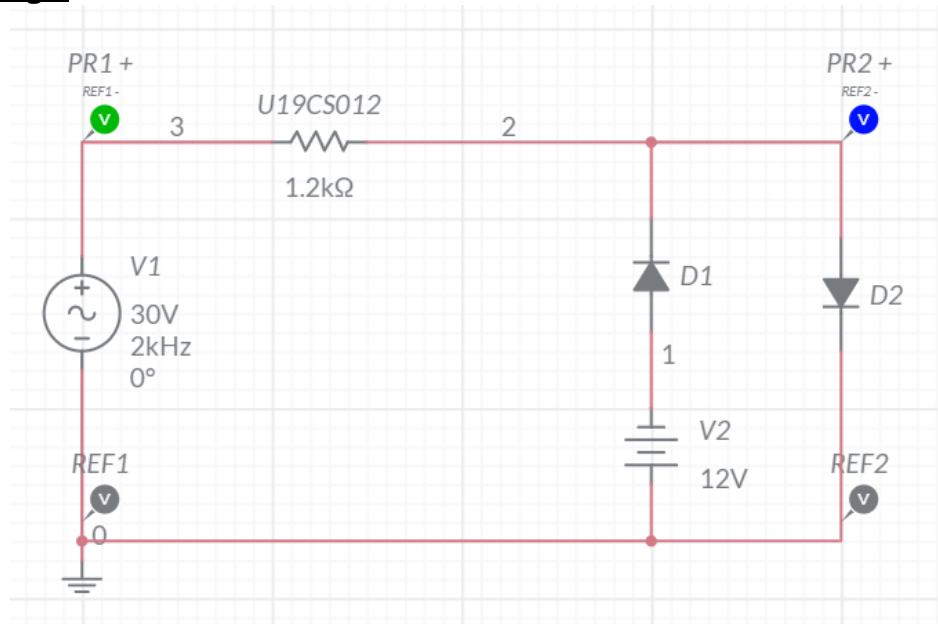


2.) Grapher Image:

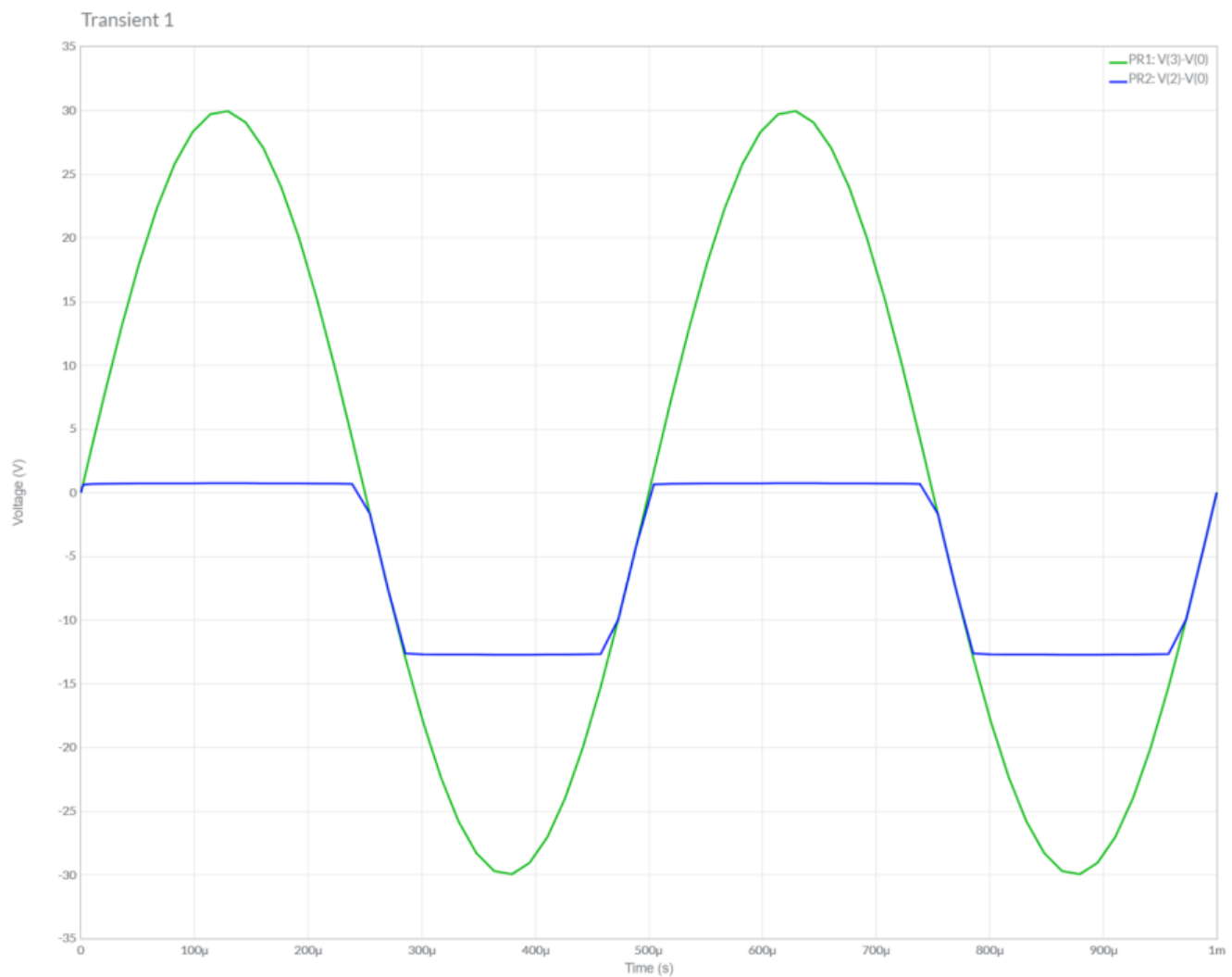

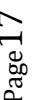

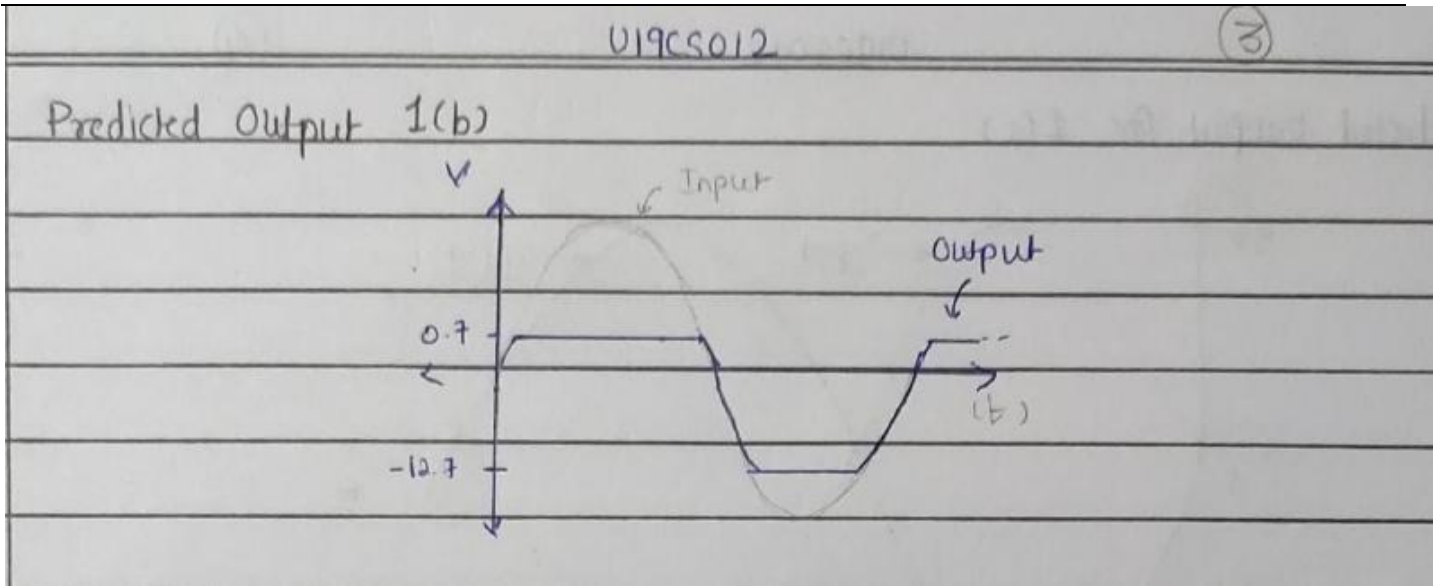


Circuit c.)

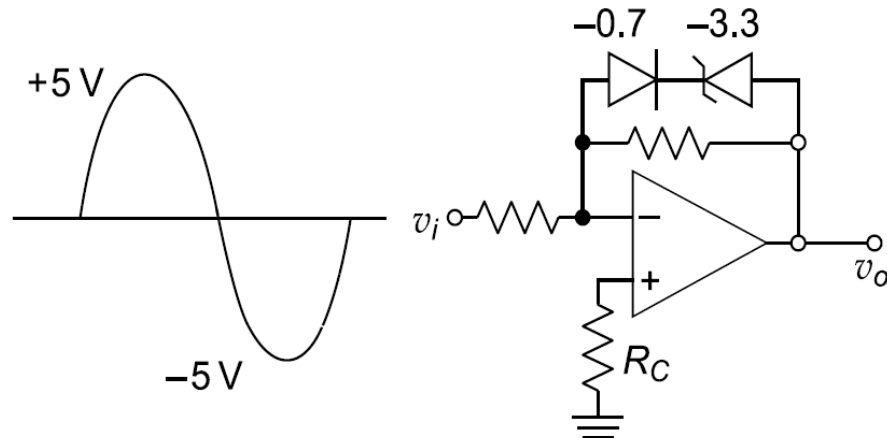




A.) Multisim Calculations:

1.) Circuit Image:

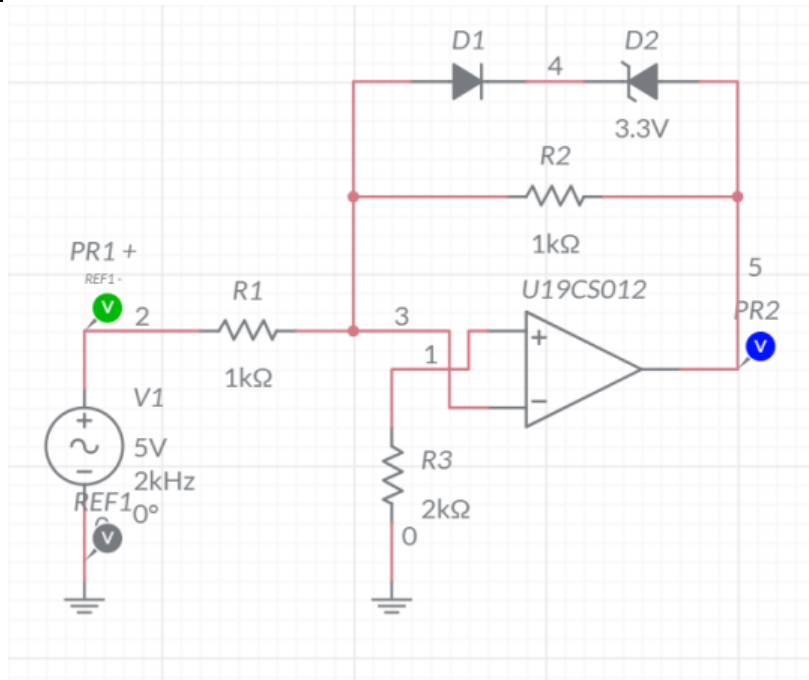

2.) Grapher Image:

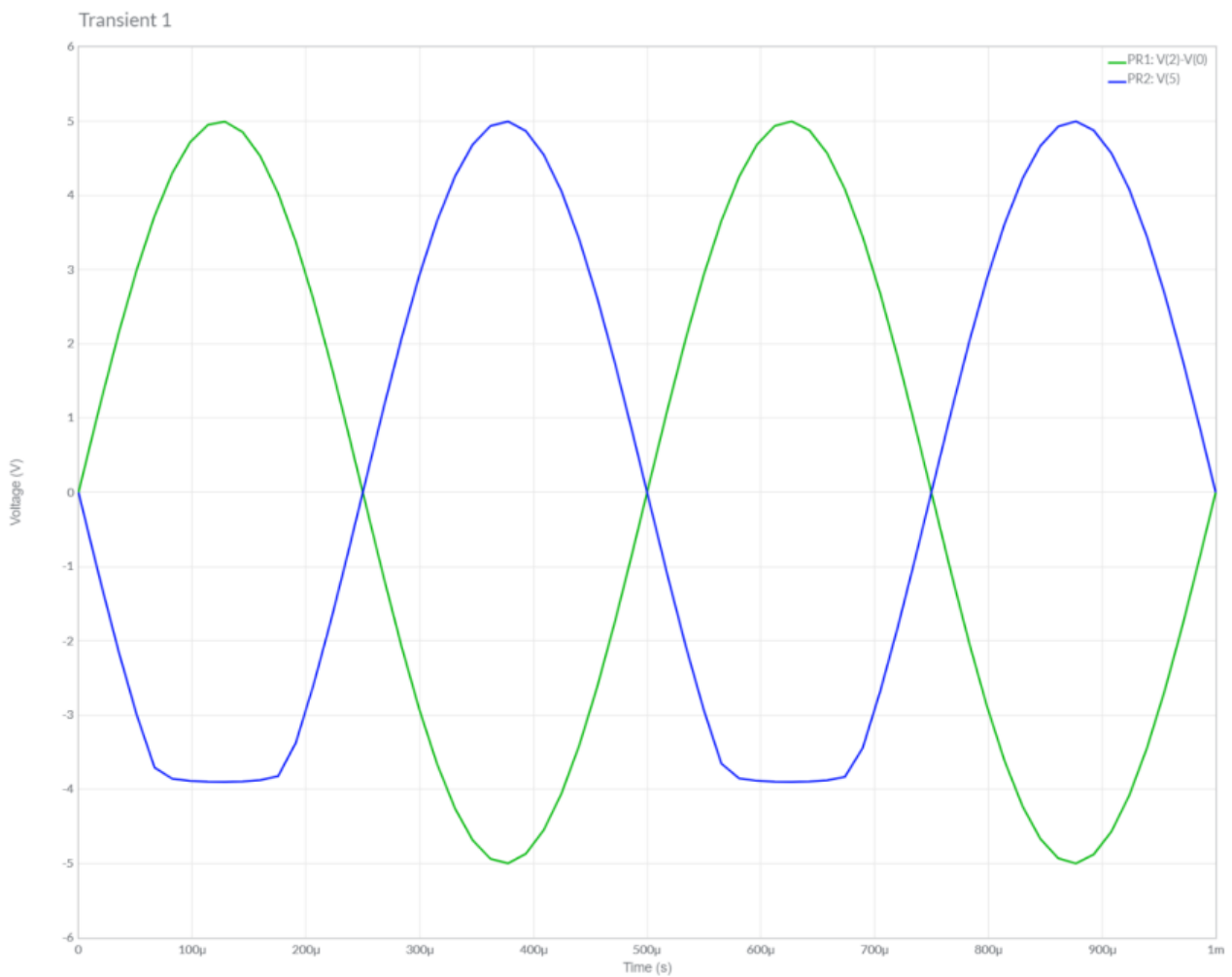



B.) Theoretical Calculations:

(1)(c) U19CS012


For $4V > V_i > 0V$, Zener diode will be reverse biased and no current will flow through diode [less than breakdown voltage]

$$\therefore V_o = -\frac{R_f}{R_i} V_i = -V_i \quad (\because R_f = R_i) \quad [4V > V_i > 0V] \quad \text{--- (1)}$$

For $V_i > 4V$, Zener diode will reach breakdown & pn diode will be forward biased. So voltage drop will be $-0.7 - 3.3 = -4V$


So, $V_o = -4V \quad [V_i > 4V] \quad \text{--- (2)}$

For $V_i < 0V$ pn diode will be reverse biased, so $\rightarrow \circ \rightarrow$ open circuit. No current will flow through diode.
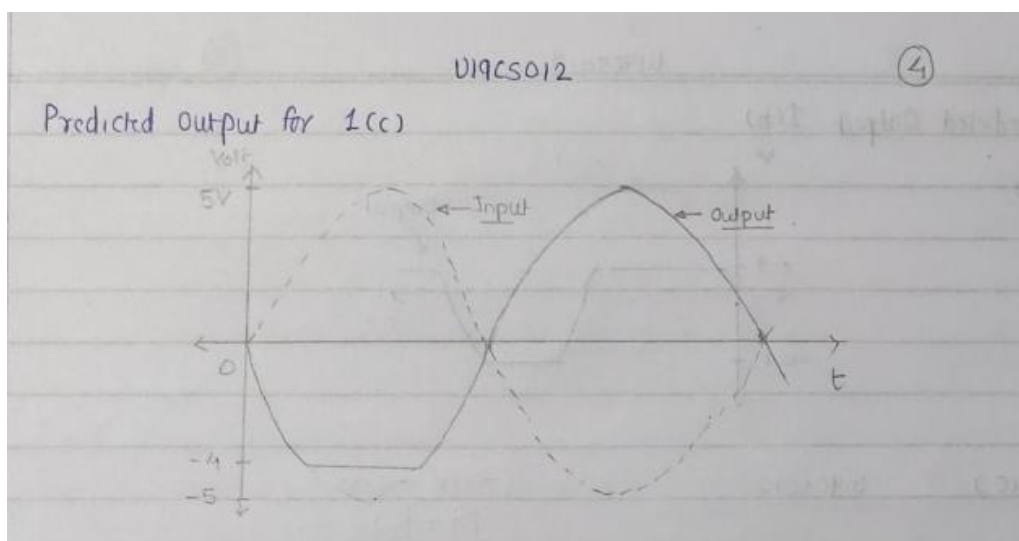
$$[V_o = -V_i] \quad V_i < 0$$

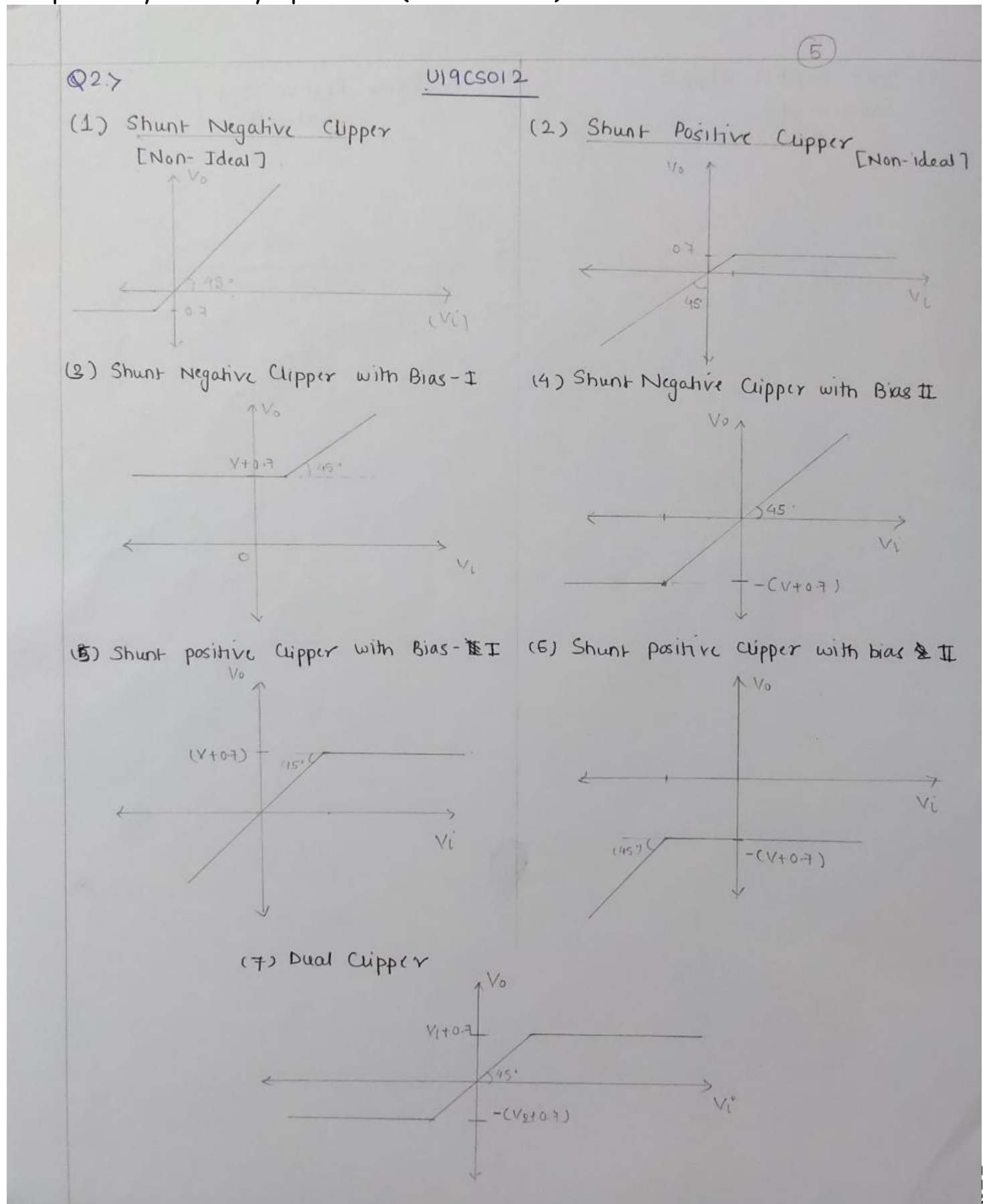
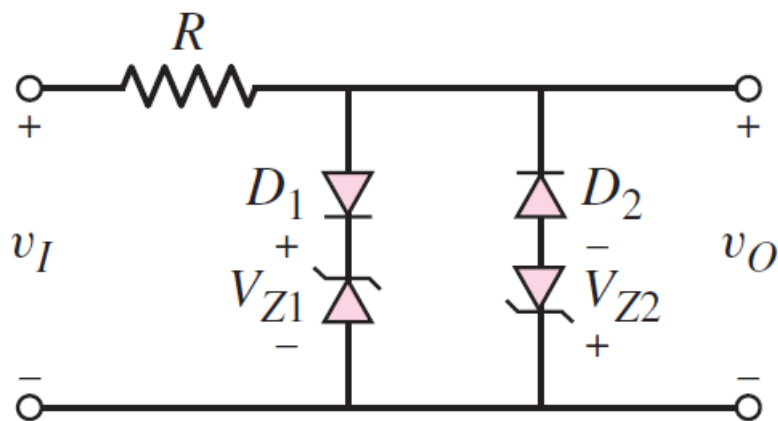


2. Draw the transfer characteristics for all the clipper configurations which are part of your today's practical (Practical - 7).






3. Assuming Symmetrical Sine wave input with peak value greater than the Zener reference voltage, predict the output and plot the Transfer Characteristics for the following Clipper Circuits:




A.) Multisim Calculations:

1.) Circuit Image:

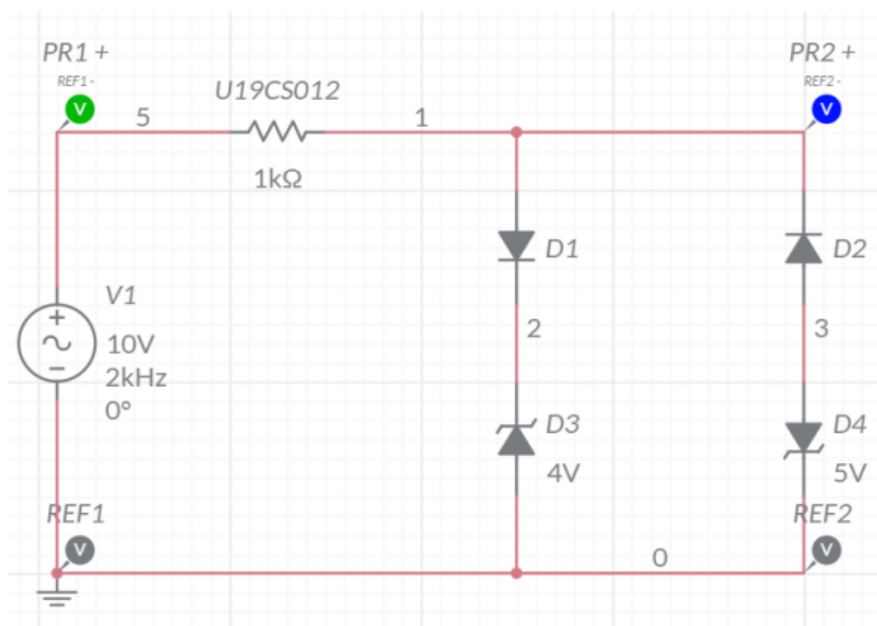



2.) Grapher Image:

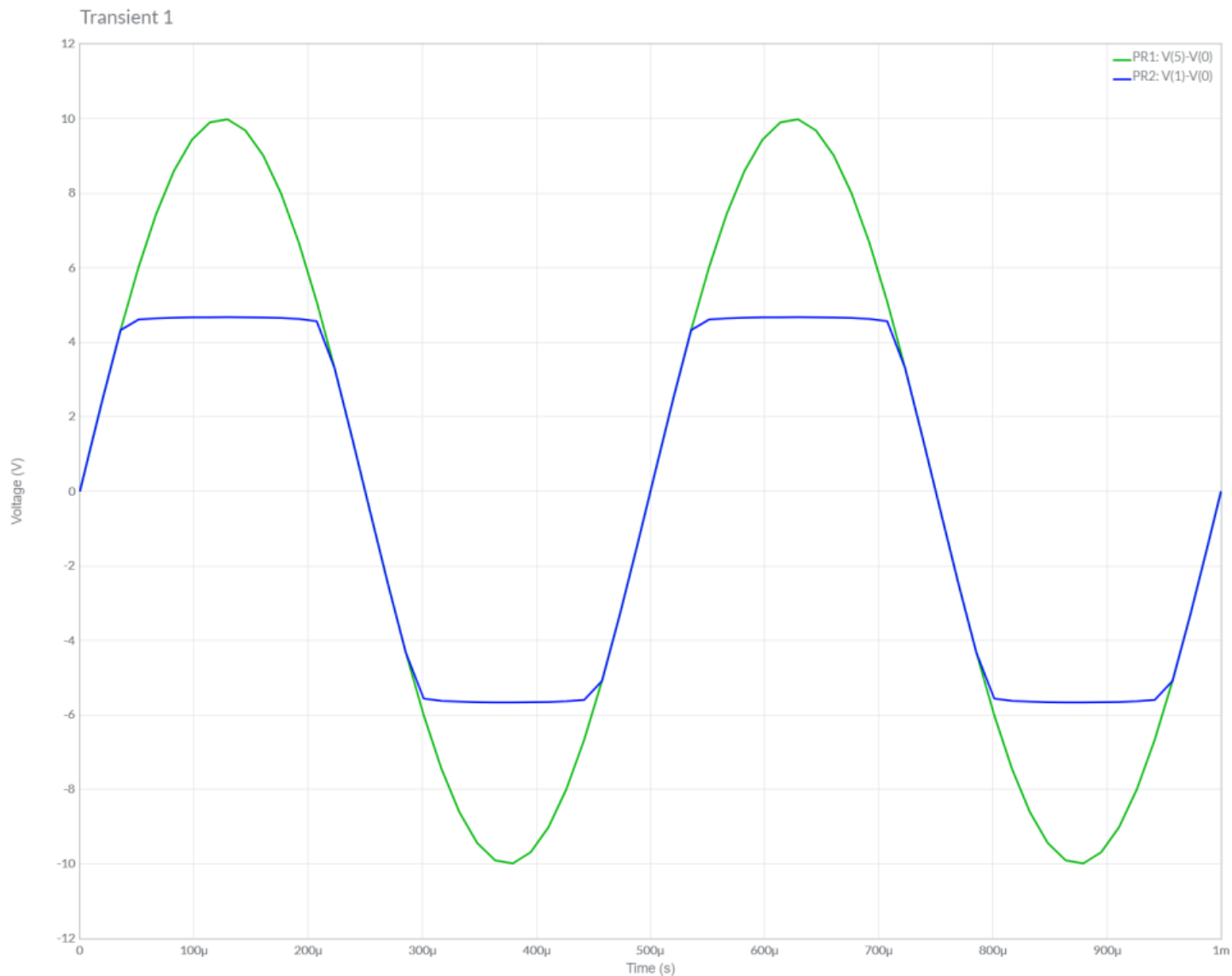



B.) Theoretical Calculations:

Q.3.7

(U19CS012) (6)

i) For $V_i > 0$, D_2 will be reverse biased, so it will be open circuit
 → For $D_1 + V_{Z1} > V_i > 0$; D_1 will be Reverse Biased and no current will flow [∴ open circuit]
 ∴ $V_o = V_i$
 For $V_i > D_1 + V_{Z1}$; D_1 will be forward biased and zener diode will reach breakdown voltage
 ∴ $V_o = D_1 + V_{Z1}$

ii) For $V_i < 0$; D_1 will be reverse biased
 So, it will be open circuit
 For $D_2 + V_{Z2} < V_i < 0$; D_2 will be reverse biased so open circuit and no current will flow.
 ∴ $V_o = V_i$
 For $V_i < D_2 + V_{Z2}$; D_2 will be forward biased and zener diode will reach Breakdown, so,
 ∴ $V_o = V_{Z1} + V_{D2}$

vision