



DELD – Tutorial 3



ECED SVNIT


Instructions For Tutorial Sessions

- Copy questions and work out detailed solutions in a neat and clean handwriting.
- Questions will be shown between 10.40 to 11.20. In the next 10 minutes you need to scan and upload your work in a **PDF format only carrying only your Admission number.**
- Mention all the details viz Full Name, Admission No, Div, Date, Tutorial No. etc on First Page
- **If two handwritings are found similar, they both will be graded 0.**



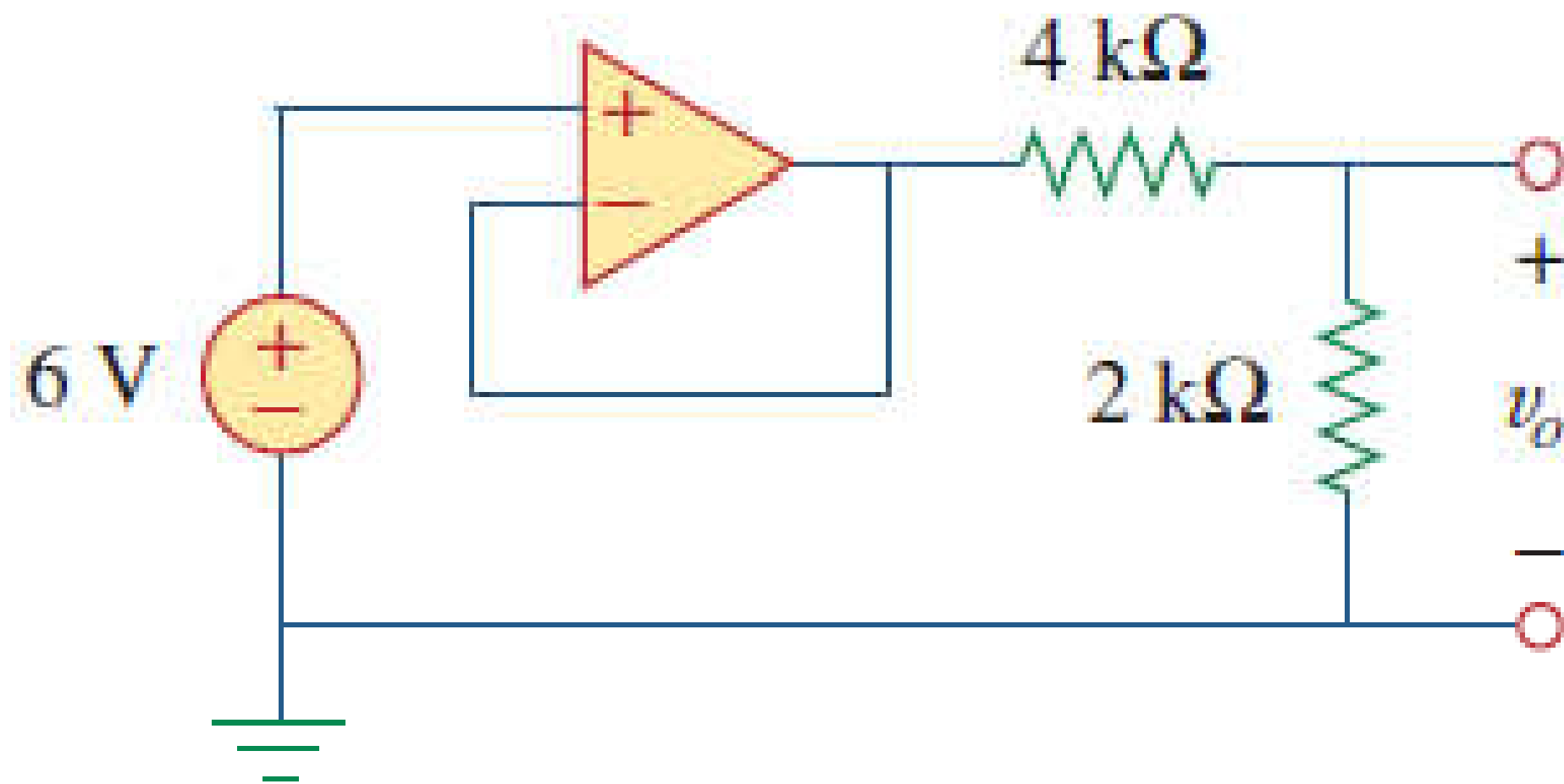
Question - 1

- The power absorbed by 4 K ohm resistor is given by_____.



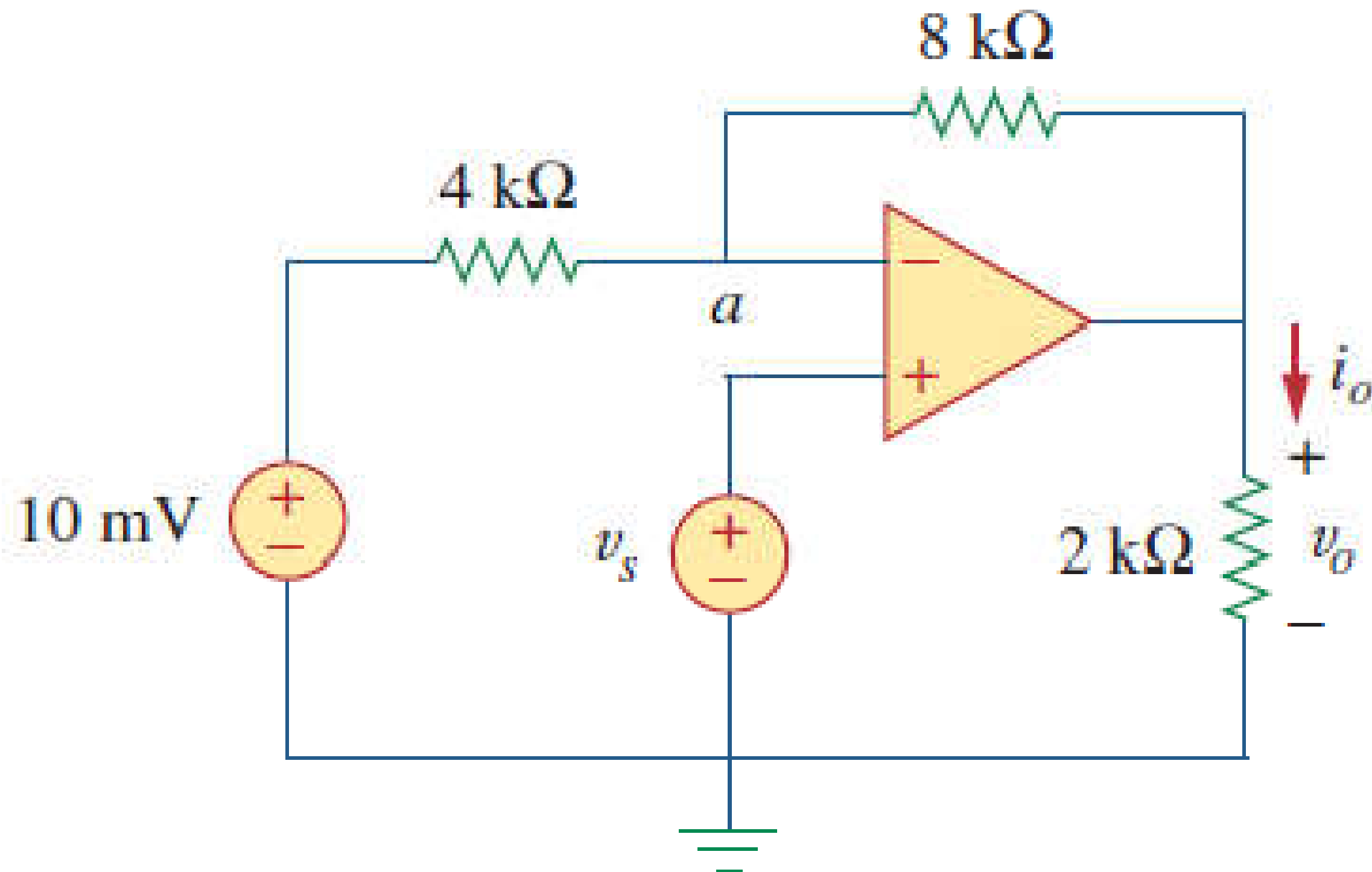
Question - 2

- If $V_s=0$, the current i_o will be_____.



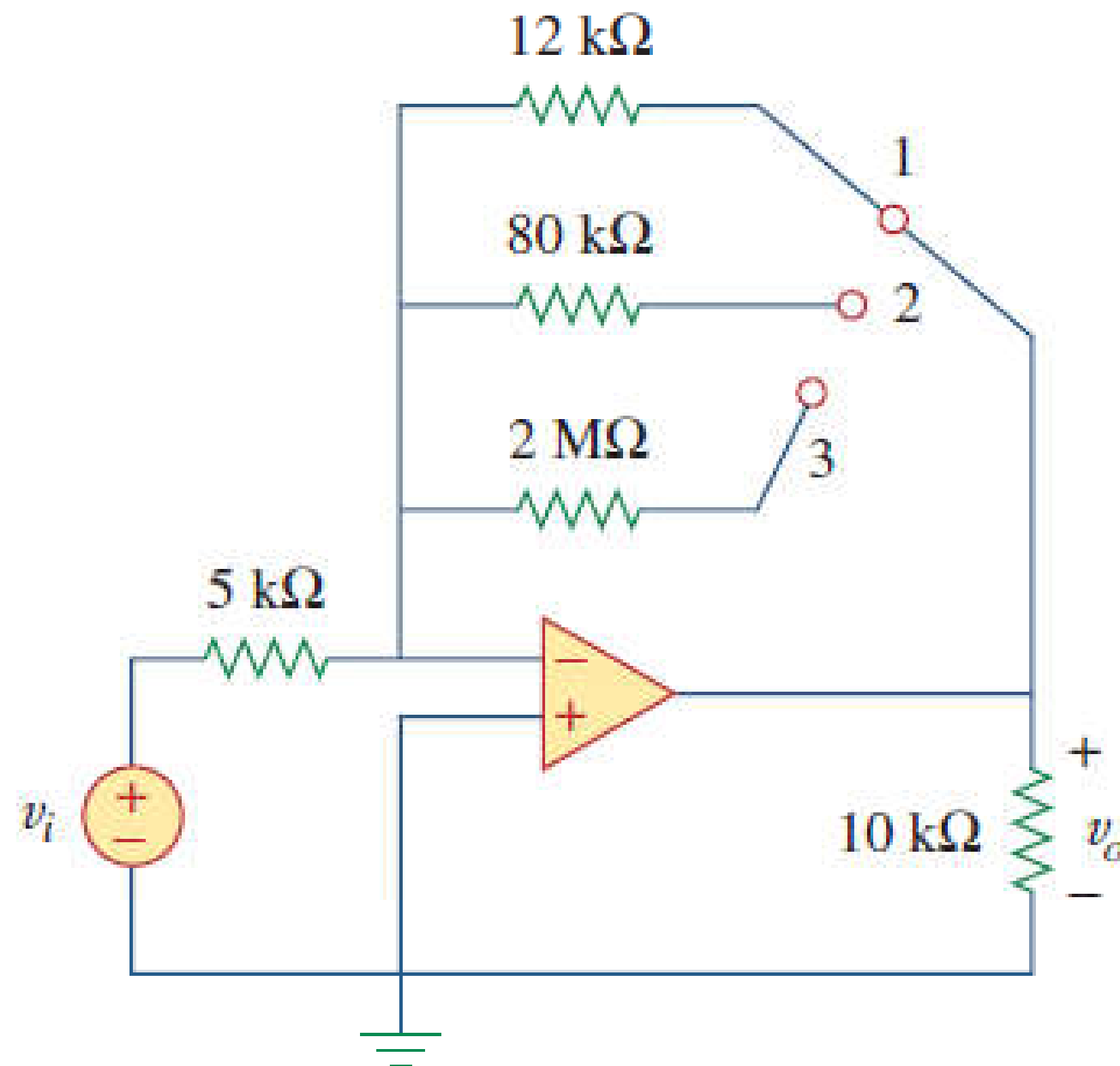
Question - 3

- Calculate the Gain when switch is at
- Pos-1, Pos – 2, Pos - 3




Question - 4

- Determine V_o in the Circuit

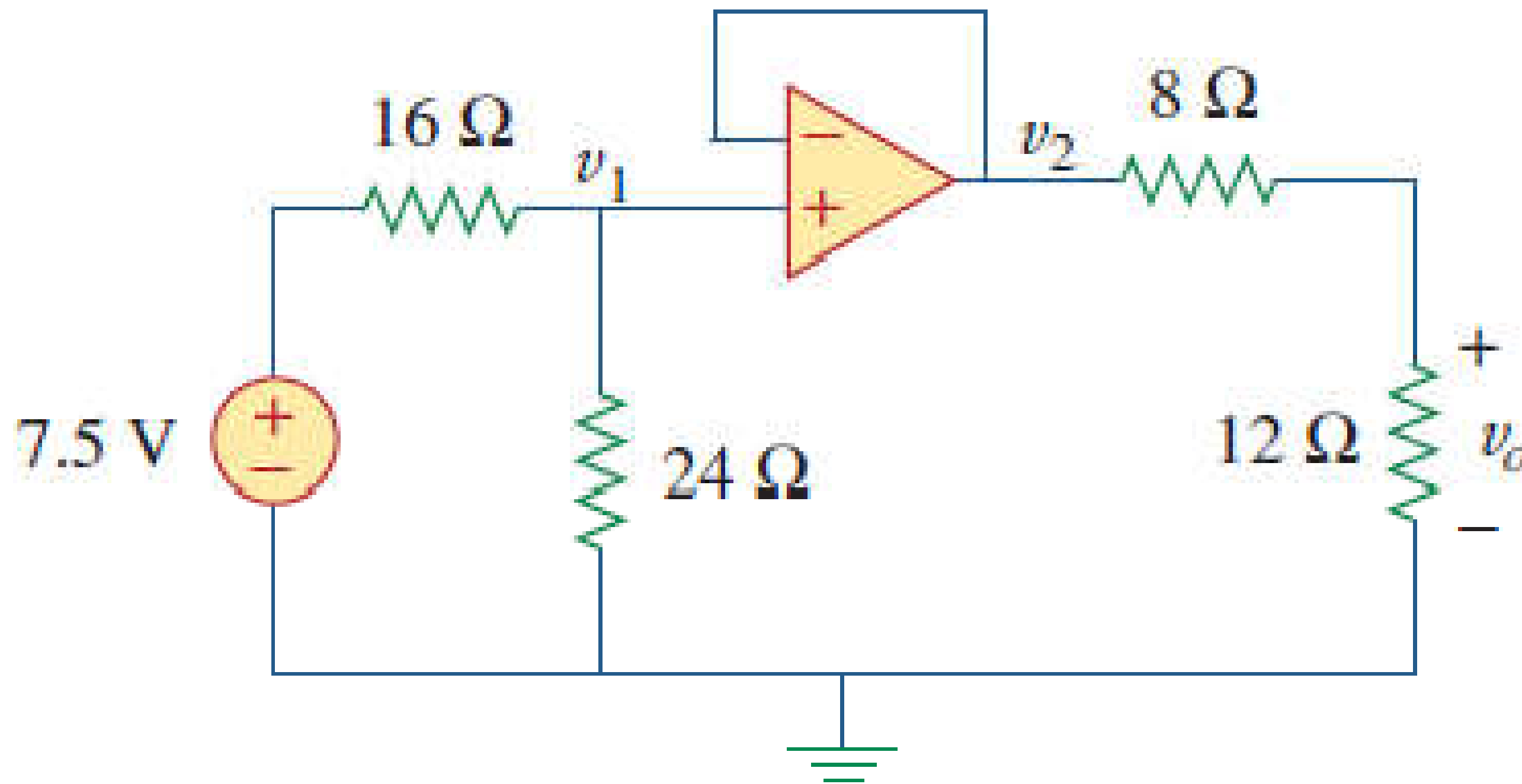

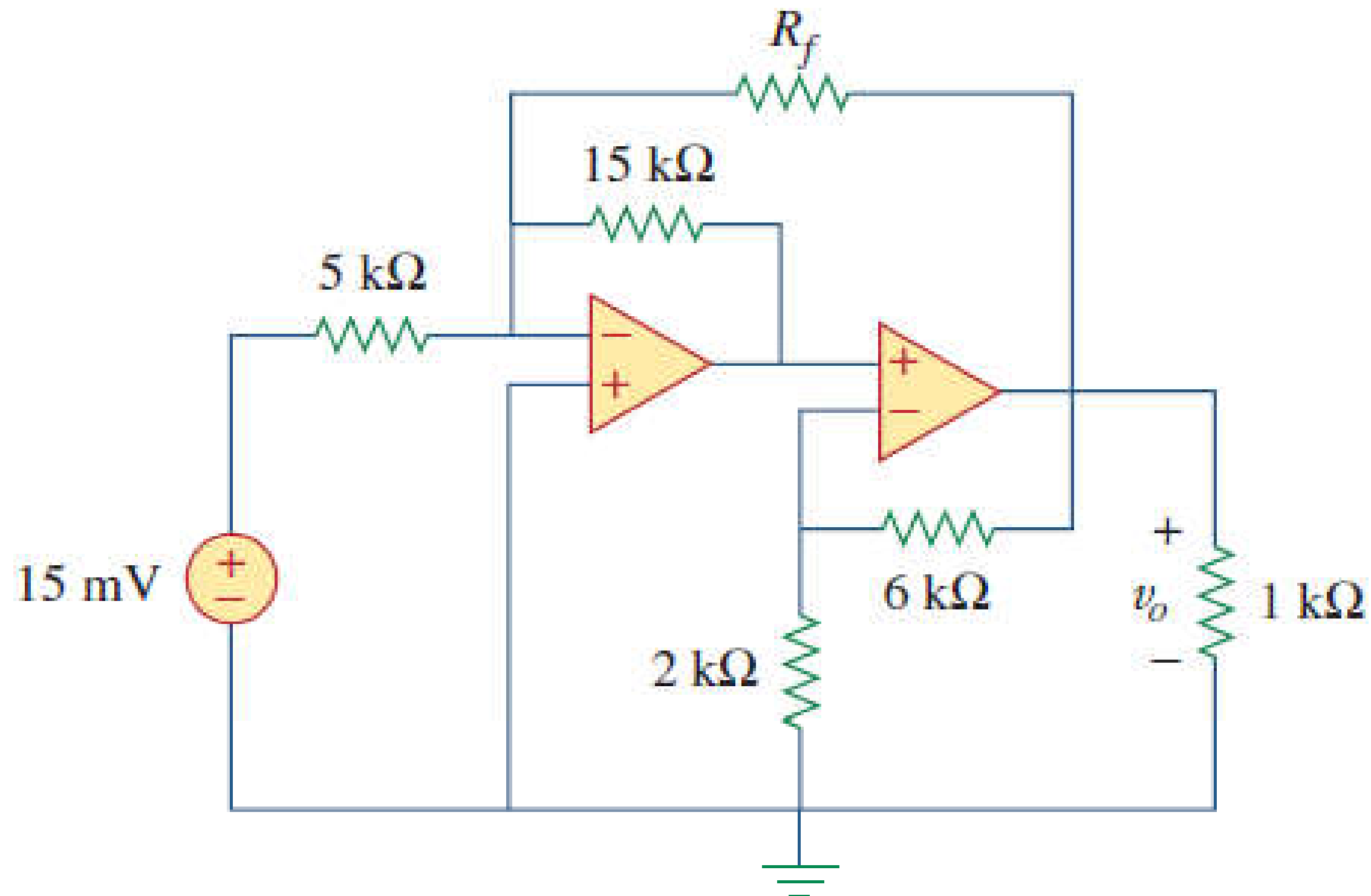
Question - 5

- Determine V_o in the Circuit assuming R_f equal to infinity



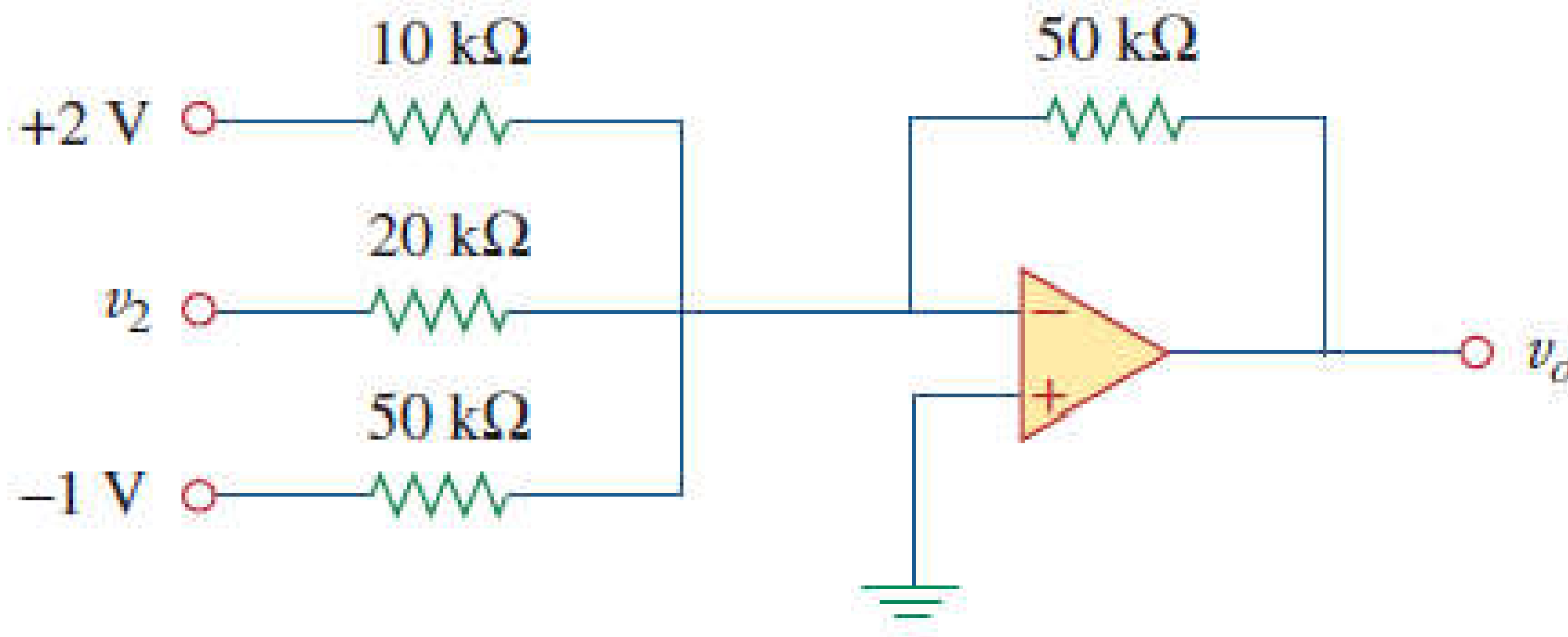Question - 6

- Determine the value of V_2 in order to make $V_o = -16.5$ Volts.



To Be Continued...

