

ELECTRONICS ENGINEERING DEPARTMENT SARDAR VALLABHBHAI NATIONAL INSTITUTE OF TECHNOLOGY, SURAT


DIGITAL ELECTRONICS & LOGIC DESIGN LAB

(EC207)


OBJECTIVES & OUTCOMES OF THIS LAB

- ▶ Acquire knowledge about different types of **diodes** and circuits
- ▶ Apply the knowledge of **Logic gates** and Boolean algebra in design of logical circuits
- ▶ Analyze the integrated and **Operational amplifier** based circuits
- ▶ Evaluate different **Transistor** based circuits and compare their performance


A FEW EXAMPLES OF APPLICATIONS

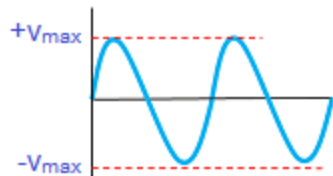


Input waveform

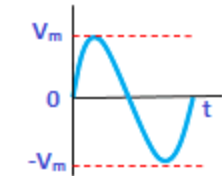

Input waveform

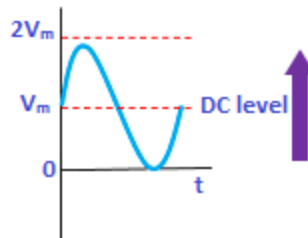

Output waveform


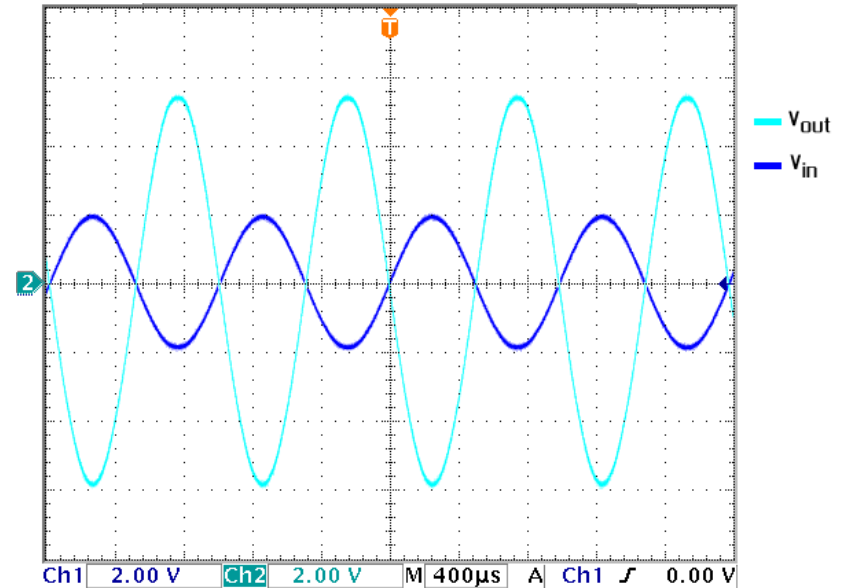


$$0 + 1 + 1 = 1$$

$$1 + 1 + 1 = 1$$

$$0 + 1 + 1 + 1 = 1$$

$$1 + 0 + 1 + 1 + 1 = 1$$

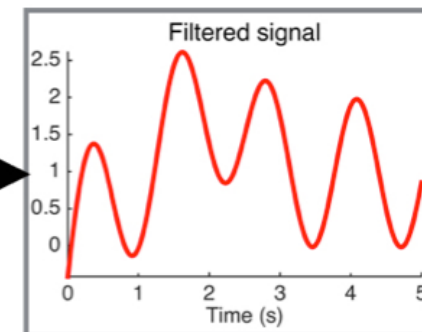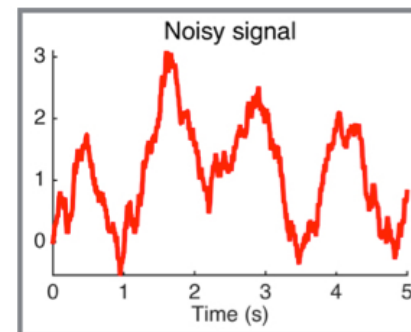

INTRODUCTION TO MULTISIM

- ▶ By National Instruments (NI)
- ▶ Tool for Schematic capture of electronic circuits
- ▶ Used to
 - ▶ simulate electronic circuits and
 - ▶ prototype Printed Circuit Boards (PCBs)


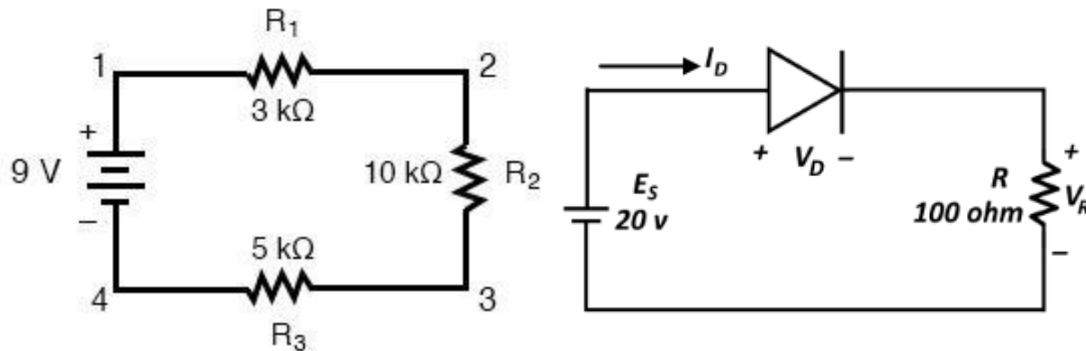


Fig.: Examples of Electronic Circuits

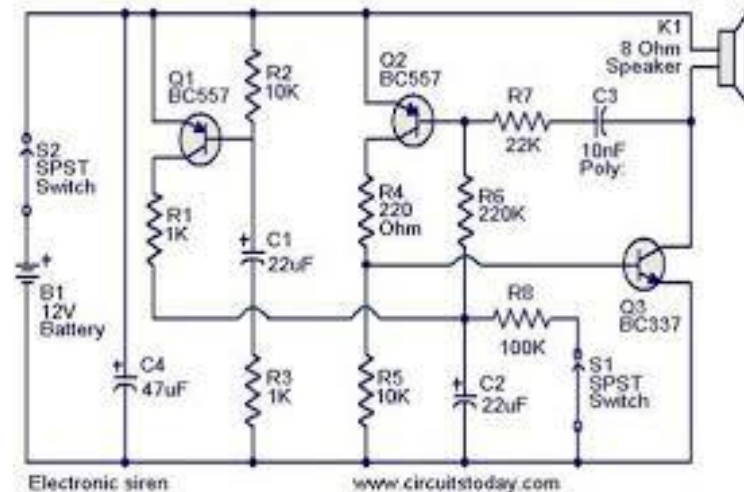

INTRODUCTION TO MULTISIM

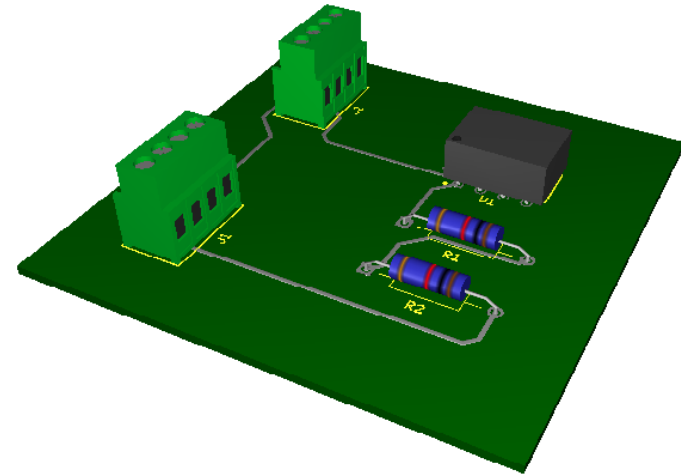
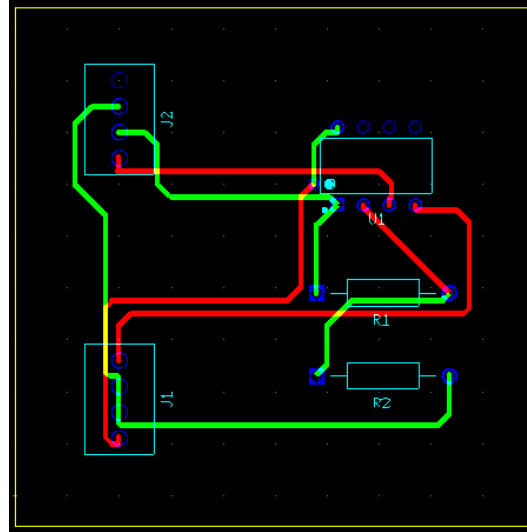
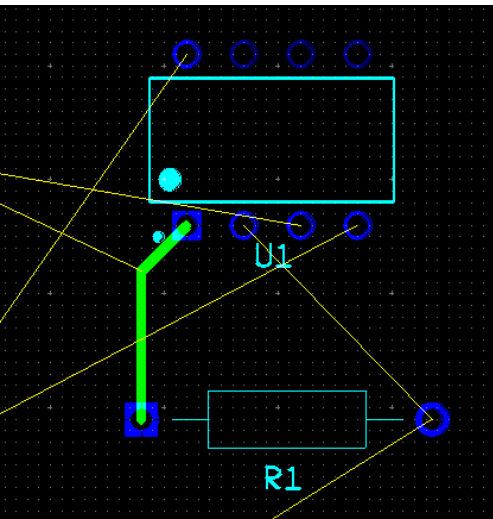


Fig.: Example- PCB Design

GETTING STARTED WITH MULTISIM

- ▶ Multisim Live is a **free online circuit simulator** that includes SPICE software, which lets you **create, learn and share electronics** circuits online.
- ▶ No installation is required!!
- ▶ Create a free profile on:
<https://lumen.ni.com/nicif/create.xhtml>

GETTING STARTED WITH MULTISIM

- ▶ After Filling details, a verification mail would be sent to registered mail id
 - ▶ Click on verification link and activate your account.
 - ▶ That's it. You're ready!!!
-
- ▶ Login to your account and lets start exploring....

Create an NI User Account

Already have an account? [Log In >](#)

Alias

First Name

Last Name

Role

Company

Email Address

Password

CREATE ACCOUNT




Discover Electronics


with Online SPICE Simulation

SEE HOW IT WORKS

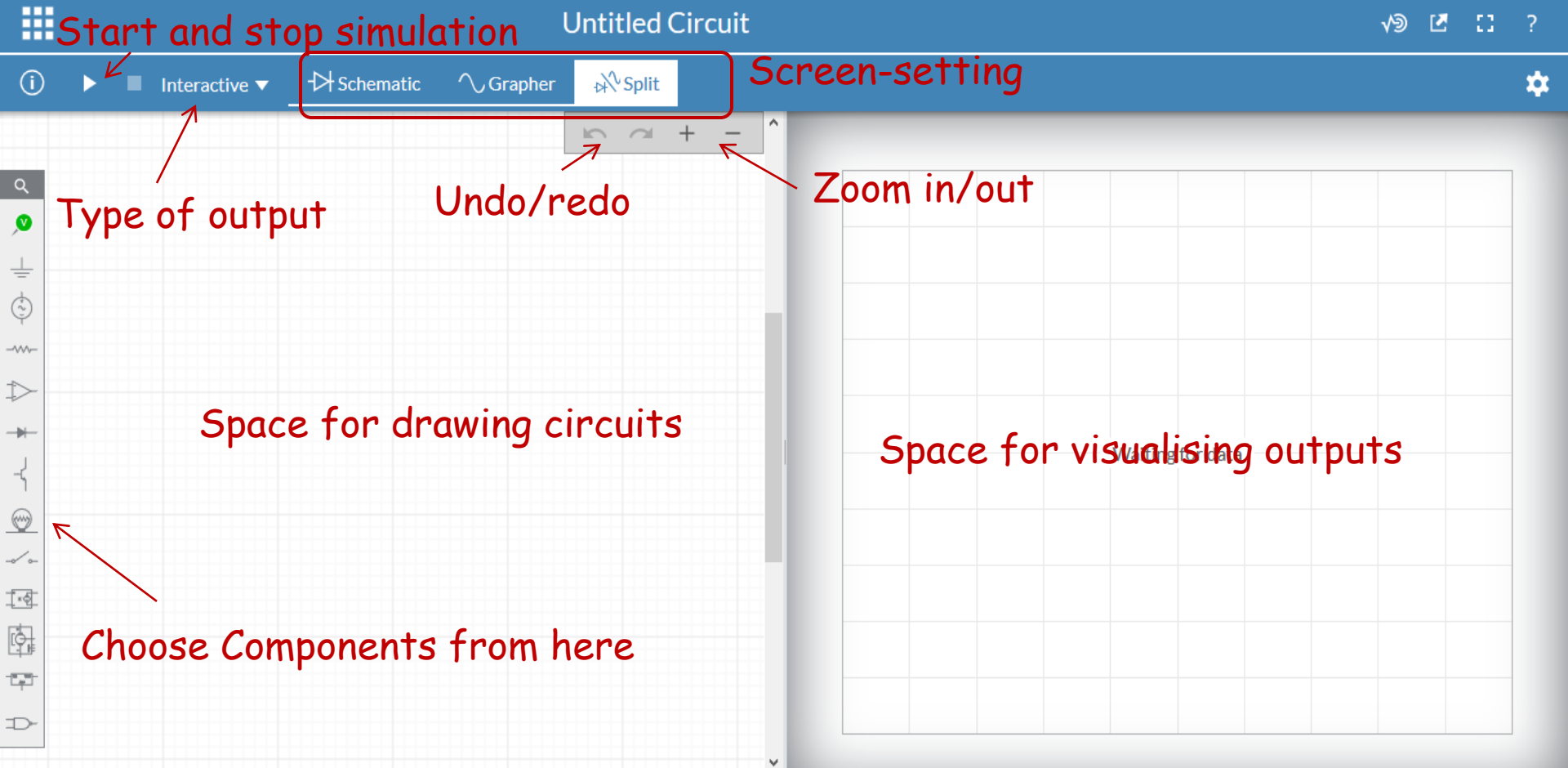- ▶ UI appears as shown.
- ▶ Click on Create Circuit



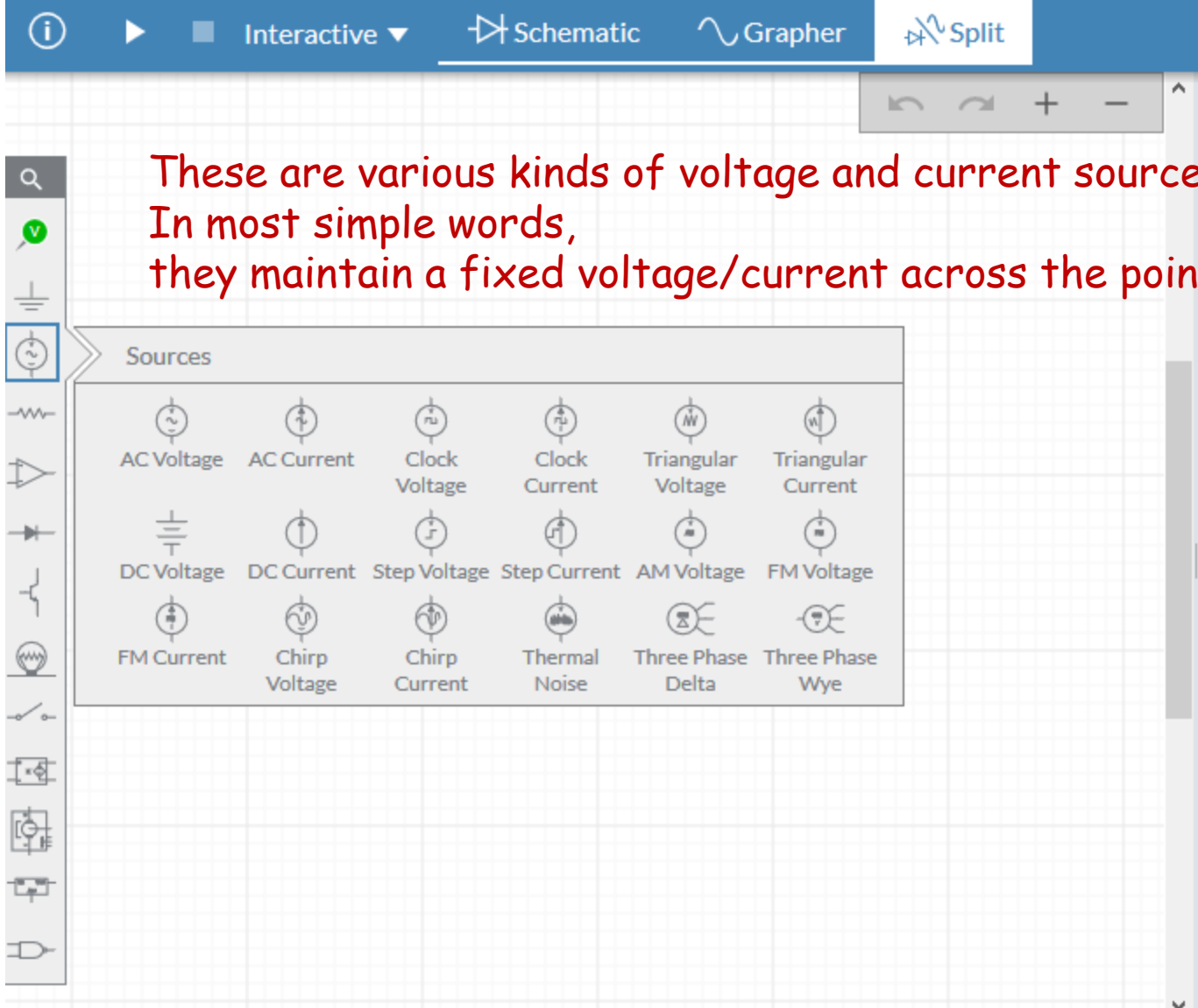- ▶ The UI loads in a couple of seconds.
- ▶ Lets understand the UI.





These are various kinds of voltage and current sources available.

In most simple words,

they maintain a fixed voltage/current across the points they are connected

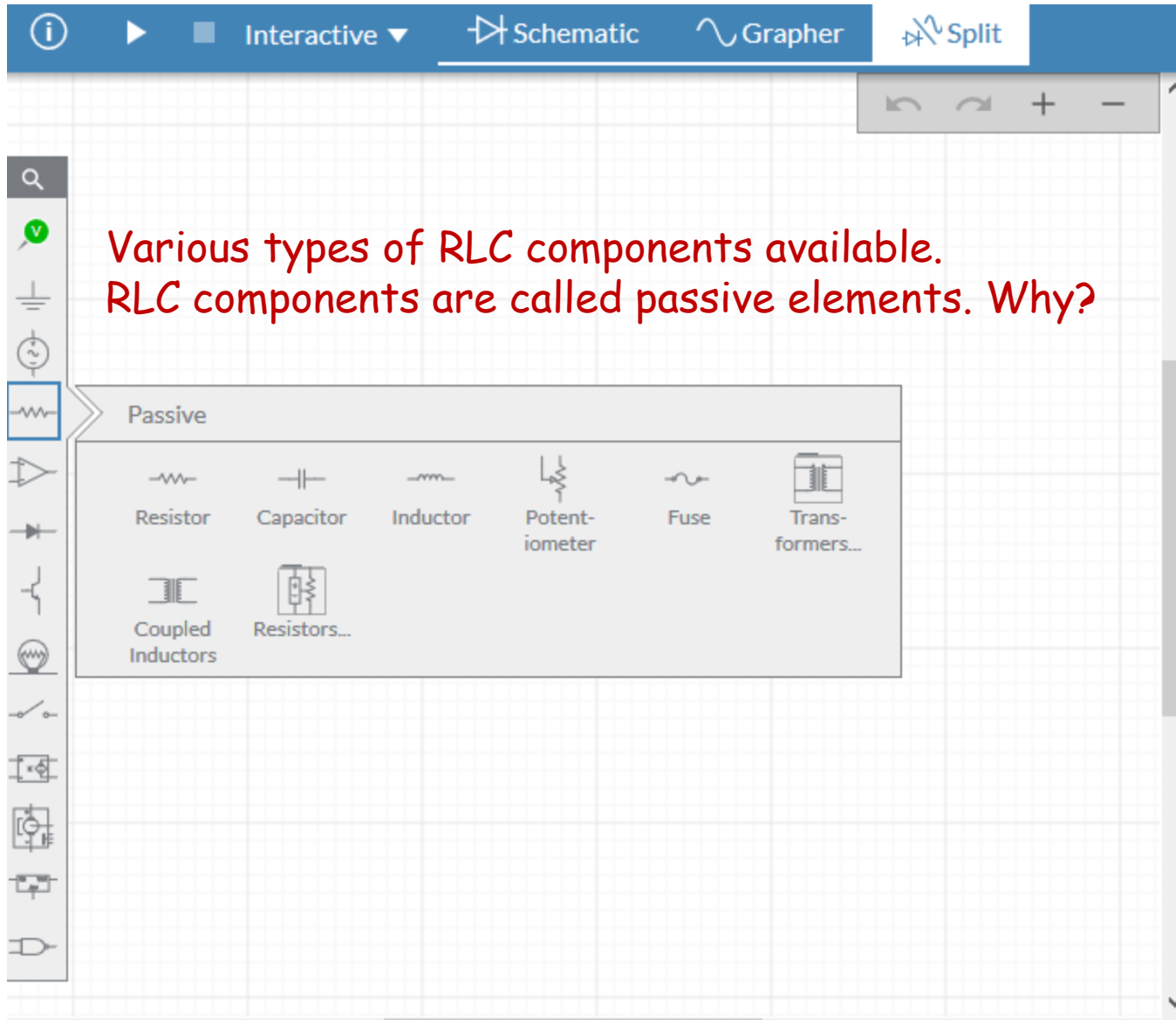- ▶ Lets explore the components available
- ▶ Some of these we shall explore as lab proceeds....



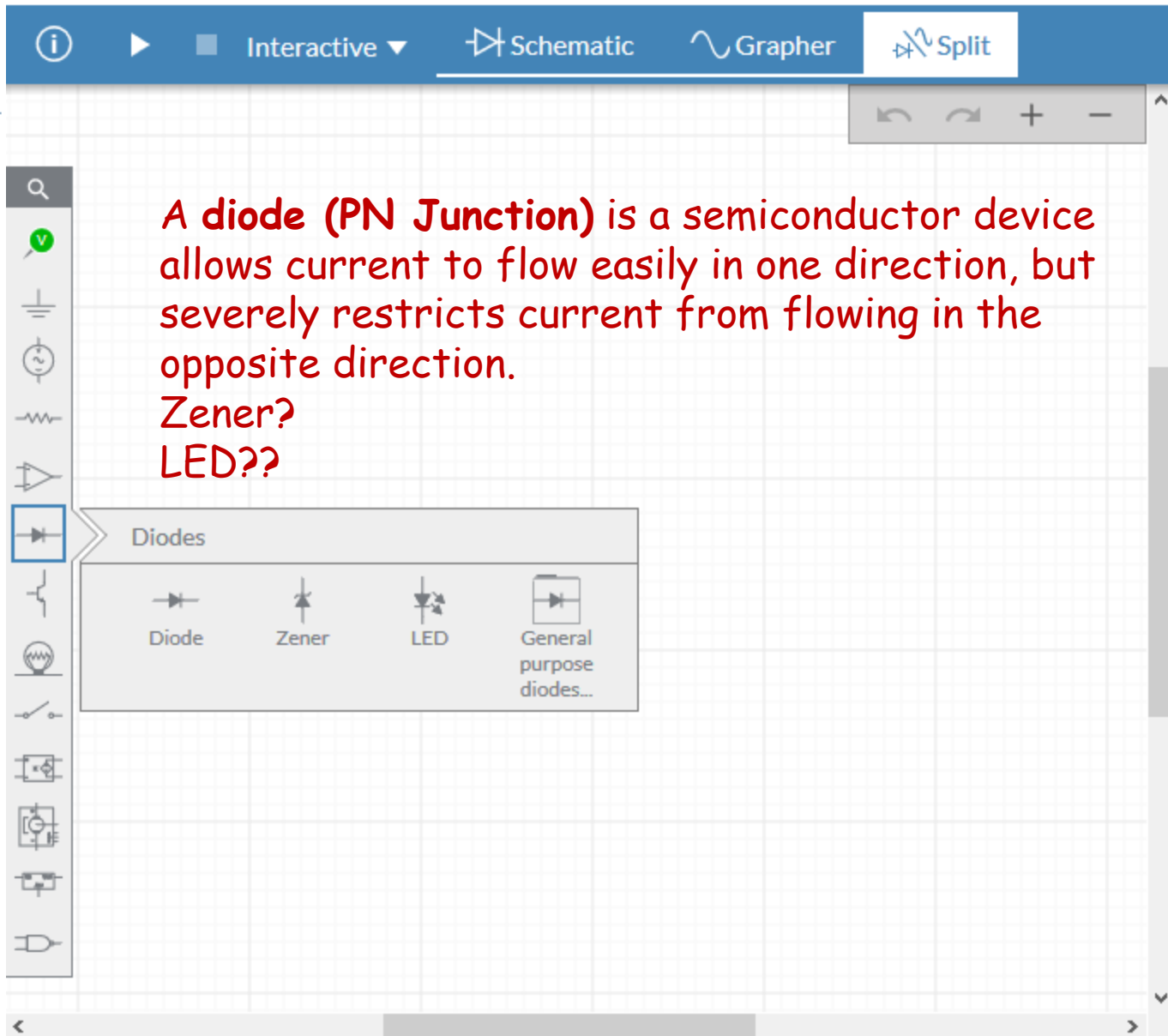
















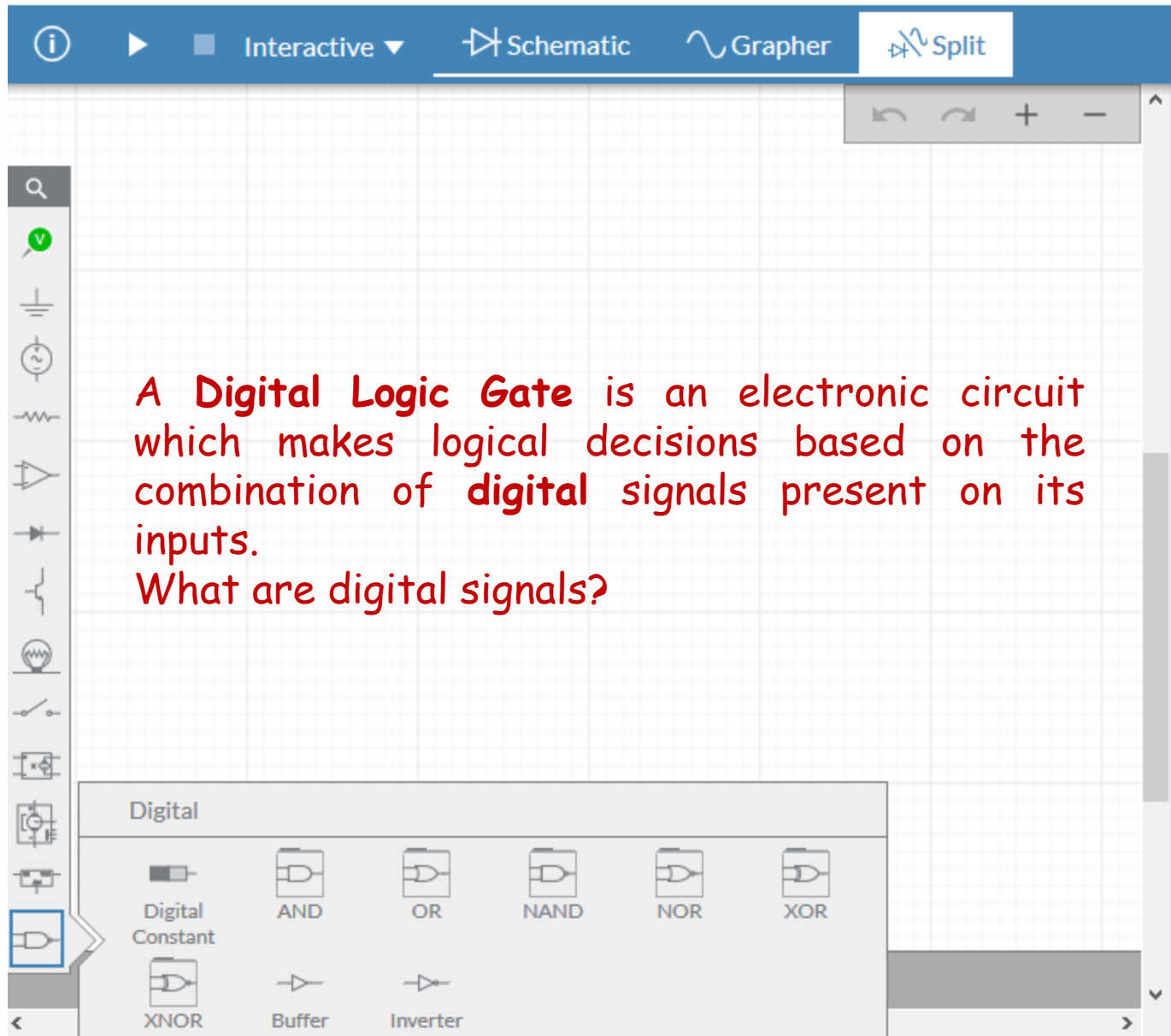
7


A transistor is a semiconductor device used to amplify or switch electronic signals and electrical power.

We'll explore more about these in upcoming labs...

Transistors


					
NPN	NPN 4T	PNP	PNP 4T	NMOS	NMOS 4T
					
PMOS	PMOS 4T	JFET N	JFET P	GaAsFET N	GaAsFET P
					
NPN...	PNP...	NMOS...			



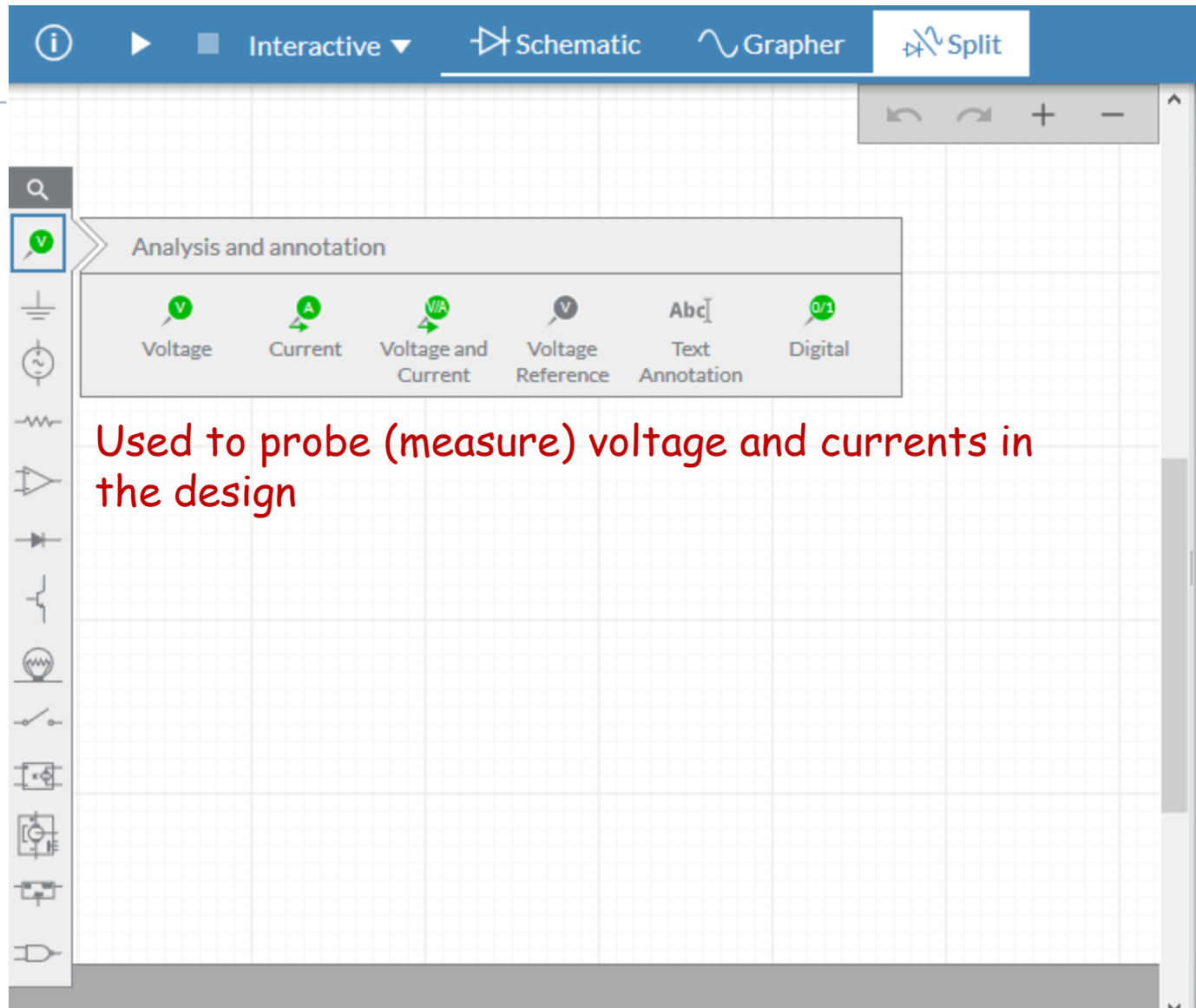


2

Identify please..

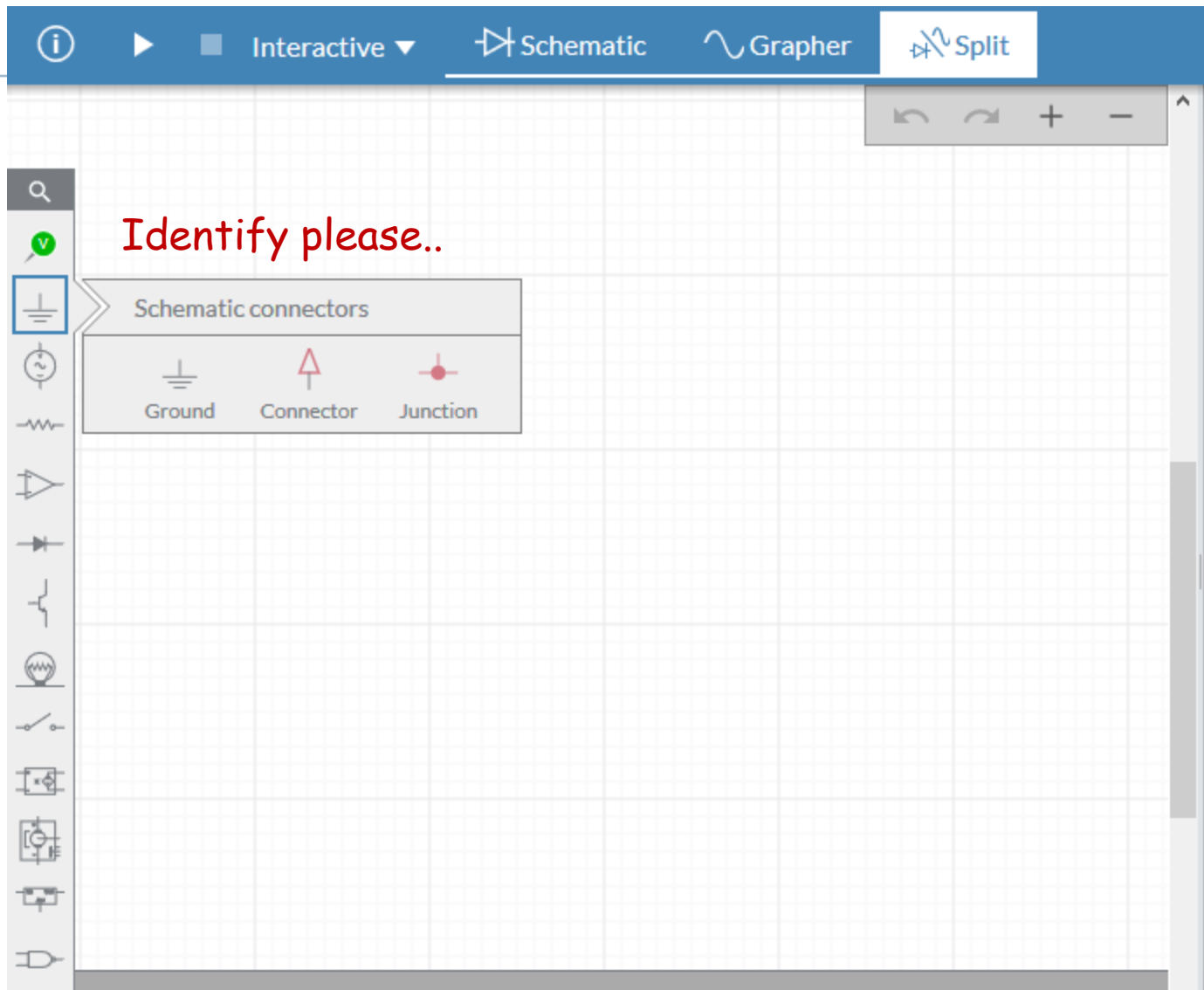


Lets Draw A simple Circuit


The screenshot displays a circuit simulation software window. The top menu bar includes tabs for 'Interactive', 'Schematic' (which is the active tab), 'Grapher', and 'Split'. Below the menu bar is a toolbar with navigation and editing icons. On the left, a vertical sidebar contains a search icon and a list of electronic components including a DC voltage source, an AC voltage source, a resistor, a diode, a capacitor, an inductor, a lamp, a switch, a MOSFET, a BJT, and a logic gate. The main workspace is a grid where a simple circuit is drawn. It consists of a DC voltage source labeled 'V1' with a value of '12V' and a resistor labeled 'R1' with a value of '1kΩ'. A red text overlay in the center-right of the workspace reads: 'Drag and Drop components to the schematic window.'

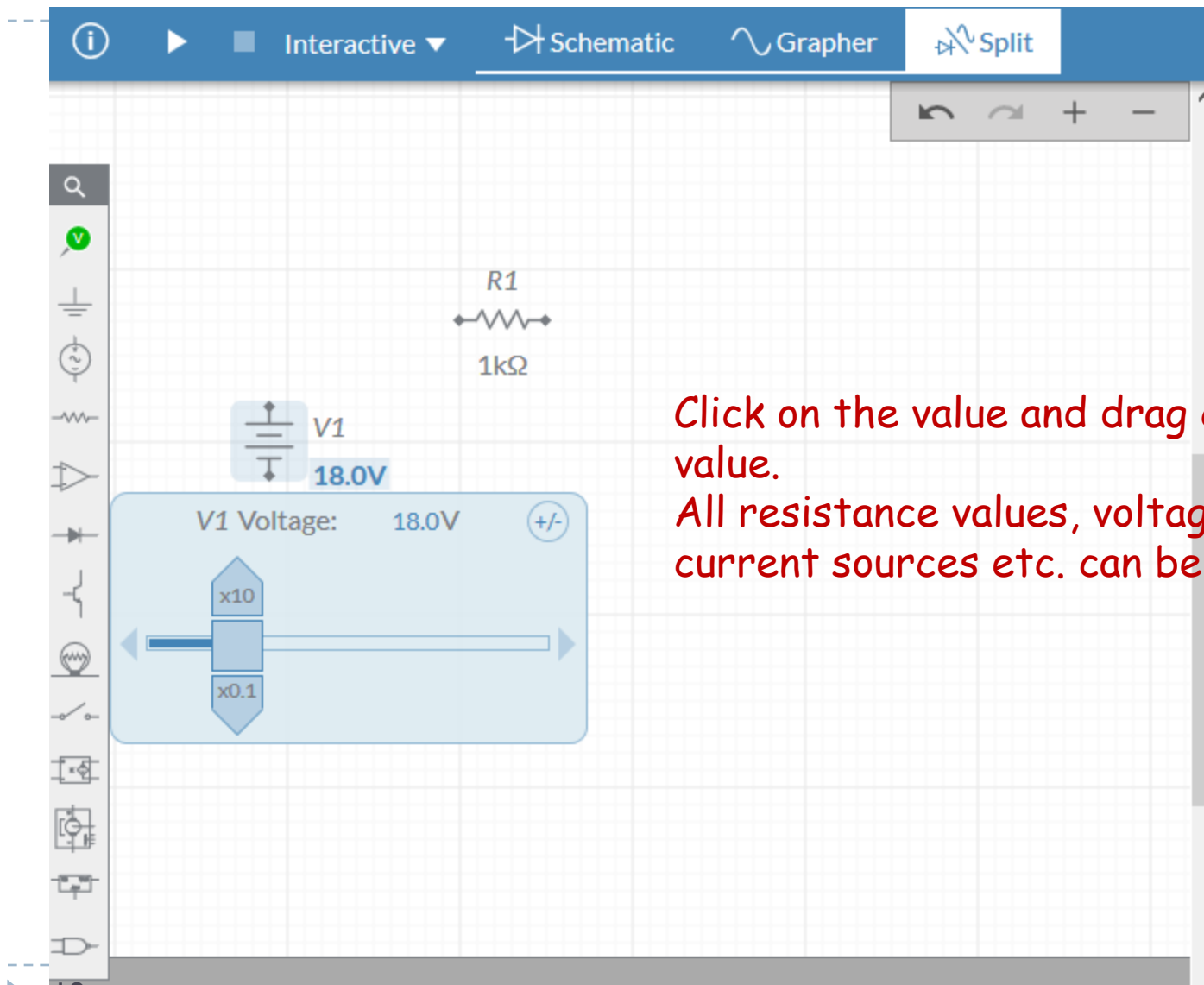

Click on the value and drag cursor to set the value.

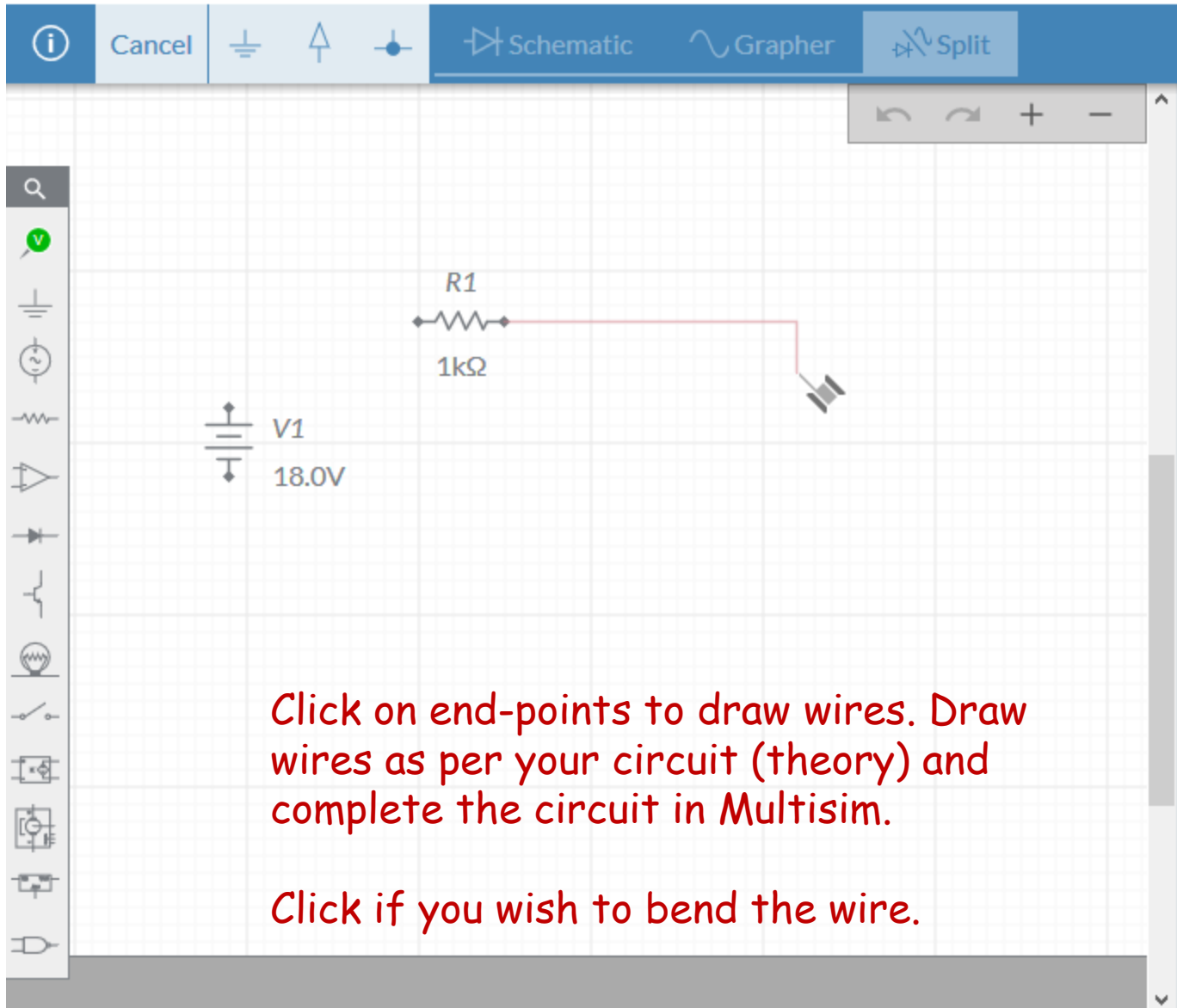All resistance values, voltage sources (values), current sources etc. can be set this way.



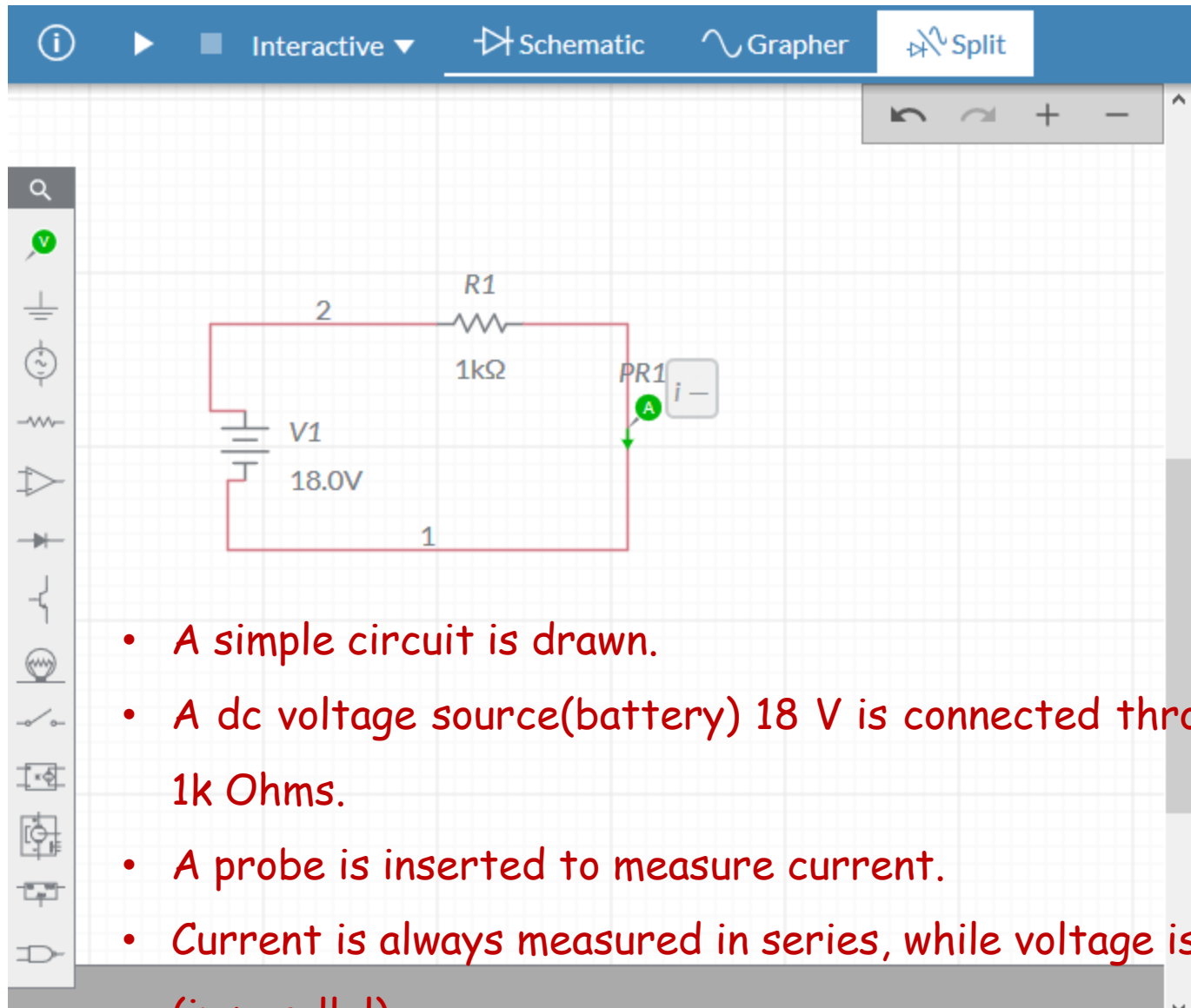

- The circuit is ready for analysis.

The screenshot shows a circuit simulation software interface. The top toolbar includes a play button (highlighted with a yellow box) and a dropdown menu for simulation types. The dropdown menu is open, showing options: Interactive, Transient (highlighted with a red box), AC Sweep, and DC Op. The circuit diagram shows a 18.0V DC voltage source (V1) connected in series with a 1kΩ resistor (R1). A probe (PR1) is connected across the resistor. The simulation menu is open, and the 'Transient' option is selected. A yellow arrow points to the play button icon, and a red arrow points to the 'Transient' option in the menu.

- Select the type of analysis as Transient.
- **Transient analysis** calculates a circuit's response over a period of time defined by the user.
- It usually is current vs time or voltage vs time
- The response will be current vs time in our case. Why?
- Guess the expected response!!
- Click start simulation



Transient




Schematic




Grapher



Split

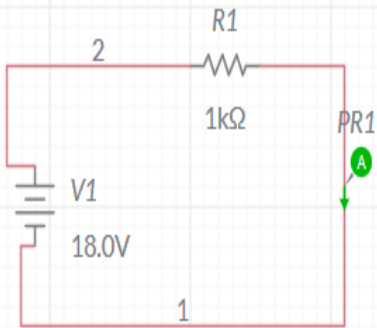


Transient 1

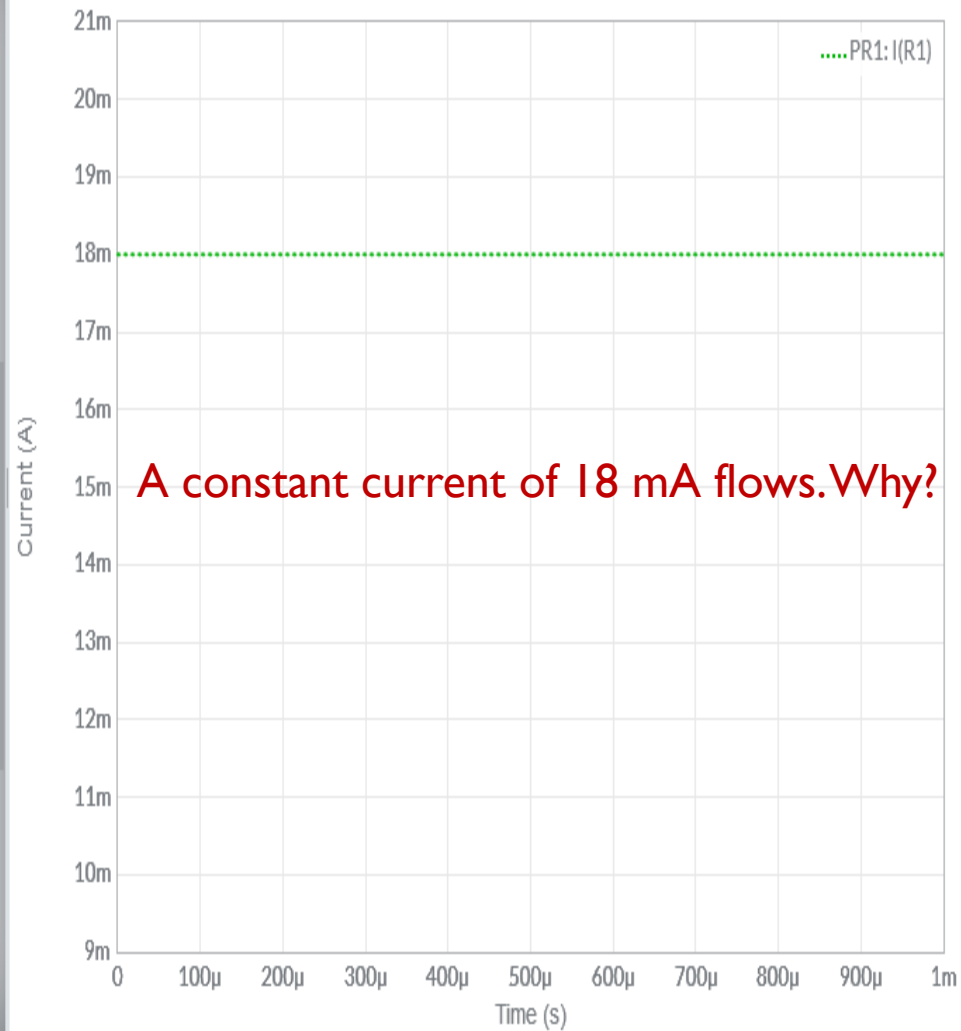

A constant current of 18 mA flows. Why?

A few examples...

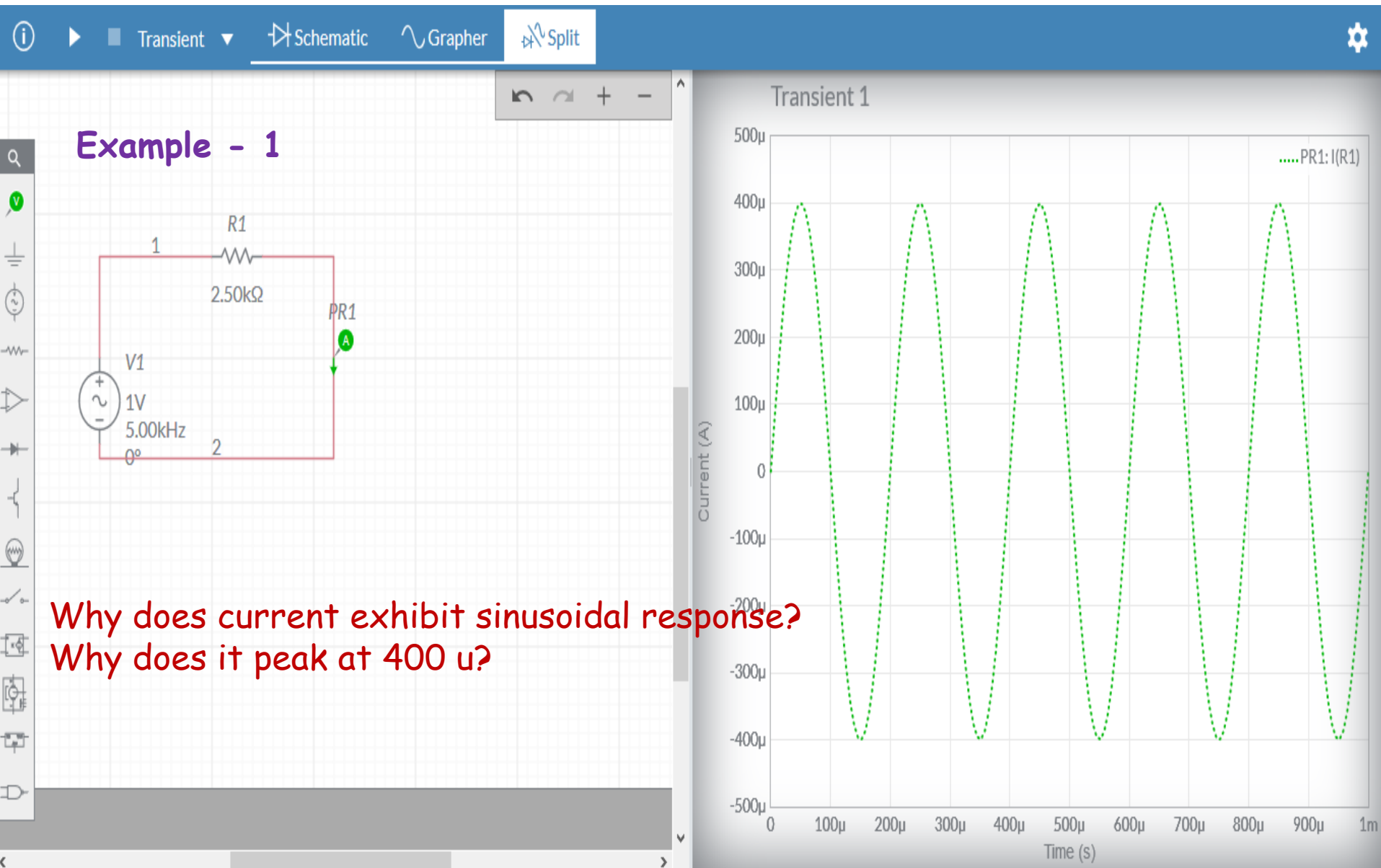



Transient



Schematic




Grapher



Split



Example - 2

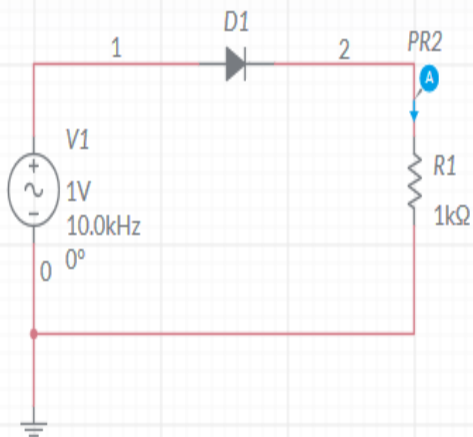


Why does the current become zero at some instance?

Why does current vary periodically?



What is drop across R1? What is drop across diode?

What is this circuit called?


Transient 1

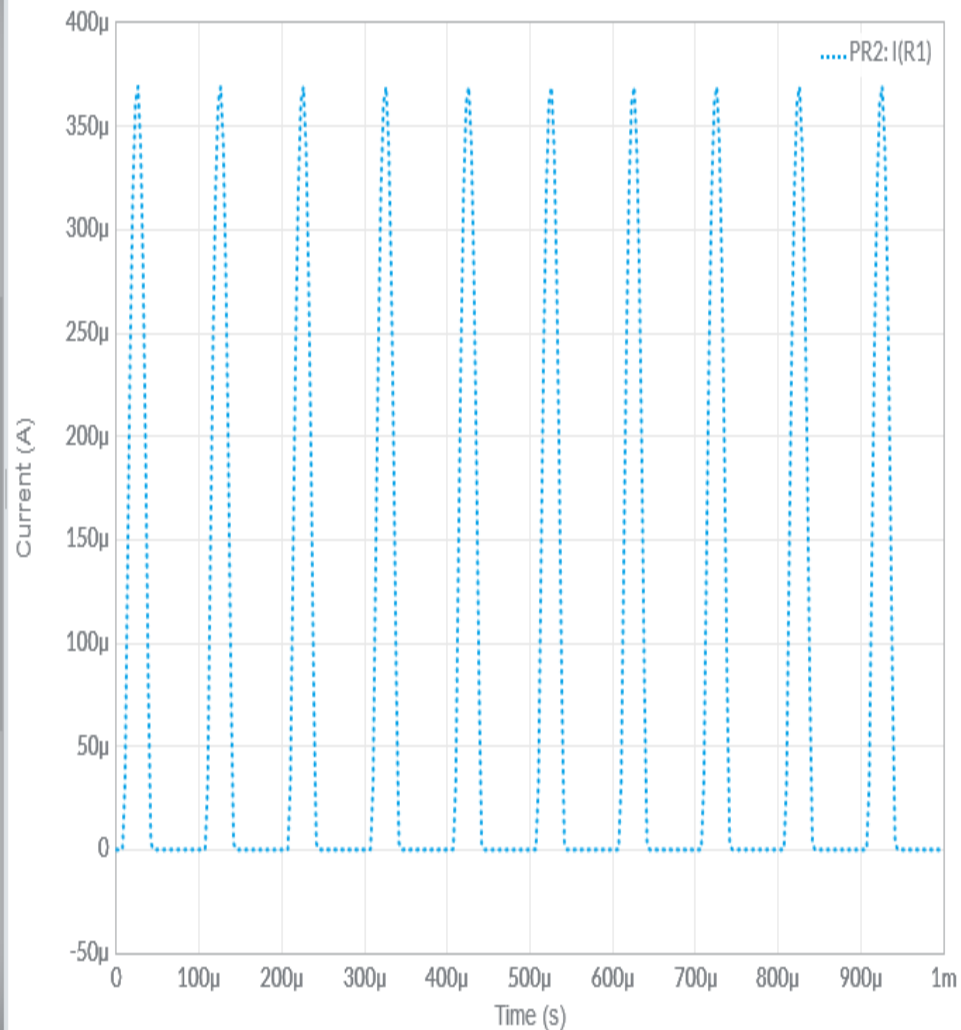

Example - 3

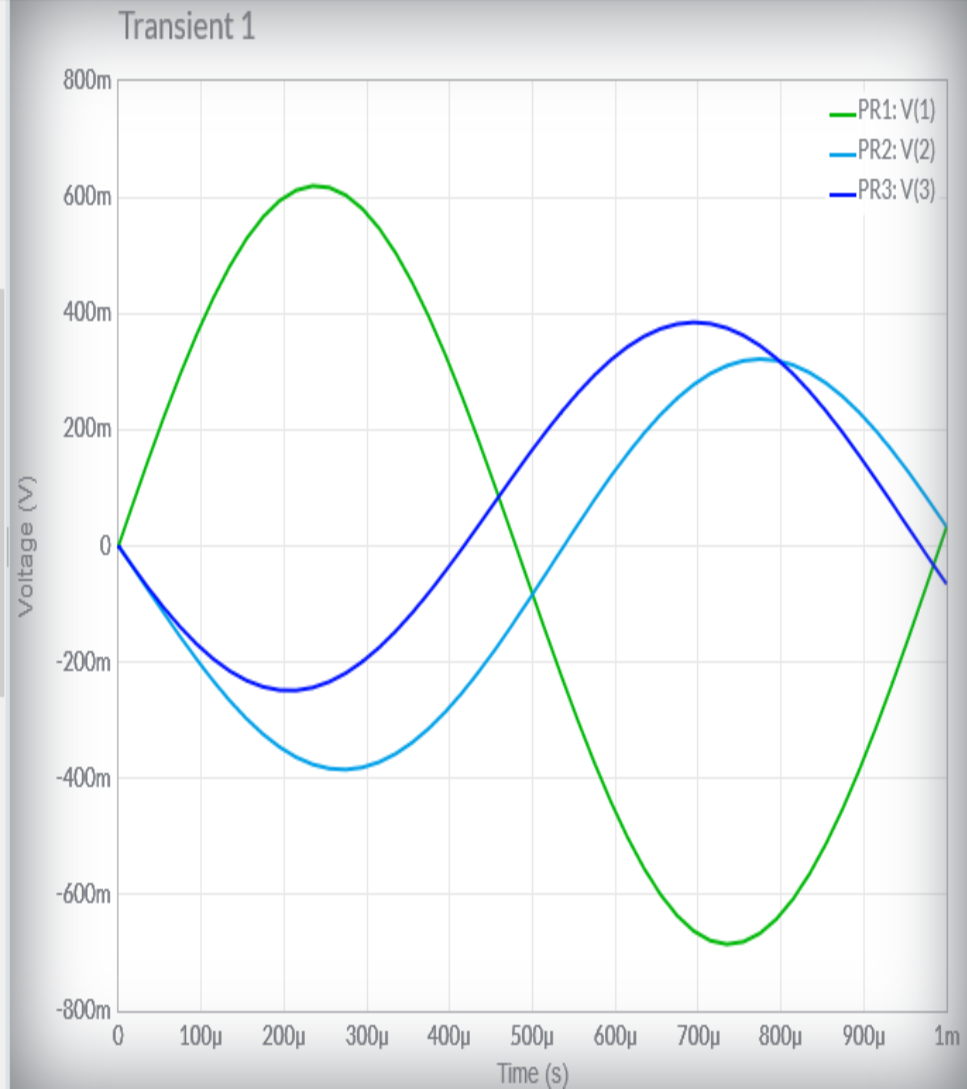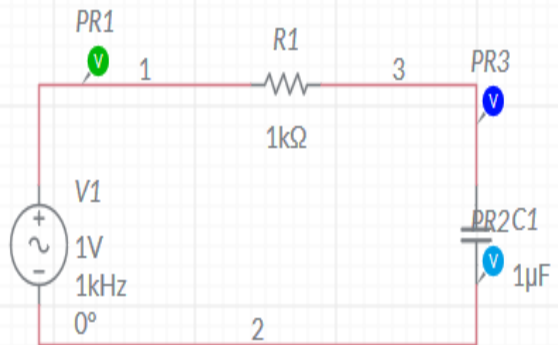


continued....

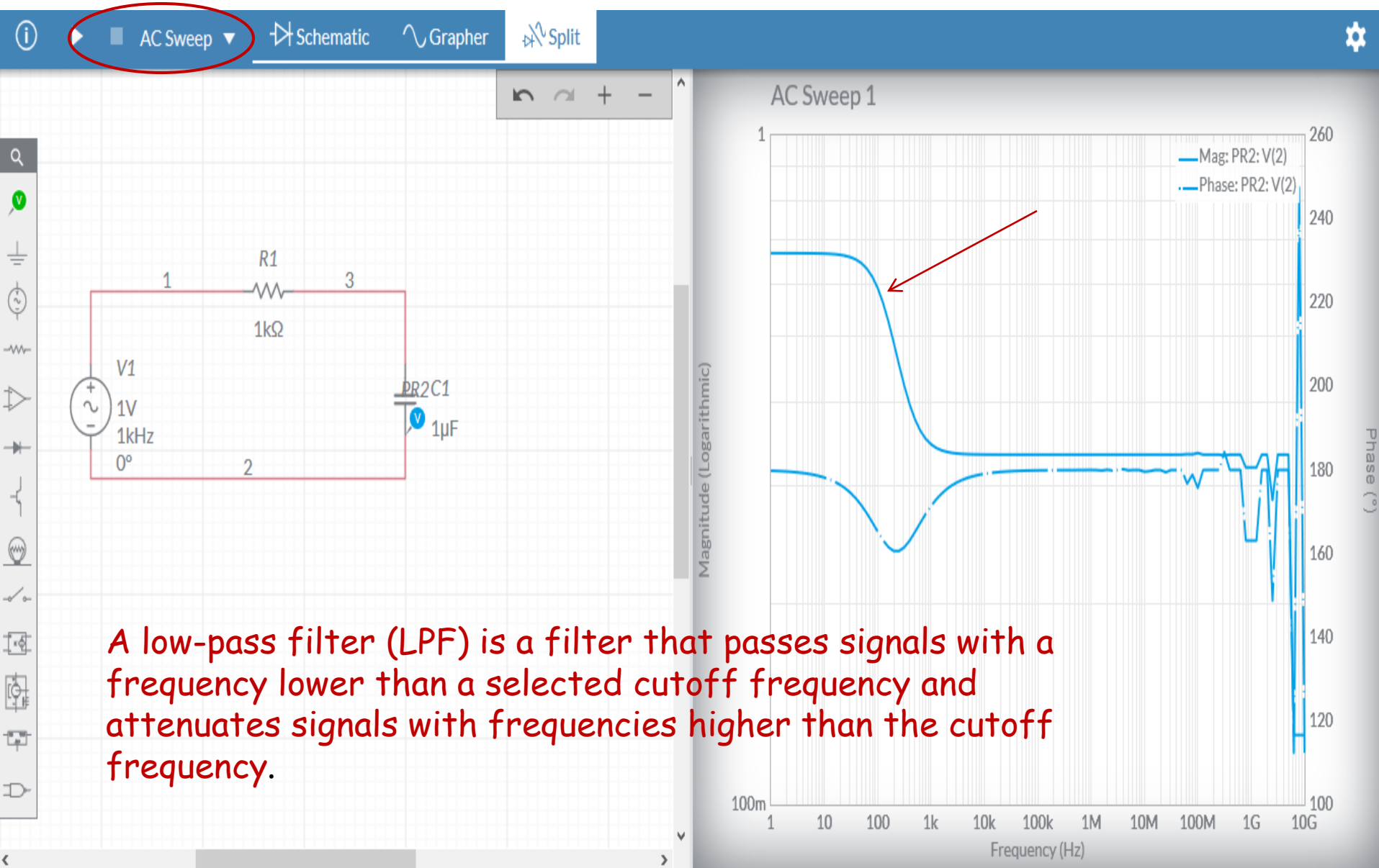


Example - 4

1.3133s Schematic Grapher Split

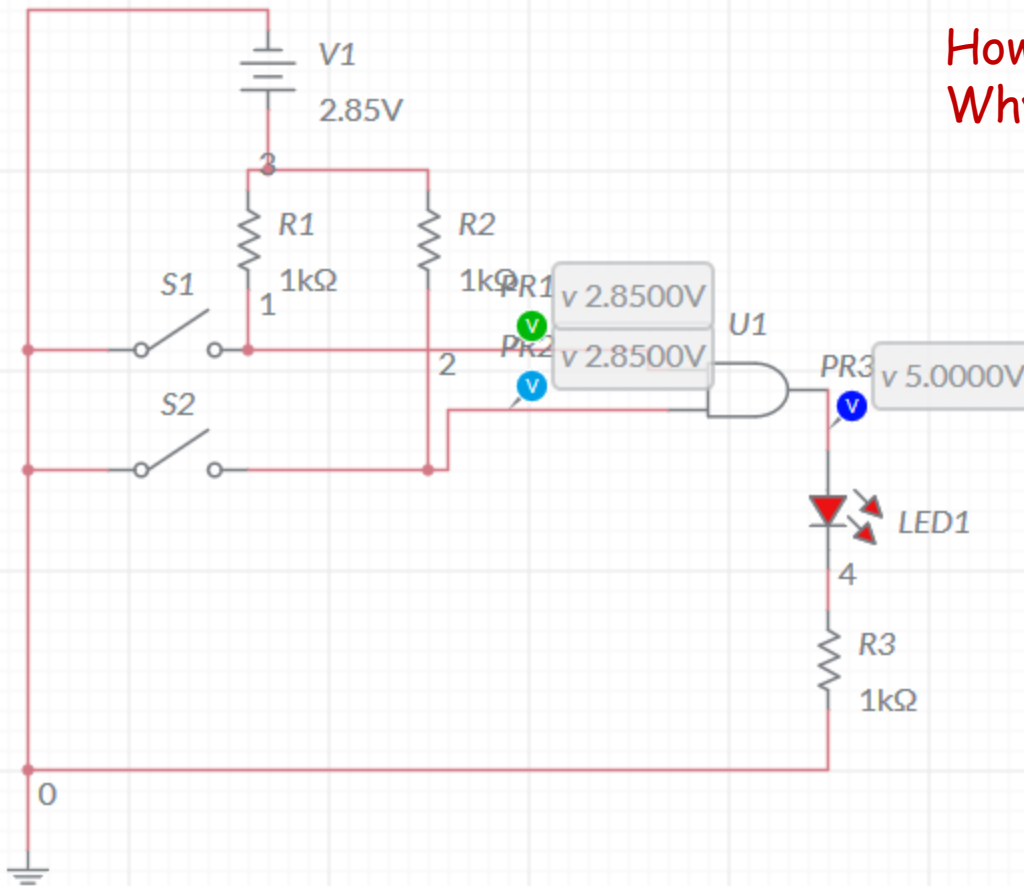

How does this circuit work?
Why is output 5V?

continued....

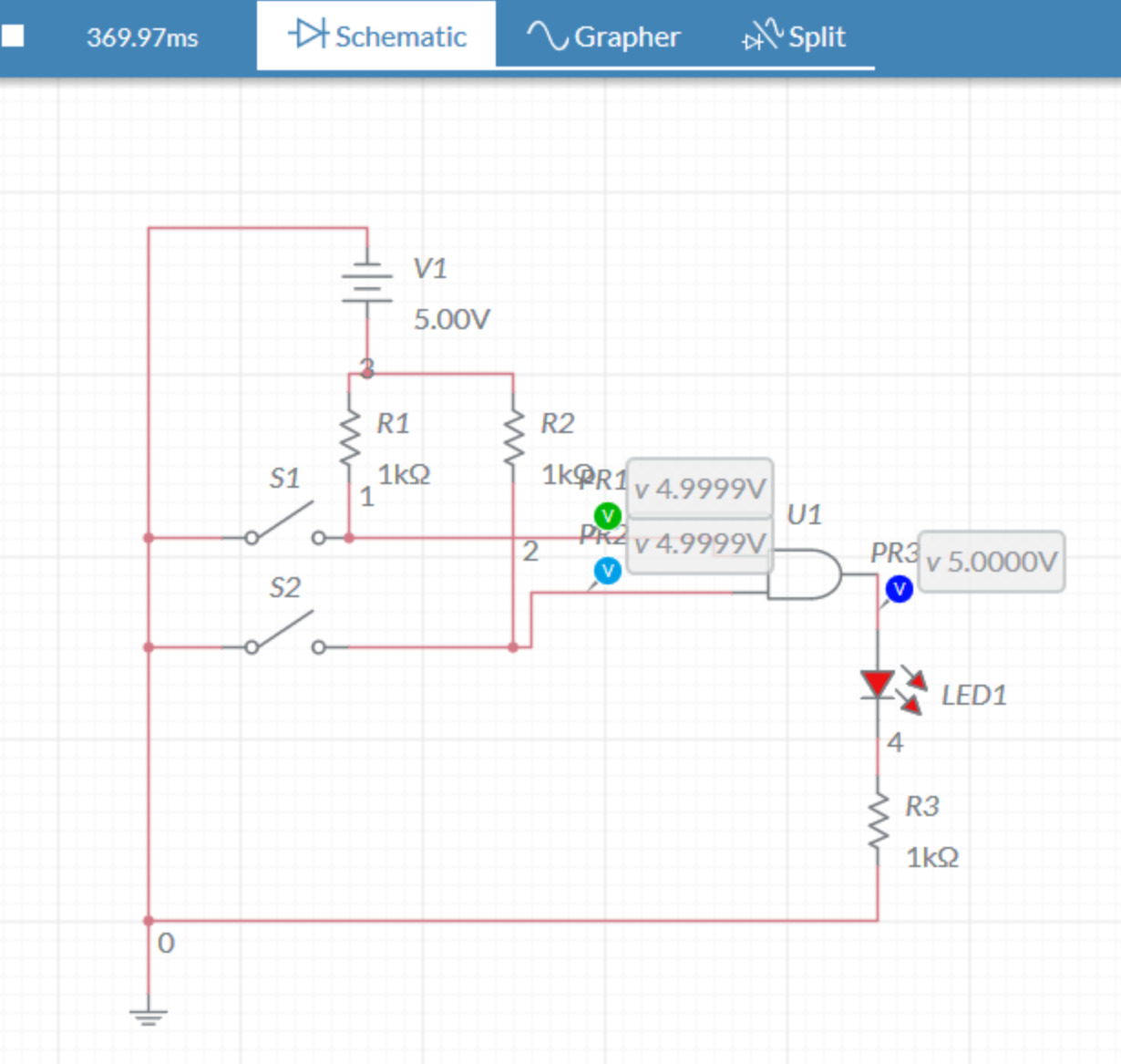


continued....

195.59ms


Schematic

Grapher

Split

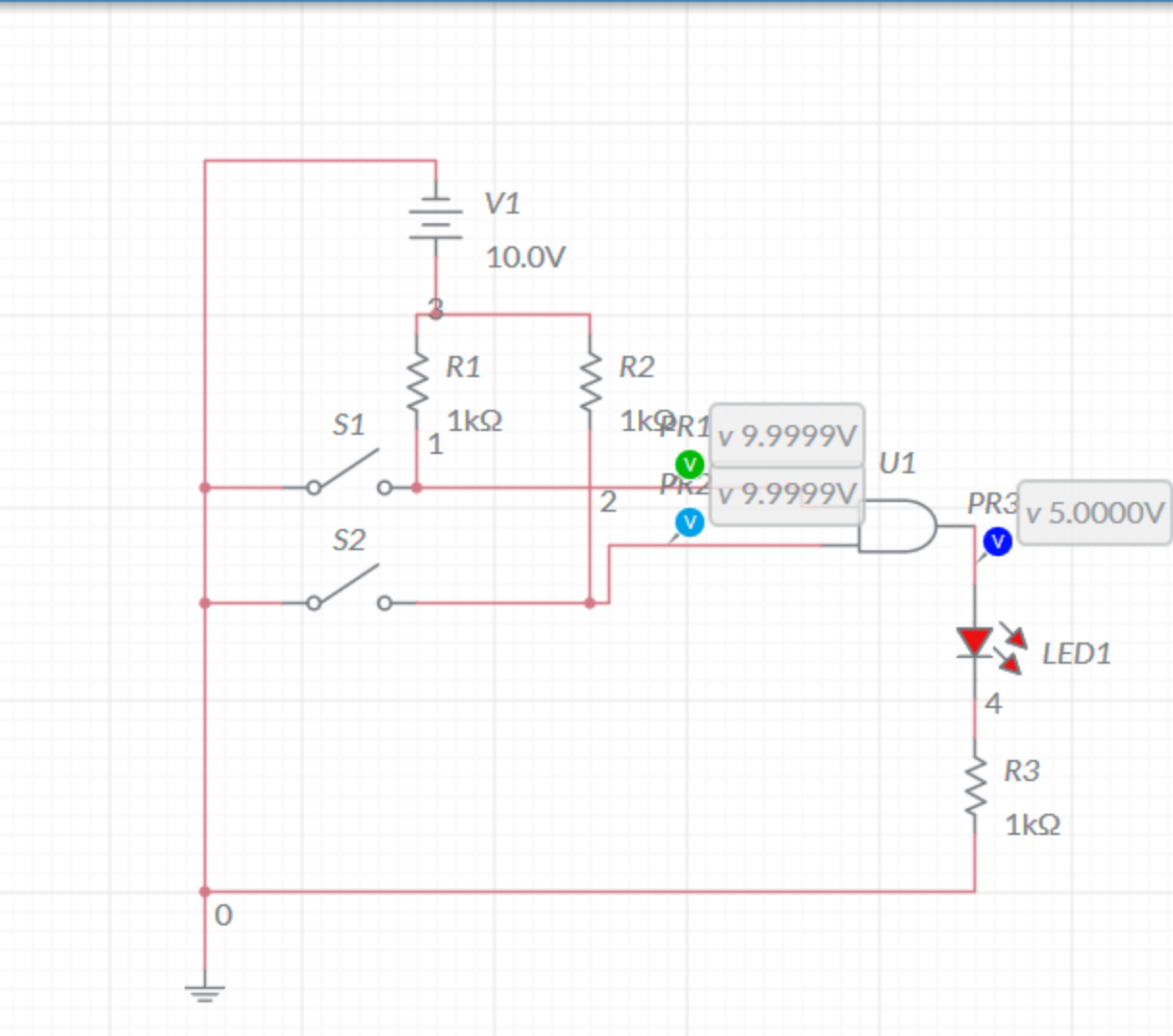


continued....

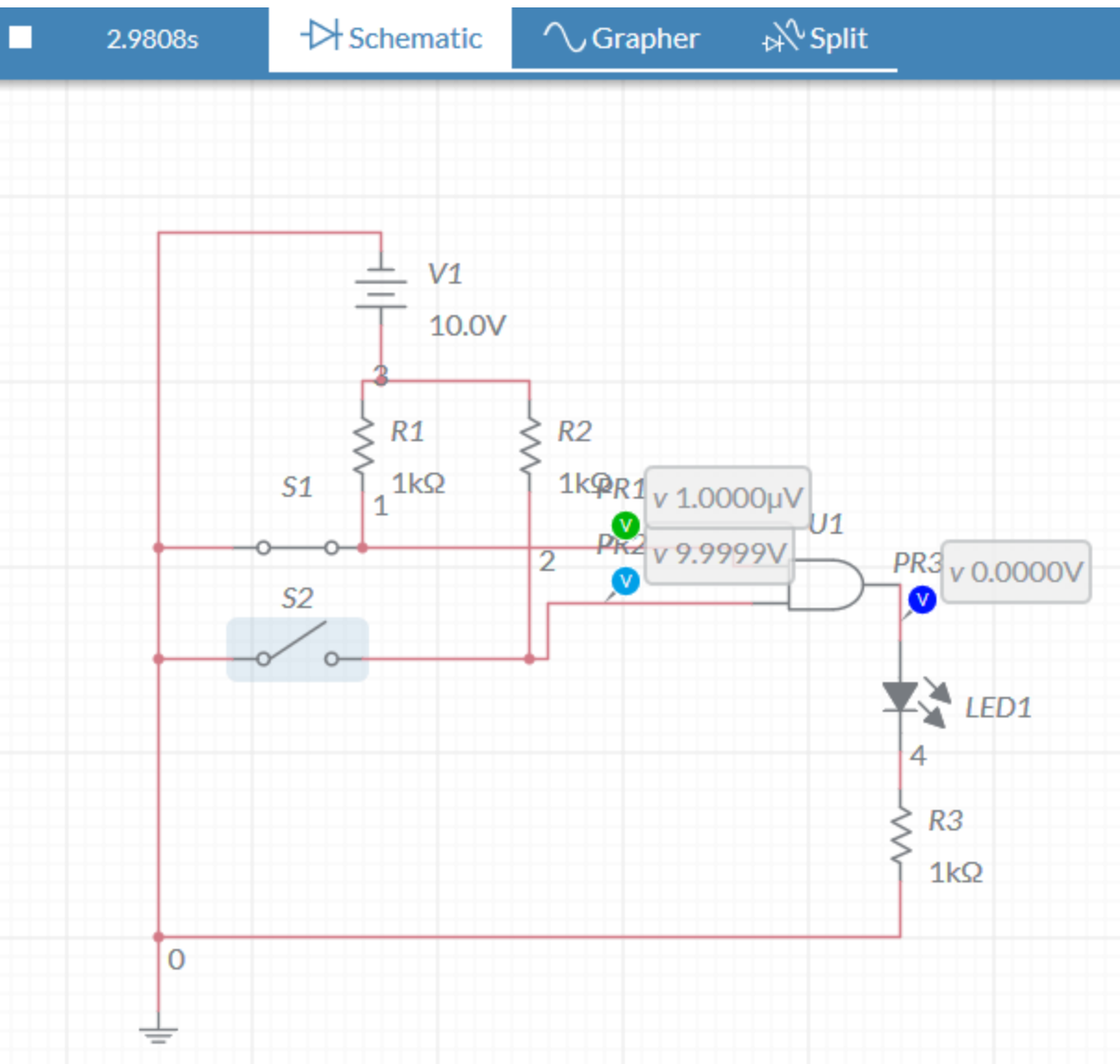


Conclusions?

Assignment - 1

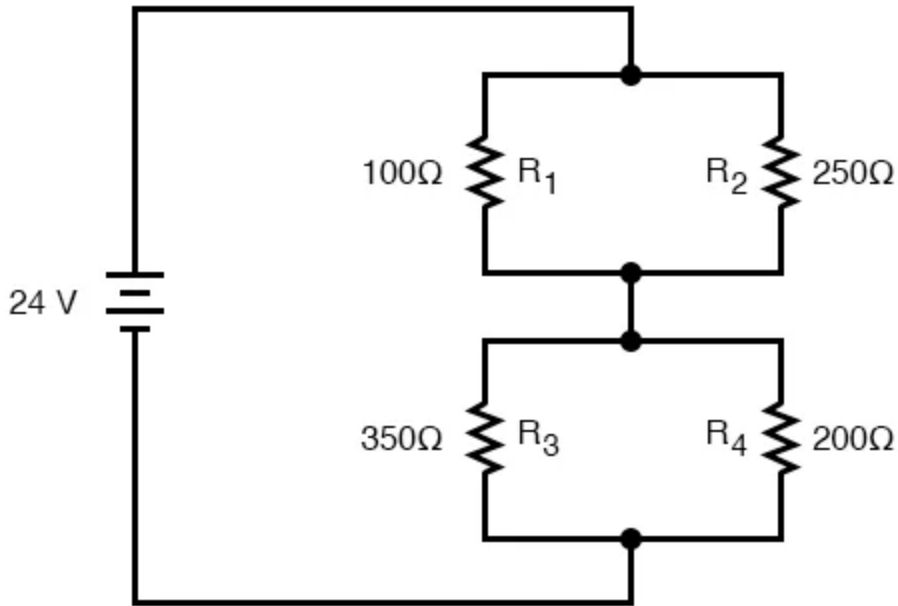

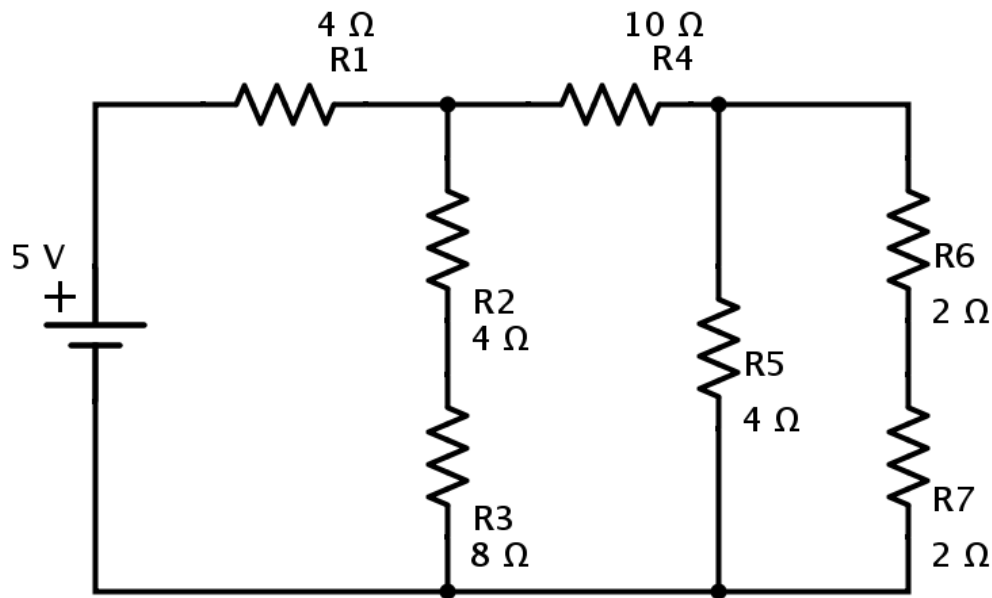- Implement the circuit as shown in Figure in Multisim online.
- Evaluate the current and voltage across each resistor using simulator.
- Compare with theoretical values.



Assignment - 2

- Implement the circuit as shown in Figure in Multisim online.
- Evaluate the current and voltage across each resistor using simulator.
- Compare with theoretical values.