



# DELD – Tutorial 4



**ECED SVNIT**

# Instructions For Tutorial Sessions

- Copy questions and work out detailed solutions in a neat and clean handwriting.
- Questions will be shown between 10.40 am to 11.20 am. In the next 10 minutes you need to scan and upload your work in a **PDF format only carrying only your Admission number.**
- Mention all the details viz Full Name, Admission No, Div, Date, Tutorial No. etc on First Page
- **If two handwritings are found similar, they both will be graded 0.**



# Question - 1

- Determine the decimal values of the signed binary numbers expressed in 1's complement form:

(a) 00010111

(b) 11101000



# Question - 2

- Evaluate following expressions using 2's complement arithmetic:

(a)  $00001000 - 00000011$

(b)  $00001100 - 11110111$

(c)  $11100111 - 00010011$

(d)  $10001000 - 11100010$



# Question - 3

- Convert each of the following decimal numbers to their equivalent BCD representation:

(a) 35


(b) 98

(c) 170

(d) 2469



# Clocked SR Flip-Flop

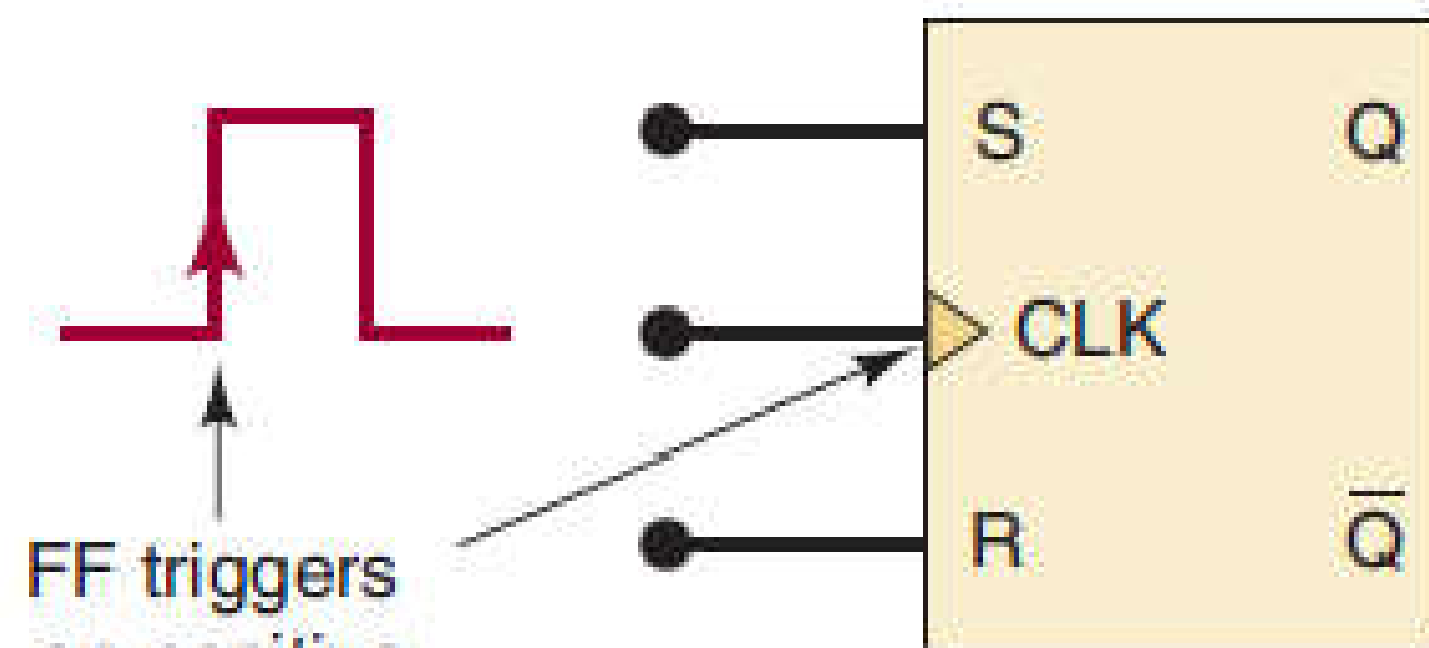

FF triggers  
on positive  
transition

(a)

Inputs			Output
S	R	CLK	Q
0	0	↑	$Q_0$ (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Ambiguous


$Q_0$  is output level prior to ↑ of CLK.  
↓ of CLK produces no change in Q.

(b)




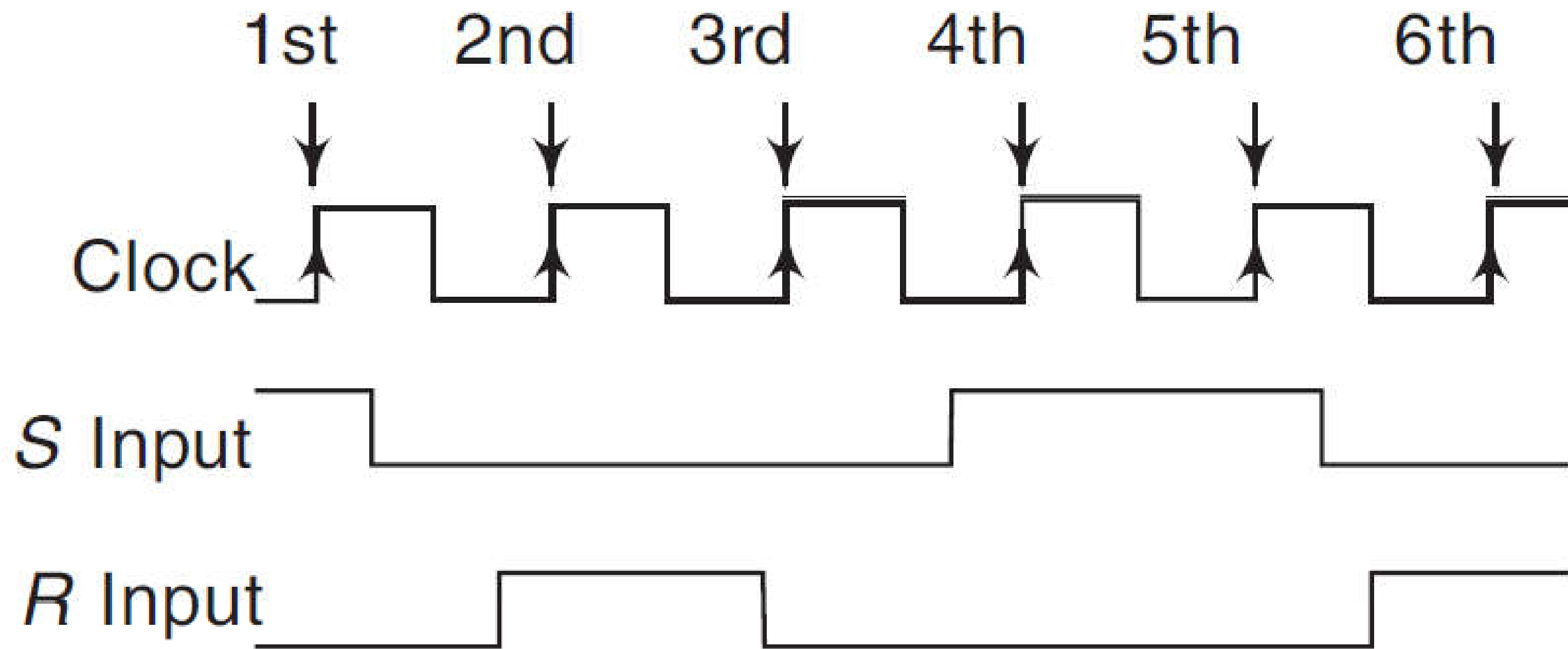
# Question - 4

- Assuming  $Q=0$  initially, Predict and draw the output waveform


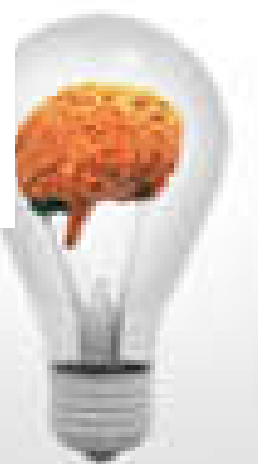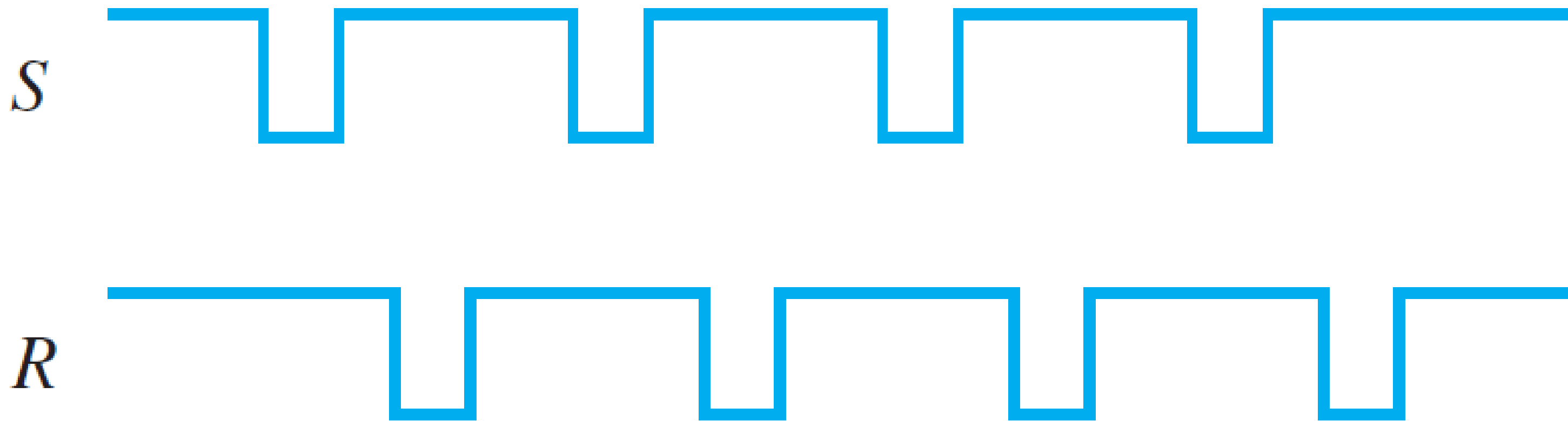
# Question - 5


- Assuming  $Q=0$  initially, if the following inputs are applied to an active low SR-Latch, predict and draw the output waveforms.




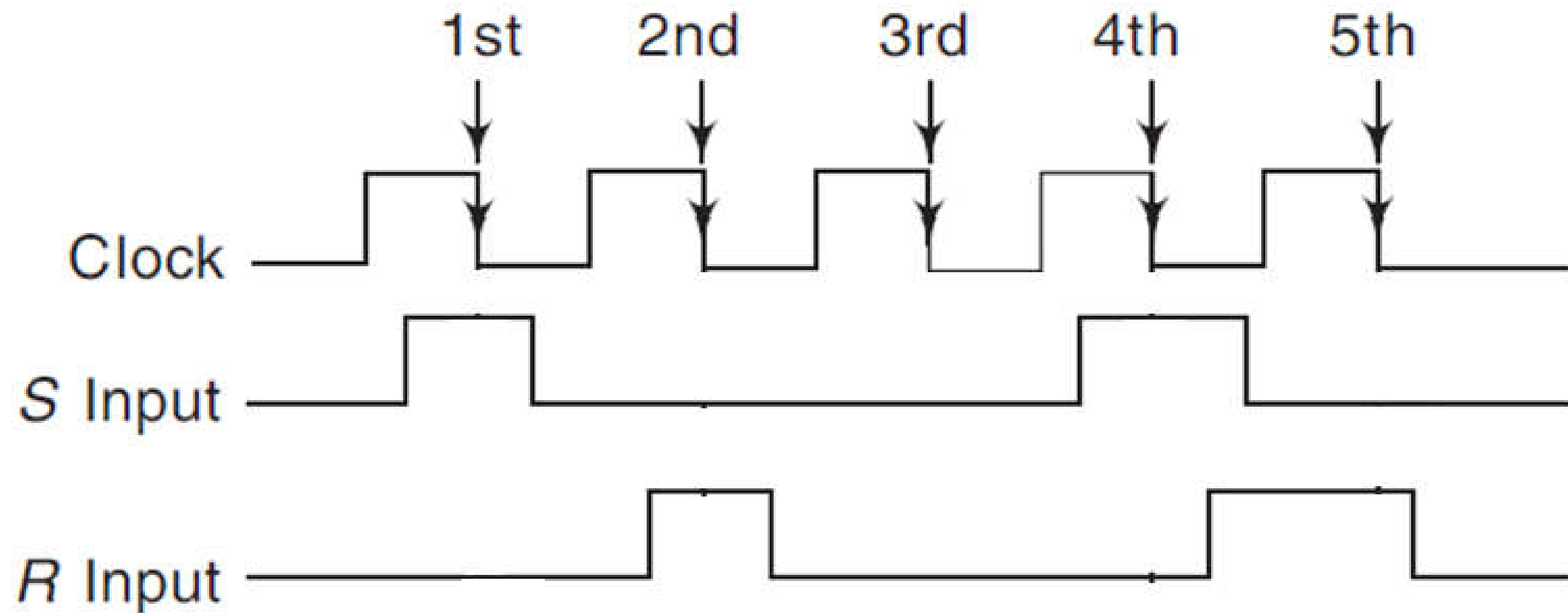
# Question - 6

- Assuming  $Q=0$  initially, Predict and draw the output waveform



# To Be Continued...

