

Analysis of Clocked (Synchronous) Sequential Circuits


- Now that we have flip-flops and the concept of memory in our circuit, we might want to determine what a circuit is doing.
- The behavior of a clocked sequential circuit is determined from its inputs, outputs and state of the flip-flops (i.e., the output of the flip-flops).
- The analysis of a clocked sequential circuit consists of obtaining a table of a diagram of the time sequences of inputs, outputs and states.
 - E.g., given a current state and current inputs, how will the state and outputs change when the next active clock edge arrives???

Analysis Procedure

- We have a basic procedure for analyzing a clocked sequential circuit:
 - Write down the **equations** for the **outputs** and the **flip-flop inputs**.
 - Using these equations, derive a **state table** which describes the next state.
 - Obtain a **state diagram** from the **state table**.
- It is the state table and/or state diagram that specifies the **behavior** of the circuit.
- Notes:
 - The **flip-flop input equations** are sometimes called the **excitation equations**.
 - The **state table** is sometimes called a **transition table**.
- We can best illustrate the procedure by doing examples...


Analysis Example

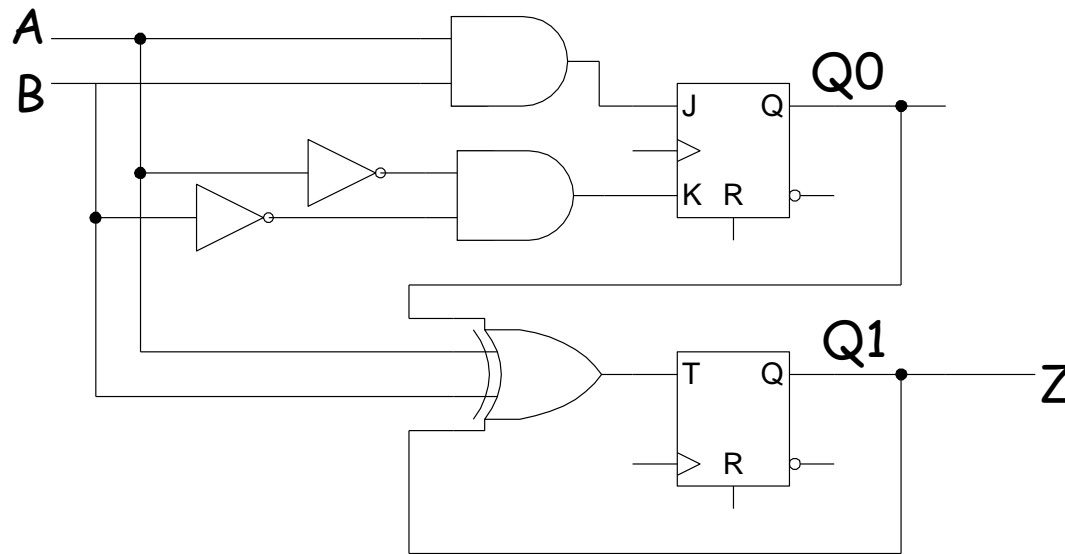- Consider the following circuit. We want to determine how it will behave.




- Observations: The circuit has two inputs **A** and **B**, one output **Z** (it happens that the output is equal to one of the flip flop outputs).

Analysis Example - More Observations

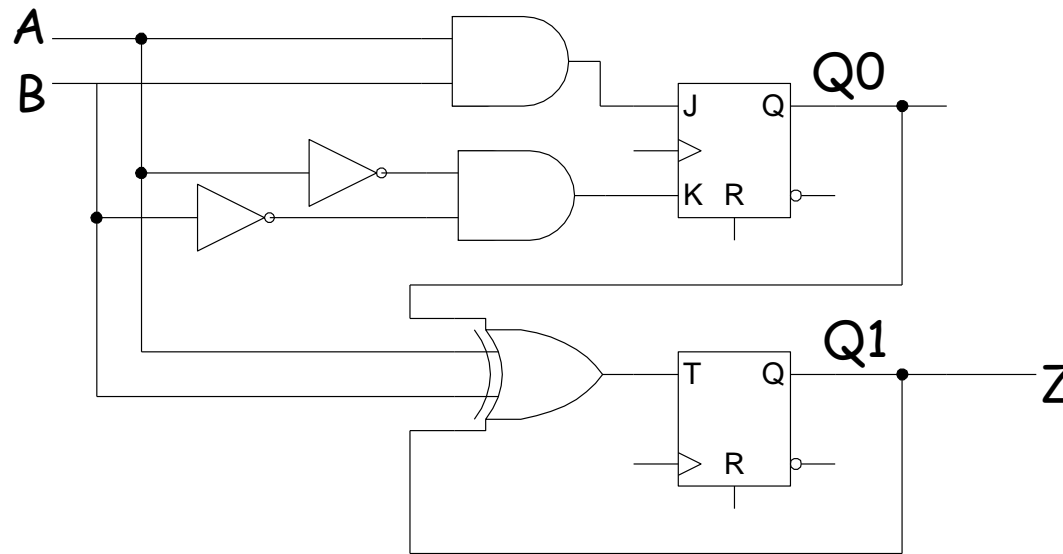

- Observations: The circuit has two flip-flops (different types) with outputs Q_0 and Q_1 (This implies that there are as many as 4 different states in the circuit, namely $Q_0Q_1 = 00, 01, 11, 10$).
- Observations: The circuit output depends on the current state (flip-flop outputs) only.

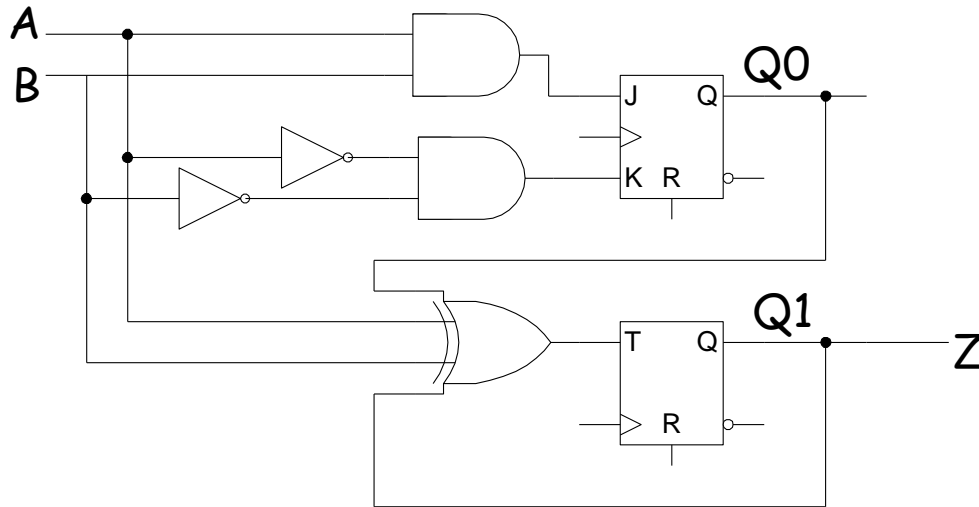Analysis Example - Flip-Flop Input Equations and Output Equations



$$Z = Q_1$$

$$J_0 = AB$$

$$K_0 = A'B'$$

$$T_1 = A \oplus B \oplus Q_0 \oplus Q_1$$

- We write down Boolean expressions for the FF inputs and the circuit outputs.
- Done in terms of the **circuit inputs** and the **current state** (flip-flop outputs) of the system.

Analysis Example - State Table

- Using the FF input equations, we can build a table showing the FF inputs (this is the first step in creating the state table):

| Current State Q_0Q_1 | J_0K_0 | | | | T_1 | | | |
|---------------------------|-----------|----|----|----|-----------|----|----|----|
| | $AB = 00$ | 01 | 10 | 11 | $AB = 00$ | 01 | 10 | 11 |
| 00 | 01 | 00 | 00 | 10 | 0 | 1 | 1 | 0 |
| 01 | 01 | 00 | 00 | 10 | 1 | 0 | 0 | 1 |
| 10 | 01 | 00 | 00 | 10 | 1 | 0 | 0 | 1 |
| 11 | 01 | 00 | 00 | 10 | 0 | 1 | 1 | 0 |

$$Z = Q_1$$

$$J_0 = AB$$

$$K_0 = A'B'$$

$$T_1 = A \oplus B \oplus Q_0 \oplus Q_1$$

Analysis Example - State Table Continued

- We now have the FF input values, and know the FF behavior (for both JKFF and TFF):

| Current State Q_0Q_1 | J_0K_0 | | | | T_1 | | | |
|---------------------------|-----------|----|----|----|-----------|----|----|----|
| | $AB = 00$ | 01 | 10 | 11 | $AB = 00$ | 01 | 10 | 11 |
| 00 | 01 | 00 | 00 | 10 | 0 | 1 | 1 | 0 |
| 01 | 01 | 00 | 00 | 10 | 1 | 0 | 0 | 1 |
| 10 | 01 | 00 | 00 | 10 | 1 | 0 | 0 | 1 |
| 11 | 01 | 00 | 00 | 10 | 0 | 1 | 1 | 0 |

| J | K | $Q(t+1)$ |
|-----|-----|----------|
| 0 | 0 | $Q(t)$ |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | $Q'(t)$ |

JKFF Behavior

| T | $Q(t+1)$ |
|-----|----------|
| 0 | $Q(t)$ |
| 1 | $Q'(t)$ |

TFF Behavior

- We can then determine the next FF output values:

| Current State Q_0Q_1 | Next State Q_0 | | | | Next State Q_1 | | | |
|------------------------|------------------|----|----|----|------------------|----|----|----|
| | $AB = 00$ | 01 | 10 | 11 | $AB = 00$ | 01 | 10 | 11 |
| 00 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 01 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 10 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 11 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |

Analysis Example - State Table Summarized

- We can (finally) write the next state information and the output values (based on current state and input values) in the **state table** format:

| Current State Q_0Q_1 | Next State Q_0Q_1 | | | | Output Z | | | |
|------------------------|---------------------|------|------|------|------------|------|------|------|
| | $AB = 00$ | 01 | 10 | 11 | $AB = 00$ | 01 | 10 | 11 |
| 00 | 00 | 01 | 01 | 10 | 0 | 0 | 0 | 0 |
| 01 | 00 | 01 | 01 | 10 | 1 | 1 | 1 | 1 |
| 10 | 01 | 10 | 10 | 11 | 0 | 0 | 0 | 0 |
| 11 | 01 | 10 | 10 | 11 | 1 | 1 | 1 | 1 |

state table

- Observation: The output **Z** (in this example) is only a function of the current state; it does not depend on the inputs.

Analysis Example - State Table Alternative Representation


- We can also write the state table in a slightly different (tabular) format if we choose. The information presented is the same.

| Current State | | Input | | Next State | | Output |
|---------------|-------|-------|-----|------------|-------|--------|
| Q_0 | Q_1 | A | B | Q_0 | Q_1 | Z |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 |

alternative state table

State Diagram

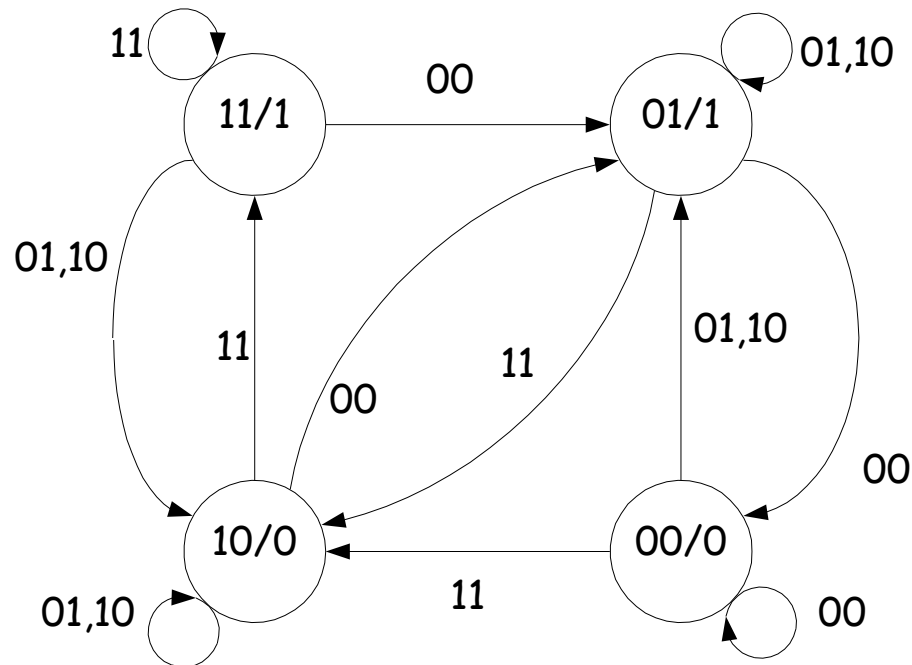- Another way to illustrate the behavior of a clocked sequential circuit is with a **state diagram**.



State Diagram Explained

- Each “bubble” (**state bubble**) in the state diagram represents one state of the system.
 - The flip-flop outputs that correspond to that state are **labeled** inside of the bubble.
- Each edge leaving a bubble represents a possible transition to another state once the active clock edge arrives.
 - The edges are **labeled** with the input values that cause the transition to occur.
- In this state diagram, the **output values** are **labeled** inside of the state bubbles.
 - We can do this because the outputs are only a function of the current state in this example.