



# Sardar Vallabhbhai National Institute of Technology, Surat

## Electronics Engineering Department

End Semester Examination, December – 2020, AY-20/21

**Subject: Digital Electronics and Logic Design (EC-207)**

Date: 09-12-2020

Time: 3 Hrs

Maximum Marks: 50

### Instructions:

1. This Question Paper Comprises of Five questions.
2. Figures to the right indicate the Maximum Marks assigned to the question.
3. Assume suitable data wherever necessary.
4. The Total time of 3 Hrs includes the time for scanning and uploading.
5. Use A4 Sheets to write answers. Mention your Admission No, Full Name and Sign on each page.

- Q.1 A** Propose and draw a circuit/circuits that can produce the waveform in Fig.1(b) from Fig.1(a). Assume non-ideal Si diodes. 4

 


Fig. 1(a)



 


Fig. 1(b)

 - B** For the circuit shown below, derive the relation between input and output. Also calculate the output voltage  $V_o$  at  $t = 6$  milli second. 3



 
- C** Predict the task performed by each stage of a two stage circuit shown below. Note that the two stages are connected using connectors. Also draw the output waveform. Given ( $R_1C_1 \gg T$ ) and ( $R_2C_2 \ll T$ ). 3




- Q.2 A** A 4 – Bit BCD Logic circuit is to be designed which can distinguish the digits that are greater than or equal to 5 from those that are less than 5. Considering the inputs as BCD numbers, design and implement the circuit (using basic logic gates) which will perform the said task. Use K-Map to simplify the expressions. 4

 **OR**

- A** Assuming  $A_3, A_2, A_1, A_0$  as inputs applied to a Parity Logic Circuit shown in figure below. Predict how many times even parity occurs? The timing diagram includes 8-bit intervals. Append the Parity bit with  $A_3A_2A_1A_0P$  (P-Parity) for all the eight input combinations. 4




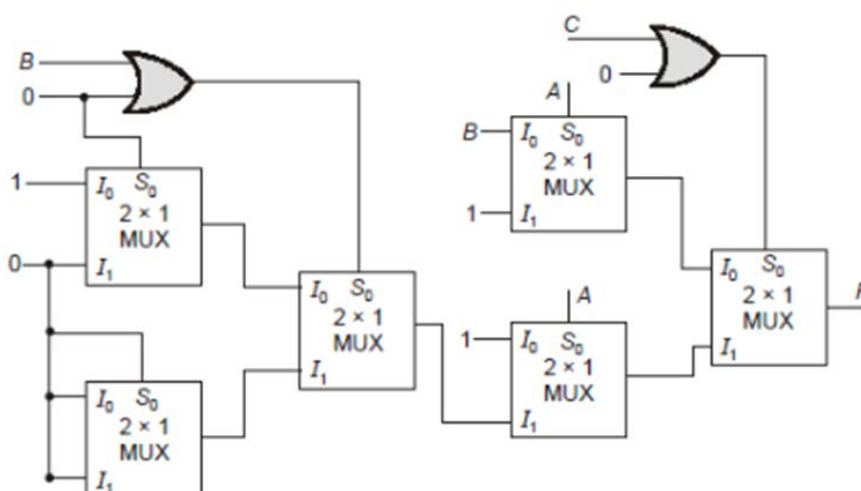- B** Determine the output expression for F in the below given circuit. Also predict the number of input combinations for which the output will be high. Draw Truth Table. 4



- C** Assuming Functions P and Q represent the Sum and Carry outputs of a Full – Adder, predict the number of input combinations for which the LED will glow. Assume Logic ‘0’ – 0 Volts and Logic ‘1’ – 5 Volts. 2

X	Y	Z	P	Q
0	0	0		
0	1	0		
0	1	1		
1	0	0		
1	1	0		
1	1	1		
0	0	1		

 


- Q.3 A** Design an Universal Shift Register to perform Shifting/Loading as per the following select inputs: 4

S1	S0	Operation
0	0	Shift Right
0	1	Parallel Shift
1	0	No Change
1	1	Shift Left


- B** The following serial data are applied to the flip-flop through via AND gates as indicated in Figure below. Determine the resulting bit-pattern data that appears on the  $Q$  output. Predict and draw the output waveform for (6 Clock-Pulses). There is one clock pulse for each bit time. Assume that  $Q$  is initially 0 and that  $PRE'$  and  $CLR'$  are HIGH. Also that the, rightmost bits are applied first. 4

 $J_1: 1\ 0\ 1\ 0\ 0\ 1\ 1;$      $J_2: 0\ 1\ 1\ 1\ 0\ 1\ 0;$      $J_3: 1\ 1\ 1\ 1\ 0\ 0\ 0$   
 $K_1: 0\ 0\ 0\ 1\ 1\ 1\ 0;$      $K_2: 1\ 1\ 0\ 1\ 1\ 0\ 0;$      $K_3: 1\ 0\ 1\ 0\ 1\ 0\ 1$




- C** The Flip-Flop below is tested for following four conditions. Is it working correctly or has a Fault? Describe your conclusion in detail. If faulty, write down what could be the possible reasons behind the fault? 2


Condition - 1

 


Condition - 2

 

Condition - 3

 

Condition - 4

 

- Q.4 A** Design an Asynchronous Down Counter using T-Flip Flops which will count the following sequence 0 – 14 – 10 – 8 – 7 – 5 – 3 - 0.....Also draw the connection diagram. 5
- B** Based on the waveforms in Fig. 4(a), what can be the most likely problem with the register circuit in Fig. 4(b)? Describe in detail. 3

 


Fig. 4(a)

 


Fig. 4(b)

- C** Using a single opamp, design a circuit to produce the following output voltage. Assume  $C=2$  micro Faraday. 2

$$v_o = - \int_0^t (v_1 + 4v_2 + 10v_3) dt$$


- Q.5 A** The following sequence of operations is performed in the Accumulator: 6

$$\begin{aligned} p_3: & A \leftarrow \bar{A} \\ p_9: & A \leftarrow A + 1 \\ p_1: & A \leftarrow A + B \\ p_3: & A \leftarrow \bar{A} \\ p_9: & A \leftarrow A + 1 \end{aligned}$$

- Determine the content of A after each micro-operation, if initially  $A=1101$  and the input  $B = 0110$ .
- Repeat for  $A = 0110$  and  $B = 1101$ .
- Predict the operation performed by the stated sequence of micro-operations.

- B** For the below circuit, considering  $x=B(A+C')$ , 4

 - Write down Present State and Next State Table
- Determine the Modulus M



----- All The Best -----