

END SEMESTER EXAM

[U19CS012]

SUBJECT : DIGITAL ELECTRONICS & LOGIC DESIGN (EC207)

ROLL NO : U19CS012

NAME : BHAGYA VINOD RANA

DIVISION : A

BRANCH : COMPUTER SCIENCE ENGINEERING (CSE)

No. of Pages :

Sign :

Bhagya

Q1. (A)


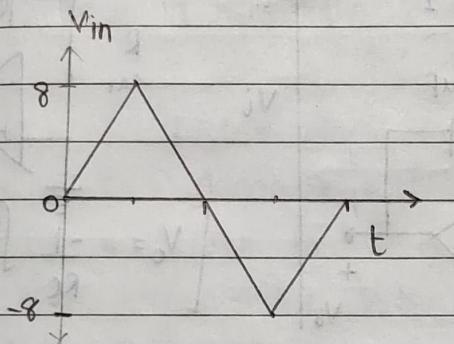


Fig 1(a)

Positive shunt diode clipper

with Bias-II

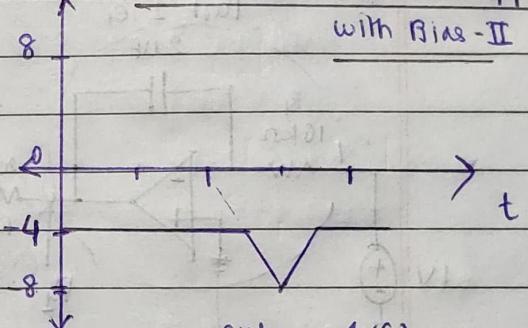


output 1(c)


Step ②

Positive clumper with positive bias


Step 1 :

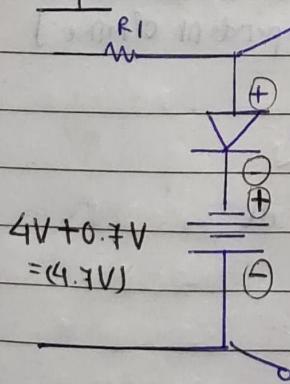

$$4V + 0.7V \\ = (4.7V)$$

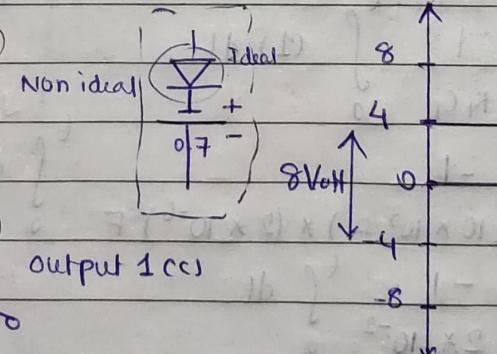

Step 2 :

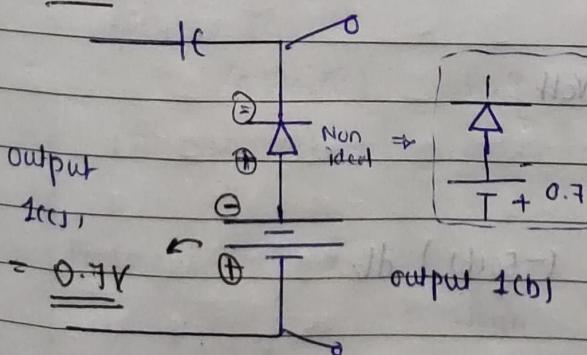

$$\text{output} \\ 1(c), \\ = 0.7V$$


Fig 1(b)

Combined
circuit

drawn on



Next page →

Ans. 1 (A)

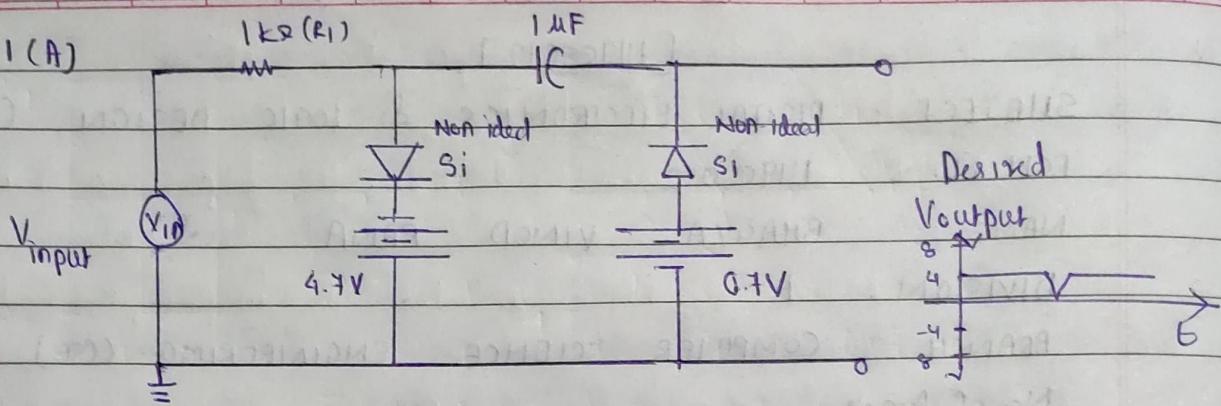

(Q1)

(B)

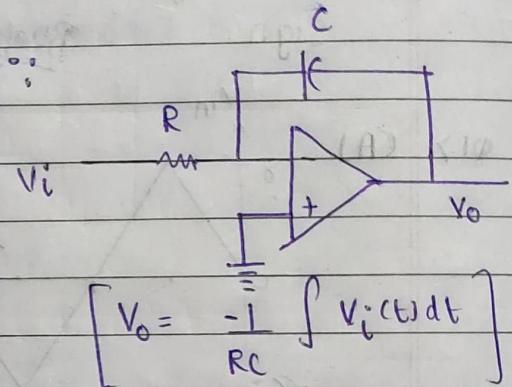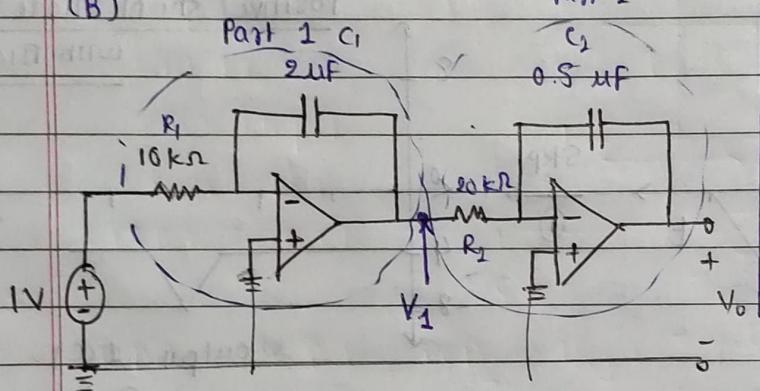

After part 1

$$\begin{aligned}
 V_1 &= -\frac{1}{R_1 C_1} \int_0^t (1) dt \\
 &= -\frac{1}{(10 \times 10^3 \Omega) \times (2 \times 10^{-6}) F} \int_0^t dt \\
 &= -\frac{1}{2 \times 10^{-2}} \int_0^t dt \\
 &= -50(t)
 \end{aligned}$$

$$(V_1) = -50(t) \text{ Volt}$$

After part 2,

$$V_o = -\frac{1}{R_2 C_2} \int_0^t (-50(t)) dt$$

U19CS012

$$V_o = \frac{50}{(20 \times 10^3) \times (0.5 \times 10^{-6})} \int_0^t (t) dt$$

$$= \frac{50}{20 \times 0.5 \times 10^{-3}} \int_0^t (t) dt$$

$$= \frac{50}{10} \times \frac{1}{5} \times (1000) \left[t^2 \right]_0^t$$

$$(2)$$

$$V_o = 2500 (t^2)$$

at time = 6 mill seconds


$$= 2500 \times (6 \times 10^{-3})^2 = (6 \times 10^{-3}) S$$

$$= 90000 \times 10^{-6}$$

$$= 9 \times 10^{-2} \text{ volt}$$

Ans: $= 0.09 \text{ Volt}$

(ICB) $= 90 \text{ mill volt}$

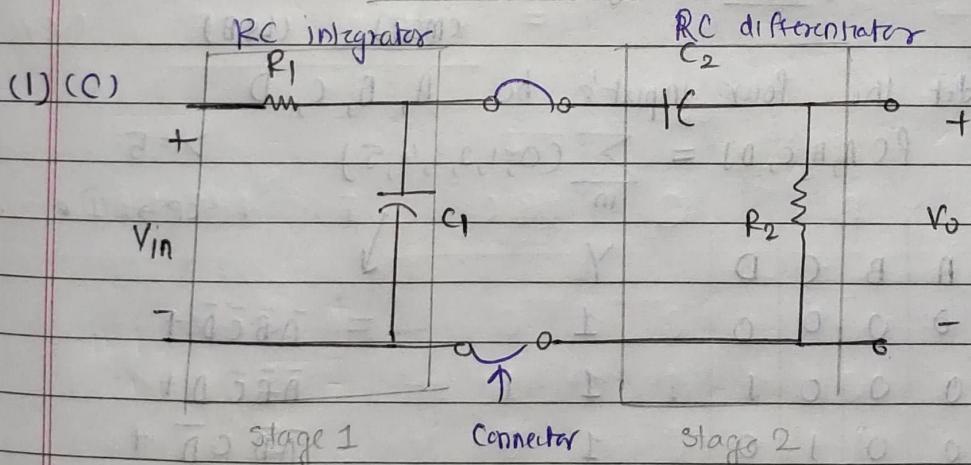


Then, Low Pass ckt \rightarrow Integrator

Rectangular \rightarrow Triangle waveform

diff (triangular) = (square wave)

U19CS012

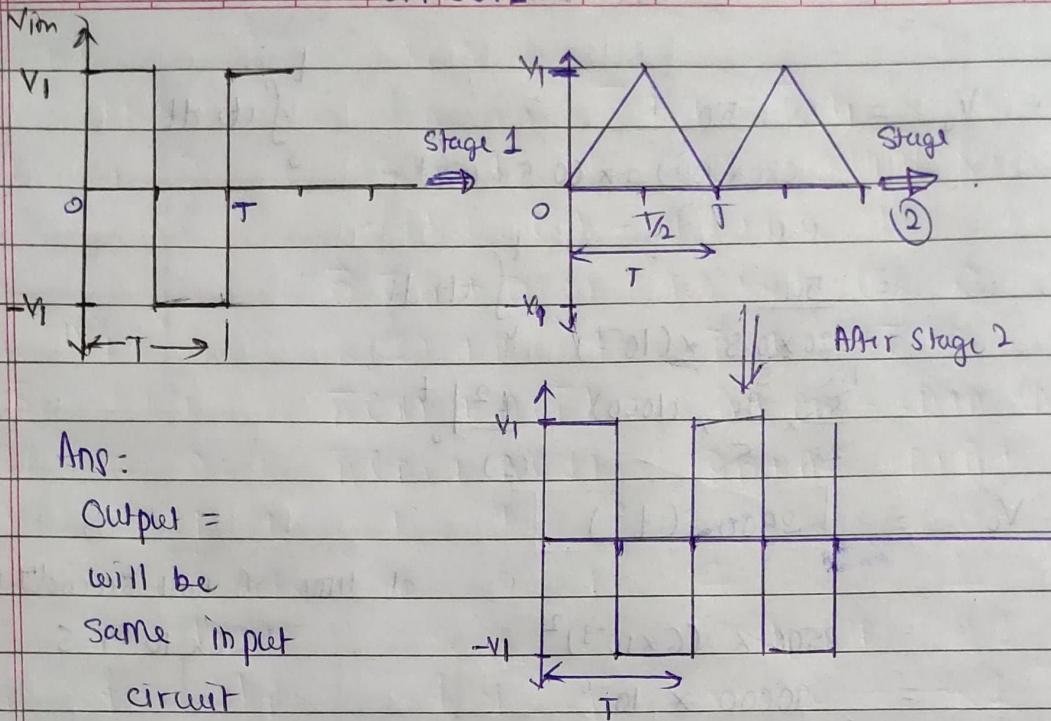

Q8.

2.7 (A) 4-BIT BCD Logic

(MSB) (LSB)

Let the four input's be A, B, C, D

$$f(A, B, C, D) = \sum_m (0, 1, 2, 3, 4, 5) \quad >= 5$$

SOP \rightarrow ① ✓

Decimal	A	B	C	D	Y	
0	0	0	0	0	1	$= \bar{A}\bar{B}\bar{C}\bar{D} +$
1	0	0	0	1	1	$\bar{A}\bar{B}\bar{C}D +$
2	0	0	1	0	1	$\bar{A}\bar{B}C\bar{D} +$
3	0	0	1	1	1	$\bar{A}\bar{B}CD +$
4	0	1	0	0	1	$\bar{A}B\bar{C}\bar{D} +$
5	0	1	0	1	1	$\bar{A}B\bar{C}D$



6	0	1	1	0	0	
7	0	1	1	1	0	$12 1100 0$
8	1	0	0	0	0	$13 1101 0$
9	1	0	0	1	0	$14 1110 0$
10	1	0	1	0	0	$15 1111 1$
11	1	0	1	1	0	

U19CS012

AB	CD	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD	$C\bar{D}$
00	00	1	1	1	1	1
01	01	0	1	1	0	1
10	10	1	0	0	1	0
11	11	0	0	0	0	0
AB	00	1	1	1	1	1
AB	01	1	1	1	0	1
AB	10	1	0	0	1	0
AB	11	0	0	0	0	0

$$F(A, B, C, D) = \overline{A}\overline{B} + \overline{A}\overline{C}$$


[Output]

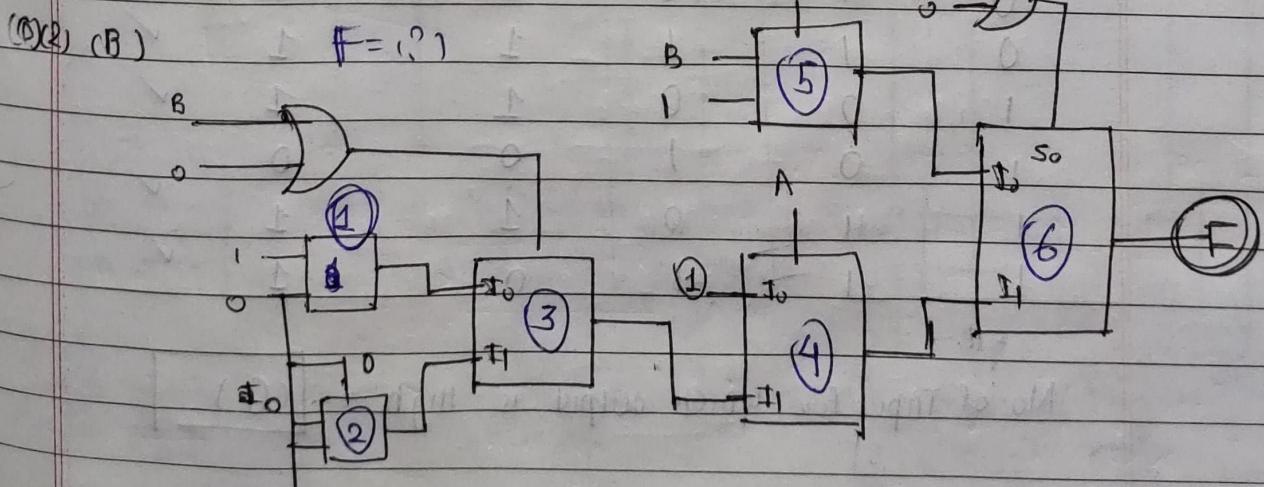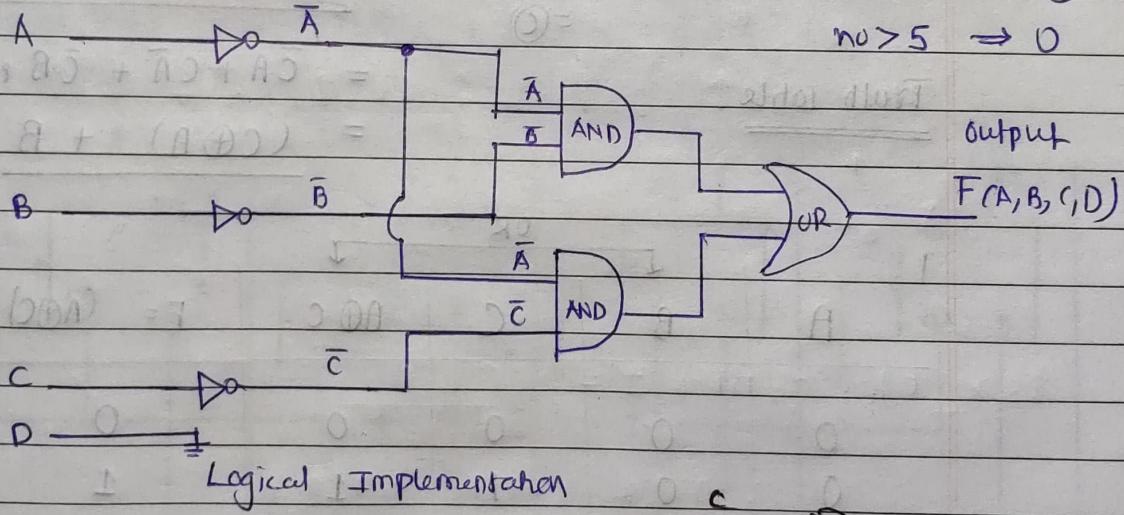

Naming of Boxes

MUX
I₀ I₁
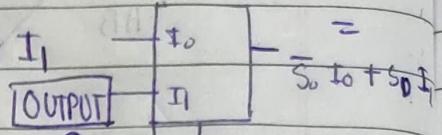
$$\text{Expression} = \overline{S_0} I_0 + S_0 \overline{I_1}$$



$$\overline{S_0}(1) + S_0(0) = 1 \cdot 1 + 0 \cdot 0 = 1$$

$$\overline{S_0}0 + S_0(0) = 1 \cdot 0 + 0 \cdot 0 = 0$$

$$\overline{B}(1) + B(0) = \overline{B} \cdot 1 = \overline{B}$$

$$\begin{array}{|c|c|} \hline 1 & \overline{B} \\ \hline \end{array} \leftarrow 4$$

$$\overline{A}(1) + A(\overline{B}) = \overline{A} + A\overline{B} = (A+A)(A+B) = \overline{A}+A$$

$$\begin{array}{|c|c|} \hline B & 1 \\ \hline \end{array} \rightarrow 5$$

$$\overline{A}(B) + A(1) = \overline{A}B + A = (B+A)$$

6

For last mux


I ₀	I ₁	S ₀	Output (F)
\downarrow	\downarrow	\downarrow	
$(B+A)$	$(A+B)$	$C+0$	$\overline{C}(B+A) + C(\overline{A}+B)$
$= \odot$			

$$\begin{aligned}
 &= \overline{C}A + C\overline{A} + \overline{C}B + CB \\
 &= (C \oplus A) + B \quad (C + \overline{C} = 1)
 \end{aligned}$$

1	OR			F = (A⊕C) + B
	A	B	C	
0	0	0	0	0
0	0	1	1	1 ✓
0	1	0	0	1 ✓
0	1	1	1	1 ✓
1	0	0	1	1 ✓
1	0	1	0	0
1	1	0	1	1 ✓
1	1	1	0	1 ✓

No. of Input for which output is High = (6)

U19CS012

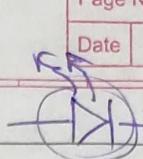Q27 (C) LED will light in Forward Bias

1a) Led glow

$$\text{if } P \oplus Q = 0$$

Sum carry

$$P = A \oplus B \oplus C_{in}$$

$$X \oplus Y \oplus Z$$

$$XY + YZ + XZ$$

$$P \oplus Q$$

$$0 \ 0 \ 0 \ 0$$

$$0$$

$$0 \leftarrow \checkmark$$

$$0 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 1$$

$$1 \ 1 \ 1 \ 1 \ 1 \ 1$$

$$0 \ 0 \ 1 \ 0 \ 1 \ 0 \ 0 \ 1 \ 0 \ 0 \ 1 \ 1$$

$$1 \ 1 \ 1 \ 1 \ 1 \ 1$$

$$0 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 1 \ 1 \ 0 \ 0 \ 1$$

$$1 \ 1 \ 1 \ 1 \ 1 \ 1$$

$$1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0$$

$$1 \ 1 \ 1 \ 1 \ 1 \ 1$$

$$1 \ 1 \ 0 \ 1 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 1$$

$$1 \ 1 \ 1 \ 1 \ 1 \ 1$$

$$1 \ 1 \ 1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \ 1$$

$$1 \ 1 \ 1 \ 1 \ 1 \ 1$$


$$1 \ 1 \ 1 \ 1 \ 1 \ 0 \ 1 \ 1 \ 1 \ 1 \ 1 \ 0$$

$$1 \ 1 \ 1 \ 1 \ 1 \ 1$$

Ans:

No. of input comb. LED will glow = (2)


Parallel output

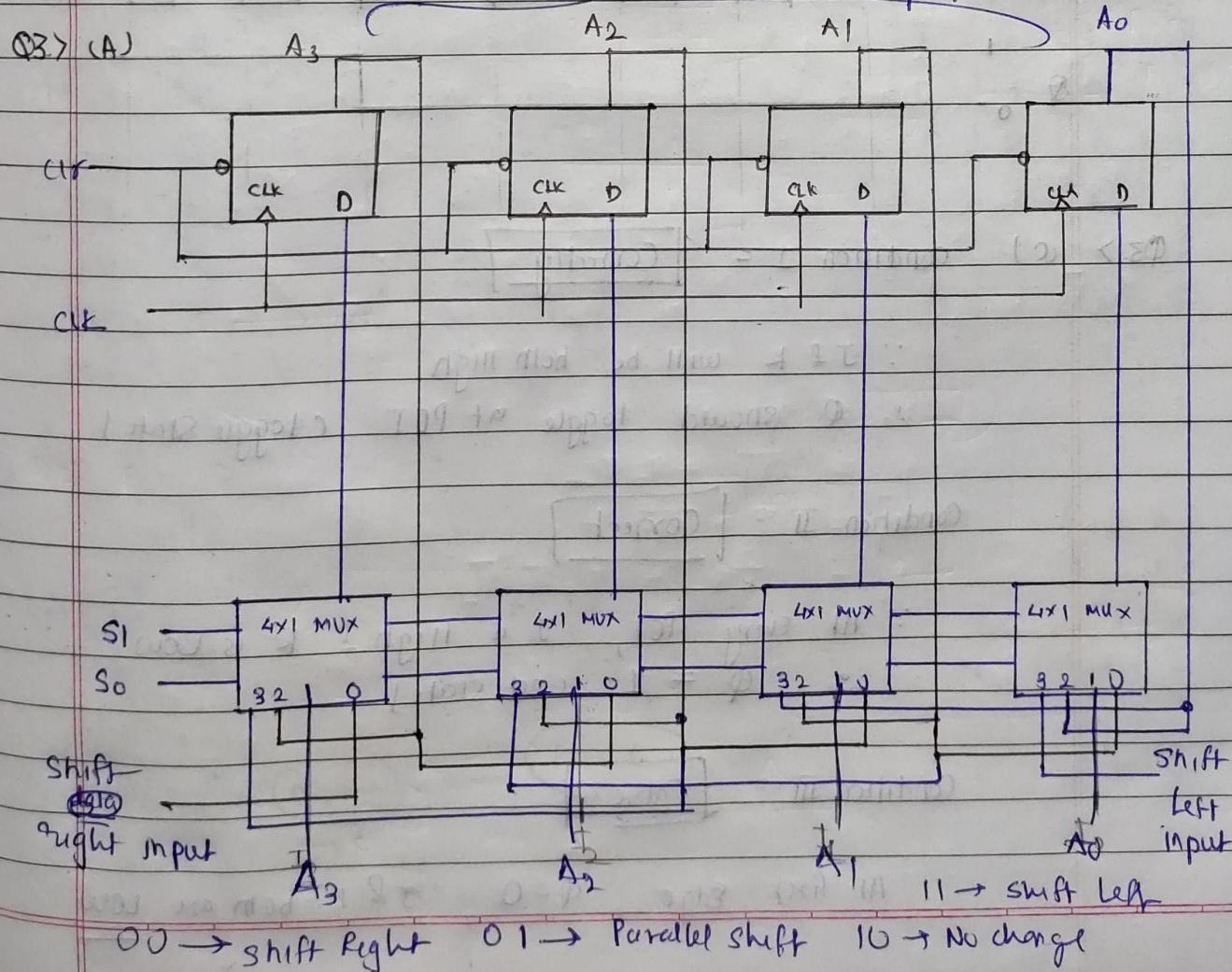

U19CS012

Q3. > (B)

	<u>J₁</u>	<u>J₂</u>	<u>J₃</u>	<u>K₁</u>	<u>K₂</u>	<u>K₃</u>	<u>J</u>	<u>K</u>	<u>Q</u>	<u>State</u>
t=0									0	
CLK=1	1	0	0	0	0	1	1	0	0	Hold
CLK=2	1	1	0	1	0	0	0	0	0	Hold
CLK=3	0	0	0	1	1	1	0	1	0	(Reset)
CLK=4	0	1	1	1	1	0	0	0	0	Hold
CLK=5	1	1	1	0	0	1	1	0	1	Set
CLK=6	0	1	1	0	1	0	0	0	1	Hold
CLK=7	1	0	1	0	1	1	0	0	0	Hold

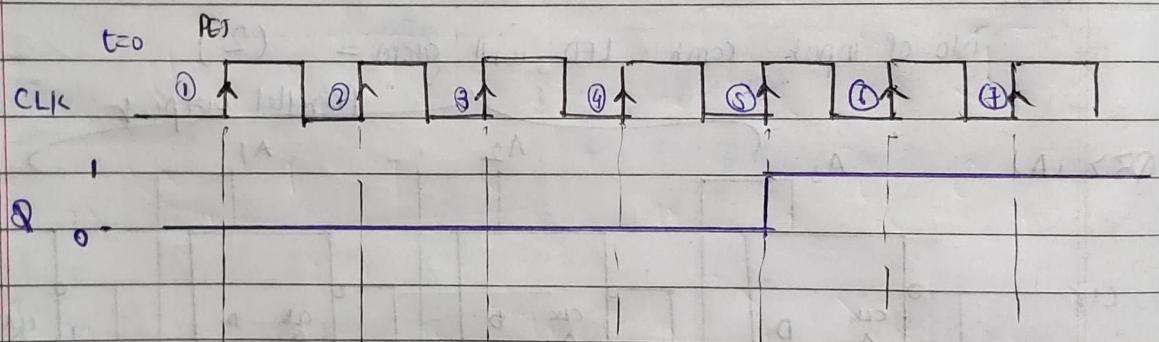Q3. > (c) condition I = Correctly

∴ J & K will be both high

∴ Q should toggle at PGT (Toggle State)

Condition II = Correct

∴ At every PGT, J is High & K is Low

∴ Q = 1 (Set State)

Condition III = False∴ At first Edge, Q=0, J & K=both are LOW

U19CS012

\therefore JK FF is in hold state

$\therefore Q \rightarrow$ no change

But it showed change

Condition 4: $J = 0 \quad K = 1 \Rightarrow$ Reset State

[FALSE]

J is Low & K is high

$\therefore Q \rightarrow 0$ (reset)

But waveform toggles, : Incorrect


$[Q_n^+, Q_{n+1}^-]$
(wing Excitation)

Q4.7 (A)

Present State

Next State

	Q_3	Q_2	Q_1	Q_0	Q_3^+	Q_2^+	Q_1^+	Q_0^+	T_3	T_2	T_1	T_0
t_n	0	0	0	0	1	1	1	0	1	1	1	0
t_{n+1}	1	1	1	0	1	0	1	0	0	1	0	0
t_{n+2}	1	0	1	0	1	0	0	0	0	0	1	0
t_{n+3}	0	1	0	0	0	1	1	1	1	1	1	1
t_{n+4}	0	1	1	1	0	1	0	1	0	0	1	0
t_{n+5}	0	1	0	1	0	0	1	1	0	1	1	0
t_{n+6}	0	0	1	1	1	0	0	0	0	0	0	1

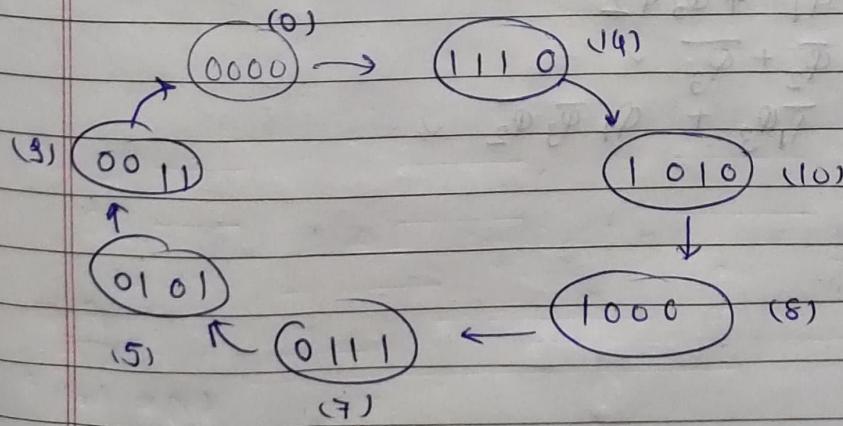

(State Diagram)

UNIQS012

$\bar{Q}_1 Q_0$	$\bar{Q}_3 Q_2$	$T_3 = \bar{Q}_1 \bar{Q}_0$	$\bar{Q}_1 Q_0$	$\bar{Q}_3 Q_2$	$T_2 = \bar{Q}_1 + Q_3 Q_2$
00	00	1 0 1 3 2	00	00	1 X 0 1 3 2
01	01	X 0 0 0 0	01	01	X 1 0 1 3 2
11	11	X 1 0 0 0	11	11	X X X 1 1 0
10	10	1 8 9 11 10	10	10	1 X 9 11 10

$\bar{Q}_1 Q_0$	$\bar{Q}_3 Q_2$	$T_1 = \bar{Q}_3 + \bar{Q}_2$	$\bar{Q}_1 Q_0$	$\bar{Q}_3 Q_2$	$T_0 = \bar{Q}_3 \bar{Q}_1 + \bar{Q}_1 \bar{Q}_3 \bar{Q}_2$
00	00	1 0 1 3 2	00	00	0 0 1 (1 3) X 2
01	01	X 1 1 1 X	01	01	0 0 1 0 0 0
11	11	1 12 13 15 0	11	11	X X X 1 1 0
10	10	1 8 X 9 X 11 10	10	10	1 X 9 11 10


$$T_3 = \bar{Q}_0 \bar{Q}_1$$

$$T_2 = \bar{Q}_1 + Q_3 Q_2$$

$$T_1 = \bar{Q}_2 + \bar{Q}_3 \checkmark$$

$$T_0 = \bar{Q}_1 \bar{Q}_3 + \bar{Q}_1 \bar{Q}_3 \bar{Q}_2 \checkmark$$

U19CS012 C100P11

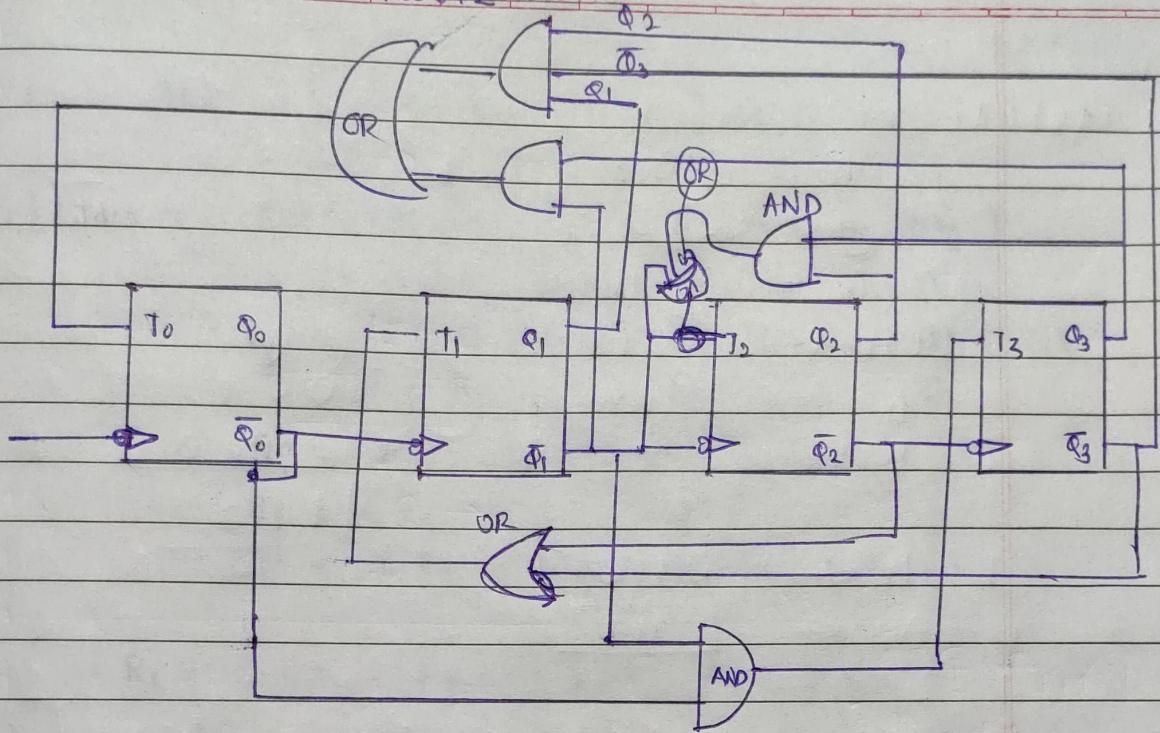

Asyn Down Counter of D-14-10-8-7-5-3-0

(4) (B)

Synchronous circuit→ All clock ~~is~~ someTwo shift ~~reg~~ right register has a problemin q_3 's D flip-flop that is the input valueof q_3 's D terminal has been shorted withpower line. Thus we have D of q_3 as always high.

All other flipflops are working fine.

U19CS012

(Q4) (C)

$$V_o = - \int_0^t (V_1 + 4V_2 + 10V_3) dt$$

(1) $I_{dia} \Rightarrow$ first make = $(-V_1 + -4V_2 - 10V_3)$

using summer circuit

$$V_1 = -\frac{R_F}{R_1} (V_1) + -\frac{R_F}{R_2} (V_2) + -\frac{R_F}{R_3} (V_3)$$

$$R_F = 1 R_1$$

$$R_F = 4 R_2$$

$$R_F = 10 R_3 \quad \text{let } R_F = [20] k\Omega$$

$$R_1 = 20 k\Omega \quad R_2 = 5 k\Omega \quad R_3 = 2 k\Omega$$

(2)

integrating


$$RC = 1$$

$$C = 2 \mu F$$

$$R = \frac{1}{C} = \frac{10^6}{2 \times 10^{-6}} = 5 \times 10^5 \Omega$$

$$= [500 k\Omega]$$

FINAL circuit

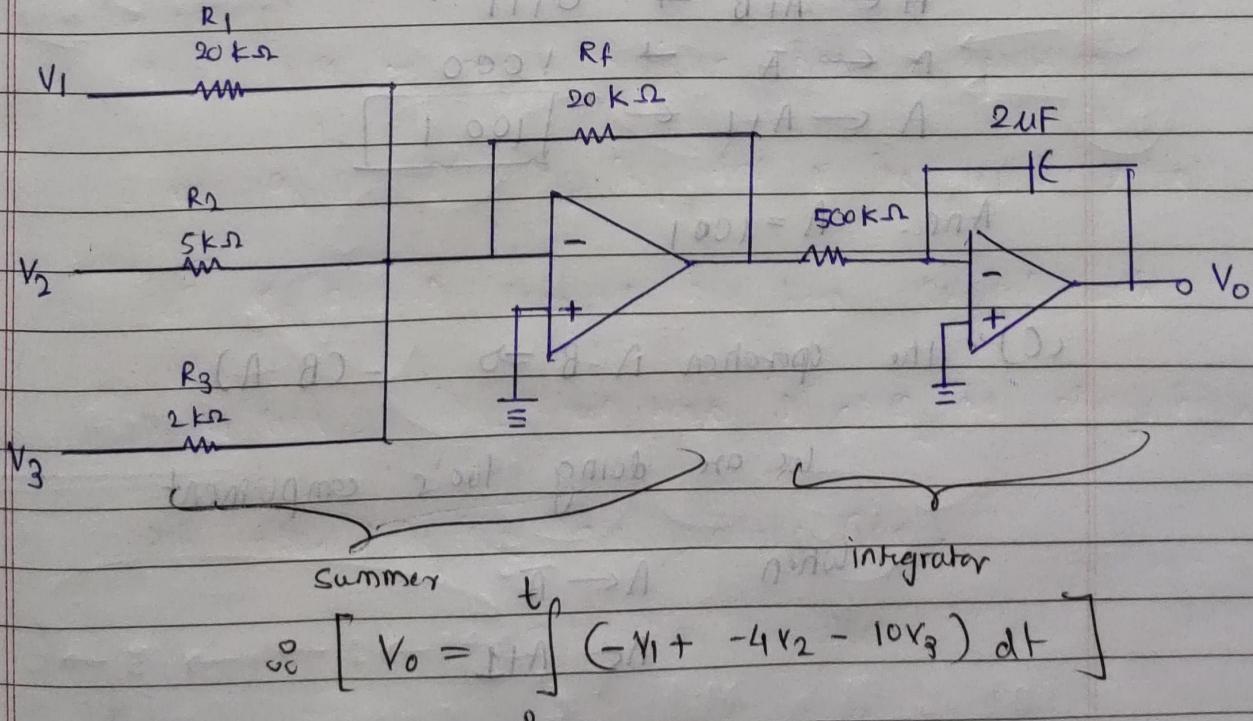

(Q5) (A)

$$A = 1101$$

$$B = 0110$$

$$\bar{A} = 0010$$

$$① A \leftarrow 0010$$

$$\begin{array}{c} A+I \\ \textcircled{A} \\ 1001 \end{array} \leftarrow \begin{array}{c} 0011 \\ \textcircled{A+B} \end{array}$$

$$\begin{array}{r} 0011 \\ + 0110 \\ \hline \end{array}$$

$$\begin{array}{r} 1001 \\ \boxed{1001} \end{array}$$

$$A \leftarrow 0110$$

$$A \leftarrow \boxed{0111}$$

Ans: content of A after micro op = $\boxed{0111}$

(B) A initially $\rightarrow 0110$

$$A \leftarrow \bar{A} \rightarrow 1001$$

$$A \leftarrow A+I \rightarrow 1010$$

$$A \leftarrow A+B \rightarrow 0111$$

$$A \leftarrow \bar{A} \rightarrow 1000$$

$$A \leftarrow A+I \leftarrow \boxed{1001}$$

Ans: $A = 1001$

(C) The operation $A-B \Rightarrow -(B-A)$

We are doing two's complement

When $A \leftarrow \bar{A}$

$A \leftarrow A+1$

$$(Q5) (B) \quad X = B(A + \bar{C}) = TA - ① \quad T^{(0_{n+1})}$$

$$TB = B + C \quad 0 \quad \frac{Q_n}{Q_n}$$

$$TC = \bar{B} + C \quad 1 \quad \underline{Q_n}$$

$A + \bar{C}$	Present State			Toggle			Next State				
	A	B	C	\bar{B}	\bar{C}	T_A	T_B	T_C	A	B	C
1	0	0	0	1	1	0	0	0	1	0	0
0	0	0	1	1	0	0	1	1	1	0	1
1	0	1	0	0	1	1	1	1	0	1	0
0	0	1	1	0	0	0	0	1	1	0	0
1	1	0	0	1	1	0	0	0	1	0	1
1	0	1	1	0	0	0	1	1	1	1	0
1	1	1	0	0	1	1	1	0	0	0	0
1	1	1	1	0	0	1	1	1	0	0	0

