

# Boolean Algebra

**Dr. Shilpi Gupta**  
**Associate Professor**  
**ECED**  
**SVNIT, Surat**

# The “WHY” Boolean Algebra

- Algebra

When we learned numbers like 1, 2, 3, we also then learned how to add, multiply, etc. with them. Boolean Algebra covers operations that we can do with 0's and 1's. Computers do these operations ALL THE TIME and they are basic building blocks of computation inside your computer program.

## Axioms, laws, theorems

We need to know some rules about how those 0's and 1's can be operated on together. There are similar axioms to decimal number algebra, and there are some laws and theorems that are good for you to use to simplify your operation.

# How does Boolean Algebra fit into the big picture?

- It is part of the Combinational Logic topics (memoryless)
  - Different from the Sequential logic topics (can store information)
- Learning Axioms and theorems of Boolean algebra
  - Allows you to design logic functions
  - Allows you to know how to combine different logic gates
  - Allows you to simplify or optimize on the complex operations

# Boolean algebra

- A Boolean algebra comprises...

- A set of elements  $B$
- Binary operators  $\{+, \bullet\}$       Boolean sum and product
- A unary operation  $\{'\}$  (or  $\{\bar{\phantom{x}}\}$ )      example:  $A'$  or  $\bar{A}$

- ...and the following axioms

- 1. The set  $B$  contains at least two elements  $\{a, b\}$  with  $a \neq b$
- 2. Closure:       $a+b$  is in  $B$        $a \bullet b$  is in  $B$
- 3. Commutative:  $a+b = b+a$        $a \bullet b = b \bullet a$
- 4. Associative:     $a+(b+c) = (a+b)+c$        $a \bullet (b \bullet c) = (a \bullet b) \bullet c$
- 5. Identity:       $a+0 = a$        $a \bullet 1 = a$
- 6. Distributive:     $a+(b \bullet c) = (a+b) \bullet (a+c)$        $a \bullet (b+c) = (a \bullet b) + (a \bullet c)$
- 7. Complementarity:  $a+a' = 1$        $a \bullet a' = 0$

# Digital (binary) logic is a Boolean algebra

## Substitute

- $\{0, 1\}$  for  $B$
- AND for  $\bullet$  Boolean Product.
- OR for  $+$  Boolean Sum.
- NOT for  $'$  Complement.

All the axioms hold for binary logic

## Definitions


- Boolean function
  - Maps inputs from the set  $\{0,1\}$  to the set  $\{0,1\}$
- Boolean expression
  - An algebraic statement of Boolean variables and operators

# Logic Gates (AND, OR, Not) & Truth Table

AND

$X \bullet Y$


$XY$

 

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

OR

$X + Y$

 


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

NOT

$\overline{X}$

$X'$

 

X	Y
0	1
1	0

# Logic functions and Boolean algebra

- Any logic function that is expressible as a truth table can be written in Boolean algebra using  $+$ ,  $\bullet$ , and  $'$

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

$Z = X \bullet Y$

X	Y	X'	Z
0	0	1	0
0	1	1	1
1	0	0	0
1	1	0	0

$Z = X' \bullet Y$

X	Y	X'	Y'	$X \bullet Y$	$X' \bullet Y'$	Z
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

$Z = (X \bullet Y) + (X' \bullet Y')$

# Two key concepts

- **Duality (a meta-theorem— *a theorem about theorems*)**
  - All Boolean expressions have logical duals
  - Any theorem that can be proved is also proved for its dual
  - Replace:  $\bullet$  with  $+$ ,  $+$  with  $\bullet$ , 0 with 1, and 1 with 0
  - Leave the variables unchanged
- **De Morgan's Theorem**
  - Procedure for complementing Boolean functions
  - Replace:  $\bullet$  with  $+$ ,  $+$  with  $\bullet$ , 0 with 1, and 1 with 0
  - Replace all variables with their complements



# Universal Gate Implementation

## NAND Gate as Universal Gate

OR Gate using NAND Gate

NOR Gate using NAND Gate

EXOR using NAND Gate

**NOR Gate as Universal Gate: TO DO**

**EX-OR Gate Using NOR gate**



# Boolean Functions

- Boolean function is described by an algebraic expression called Boolean expressions which consists of binary variables and logic operation symbols.
- Mathematical functions can be expressed in two ways:

An **expression** is  
finite but not unique

$$\begin{aligned}f(x,y) &= 2x + y \\ &= x + x + y \\ &= 2(x + y/2) \\ &= \dots\end{aligned}$$

A **function table** is  
unique

x	y	f(x,y)
0	0	0
...	...	...
2	2	6
...	...	...
23	41	87
...	...	...

We can represent logical functions in two analogous ways too:

- A finite, but non-unique **Boolean expression**.
- A **truth table**, which will turn out to be unique.

# Boolean expressions

- We can use these basic operations to form more complex expressions:

$$f(x,y,z) = (x + y')z + x'$$

- $f$  is the name of the function.
- $(x, y, z)$  are the **input variables**, each representing 1 or 0. Listing the inputs is optional, but sometimes helpful.
- A **literal** is any occurrence of an input variable or its complement. The function above has four literals:  $x$ ,  $y'$ ,  $z$ , and  $x'$ .
- Precedence is important, but not too difficult.
  - NOT has the highest precedence, followed by AND, and then OR.
  - Fully parenthesized, the function above would be kind of messy:

$$f(x,y,z) = (((x + (y'))z) + x')$$

# Useful laws and theorems

Identity:  $X + 0 = X$

Dual:  $X \bullet 1 = X$

Null:  $X + 1 = 1$

Dual:  $X \bullet 0 = 0$

Idempotent:  $X + X = X$

Dual:  $X \bullet X = X$

Involution:  $(X')' = X$

Complementarity:  $X + X' = 1$

Dual:  $X \bullet X' = 0$

Commutative:  $X + Y = Y + X$

Dual:  $X \bullet Y = Y \bullet X$

Associative:  $(X+Y)+Z=X+(Y+Z)$

Dual:  $(X \bullet Y) \bullet Z = X \bullet (Y \bullet Z)$

Distributive:  $X \bullet (Y+Z) = (X \bullet Y) + (X \bullet Z)$

Dual:  $X + (Y \bullet Z) = (X + Y) \bullet (X + Z)$

Uniting:  $X \bullet Y + X \bullet Y' = X$

Dual:  $(X + Y) \bullet (X + Y') = X$

## Proof of law with Truth table

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$(A + B) + C = A + (B + C)$$

# Useful laws and theorems (con't)

Absorption:  $X + X \bullet Y = X$       Dual:  $X \bullet (X + Y) = X$

Absorption (#2):  $(X + Y') \bullet Y = X \bullet Y$       Dual:  $(X \bullet Y') + Y = X + Y$

$$x + \bar{x}y = x + y$$

$$(x + y)(x + z) = x + yz$$

de Morgan's:  $(X + Y + \dots)' = X' \bullet Y' \bullet \dots$       Dual:  $(X \bullet Y \bullet \dots)' = X' + Y' + \dots$

Duality:  $(X + Y + \dots)^D = X \bullet Y \bullet \dots$       Dual:  $(X \bullet Y \bullet \dots)^D = X + Y + \dots$

Multiplying & factoring:  $(X + Y) \bullet (X' + Z) = X \bullet Z + X' \bullet Y$   
Dual:  $X \bullet Y + X' \bullet Z = (X + Z) \bullet (X' + Y)$

Consensus:  $(X \bullet Y) + (Y \bullet Z) + (X' \bullet Z) = X \bullet Y + X' \bullet Z$   
Dual:  $(X + Y) \bullet (Y + Z) \bullet (X' + Z) = (X + Y) \bullet (X' + Z)$

# Proofing the theorems using axioms

- Idempotency:  $x + x = x$

Proof:

$$\begin{aligned}x + x &= (x + x) \bullet 1 && \text{by identity} \\&= (x + x) \bullet (x + x') && \text{by complement} \\&= x + x \bullet x' && \text{by distributivity} \\&= x + 0 && \text{by complement} \\&= x && \text{by identity}\end{aligned}$$

- Idempotency:  $x \bullet x = x$

Proof:

$$\begin{aligned}x \bullet x &= (x \bullet x) + 0 && \text{by identity} \\&= (x \bullet x) + (x \bullet x') && \text{by complement} \\&= x \bullet (x + x') && \text{by distributivity} \\&= x \bullet 1 && \text{by complement} \\&= x && \text{by identity}\end{aligned}$$



# Theorems

Prove the uniting theorem--  $X \bullet Y + X \bullet Y' = X$

Distributive	$X \bullet Y + X \bullet Y' = X \bullet (Y + Y')$
Complementarity	$= X \bullet (1)$
Identity	$= X$

Prove the absorption theorem--  $X + X \bullet Y = X$

Identity	$X + X \bullet Y = (X \bullet 1) + (X \bullet Y)$
Distributive	$= X \bullet (1 + Y)$
Null	$= X \bullet (1)$
Identity	$= X$

To Prove

$$A + \bar{A}B = A + B$$

$$(A + B)(A + C) = A + BC$$

More proves

$$(A + \bar{B} + AB)(A + \bar{B})(\bar{A}B) = 0$$

$$A + \bar{A}B + AB = A + B$$

*Simplify the following expression*

$$Y = \overline{(\bar{A}B + \bar{A} + AB)}$$



# Theorems

Prove the consensus theorem--

$$(XY)+(YZ)+(X'Z)= XY+X'Z$$

Complementarity  $XY+YZ+X'Z = XY+(X+X')YZ + X'Z$

Distributive  $= XYZ+XY+X'YZ+X'Z$

- Use absorption  $\{AB+A=A\}$  with  $A=XY$  and  $B=Z$

$$= XY+X'YZ+X'Z$$

Rearrange terms  $= XY+X'ZY+X'Z$

- Use absorption  $\{AB+A=A\}$  with  $A=X'Z$  and  $B=Y$

$$XY+YZ+X'Z = XY+X'Z$$

# Logic simplification

Example:

$$Z = A'BC + AB'C' + AB'C + ABC' + ABC$$

$$\begin{aligned} &= A'BC + AB'(C' + C) + AB(C' + C) && \text{distributive} \\ &= A'BC + AB' + AB && \text{complementary} \\ &= A'BC + A(B' + B) && \text{distributive} \\ &= A'BC + A && \text{complementary} \\ &= BC + A && \text{absorption \#2 Duality} \end{aligned}$$

$$(X \bullet Y') + Y = X + Y \text{ with } X=BC \text{ and } Y=A$$

# Algebraic manipulation

$$x'y' + xyz + x'y$$

$$= x'(y' + y) + xyz \text{ [Distributive; } x'y' + x'y = x'(y' + y) \text{ ]}$$

$$= x' \bullet 1 + xyz \text{ [ Axiom 5; } y' + y = 1 \text{ ]}$$

$$= x' + xyz \text{ [ Axiom 2; } x' \bullet 1 = x' \text{ ]}$$

$$= (x' + x)(x' + yz) \text{ [ Distributive ]}$$

$$= 1 \bullet (x' + yz) \text{ [ Axiom 5; } x' + x = 1 \text{ ]}$$

$$= x' + yz \text{ [ Axiom 2 ; } x' \bullet 1 = x' \text{ ]}$$

## More Problems:-

$$A\bar{B} + \bar{A}B + \bar{A}\bar{B} + AB$$

$$(AB + C)(AB + D)$$

$$AB + ABC + A\bar{B} = A \quad (\text{Prove})$$



# De Morgan's Theorem

Use de Morgan's Theorem to find complements

Example:  $F = (A+B) \bullet (A'+C)$ , so  $F' = (A' \bullet B') + (A \bullet C')$

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

A	B	C	F'
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

# Complement of a function

- The complement of a function always outputs 0 where the original function outputted 1, and 1 where the original produced 0.
- In a truth table, we can just exchange 0s and 1s in the output column(s)

$$f(x,y,z) = x(y'z' + yz)$$

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



x	y	z	f'(x,y,z)
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

# Complementing a function algebraically

$$f(x,y,z) = x(y'z' + yz)$$

$$\begin{aligned} f'(x,y,z) &= (x(y'z' + yz))' && \text{[ complement both sides ]} \\ &= x' + (y'z' + yz)' && \text{[ because } (xy)' = x' + y' \text{ ]} \\ &= x' + (y'z')' (yz)' && \text{[ because } (x + y)' = x' y' \text{ ]} \\ &= x' + (y + z)(y' + z') && \text{[ because } (xy)' = x' + y', \text{ twice} \end{aligned}$$

- You can use DeMorgan's law to keep “pushing” the complements inwards
- You can also take the dual of the function, and then complement each literal
  - If  $f(x,y,z) = x(y'z' + yz)...$
  - ...the dual of  $f$  is  $x + (y' + z')(y + z)...$
  - ...then complementing each literal gives  $x' + (y + z)(y' + z')...$
  - ...so  $f'(x,y,z) = x' + (y + z)(y' + z')$

# Canonical Forms

- Any boolean function that is expressed as a **sum of minterms** or as a **product of maxterms** is said to be in its **canonical form**.
- A **minterm** is a special product of literals, in which each input variable appears exactly once.
- A function with  $n$  variables has  $2^n$  minterms (since each variable can appear complemented or not) A three-variable function, such as  $f(x,y,z)$ , has  $2^3 = 8$  minterms:

$$\begin{array}{l} x'y'z' \\ xy'z' \end{array}$$

$$\begin{array}{l} x'y'z \\ xy'z \end{array}$$

$$\begin{array}{l} x'yz' \\ xyz' \end{array}$$

$$\begin{array}{l} x'yz \\ xyz \end{array}$$

# Minterms

- Each minterm is true for exactly one combination of inputs:

Minterm	Is true when...	Shorthand
$x'y'z'$	$x=0, y=0, z=0$	$m_0$
$x'y'z$	$x=0, y=0, z=1$	$m_1$
$x'yz'$	$x=0, y=1, z=0$	$m_2$
$x'yz$	$x=0, y=1, z=1$	$m_3$
$xy'z'$	$x=1, y=0, z=0$	$m_4$
$xy'z$	$x=1, y=0, z=1$	$m_5$
$xyz'$	$x=1, y=1, z=0$	$m_6$
$xyz$	$x=1, y=1, z=1$	$m_7$

# Sum of minterms form

- Every function can be written as a **sum of minterms**, which is a special kind of sum of products form
- The sum of minterms form for any function is *unique*
- If you have a truth table for a function, you can write a sum of minterms expression just by picking out the rows of the table where the function output is 1 (**1-minterm**).

x	y	z	f(x,y,z)	f'(x,y,z)
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

$$\begin{aligned}f &= x'y'z' + x'y'z + x'yz' + x'yz + xyz' \\&= m_0 + m_1 + m_2 + m_3 + m_6 \\&= \Sigma(0,1,2,3,6)\end{aligned}$$

$$\begin{aligned}f' &= xy'z' + xy'z + xyz \\&= m_4 + m_5 + m_7 \\&= \Sigma(4,5,7)\end{aligned}$$

f' contains all the minterms not in f

# Sum of minterms: practise

$F = x + yz$ , how to express this in the sum of minterms?

$$= x(y + y')(z + z') + (x + x')yz$$

$$= xyz + xyz' + xy'z + xy'z' + xyz + x'yz$$

$$= x'yz + xy'z' + xy'z + xyz' + xyz$$

$$= \Sigma(3,4,5,6,7)$$

or, convert the expression into truth-table and then read the minterms from the table

# Maxterms


- A **maxterm** is a *sum* of literals, in which each input variable appears exactly once.
- A function with  $n$  variables has  $2^n$  maxterms

$$\begin{array}{cccc} x' + y' + z' & x' + y' + z & x' + y + z' & x' + y + z \\ x + y' + z' & x + y' + z & x + y + z' & x + y + z \end{array}$$

- The maxterms for a three-variable function  $f(x,y,z)$ :

Maxterm	Is false when...	Shorthand
$x + y + z$	$x=0, y=0, z=0$	$M_0$
$x + y + z'$	$x=0, y=0, z=1$	$M_1$
$x + y' + z$	$x=0, y=1, z=0$	$M_2$
$x + y' + z'$	$x=0, y=1, z=1$	$M_3$
$x' + y + z$	$x=1, y=0, z=0$	$M_4$
$x' + y + z'$	$x=1, y=0, z=1$	$M_5$
$x' + y' + z$	$x=1, y=1, z=0$	$M_6$
$x' + y' + z'$	$x=1, y=1, z=1$	$M_7$

 - Each maxterm is *false* for exactly one combination of inputs:





# Product of maxterms form

- Every function can be written as a *unique product of maxterms*
- If you have a truth table for a function, you can write a product of maxterms expression by picking out the rows of the table where the function output is 0 (**0-maxterm**).

x	y	z	f(x,y,z)	f'(x,y,z)
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

O/P

SOP min

$$\begin{aligned}
 f &= (x' + y + z)(x' + y + z')(x' + y' + z) \\
 &= M_4 M_5 M_7 \\
 &= \prod(4,5,7)
 \end{aligned}$$

POS

Max

O/P → 0

$$\prod m(4,5,7)$$

$$\begin{aligned}
 f' &= (x + y + z)(x + y + z')(x + y' + z) \\
 &\quad (x + y' + z')(x' + y' + z) \\
 &= M_0 M_1 M_2 M_3 M_6 \\
 &= \prod(0,1,2,3,6)
 \end{aligned}$$

SOP

O/P → 1

SOP

$$\sum m(0,1,2)$$

f' contains all the maxterms not in f

x, y, z

M<sub>4</sub>  
M<sub>5</sub>  
M<sub>7</sub>

# Product of maxterms: practise

- $F = \overline{x'y'} + xz$ , how to express this in the product of maxterms?

$$= (\overline{x'y'} + x)(\overline{x'y'} + z)$$

$$= (\overline{x' + x})(\overline{y' + x})(\overline{x' + z})(\overline{y' + z})$$

$$= (\overline{x + y'})(\overline{x' + z})(\overline{y' + z})$$

$$= (\overline{x + y' + zz'})(\overline{x' + z + yy'})(\overline{xx' + y' + z})$$

$$= (\overline{x + y' + z})(\overline{x + y' + z'})(\overline{x' + y + z})(\overline{x' + y' + z})(\overline{x + y' + z})(\overline{x' + y' + z})$$

$$= (\overline{x + y' + z})(\overline{x + y' + z'})(\overline{x' + y + z})(\overline{x' + y' + z})$$

$$= \prod(2,3,4,6)$$

Std. POS

$$xy + (z + z')$$

$$xyz + xyz'$$

Std.

Canonical

POS

Std. POS

SOP  
Std SOP

$$F(A,B,C) = (A+B)(A'+C)(B'+C')$$

or, convert the expression into truth-table and then read the minterms from the table

# Minterms and maxterms are related

- Any minterm  $m_i$  is the *complement* of the corresponding maxterm  $M_i$

Minterm	Shorthand	Maxterm	Shorthand
$x'y'z'$	$m_0$	$x + y + z$	$M_0$
$x'y'z$	$m_1$	$x + y + z'$	$M_1$
$x'yz'$	$m_2$	$x + y' + z$	$M_2$
$x'yz$	$m_3$	$x + y' + z'$	$M_3$
$xy'z'$	$m_4$	$x' + y + z$	$M_4$
$xy'z$	$m_5$	$x' + y + z'$	$M_5$
$xyz'$	$m_6$	$x' + y' + z$	$M_6$
$xyz$	$m_7$	$x' + y' + z'$	$M_7$

$$\begin{aligned}
 & (xy'z')' \\
 & \quad x' + y + z \\
 \hline
 & (m_4)' = M_4
 \end{aligned}$$

- For example,  $\underline{m_4}' = M_4$  because  $(xy'z')' = x' + y + z$

# Converting between canonical forms

- We can convert a sum of minterms to a product of maxterms

From before  
and

$$f = \Sigma(0,1,2,3,6)$$
$$f' = \Sigma(4,5,7)$$
$$= m_4 + m_5 + m_7$$

complementing  $(f')' = (m_4 + m_5 + m_7)'$

so

$$f = m_4' m_5' m_7' \quad [\text{DeMorgan's law}]$$
$$= M_4 M_5 M_7 \quad [\text{By the previous page}]$$
$$= \Pi(4,5,7)$$

$f^h$   
 $SOP \rightarrow POS$   
 $f^h$   
 $POS$

- In general, just replace the minterms with maxterms, using maxterm numbers that **don't appear** in the sum of minterms:

$$f = \Sigma(0,1,2,3,6)$$
$$= \Pi(4,5,7)$$

- The same thing works for converting from a product of maxterms to a sum of minterms

# Standard Forms

- Any boolean function that is expressed as a **sum of products (SOP)** or as a **product of sums (POS)**, where each product-term or sum-term may require **fewer than (n-1) operations**, is said to be in its **standard form**.
- Standard forms are **not unique**, there can be several different SOPs and POSs for a given function.
- A SOP expression contains:
  - Only OR (sum) operations at the “outermost” level
  - Each term (**implicant**) must be a product of literals

$$\underline{f(x,y,z) = xy + x'yz + xy'z}$$

- A POS expression contains:
  - Only AND (product) operations at the “outermost” level
  - Each term (**implicate**) must be a sum of literals

$$f(x,y,z) = (x' + y')(x + y' + z')(x' + y + z')$$

# Minimization of Switching Function

$$F = X'Y'Z + XY + X'Y'$$

K'MAP

2D

	Y	Y'
X'	0 X'Y'	1 X'Y
X	2 XY'	3 XY

3 Variable

	YZ 00	01	11	10
X'	0	1	0	0
X	4	5	7	6

Algebraic Manipulation

Theorem, Laws

X	Y'	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

0	1
0	0
0	1
1	1
1	0
1	3

# 4 V - K-MAP

WX	YZ			
	$YZ'$	$Y'Z$	$YZ$	$Y'Z'$
$W'X'$	0 <u>1</u>	1	3	2
$W'X$	4	5	7	6
$WX$	12	13	15	14
$WX'$	8	9	11	10

②  $Y Z$

	<u>WX/YZ</u>				F
	$W'X'$	$W'X$	$WX'$	$WX$	
0	1	0	0	0	1
1	0	1	0	0	1
2	0	0	1	0	1
3	0	0	0	1	0
4	0	0	0	0	0
5	0	0	0	0	0
6	0	0	0	0	0
7	0	0	0	0	0
8	0	0	0	0	0
9	0	0	0	0	0
10	0	0	0	0	0
11	0	0	0	0	0
12	0	0	0	0	0
13	0	0	0	0	0
14	0	0	0	0	0
15	0	0	0	0	0
16	0	0	0	0	0

YZ WX

	A	B	C	Y
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

$$\Sigma m(0, 3, 5, 7)$$

BC

	B'C'	B'C	BC	BC'
A'	0	1	3	2
A	4	5	7	6

Minimize Group

$$2^0, 2^1, 2^2, 2^3, 2^4$$

$$= 1$$

1, 2, 4, 8, 16
----------------

6



# Two variable K Map

$m_0$	$m_1$
$m_2$	$m_3$

(a)

		$y$	
		0	1
$x$	0	$x'y'$	$x'y$
	1	$xy'$	$xy$

(b)

		$y$	
		0	1
$x$	0		
	1		1

(a)  $xy$

		$y$	
		0	1
$x$	0		1
	1	1	1

(b)  $x + y$

# 3- variable K-Map

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

		$yz$		$y$	
$x$		00	01	11	10
$x$	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
	1	$xy'z'$	$xy'z$	$xyz$	$xyz'$

$z$

$$F(x, y, z) = \Sigma(2, 3, 4, 5)$$

		$yz$		$y$	
$x$		00	01	11	10
$x$	0			1	1
	1	1	1		

$z$

Simplify the Boolean function

$$F(x, y, z) = \Sigma(3, 4, 6, 7)$$

		$yz$		$y$	
$x$		00	01	11	10
$x$	0			1	
	1	1		1	1

$$F = A'C + A'B + AB'C + BC$$

		$BC$		$B$	
$A$		00	01	11	10
$A$	0		1	1	1
	1		1	1	

Simplify the Boolean function

$$F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$$

		$yz$		$y$	
$x$		00	01	11	10
$x$	0	1			1
	1	1	1		1

$$\Sigma(0, 2, 4, 5, 6) = z' + xy'$$

$$A'C + A'B + AB'C + BC = C + A'B$$

# 4- Variable K-Map

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$

(a)


		$y$			
		$yz$			
		00	01	11	10
$w$	$x$				
00		$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
01		$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
11		$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
10		$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		$z$			

}  $x$

(b)

Simplify the Boolean function

 
$$F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$



$$y' + w'z' + xz'$$

Simplify the Boolean function

$$F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

 

$$B'D' + B'C' + A'CD'$$

# PRODUCT OF SUMS SIMPLIFICATION

Simplify the following Boolean function in (a) sum of products and (b) product of sums.

$$F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$$

$$F = B'D' + B'C' + A'C'D$$

$$F = (A' + B')(C' + D')(B' + D)$$

		<i>CD</i>		<i>C</i>	
		00	01	11	10
<i>AB</i>	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1

*A* { 00, 01, 11, 10 } *B* { 00, 01, 11, 10 } *D* { 00, 01, 11, 10 }

# Completely and Incompletely Specified Logic Functions

Logical functions are of two types:

1. completely specified logical function
2. incompletely specified logical function

A logical function whose output is specified for all possible input combination called completely specified logical function.

A logical function whose output may not be specified for certain input combinations/conditions or for which a certain input combinations may never occur is called incomplete specified logical function.

Inputs			Output
A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	X

## Minimization of Incompletely Specified Logic Functions

- For a four bit binary 9's complementary circuit input  $> 9$  is not possible or output for input  $> 9$  is do not care. So, we put the do not care conditions for all  $WXYZ$  in the O/P.

$$w = \sum m(0,1) + \sum d(10,11,12,13,14,15) = f(A,B,C,D)$$

$$X = \sum m(2,3,4,5) + \sum d(10,11,12,13,14,15) = f(A,B,C,D)$$

$$Y = \sum m(2,3,6,7) + \sum d(10,11,12,13,14,15) = f(A,B,C,D)$$

$$Z = \sum m(0,2,4,6,8) + \sum d(10,11,12,13,14,15)$$



Simplify the Boolean function

$$F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$$

that has the don't-care conditions

$$d(w, x, y, z) = \Sigma(0, 2, 5)$$


		y			
		yz			
		00	01	11	10
w	wx	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		z			


(a)  $F = yz + w'x'$

		y			
		yz			
		00	01	11	10
w	wx	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		z			

(b)  $F = yz + w'z$

# Combinational Logic

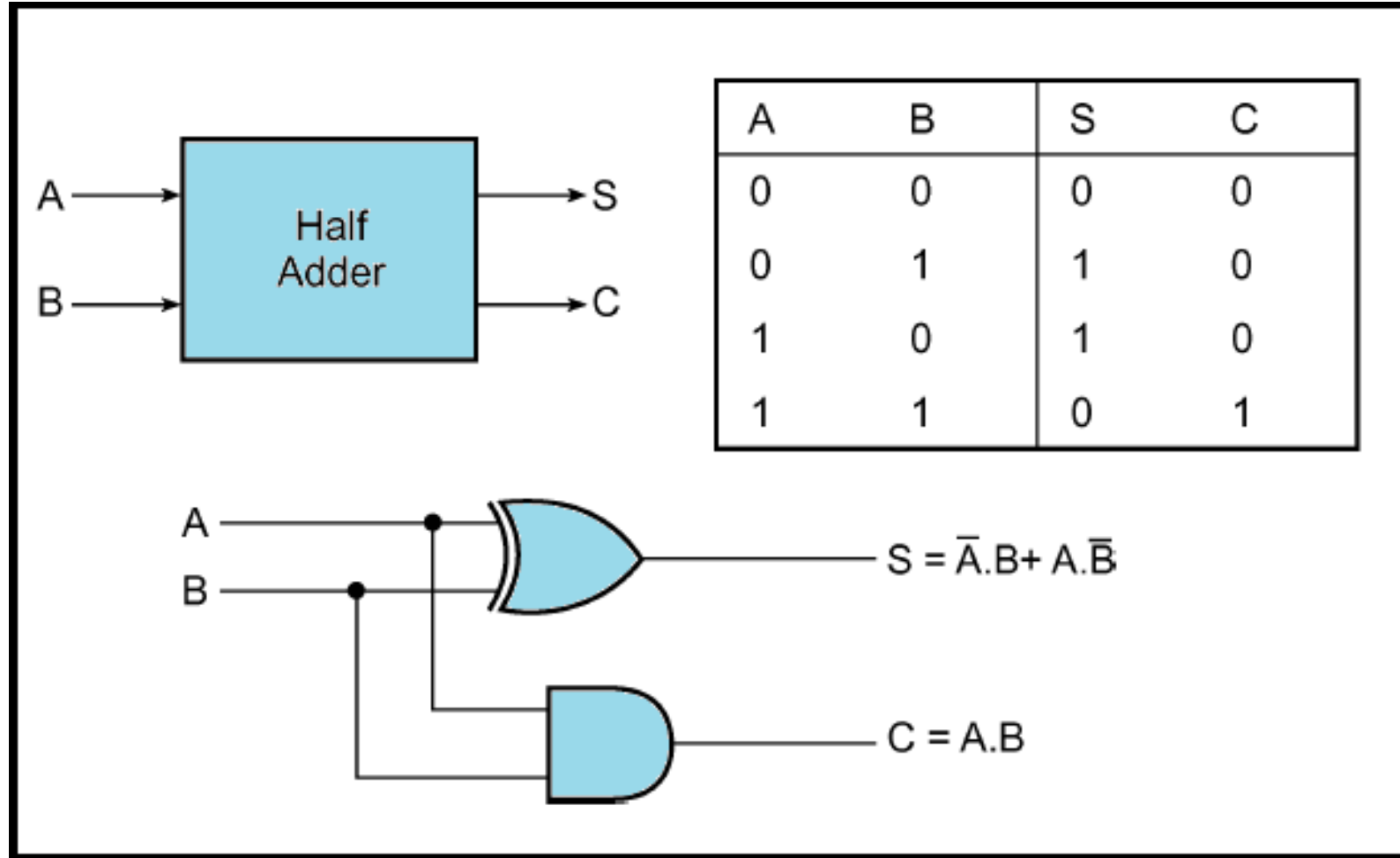

 

Inputs			Outputs	
A	B	C <sub>in</sub>	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

For Sum

A \ BC	00	01	11	10
0		1		1
1	1		1	

$$\therefore \text{Sum} = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC)$$


$$= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \quad (\because \bar{x}y + x\bar{y} = x \oplus y)$$

$$= A \oplus B \oplus C$$



For carry

A \ BC	00	01	11	10
0			1	
1		1	1	1

$$\text{Carry} = AB + BC + AC$$

 


# FULL ADDER Using HALF ADDERS

 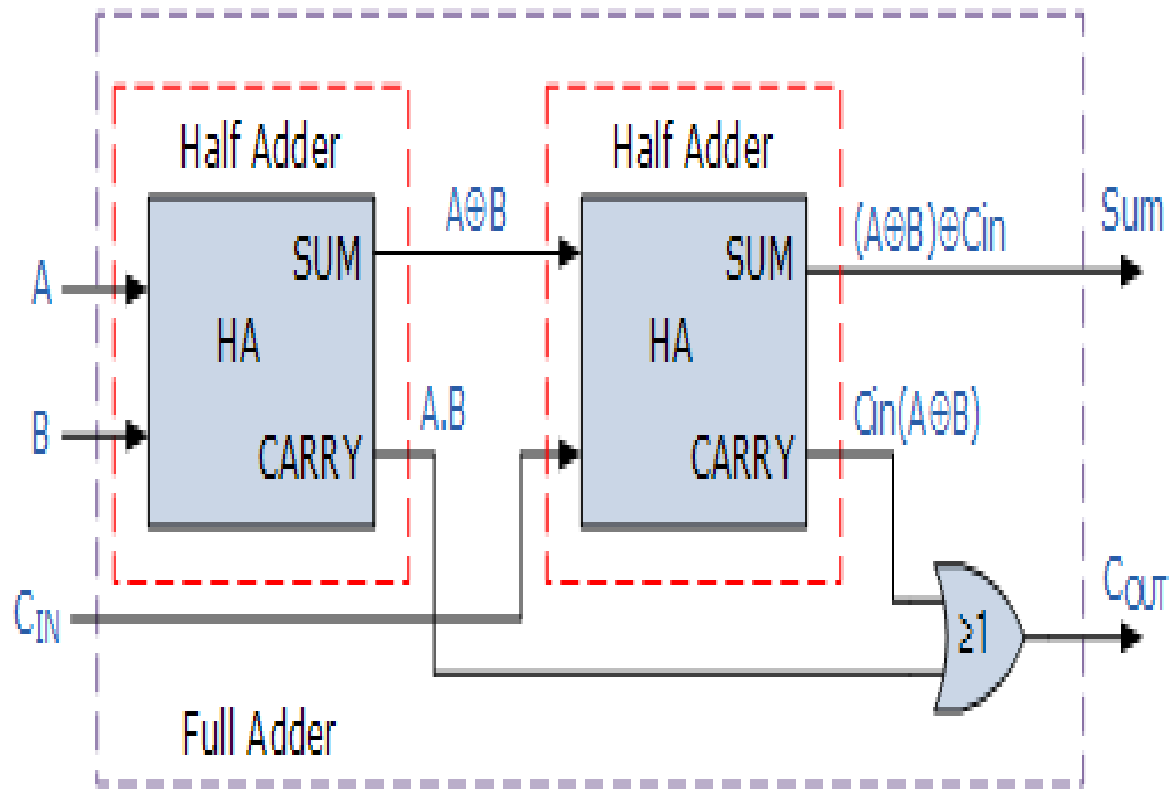

# Full Subtractor

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 

For Difference :-

A \ B	B			
	00	01	11	10
0		1		1
1	1		1	

$$\therefore \text{Difference} = A \oplus B \oplus C_n$$



$$\begin{aligned}
 \therefore \text{Difference} &= \bar{A} \bar{B} C_n + \bar{A} B \bar{C}_n + A \bar{B} \bar{C}_n + A B C_n \\
 &= \bar{A} (\bar{B} C_n + B \bar{C}_n) + A (\bar{B} \bar{C}_n + B C_n) \\
 &= \bar{A} (\bar{B} \oplus C_n) + A (B \oplus C_n) = \bar{A} (\bar{B} \oplus C_n) + A (B \oplus C_n) \\
 &= A \oplus B \oplus C_n = A \oplus B \oplus C_n
 \end{aligned}$$

For Cout :-

A \ B	B			
	00	01	11	10
0		1	1	1
1			1	

$$\therefore C_{out} = \bar{A} B + \bar{A} B C_n + A B C_n$$
 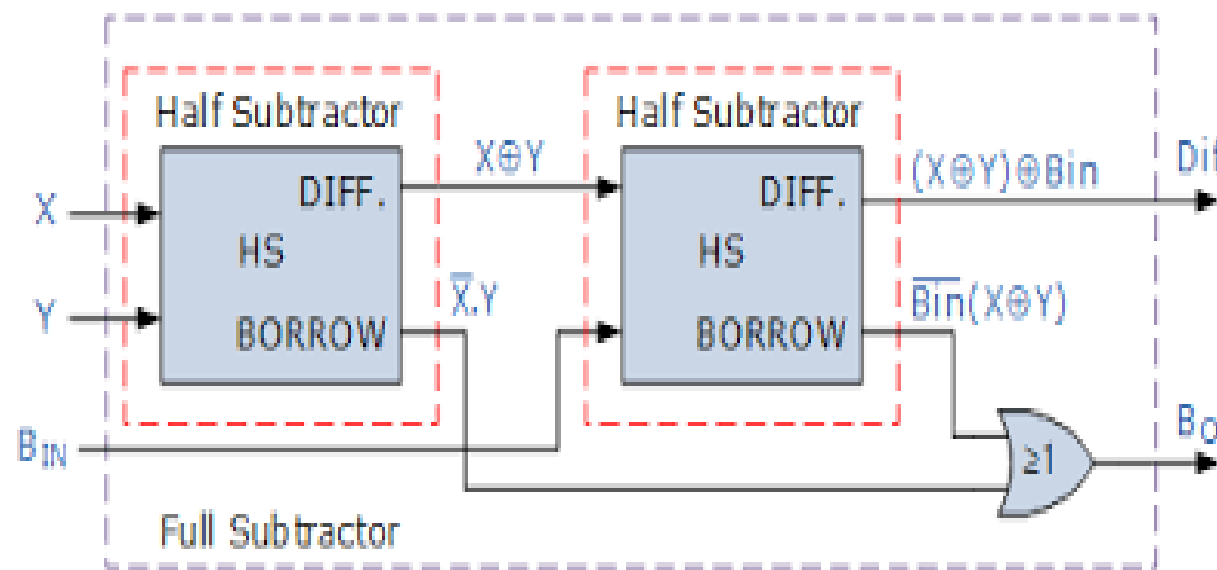
$$\therefore C_{out} = \bar{A} B + \bar{A} B C_n + A B C_n$$





# Binary to Gray Code Conversion

Decimal Number

4 bit Binary  
Number

ABCD

4 bit Gray  
Code

G<sub>1</sub>G<sub>2</sub>G<sub>3</sub>G<sub>4</sub>

0  
1  
2  
3  
4  
5  
6  
7  
8  
9  
10  
11  
12  
13  
14  
15

0 0 0 0  
0 0 0 1  
0 0 1 0  
0 0 1 1  
0 1 0 0  
0 1 0 1  
0 1 1 0  
0 1 1 1  
1 0 0 0  
1 0 0 1  
1 0 1 0  
1 0 1 1  
1 1 0 0  
1 1 0 1  
1 1 1 0  
1 1 1 1

0 0 0 0  
0 0 0 1  
0 0 1 1  
0 0 1 0  
0 1 1 0  
0 1 1 1  
0 1 0 1  
0 1 0 0  
1 1 0 0  
1 1 0 1  
1 1 1 1  
1 1 1 0  
1 0 1 0  
1 0 1 1  
1 0 0 1  
1 0 0 0

# Simplification using K-maps:

$G_3$

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

$$G_3 = B_3$$

$G_2$

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

$$G_2 = \overline{B_3} B_2 + B_3 \overline{B_2}$$

$$G_2 = B_3 \oplus B_2$$

$G_1$

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1

$$G_1 = B_2 \overline{B_1} + \overline{B_2} B_1$$

$$G_1 = B_2 \oplus B_1$$


$G_0$

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$G_0 = \overline{B_1} B_0 + B_1 \overline{B_0}$$

$$G_0 = B_1 \oplus B_0$$

## Logic Diagram:

 

# Gray Code to Binary Code Conversion

Truth Table:

INPUT ( GRAY CODE)					OUTPUTS (BINARY)				Binary
G3	G2	G1	G0		B3	B2	B1	B0	
0	0	0	0		0	0	0	0	
0	0	0	1		0	0	0	1	
0	0	1	0		0	0	1	1	
0	0	1	1		0	0	1	0	
0	1	0	0		0	1	1	1	
0	1	0	1		0	1	1	0	
0	1	1	0		0	1	0	0	
0	1	1	1		0	1	0	1	
1	0	0	0		1	1	1	1	
1	0	0	1		1	1	1	0	
1	0	1	0		1	1	0	0	
1	0	1	1		1	1	0	1	
1	1	0	0		1	0	0	0	
1	1	0	1		1	0	0	1	
1	1	1	0		1	0	1	1	
1	1	1	1		1	0	1	0	

## Simplification using K-Maps:

B<sub>3</sub>

$G_3 \backslash G_2 \quad G_1, G_0$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

$$B_3 = G_3$$

B<sub>2</sub>

$G_3 \backslash G_2 \quad G_1, G_0$	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

$$B_2 = \overline{G_3} G_2 + G_3 \overline{G_2}$$

$$B_2 = G_3 \oplus G_2$$

B<sub>1</sub>

$G_3 \backslash G_2 \quad G_1, G_0$	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	0	0	1	1
10	1	1	0	0

$$B_1 = \overline{G_3} \overline{G_2} G_1 + \overline{G_3} G_2 G_1 + \overline{G_3} G_2 \overline{G_1} + G_3 \overline{G_2} \overline{G_1}$$

$$= G_1 (\overline{G_3} \overline{G_2} + \overline{G_3} G_2) + \overline{G_1} (\overline{G_3} G_2 + G_3 \overline{G_2})$$

$$= G_1 (\overline{G_3} \oplus G_2) + \overline{G_1} (G_3 \oplus G_2)$$

$$= G_1 \oplus G_3 \oplus G_2$$

$$B_1 = G_1 \oplus B_2$$


## Simplification using K-Maps:

		<u>B<sub>0</sub></u>			
<u>A<sub>3</sub>A<sub>2</sub></u>	<u>A<sub>1</sub>A<sub>0</sub></u>	00	01	11	10
	00	0	1	0	1
01	1	0	1	0	1
11	0	1	0	1	0
10	1	0	1	0	1

$$\begin{aligned}
 B_0 &= \overline{A_3} \overline{A_2} \overline{A_1} A_0 + \overline{A_3} \overline{A_2} A_1 \overline{A_0} + \overline{A_3} A_2 \overline{A_1} \overline{A_0} + \overline{A_3} A_2 A_1 A_0 \\
 &\quad + \overline{A_3} A_2 \overline{A_1} A_0 + \overline{A_3} A_2 A_1 \overline{A_0} + \overline{A_3} A_2 A_1 A_0 \\
 &= \overline{A_3} \overline{A_2} (\overline{A_1} A_0 + A_1 \overline{A_0}) + \overline{A_3} A_2 (\overline{A_1} \overline{A_0} + A_1 A_0) \\
 &\quad + \overline{A_3} A_2 (\overline{A_1} A_0 + A_1 \overline{A_0}) + \overline{A_3} A_2 (\overline{A_1} \overline{A_0} + A_1 A_0) \\
 &= \overline{A_3} \overline{A_2} (A_1 \oplus A_0) + \overline{A_3} A_2 (\overline{A_1} \oplus \overline{A_0}) \\
 &\quad + \overline{A_3} A_2 (A_1 \oplus A_0) + \overline{A_3} A_2 (\overline{A_1} \oplus \overline{A_0}) \\
 &= (A_1 \oplus A_0) (\overline{A_3} \overline{A_2} + \overline{A_3} A_2) + (\overline{A_1} \oplus \overline{A_0}) (\overline{A_3} \overline{A_2} + \overline{A_3} A_2) \\
 &= (A_1 \oplus A_0) (\overline{A_3} \oplus \overline{A_2}) + (\overline{A_1} \oplus \overline{A_0}) (\overline{A_3} \oplus \overline{A_2}) \\
 &= A_0 \oplus A_1 \oplus A_2 \oplus A_3
 \end{aligned}$$

$$B_0 = A_0 \oplus B_1$$

## Logic Diagram:

 




# What is a Multiplexer (MUX)?


- A MUX is a digital switch that has multiple inputs (sources) and a single output (destination).
- The select lines determine which input is connected to the output.
- MUX Types
  - 2-to-1 (1 select line)
  - 4-to-1 (2 select lines)
  - 8-to-1 (3 select lines)
  - 16-to-1 (4 select lines)

Multiplexer  
Block Diagram

 




# Typical Application of a MUX

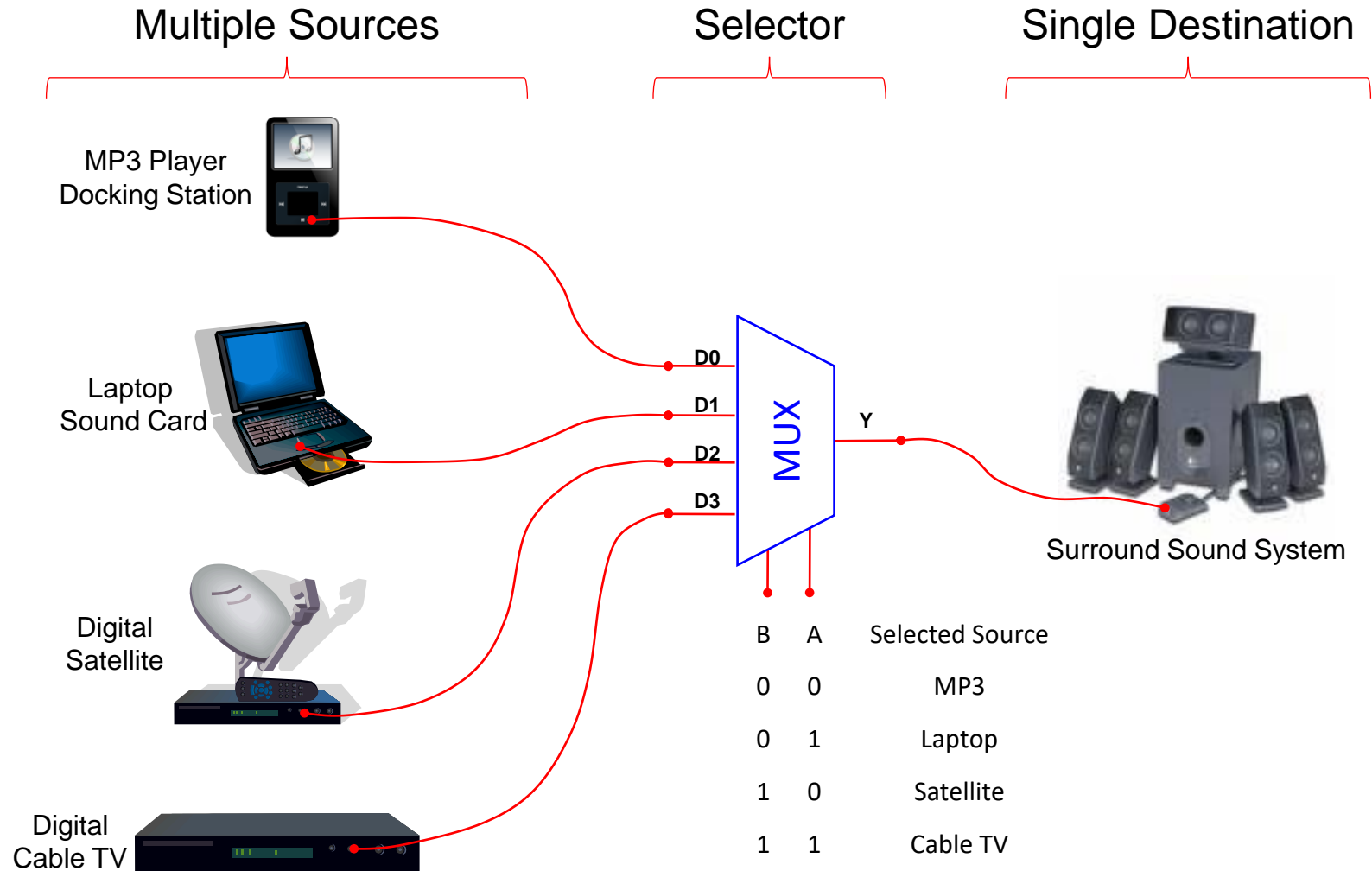

# Multiplexer/Demultiplexers

Multiplexing means Generally a  $(n : 1)$  multiplexer or a data selector contains the following:

 1.  $n$  number of inputs of the multiplexer
2. only one output of the multiplexer
3.  $m$  select/Address lines
4. one strobe/enable input (optional)




All inputs and outputs should be purely logical or binary input.

For  $n : 1$  multiplexer, each input will be selected at the single output at any instant of time, depends upon the input applied to the select/address inputs. Switching circuit connects a particular input to the output.

Here  $m$  and  $n$  are related by  $2^m = n$


# Design of a 2/1 Mux

- 2/1 mux Block Diagram


 


- Truth Table

S	D <sub>1</sub>	D <sub>0</sub>	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


# 4-to-1 Multiplexer (MUX)

  


B	A	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

# 4-to-1 Multiplexer Waveforms

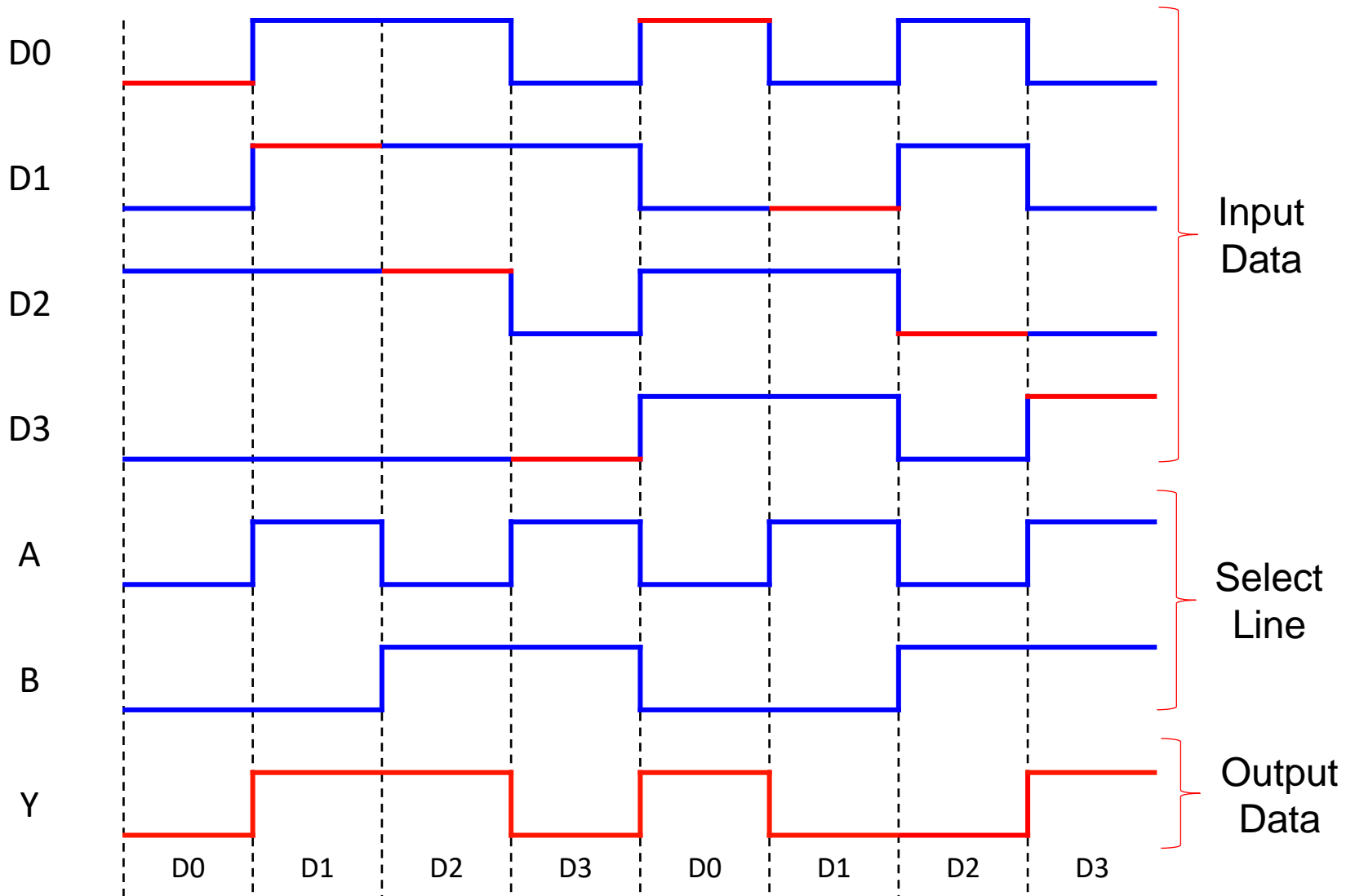

# Medium Scale Integration MUX

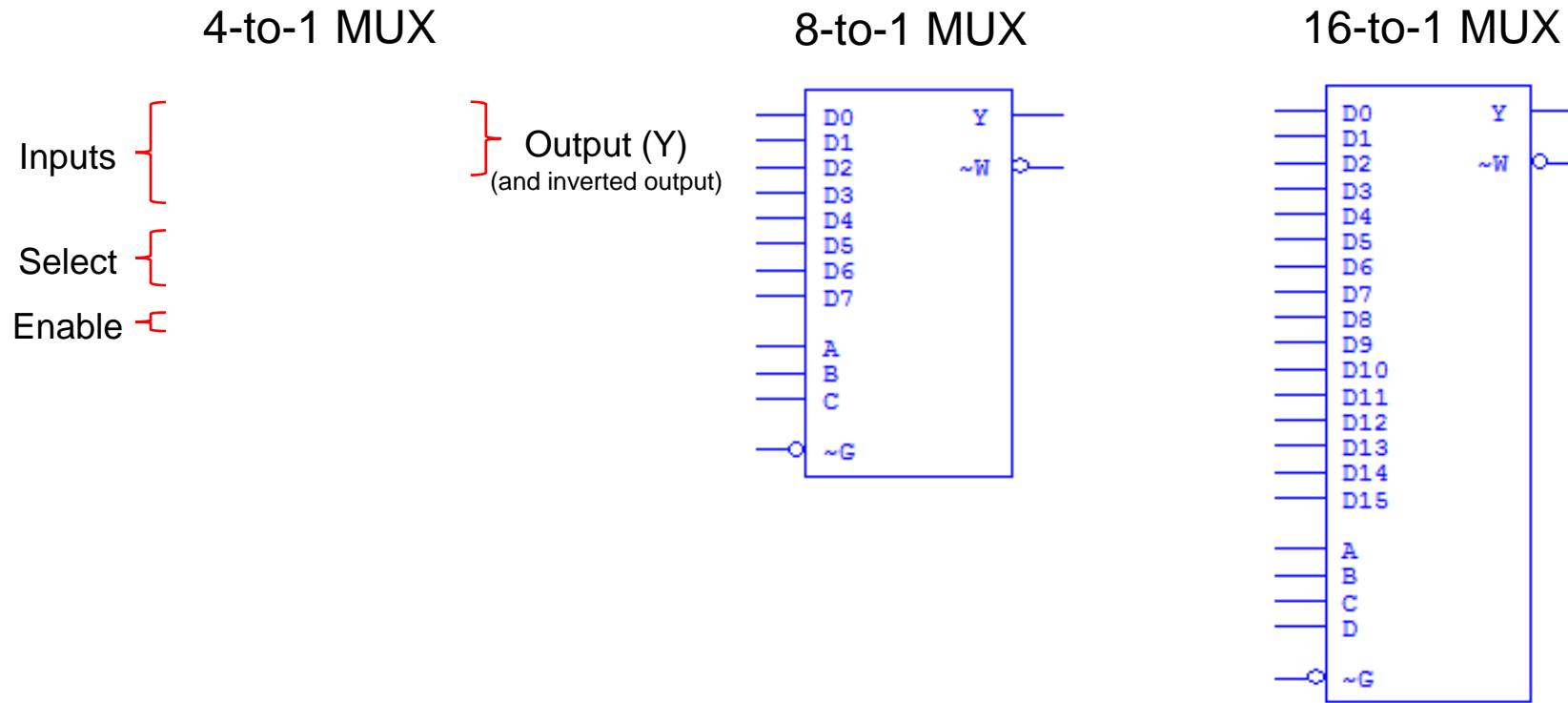


When two or more MUX are enclosed with in single chip

Selection and enable inputs in multiple unit IC may be common to all multiplexers. A Quadruple 2 to 1 line multiplexer IC is shown here.

It has 4 MUX each capable of selecting one of 2 input lines.

 O/P Y1 can be selected to be equal to either A1 or B1..similarly others





Function table

$E$	$S$	Output $Y$
1	$X$	all 0's
0	0	select $A$
0	1	select $B$

# Boolean Function Implementation

For implementing any Boolean function of  $n$  variable with  $2^n$  to 1 MUX is possible. However more optimize way is also there.

If we have Boolean function of  $n+1$  variable then out of it 1 is used for input data and rest  $n$  are used as select I/P.


If  $A$  is a single variable then input of MUX are to be chosen either  $A$  or  $A'$  or 1 or 0.

By judicious use of these four values to inputs and others as select I/P variables one can implement any Boolean function of  $n+1$  variables using  $2^n$  to 1 MUX.

$$F(A, B, C) = \Sigma(1, 3, 5, 6)$$

	$I_0$	$I_1$	$I_2$	$I_3$
$A'$	0	①	2	③
$A$	4	⑤	⑥	7
	0	1	$A$	$A'$

(c) Implementation table

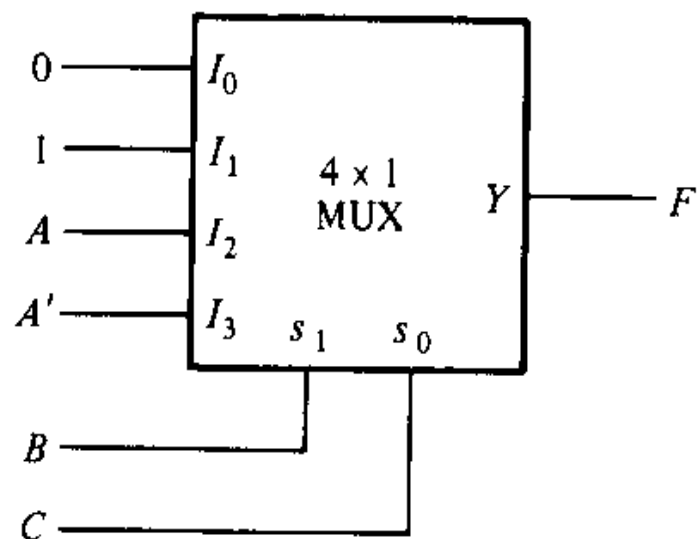

(a) Multiplexer implementation


Minterm	$A$	$B$	$C$	$F$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

(b) Truth table

$$F(A, B, C) = \Sigma(1, 2, 4, 5)$$

$A$	$B$	$C$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

(a) Truth table

 

(b) Multiplexer implementation


	$I_0$	$I_1$	$I_2$	$I_3$
$C'$	0	(2)	(4)	6
$C$	(1)	3	(5)	7
	$C$	$C'$	1	0

(c) Implementation table


Implement the following function with a multiplexer:

$$F(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15)$$


	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	①	①	2	③	④	5	6	7
$A$	⑧	⑨	10	11	12	13	14	⑮
	1	1	0	$A'$	$A'$	0	0	$A$

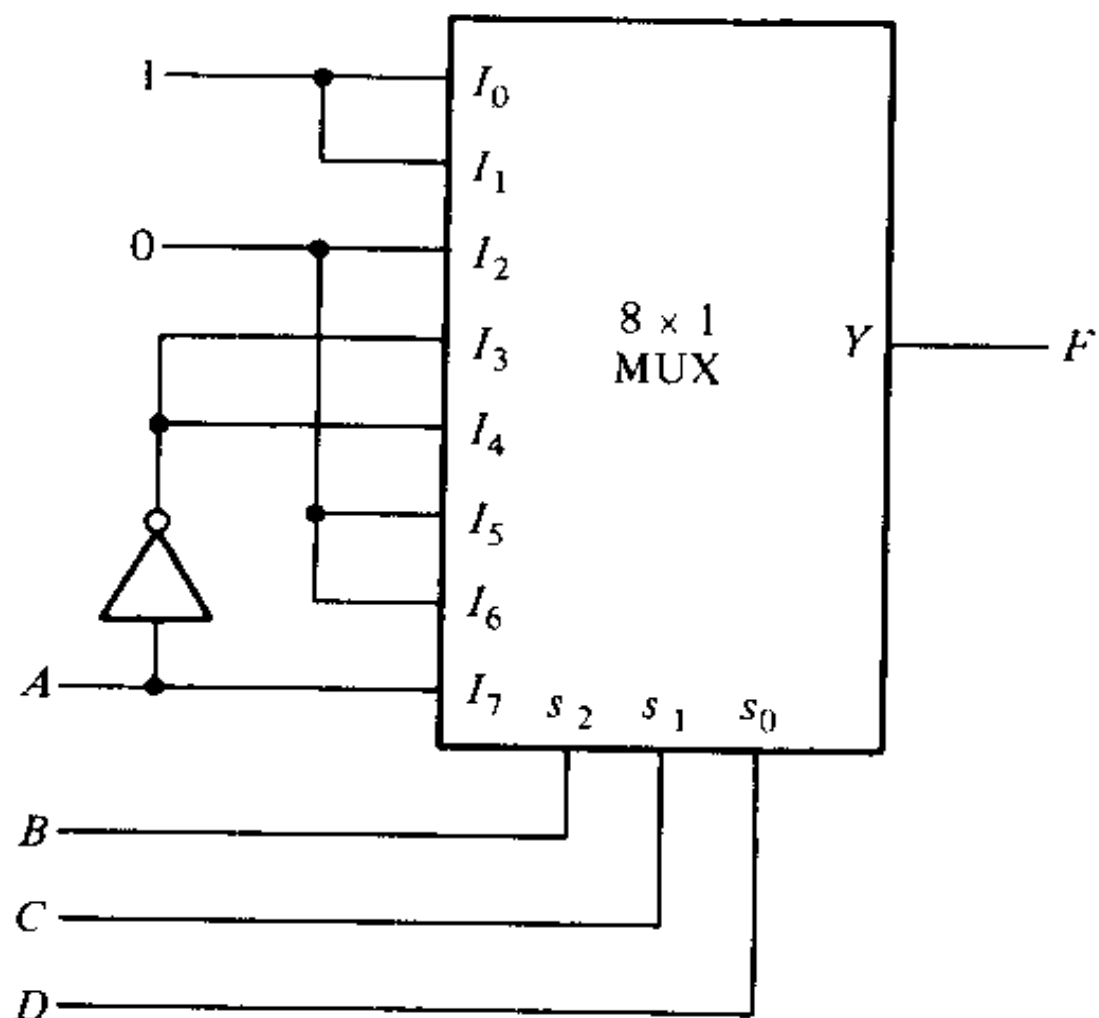
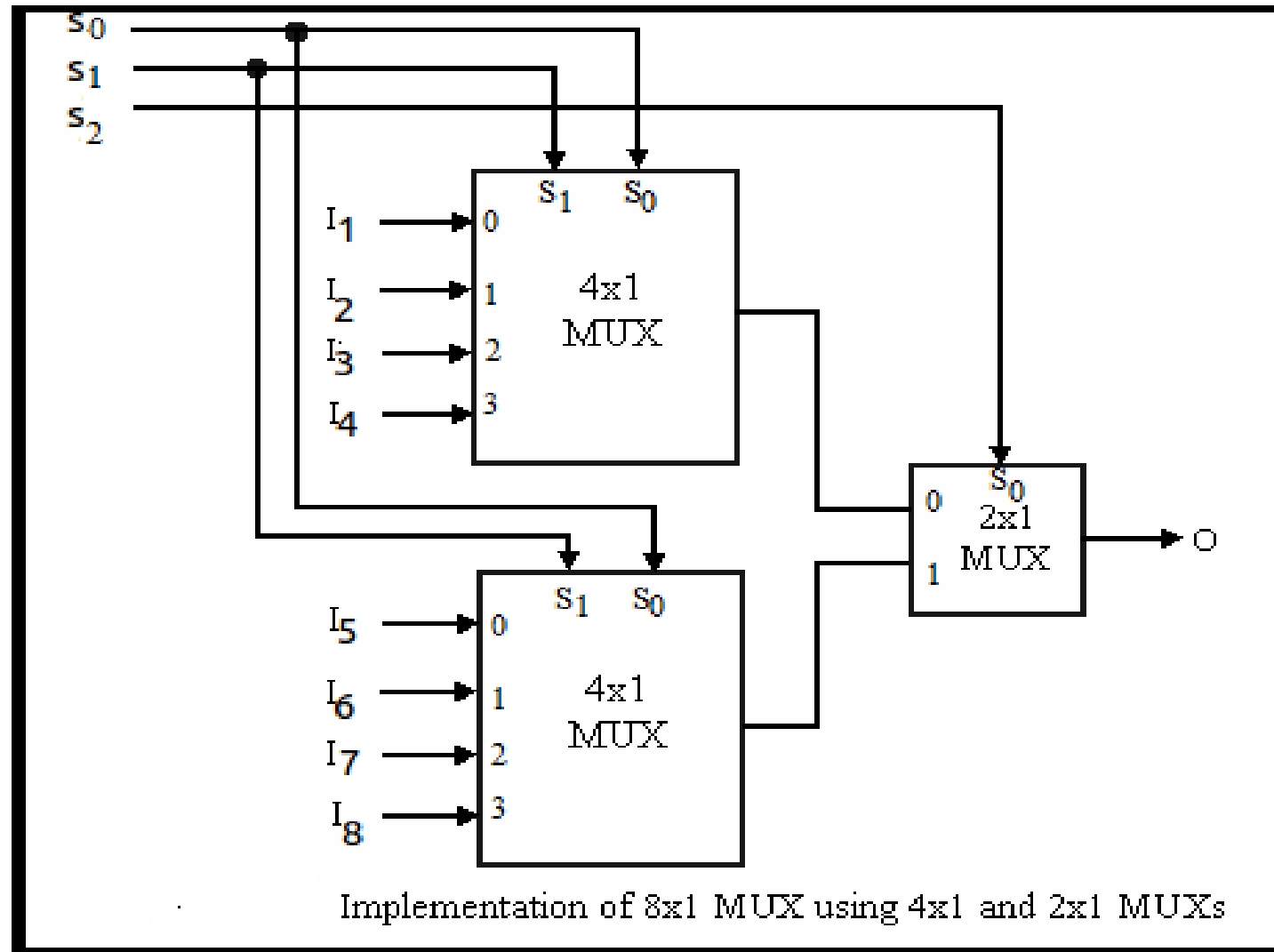
# Higher order MUX 8:1 MUX using 4:1 MUXs



# 8:1 MUX using two 4:1 MUX

 


S2	S1	S0	Y
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$


$$\begin{aligned}
 n &= 8 \\
 8/4 &= 2 \\
 &\quad \downarrow + \\
 2/4 &= 0.5 \quad = 2.5 \\
 &\quad \text{LEARN}
 \end{aligned}$$

# 16:1 MUX using 4:1 MUX

Inputs

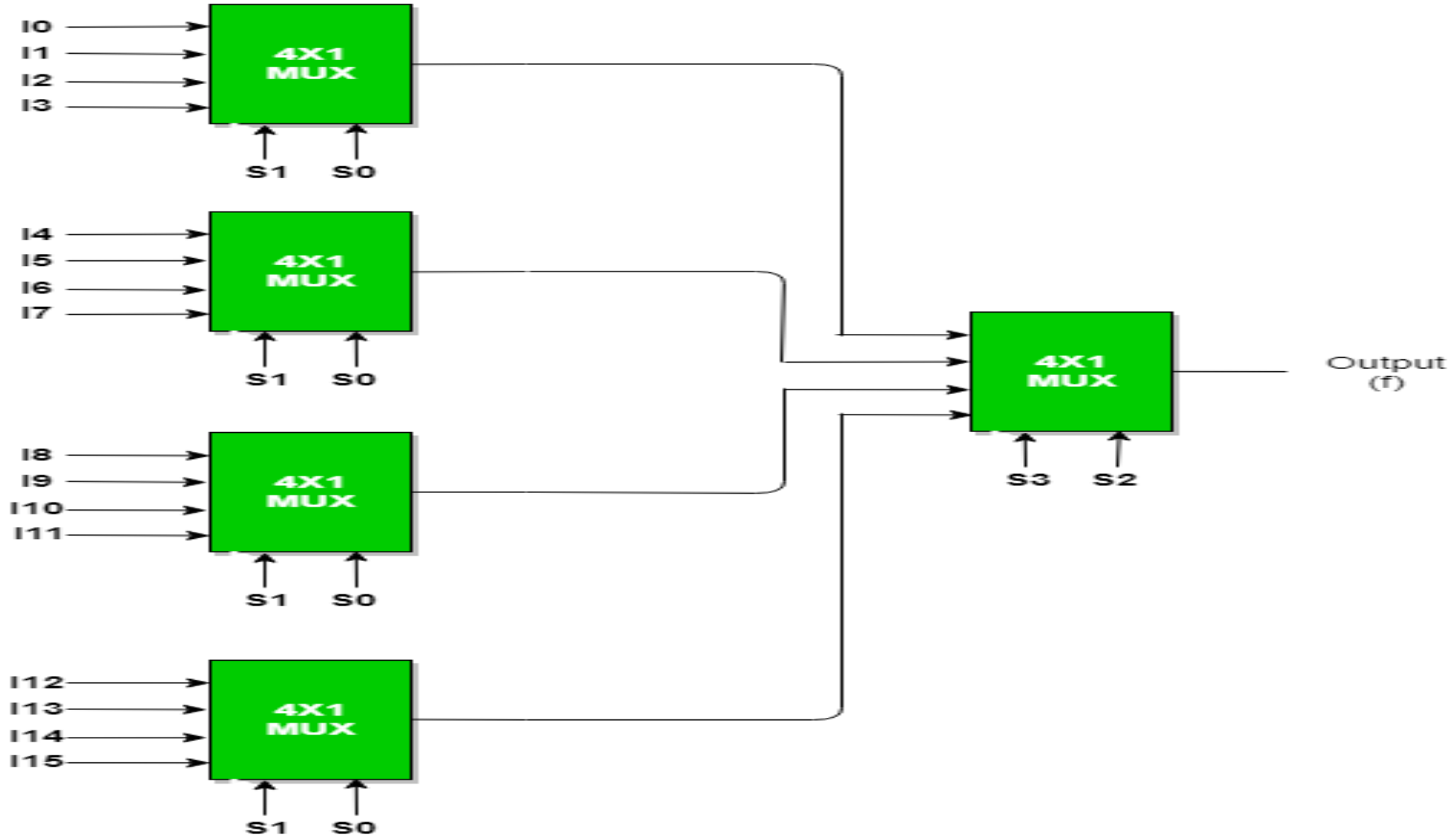



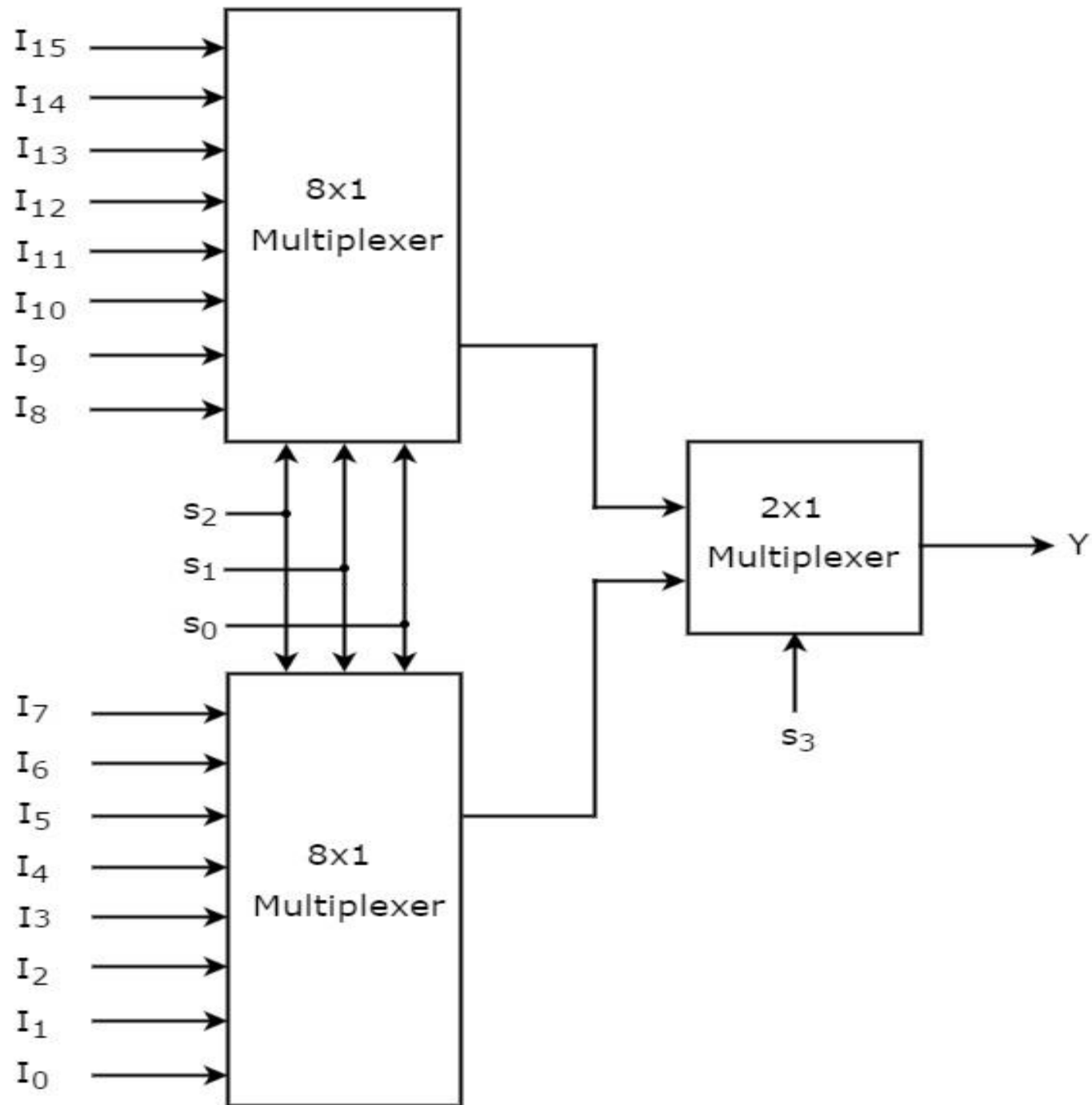


16:1 MUX using 8:1  
MUX


# What is a Demultiplexer (DEMUX)?

- A DEMUX is a digital switch with a single input (source) and a multiple outputs (destinations).
- The select lines determine which output the input is connected to.
- DEMUX Types
  - 1-to-2 (1 select line)
  - 1-to-4 (2 select lines)
  - 1-to-8 (3 select lines)
  - 1-to-16 (4 select lines)


Demultiplexer  
Block Diagram

 

# Typical Application of a DEMUX

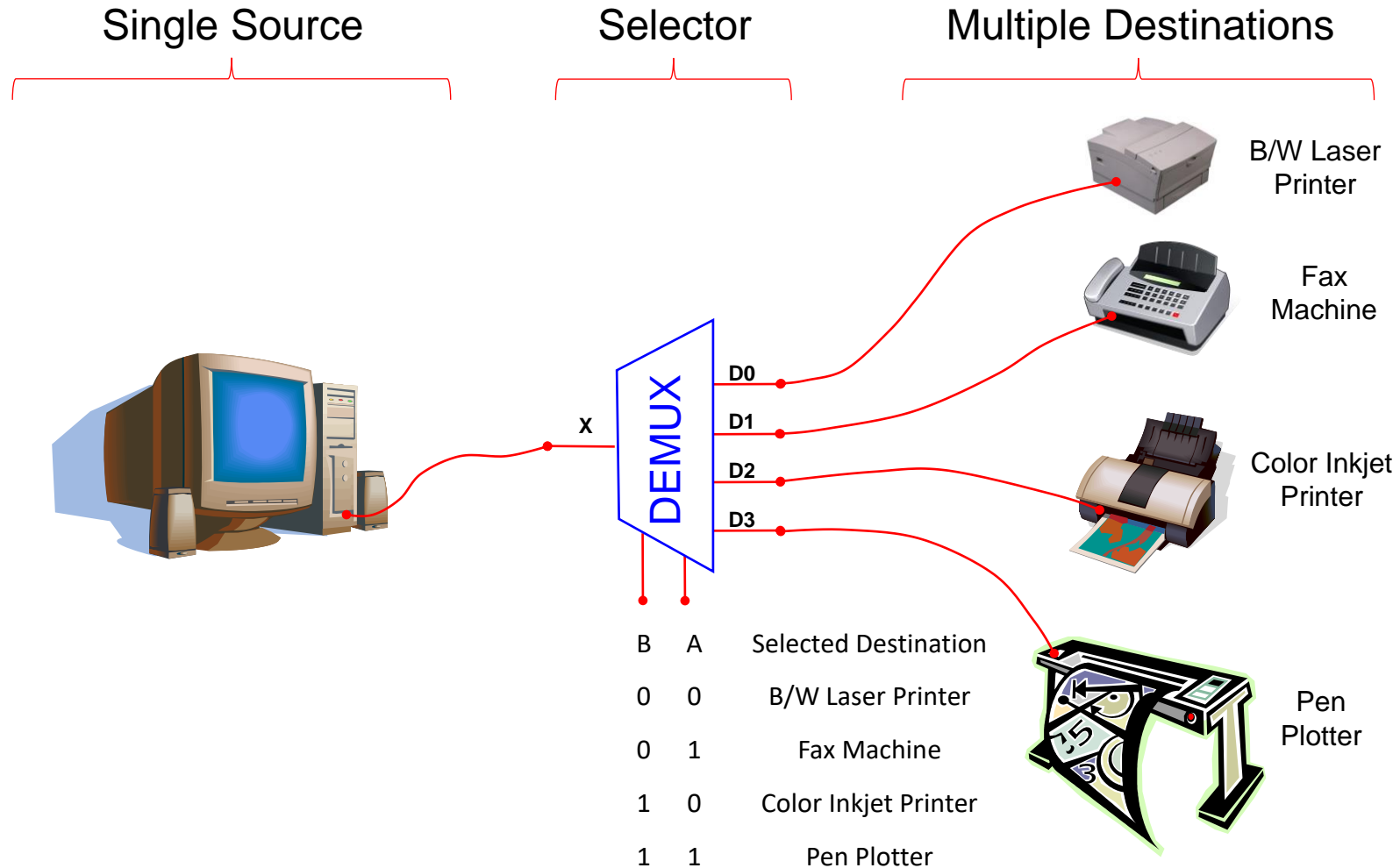



# 1: 2 Demux

 



Select (S)	Input (IN)	Out 1	Out 2
0	0	0	0
0	1	0	1
1	0	0	0
1	1	1	0

Enable	Select	Output	
E	S	Y0	Y1
0	x	0	0
1	0	0	D <sub>in</sub>
1	1	D <sub>in</sub>	0

x = Don't care

  


# 1-to-4 Demultiplexer (DeMUX)

  


B	A	D0	D1	D2	D3
0	0	X	0	0	0
0	1	0	X	0	0
1	0	0	0	X	0
1	1	0	0	0	X

# 1-to-4 De-Multiplexer Waveforms

 




# 1:8 Demux with Enable Input

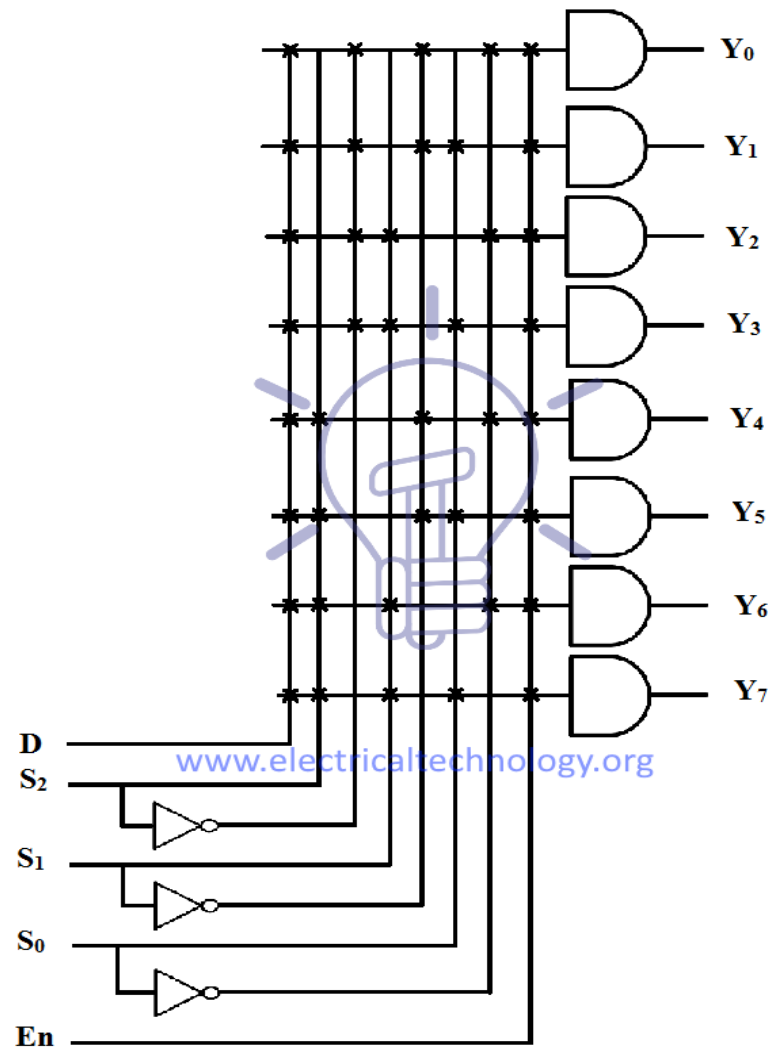

INPUT					OUTPUT							
En	D	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>
0	X	X	X	X	0	0	0	0	0	0	0	0
1	X	0	0	0	D	0	0	0	0	0	0	0
1	X	0	0	1	0	D	0	0	0	0	0	0
1	X	0	1	0	0	0	D	0	0	0	0	0
1	X	0	1	1	0	0	0	D	0	0	0	0
1	X	1	0	0	0	0	0	0	D	0	0	0
1	X	1	0	1	0	0	0	0	0	D	0	0
1	X	1	1	0	0	0	0	0	0	0	D	0
1	X	1	1	1	0	0	0	0	0	0	0	D



# Medium Scale Integration DEMUX

  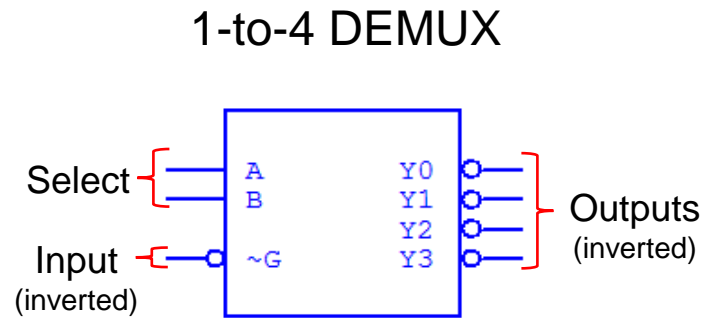


Note : Most Medium Scale Integrated (MSI) DEMUXs , like the three shown, have outputs that are inverted. This is done because it requires few logic gates to implement DEMUXs with inverted outputs rather than no-inverted outputs.



# Demultiplexer Tree 1:4 using 1:2 Demux

Truth Table


$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	$D_{in}$	0
0	1	0	0	0	$D_{in}$
1	0	$D_{in}$	0	0	0
1	1	0	0	0	0

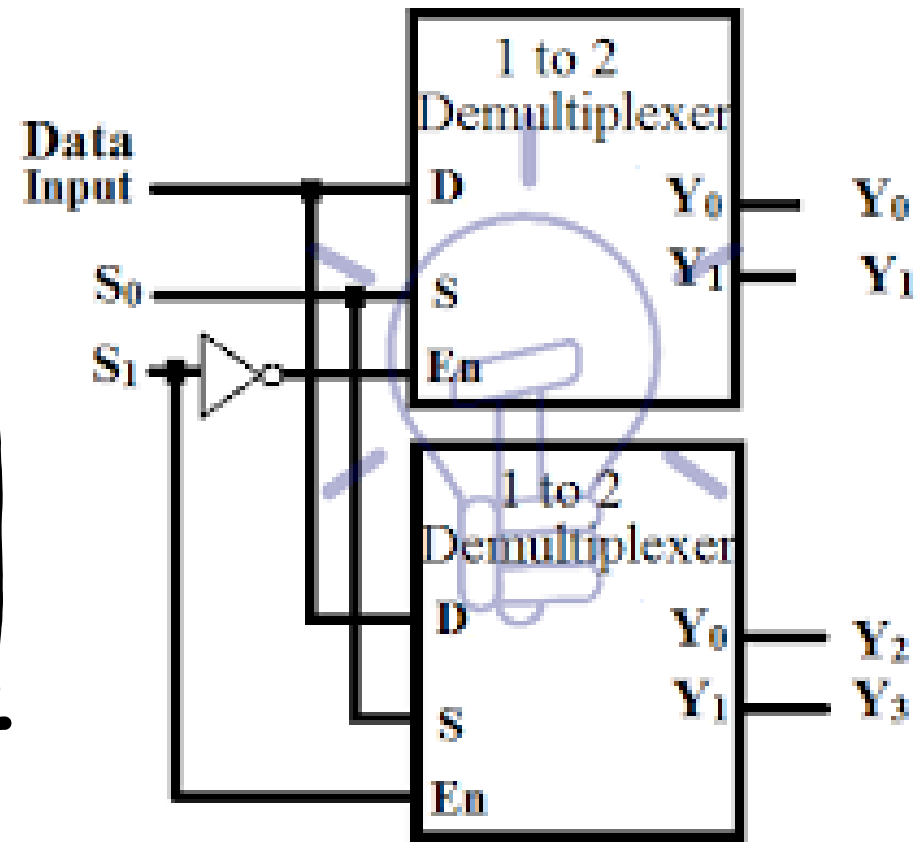

# 1:8 DeMUX Using 1:4

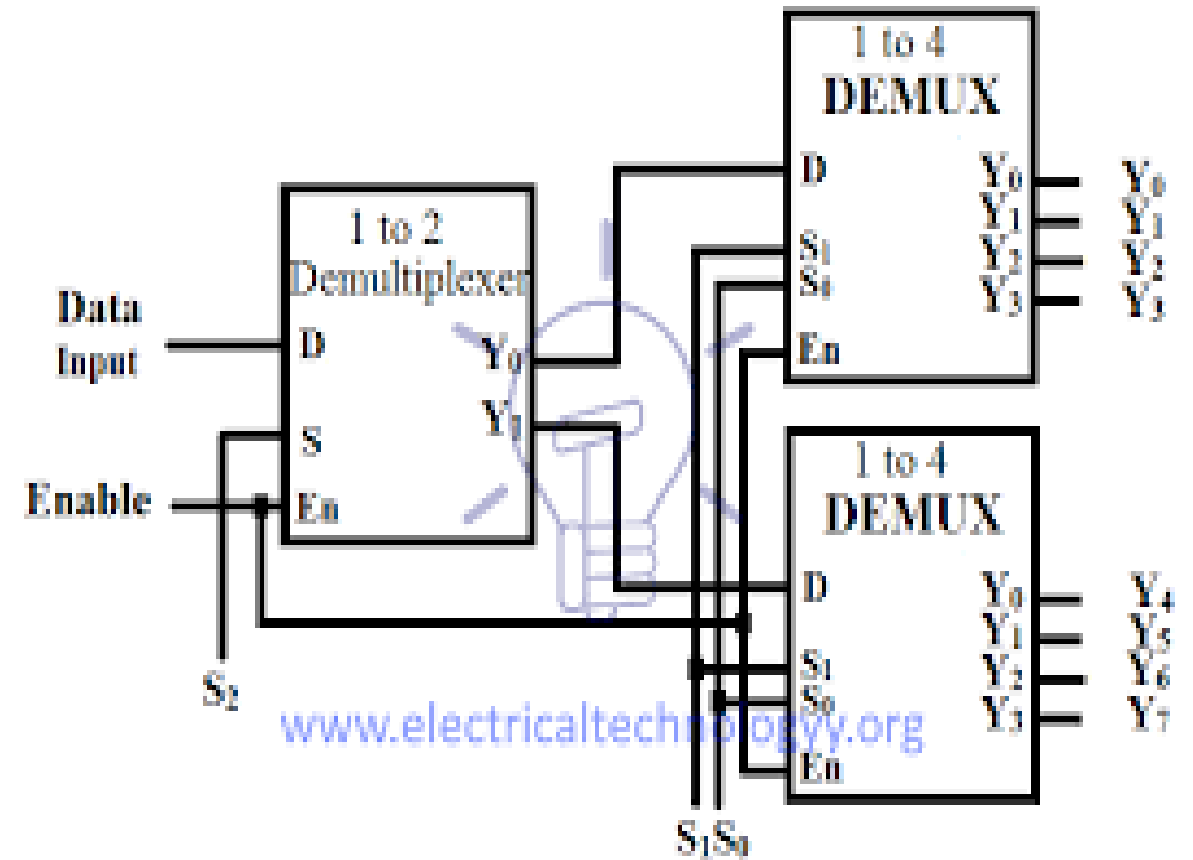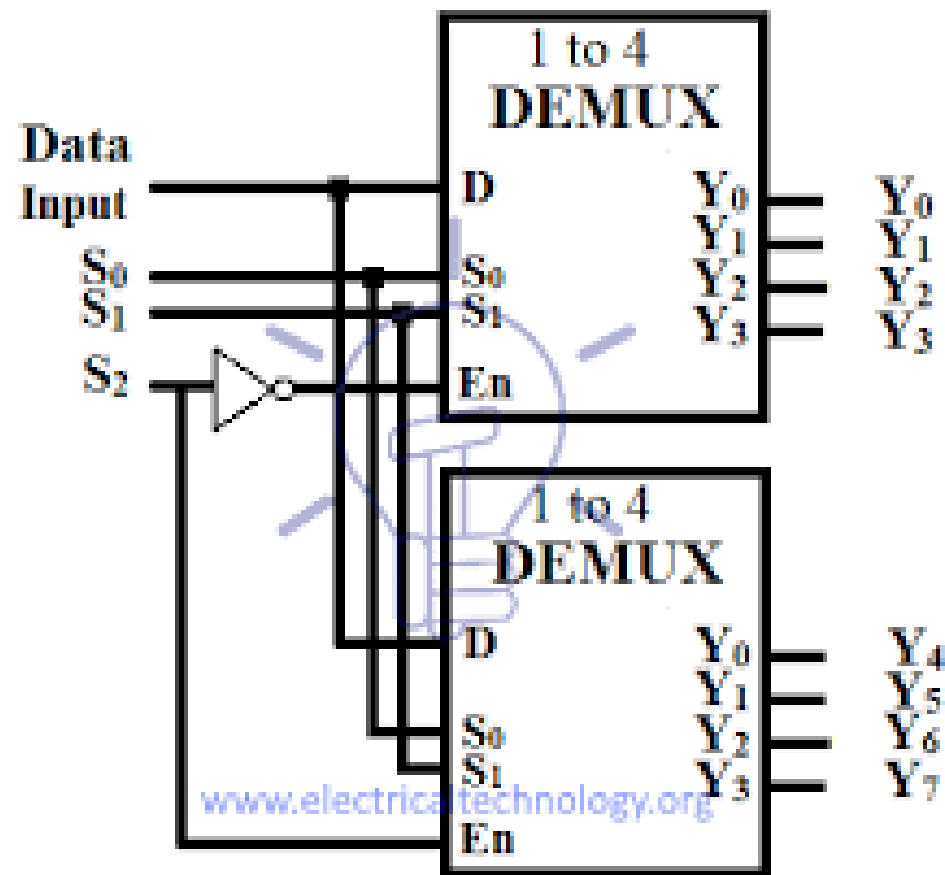


# Full Adder using 1:8 De MUX

 

**LEARN**

$$D(x,y,z) = \sum m(1,2,4,7)$$

$$B(x,y,z) = \sum m(1,2,3,7)$$

 


Draw 1:64 demultiplexer using 1:16 demux and 1: 4 demux

# Comparator




A	B	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

 

# 2-Bit Magnitude Comparator

Table 1. Truth Table of 2-Bit Magnitude Comparator

INPUT				OUTPUT		
A1	A0	B1	B0	A>B	A=B	A<B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	0	1	0
1	1	1	1	0	1	0

 

		$f(A>B)$					
		$B_1B_0$		00	01	11	10
$A_1A_0$	00	0	0	0	0		
	01	1	0	0	0		
	11	1	1	0	1		
	10	1	1	0	0		

We get the equation as  $f(A>B)$

$$= A_1\bar{B}_1 + A_0\bar{B}_1\bar{B}_0 + A_1A_0\bar{B}_0$$

K-Map for  $A<B$ :

		$B_1B_0$			
		00	01	11	10
$A_1A_0$	00	0	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	10	0	0	1	0

For  $A<B$

$$Y_1 = \bar{A}_1\bar{A}_0B_0 + \bar{A}_1B_1 + \bar{A}_0B_1B_0$$

K-Map for  $A=B$ :

		$B_1B_0$			
		00	01	11	10
$A_1A_0$	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	1

For  $A=B$

$$Y_2 = \bar{A}_1\bar{A}_0\bar{B}_1\bar{B}_0 + \bar{A}_1A_0\bar{B}_1B_0 + A_1A_0B_1B_0 + A_1\bar{A}_0B_1\bar{B}_0$$



# Binary Serial Adder

Let Register-1 hold the first number and register 2 holds the other no.

The D FF is cleared initially so  $Q=0$  and  $C_{in}=0$ .

The serial o/p (SO) of the two registers will provide the LSBs of the two number.


They will act bits a and b for full adder.

The FA will add these bits and produce sum and carry out  $C_o$ .

Thus addition of LSB is complete.

Now a clock pulse is applied to both the shift registers.

 Hence the two numbers are right shifted by one bit each.



The clock pulse gets applied to the D FF also and  $Q = C_{in} = C_{out} = 0$ .  
The adder adds the two bits available at the SO outputs of the two registers


## Advantages

The addition of a pair of bits only takes place at any instant of time  
(n-1) number of clock cycles are required to complete the addition  
The process of addition continues until the shift right control is disabled  
Sum is available in the serial form


## Drawback

- i) More time is required to complete the addition
- ii) A complicated ckt is required
- iii) The ckt contains more no of components
- iv) The Sum and Carry are available in the serial form hence result can't be observed at once.


Fig: Serial Adder

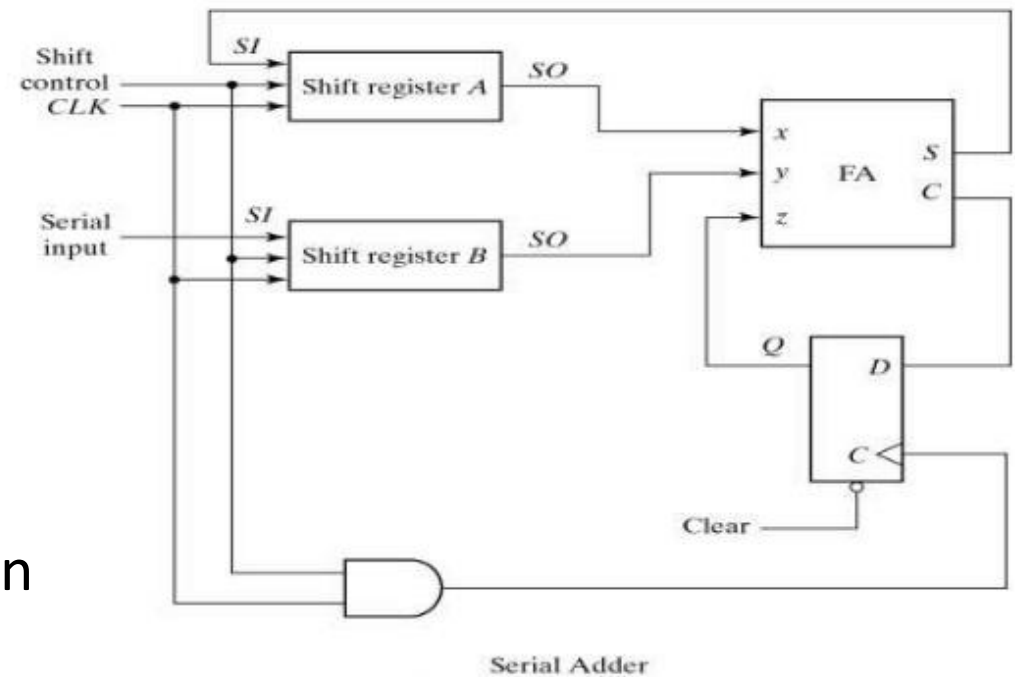

# Binary Parallel Adder

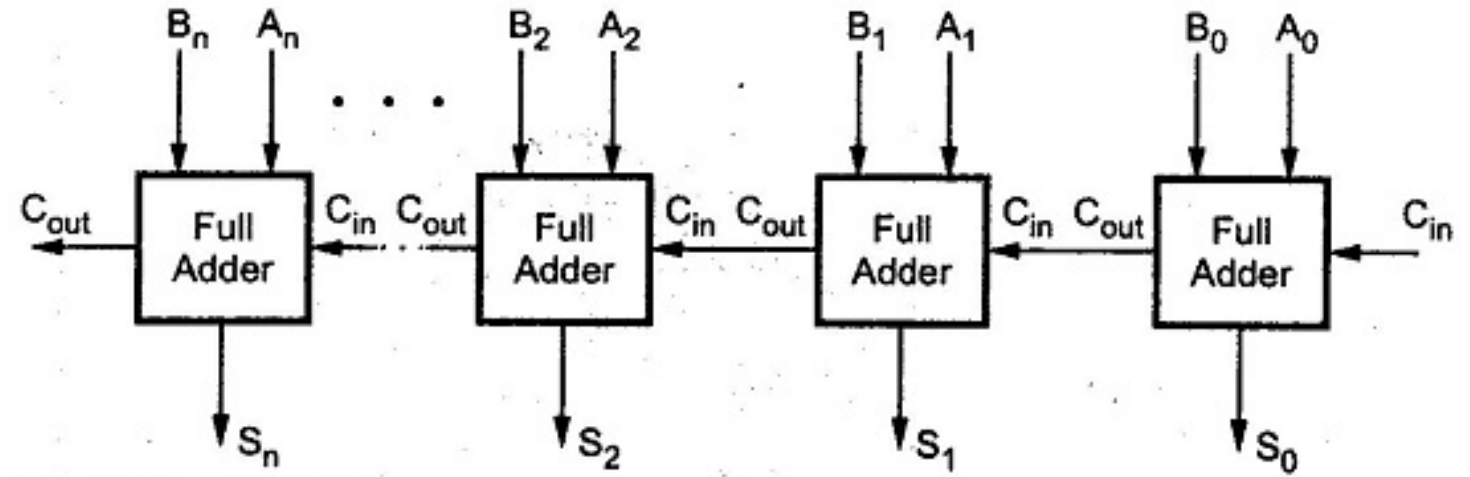

N-Bit Parallel Adder

 

# Cascading of Adders


 


Fig2. Cascading of two IC 7483s

# Binary Parallel Subtractor

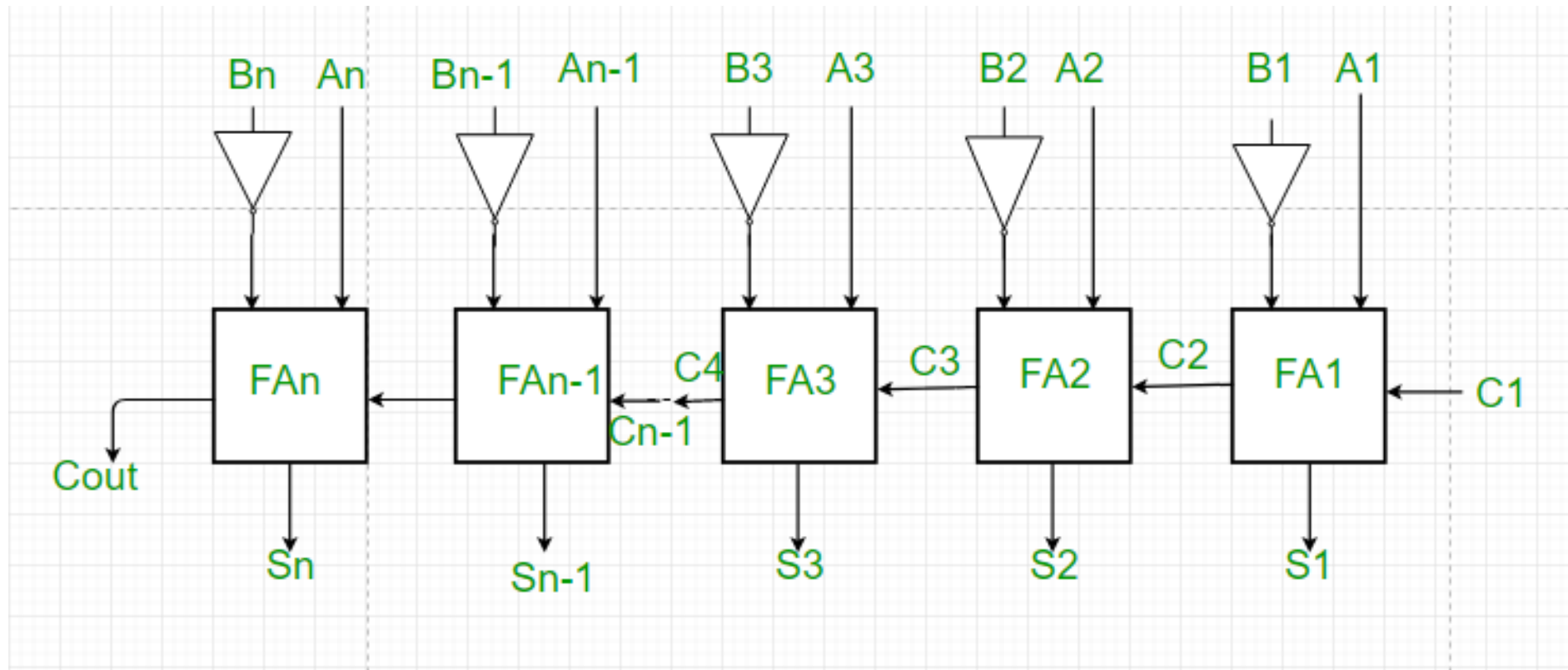

# Propagation delay in Parallel adder

