



Sardar Vallabhbhai National Institute of Technology, Surat

ECED Department

Subject: Digital Electronics and Logic Design (EC-207)

B.Tech Computer Engineering, Sem-III, Div - (A)

Date: 24-09-2020

Assignment for Practical - 7

1. Determine and plot the output voltage waveform for the given circuits. Also verify the same using Multisim.

a	
b	
c	

2. Draw the transfer characteristics for all the clipper configurations which are part of your today's practical (Practical – 7).
3. Assuming Symmetrical Sine wave input with peak value greater than the Zener reference voltage, predict the output and plot the Transfer Characteristics for the following Clipper Circuits:

