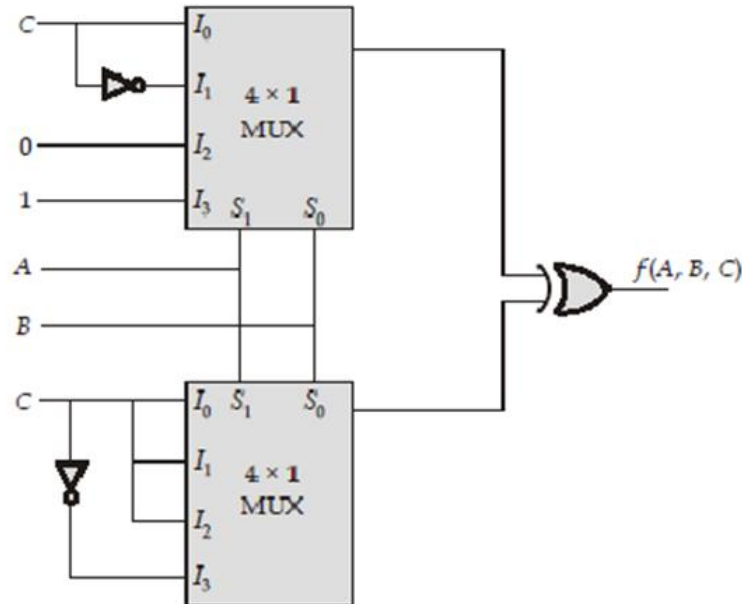


ASSIGNMENT-12


U19CS012

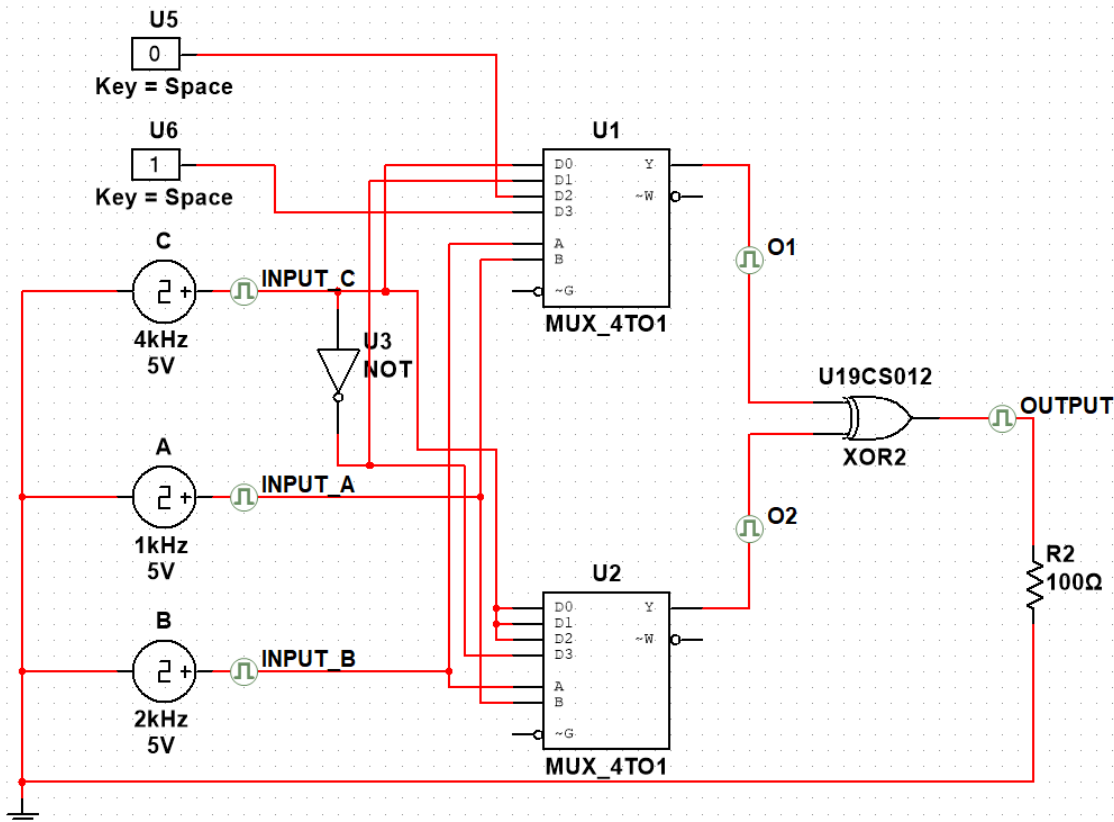1. Solve for output Function/Functions. Also verify the same using Multisim.




"A" Batch Question

Circuit Diagram [Multisim Implementation]



Grapher Image [Transient]

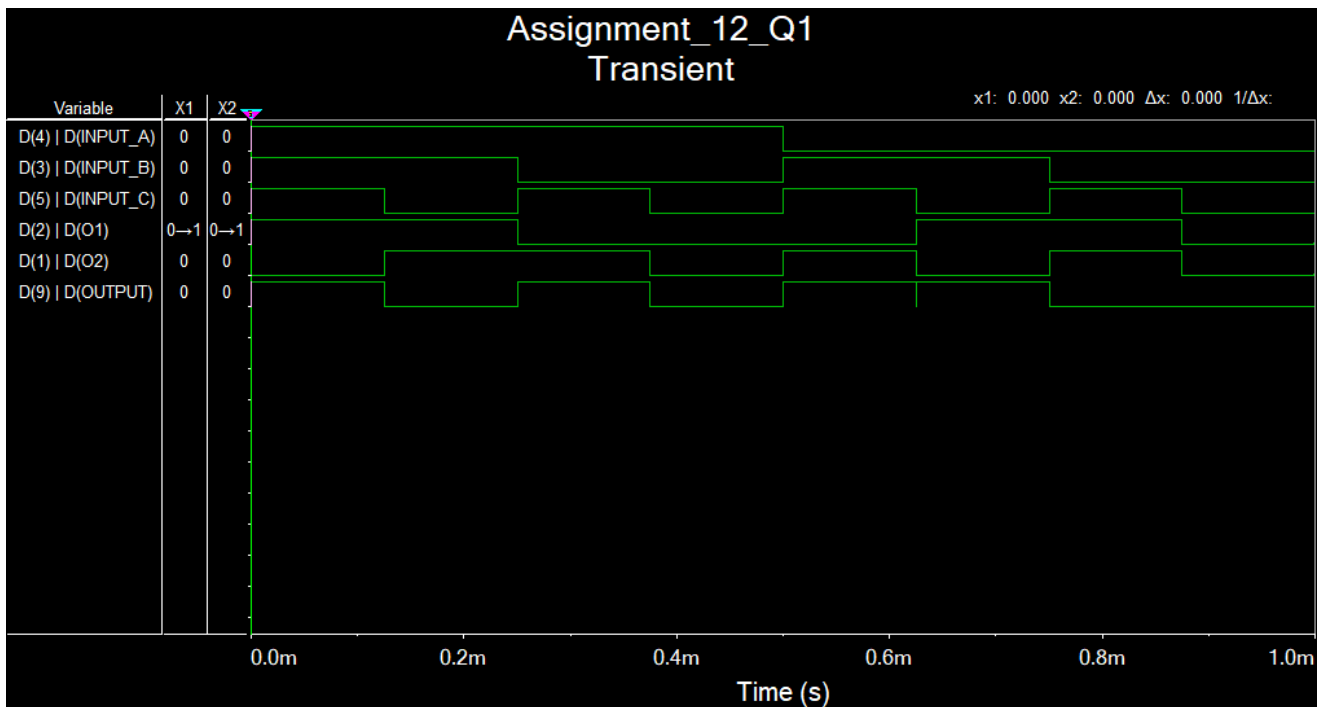

Theoretical Solution

UI9CS012 DEED Ass-12

Q.1.7 Theoretical Calculation

A	B	C	O1	O2	$f = O1 \oplus O2$
0	0	0	0	0	0
0	0	1	1	1	0
0	1	0	1	0	1
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	1	0
1	1	1	1	0	1

Result ↑

$$F(A, B, C) = \sum m(2, 3, 5, 7)$$

A \ BC	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	BC 11	$B\bar{C}$ 10
\bar{A} 0	0	1	1	1
A 1	0	1	1	0

$f = \bar{A}B + AC$

Minimized Expression using k-map

2. Design, implement and verify using Multisim: BCD to Excess - 3 Code Converter

BCD(8421)				Excess-3			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Theoretical Solution

UI9CS012 [DELD Ass-12]

Left Karnaugh Map (W):

CD \ AB	00	01	11	10
00 ($\bar{A}\bar{B}$)	0	1	3	2
01 ($\bar{A}B$)	4	1	5	7
11 (AB)	12	X	13	X
10 ($A\bar{B}$)	8	1	9	X


Right Karnaugh Map (X):

CD \ AB	00	01	11	10
00 ($\bar{A}\bar{B}$)	0	1	3	2
01 ($\bar{A}B$)	4	1	5	7
11 (AB)	12	X	13	X
10 ($A\bar{B}$)	8	1	9	X


Logic Expressions:

$$W = A + BC + BD$$

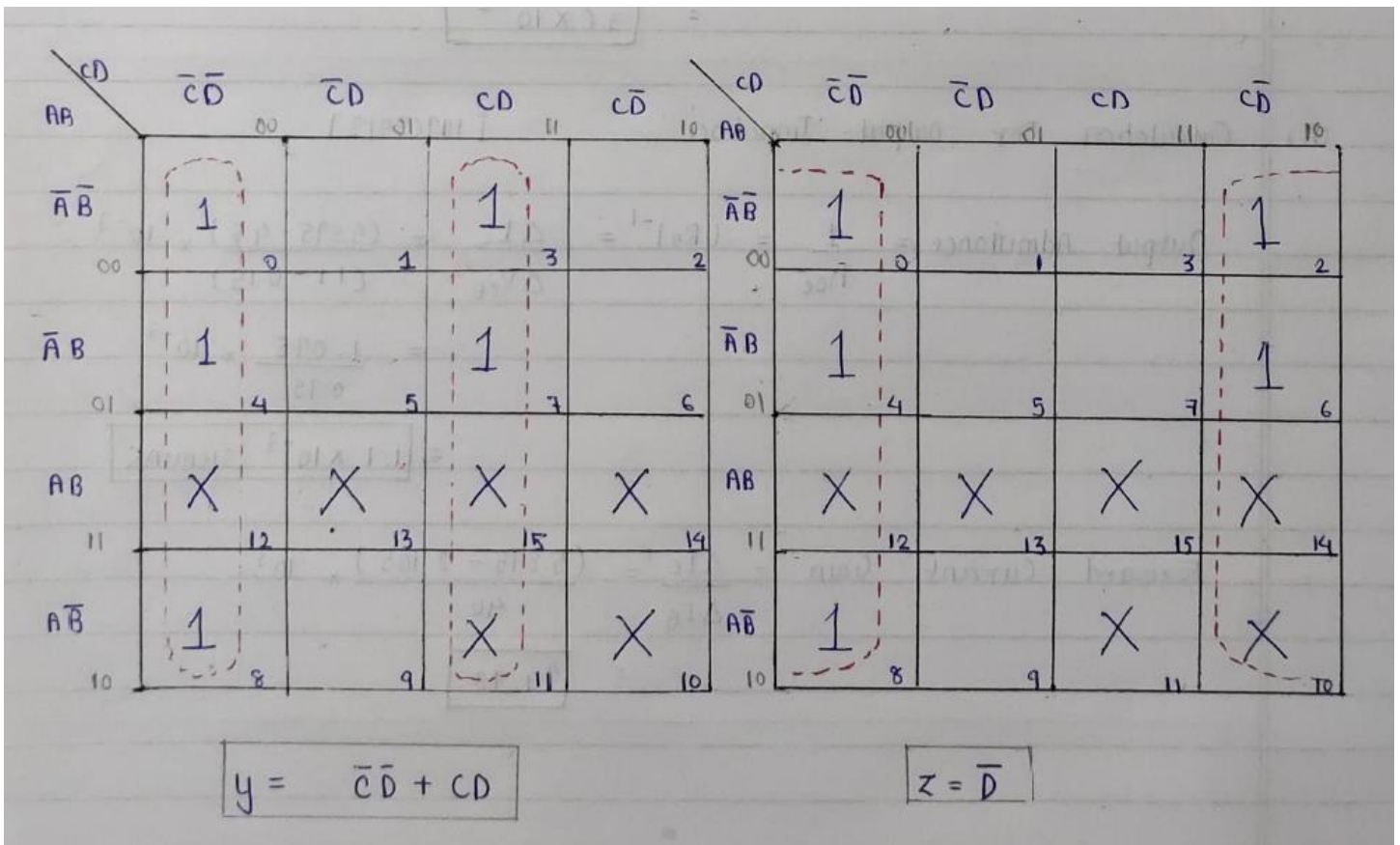
$$X = B\bar{C}\bar{D} + \bar{B}D + \bar{B}C$$



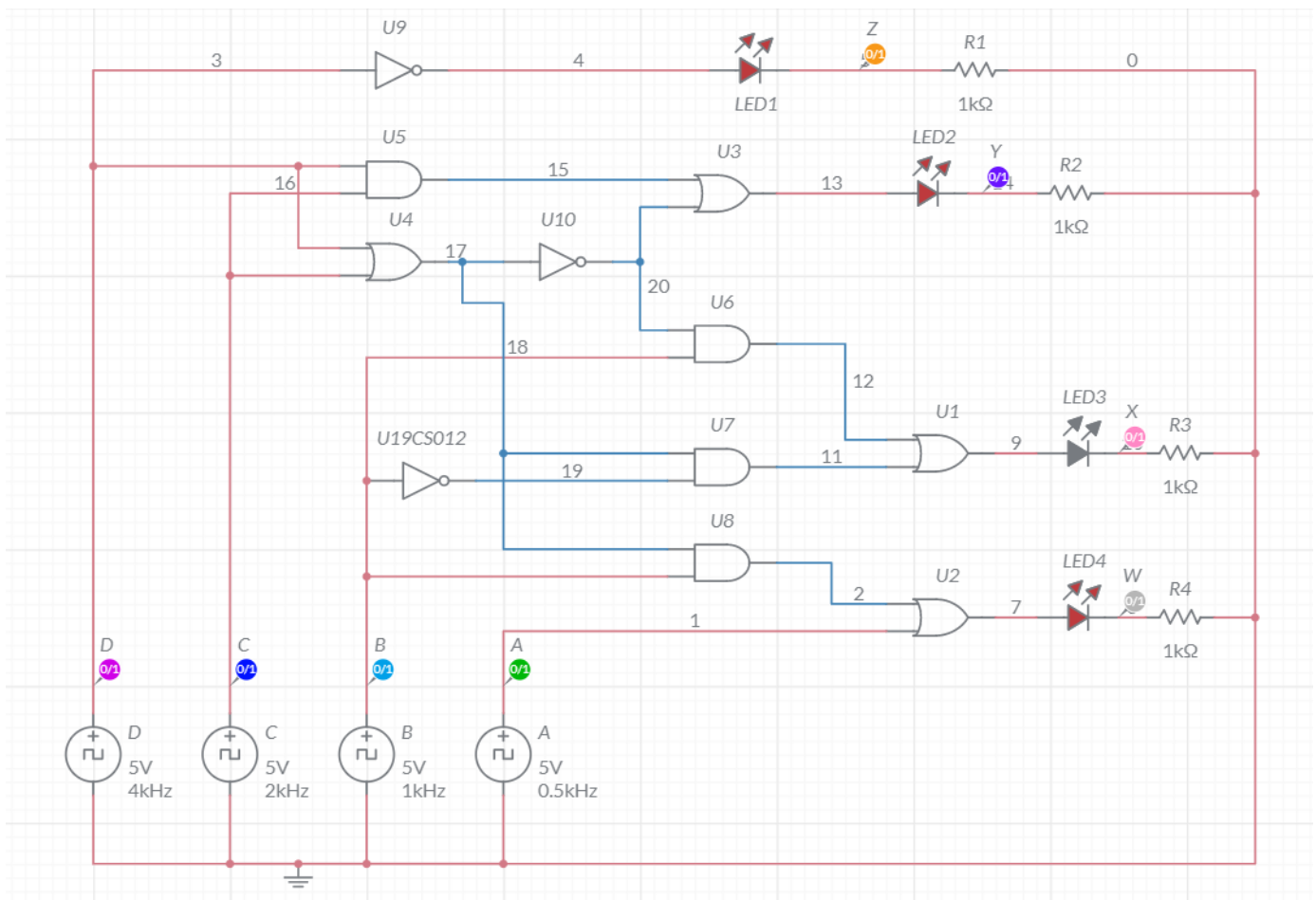Circuit Diagram [Multisim Implementation]



Grapher Image [Transient]

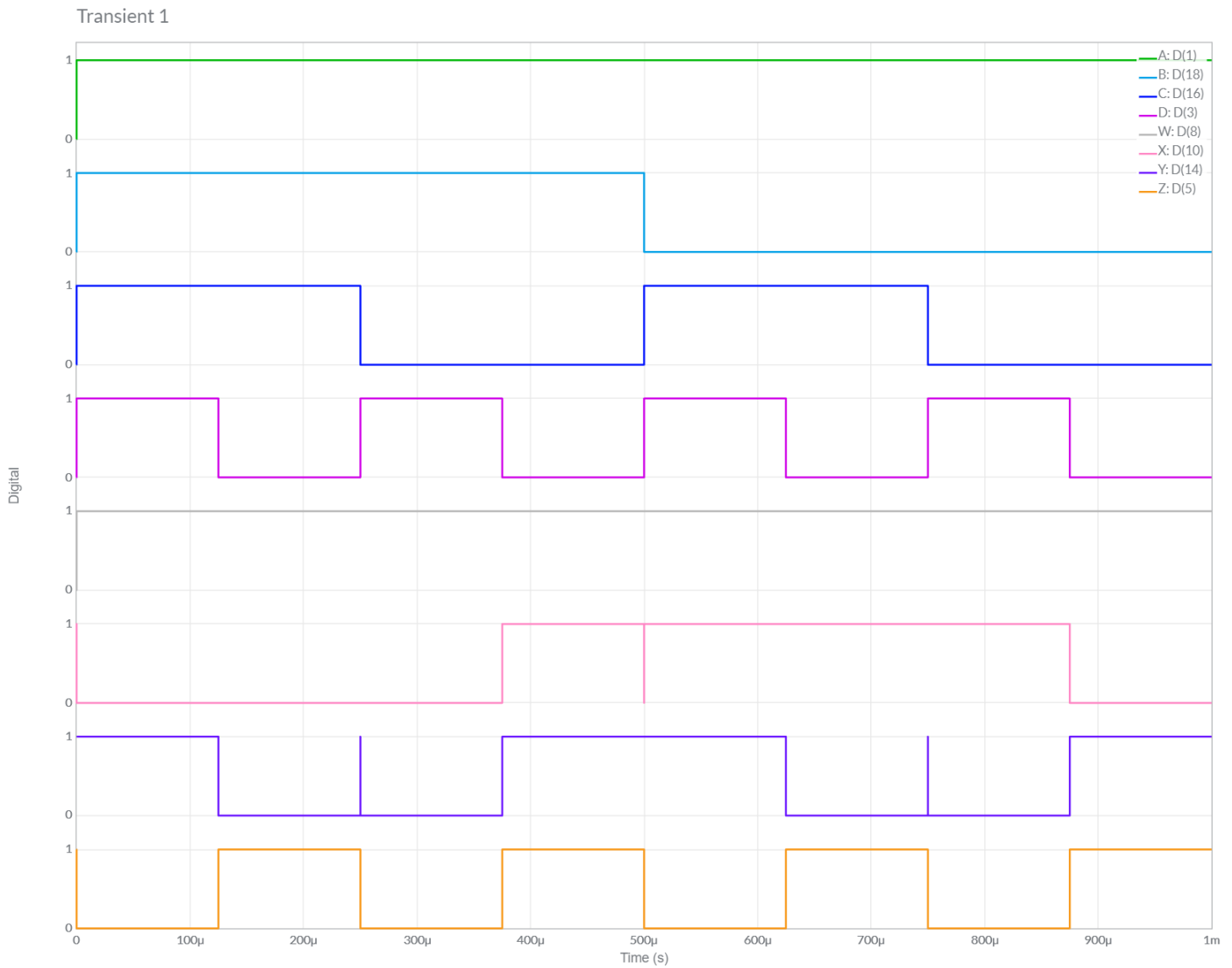

D.) CONCLUSION:

We have Successfully Implemented Particular Circuit [$A'B + AC$] and BCD to Excess-3 Convertor and **verified** our **MULTISIM Outputs** and **Results** from Theoretical Calculations.

Hence Results Both Theoretical Calculation and Multisim Implementation have been verified to be **same** and The Experiment has Been Successfully Performed.