


# ASSIGNMENT-4

U19CS012

Design the below given circuits. Verify their Functionality with the help of Multisim.

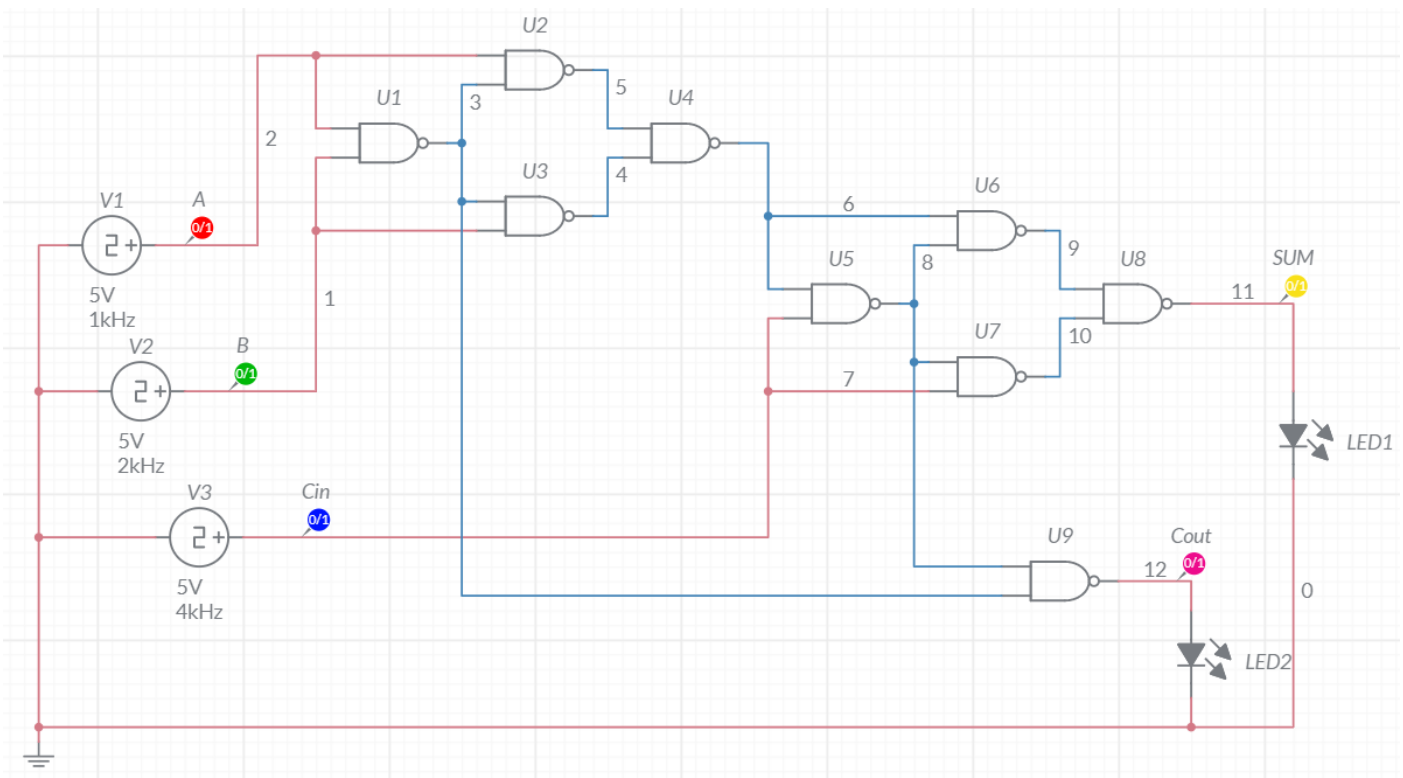1. Full Adder using least number of NAND Gates.


a.) Implement the circuit in Multisim online



b.) Truth Table

	INPUTS			OUTPUTS	
	A	B	Cin	Cout	SUM
1	0	0	0	0	0
2	0	0	1	0	1
3	0	1	0	0	1
4	0	1	1	1	0
5	1	0	0	0	1
6	1	0	1	1	0
7	1	1	0	1	0
8	1	1	1	1	1

c.) Timing Graph

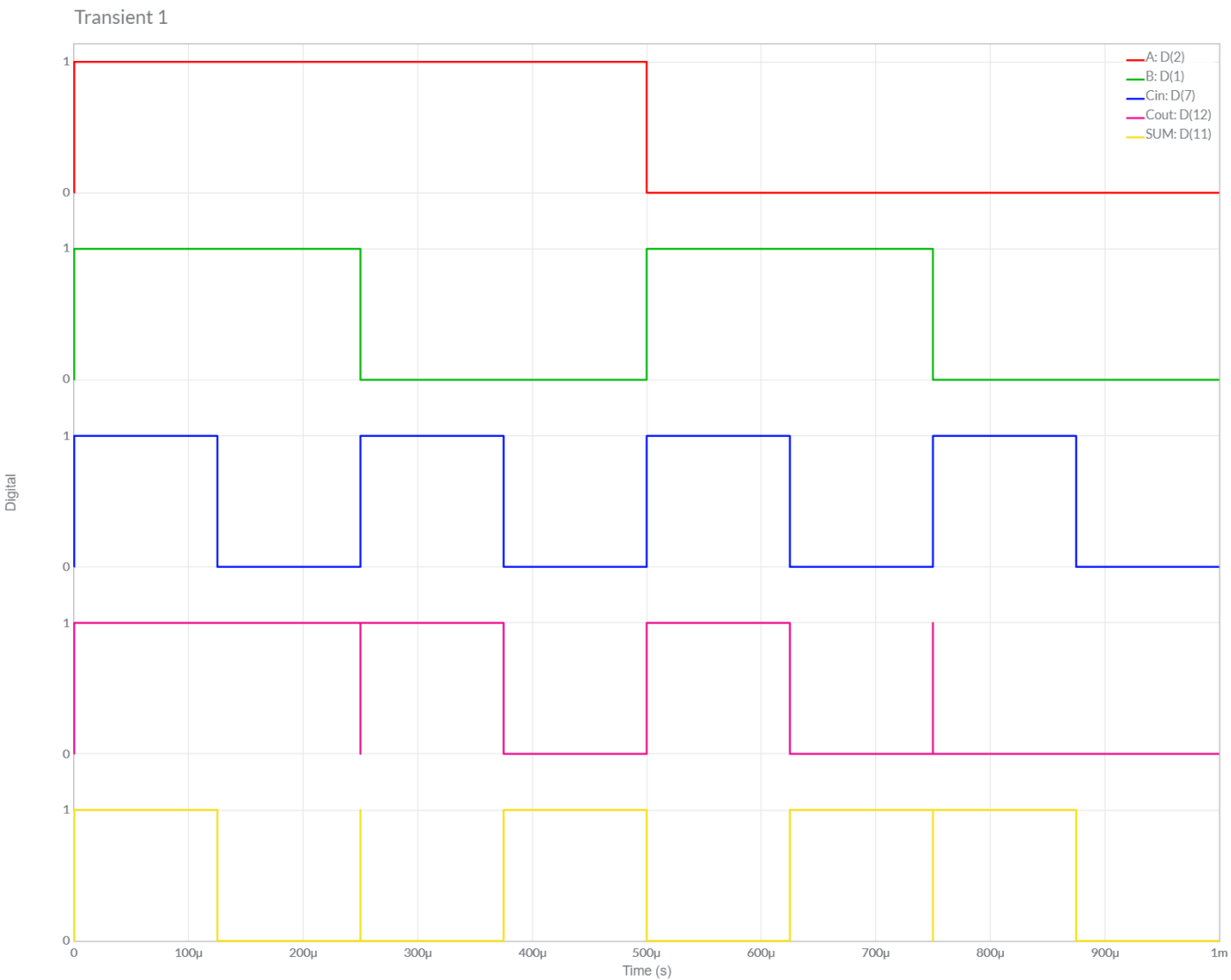


d.) Conclusion

We can observe from Above Graph and Truth Table, Both the *Theoretical* and *Multisim* Values of Given Circuit are **Equal**.  
Hence, Experiment is Performed Successfully (without any Error) & Functionality of Circuit is verified.

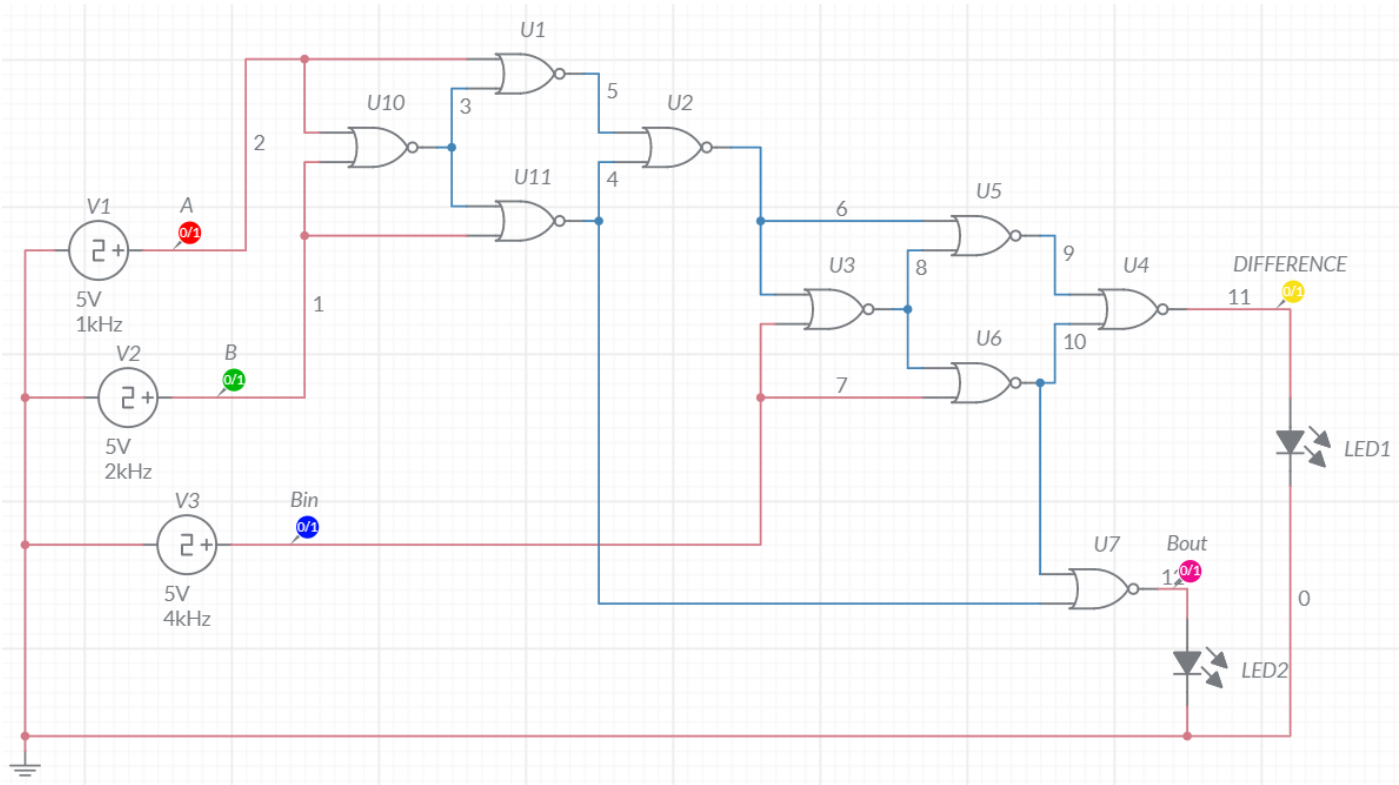2. Full Subtractor using least number of NOR Gates.


a.) Implement the circuit in Multisim online



c.) Truth Table

INPUTS				OUTPUTS	
	A	B	Bin	Bout	DIFF
1	0	0	0	0	0
2	0	0	1	1	1
3	0	1	0	1	1
4	0	1	1	1	0
5	1	0	0	0	1
6	1	0	1	0	0
7	1	1	0	0	0
8	1	1	1	1	1

b.) Timing Graph

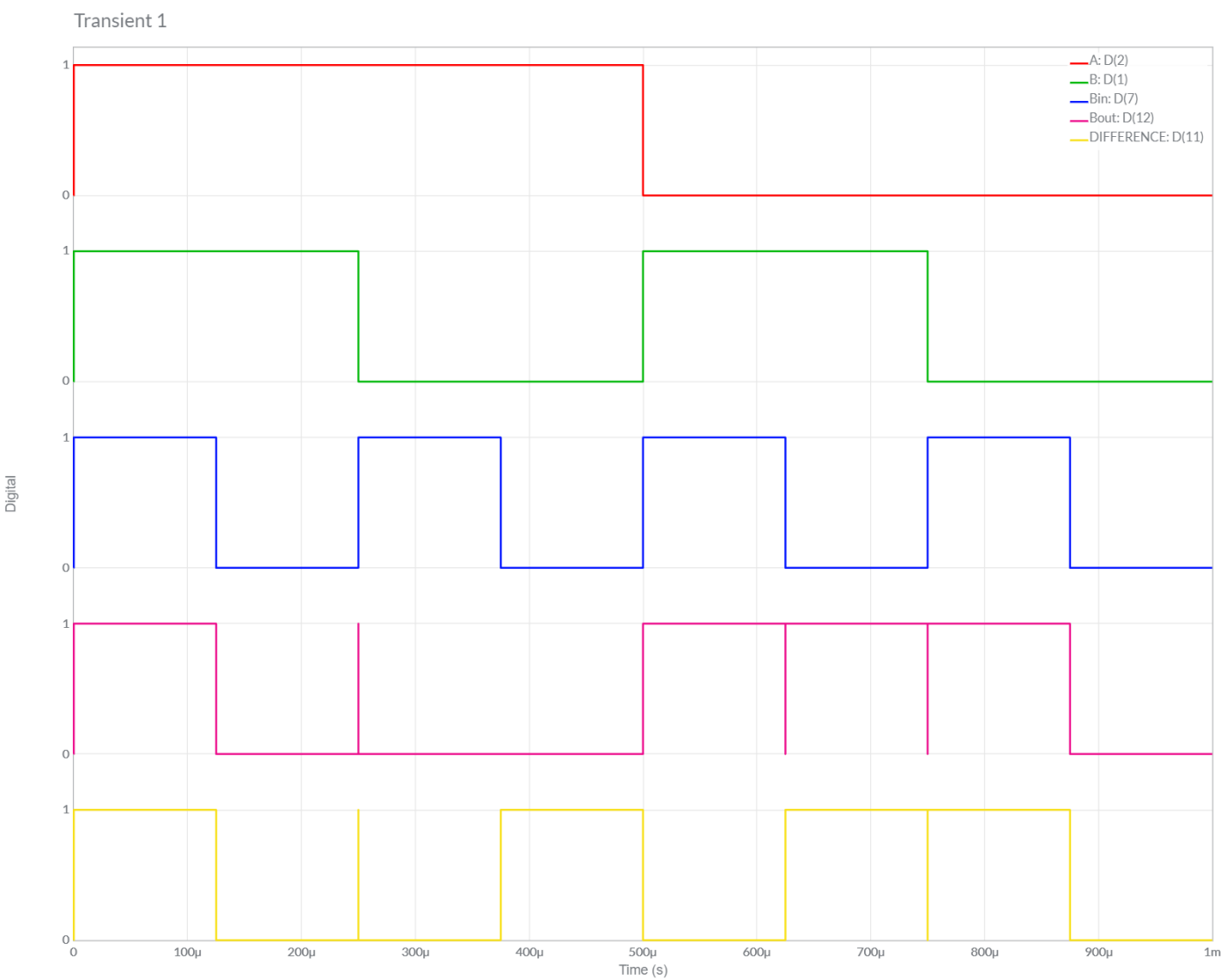


d.) Conclusion

We can observe from Above Graph and Truth Table, Both the *Theoretical* and *Multisim* Values of Given Circuit are **Equal**.


Hence, Experiment is Performed Successfully (without any Error) & Functionality of Circuit is verified.

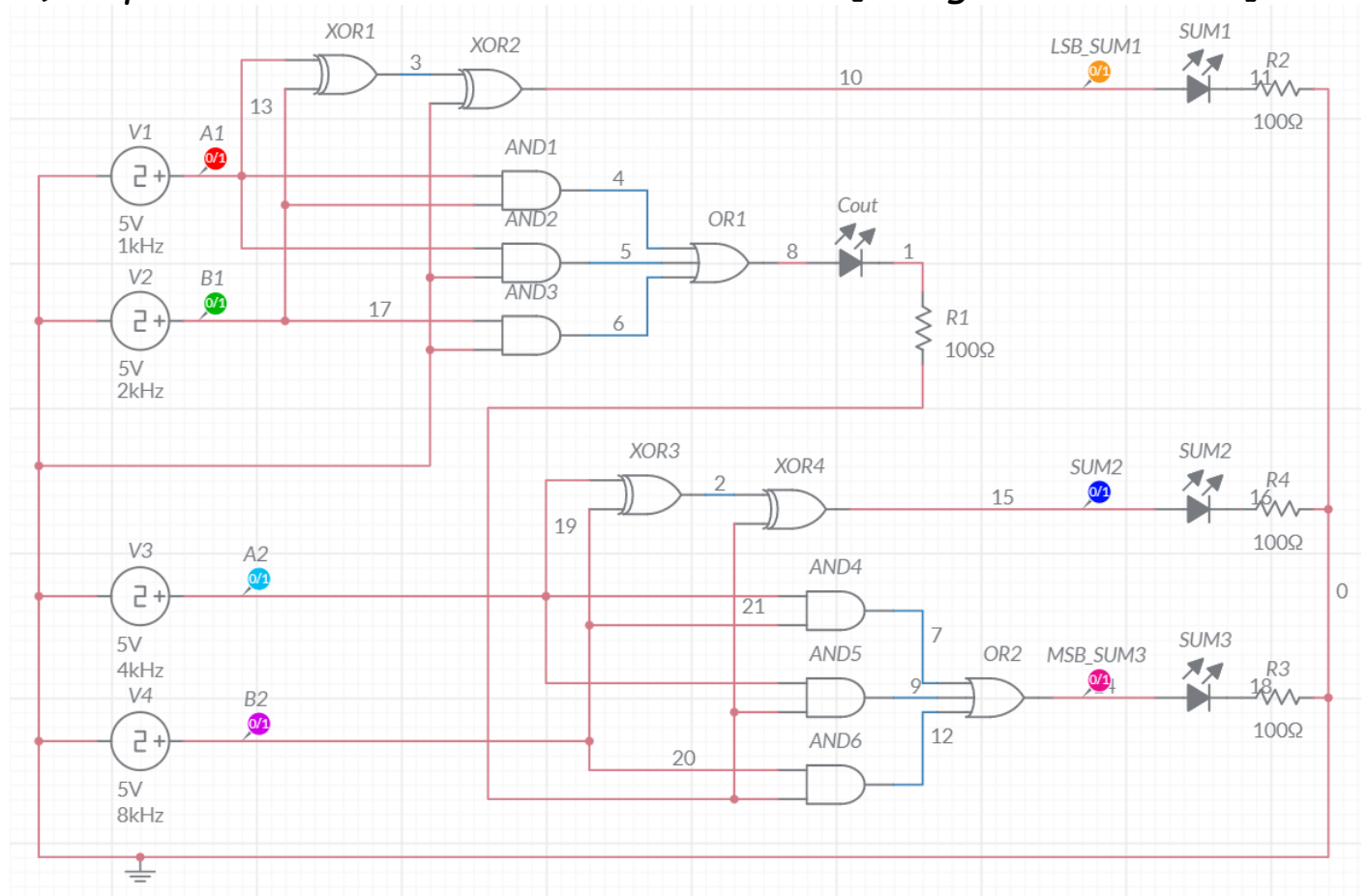3. Two bit Adder circuit using Full Adders. Attach screenshots for any four input combinations.


a.) Implement the circuit in Multisim online [Using 2 Full Adders]



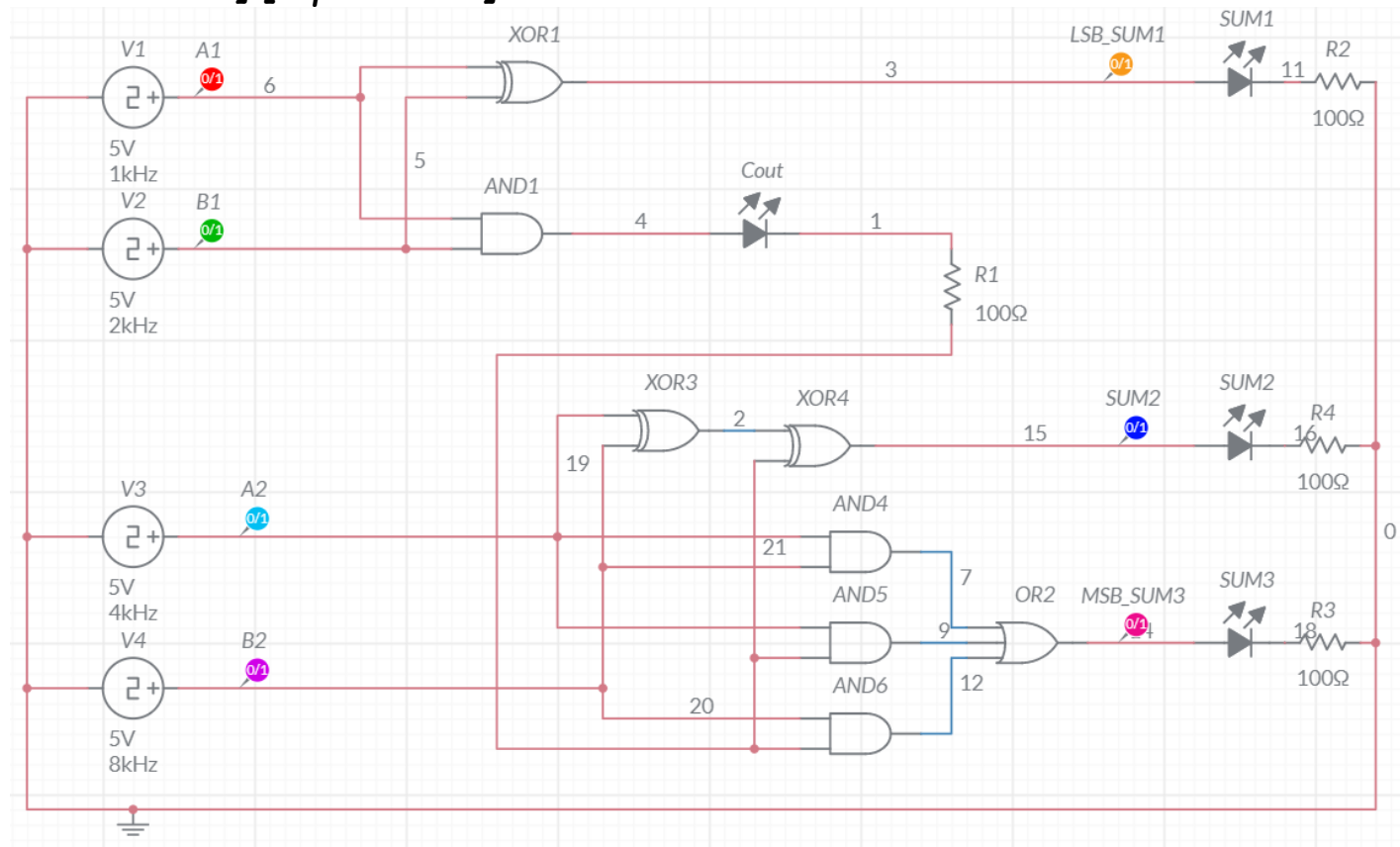b.) Implement the circuit in Multisim online [Using 1 Full Adders + 1 Half Adder] [Optimized]



c.) Timing Graph [Same for Both Circuit]

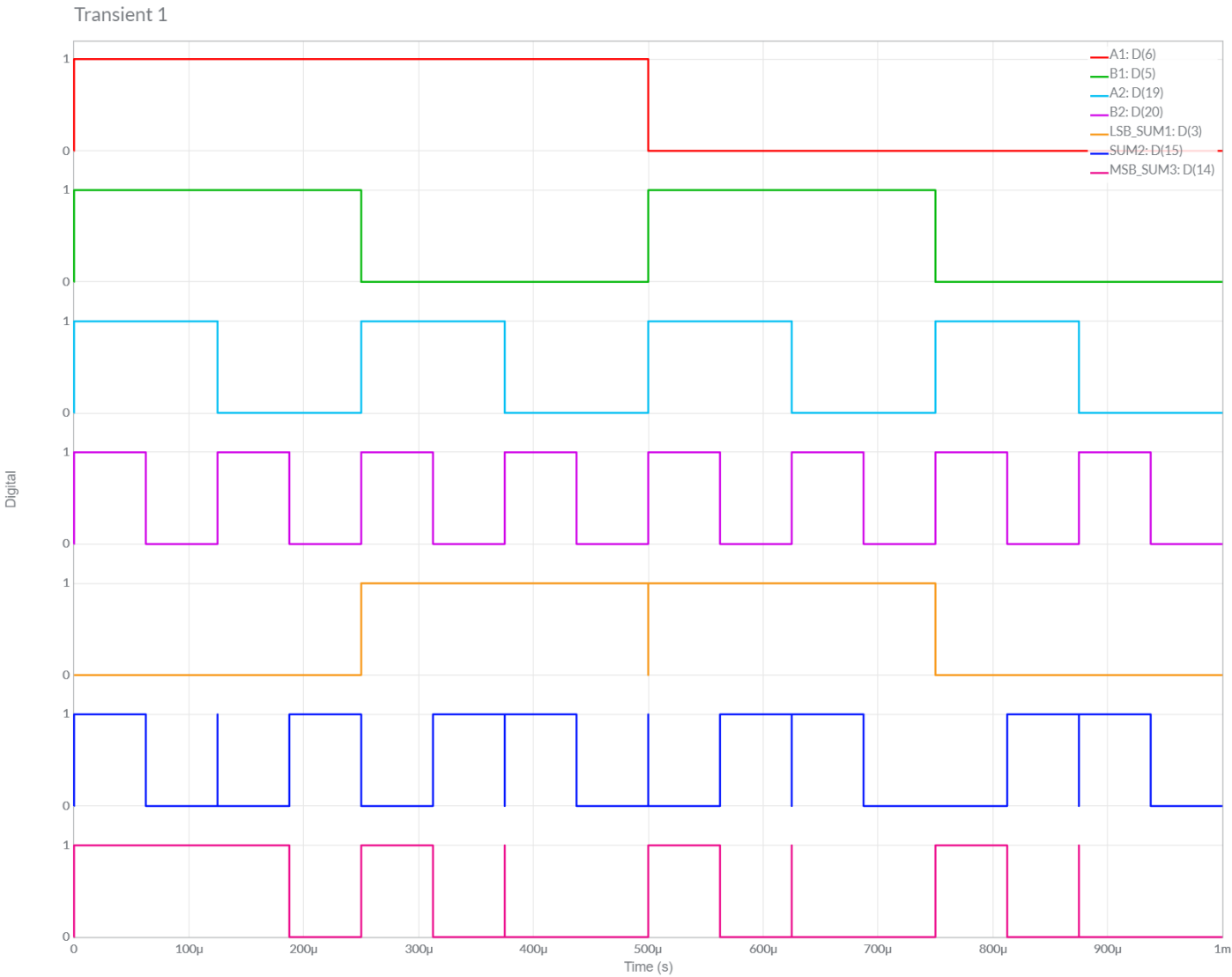

c.) Truth Table

	INPUTS				OUTPUTS		
	A1	B1	A2	B2	LSB(SUM1)	SUM2	MSB(SUM3)
1	0	0	0	0	0	0	0
2	0	0	0	1	0	1	0
3	0	0	1	0	0	1	0
4	0	0	1	1	0	0	1
5	0	1	0	0	1	0	0
6	0	1	0	1	1	1	0
7	0	1	1	0	1	1	0
8	0	1	1	1	1	0	1
9	1	0	0	0	1	0	0
10	1	0	0	1	1	1	0
11	1	0	1	0	1	1	0
12	1	0	1	1	1	0	1
13	1	1	0	0	0	1	0
14	1	1	0	1	0	0	1
15	1	1	1	0	0	0	1
16	1	1	1	1	0	1	1

#### d.) Conclusion

We can observe from Above Graph and Truth Table, Both the *Theoretical* and *Multisim* Values of Given Circuit are **Equal**.

Hence, Experiment is Performed Successfully (without any Error) & Functionality of Circuit is verified.