

Prepare the circuits to take two 8-bit binary numbers as input and output their sum as following:

- a. $2x$
- b. $2x + y$
- c. Average of two 8-bit binary numbers
- d. x^2
- e. xy
- f. x'
- g. x^6