

DELD



Unit 1



PN Diode and Transistor

Electronics Engineering Department

P – Type Semiconductor



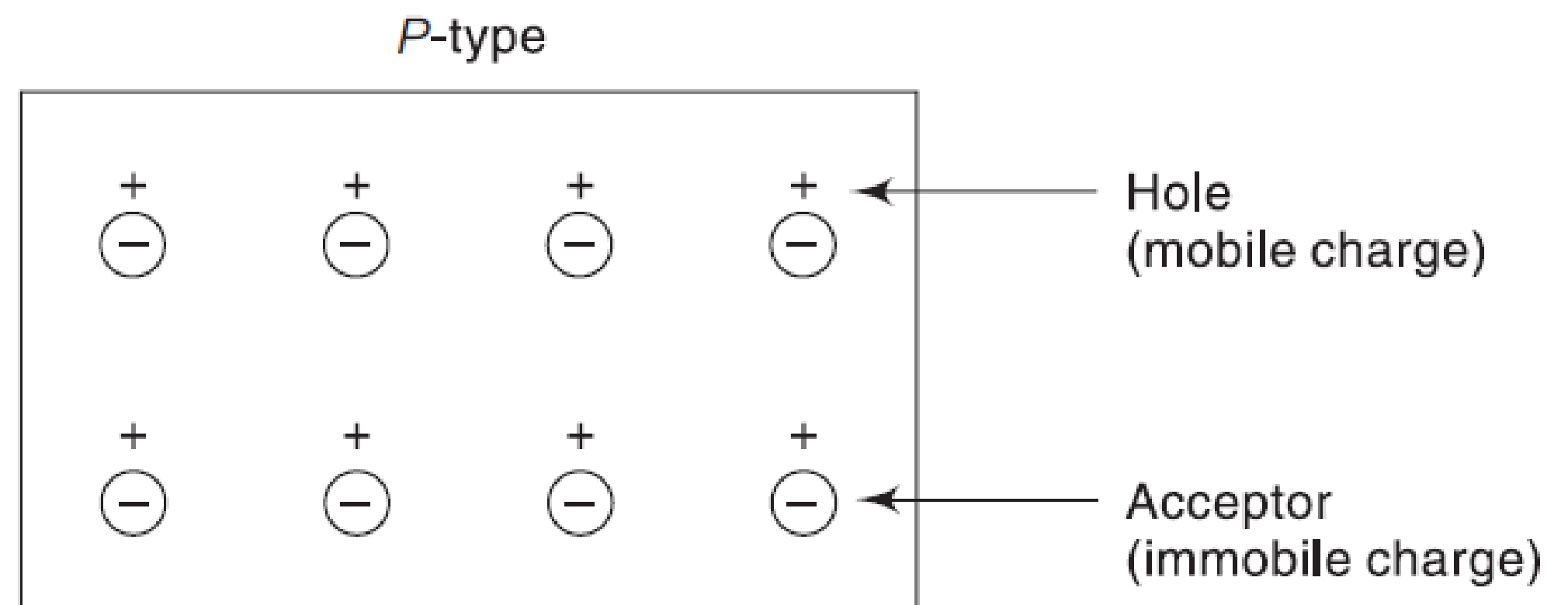
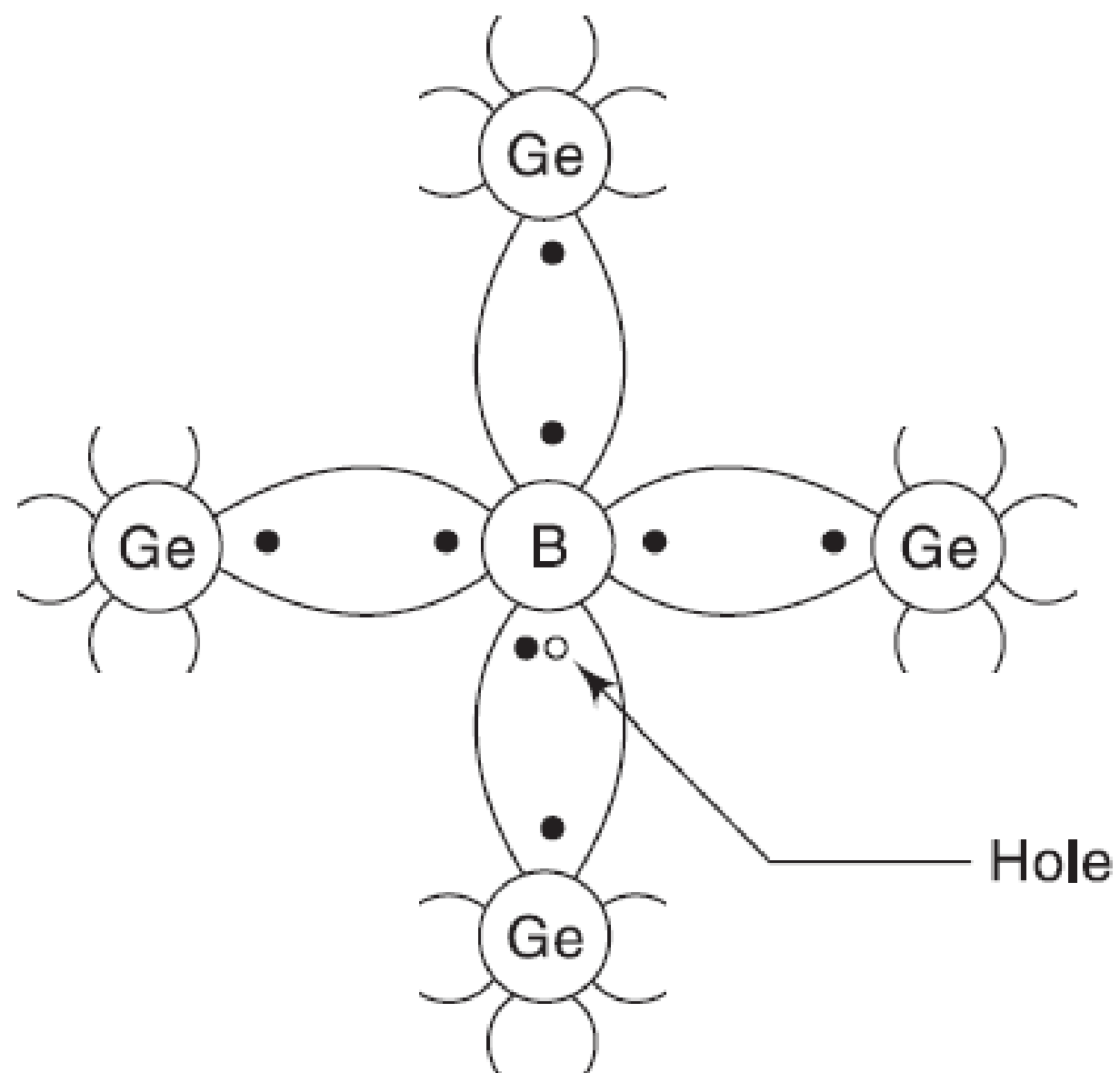
Germanium doped with Boron (Trivalent Impurity)




N – Type Semiconductor



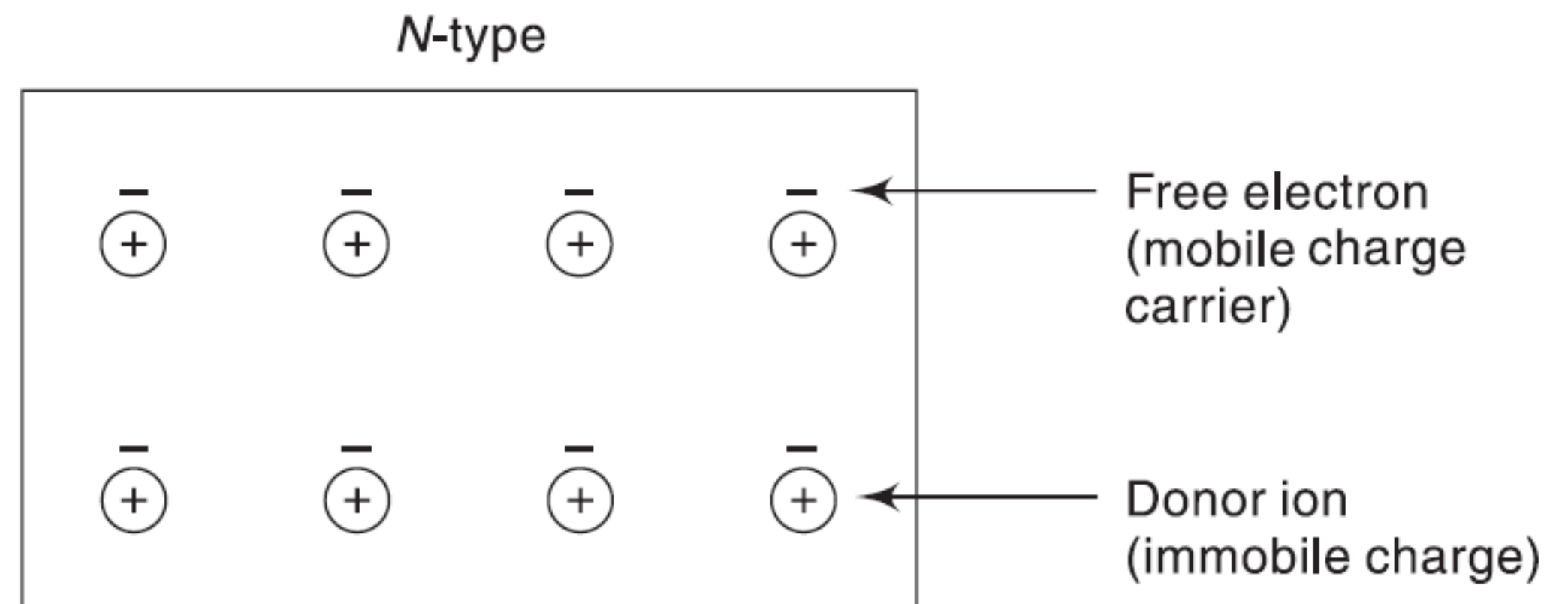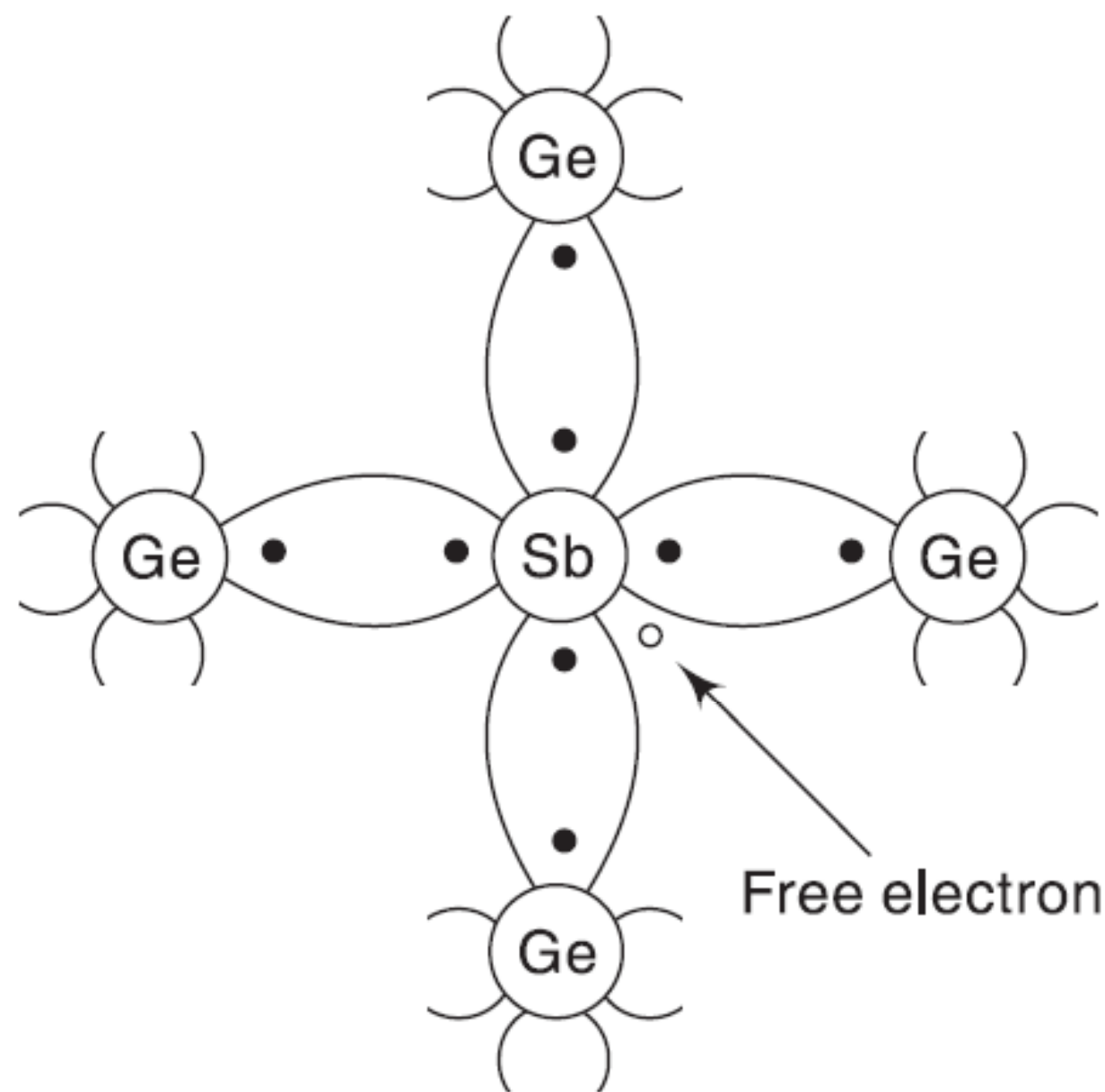
Germanium doped with Antimony (Pentavalent Impurity)



PN Junction

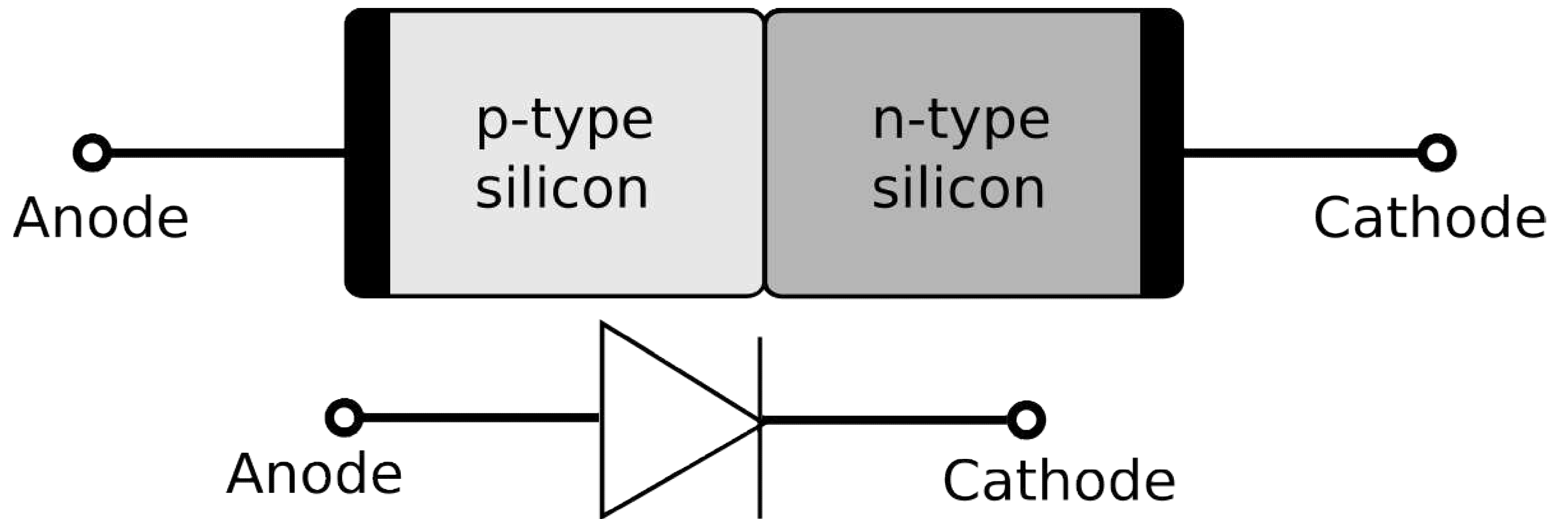

Depletion Layer

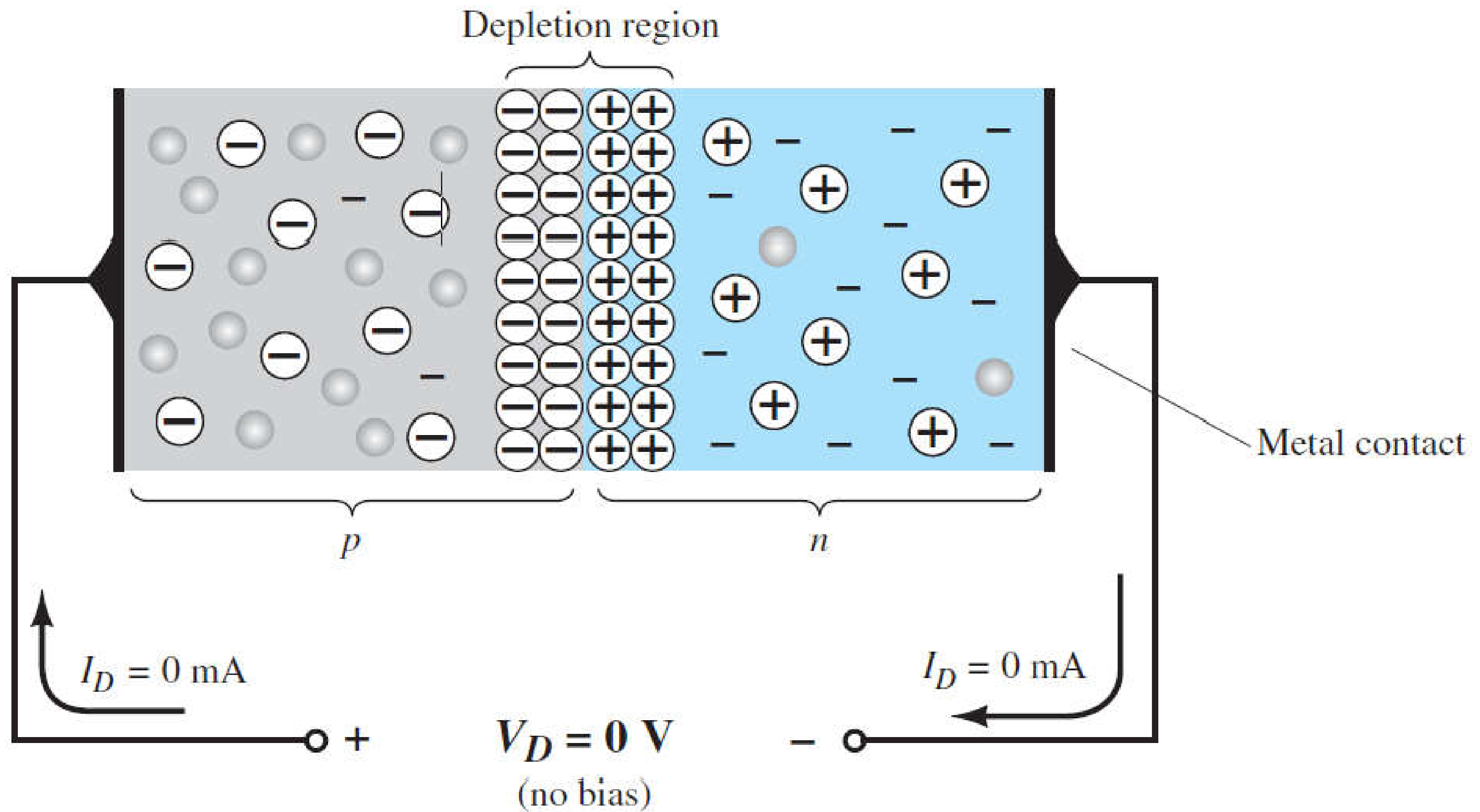

Depletion Layer



- ❑ The excess electrons in the N- Region cross the junction and combine with the excess holes in the P – region.
- ❑ N- Region loses electrons and becomes positively charged
- ❑ P - Region loses holes and becomes negatively charged
- ❑ At some point this migration stops (Concentration becomes same)
- ❑ Any additional electrons from N side are repelled by the negative charge of the P – Region
- ❑ Similarly, additional holes from the P side are repelled by the positive charge of the N –Region

Depletion Layer Cont...




- ❑ This results in a thin layer on both the sides at the junction which contains only immobile charge carriers. This is known as depletion layer. Range is in micrometers
- ❑ Width depends on doping
- ❑ Heavily doped – less width and vice-versa
- ❑ Electrons in the N region have to climb the potential hill in order to reach the P – Region. This potential is known as Potential Barrier.
- ❑ Ge – 0.3 volts, Silicon – 0.7 volts


Forward Bias



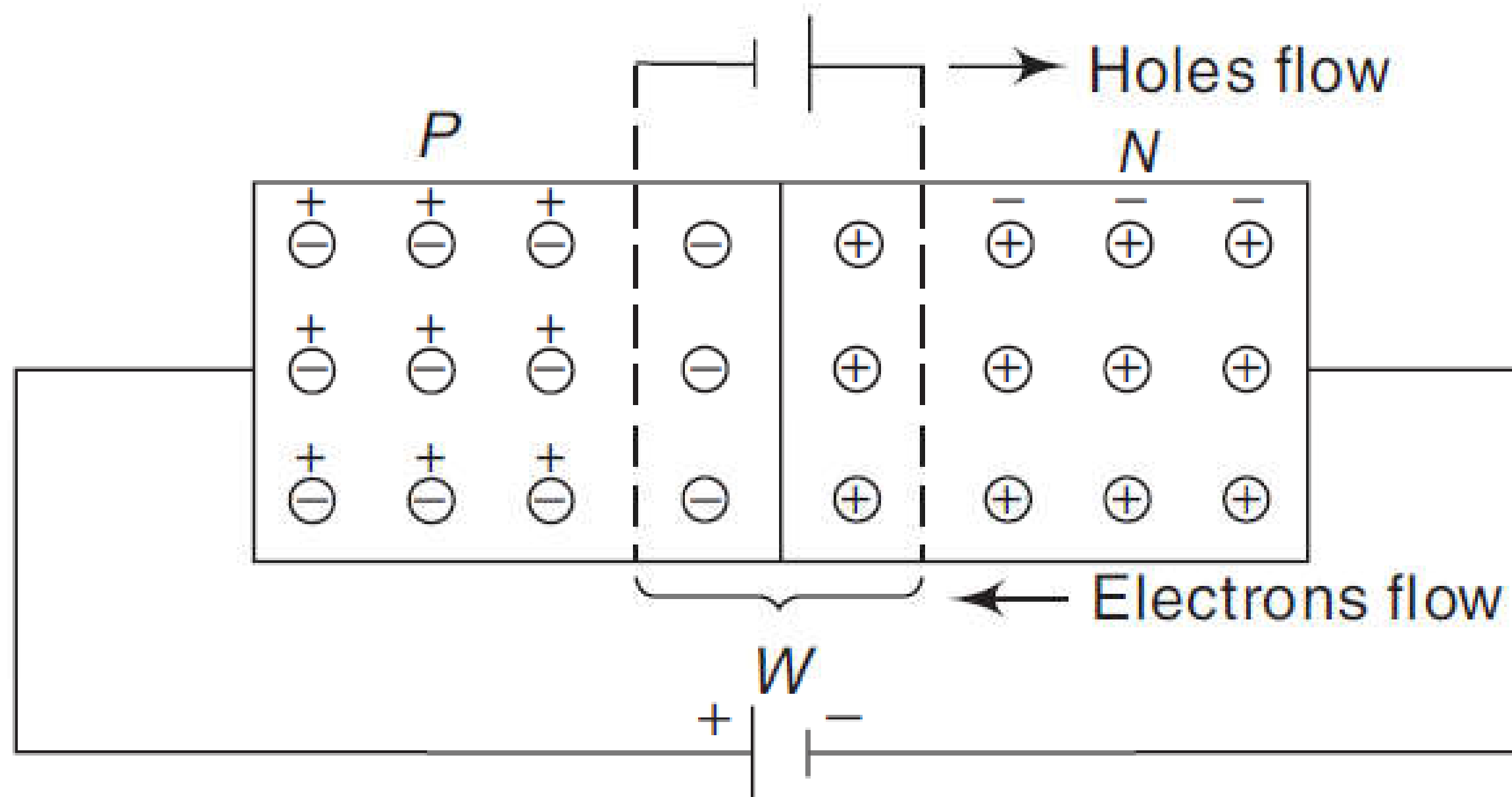- ❑ Positive terminal of the battery is connected to p-region and negative terminal is connected to n-region
- ❑ Width of depletion layer decreases
- ❑ Current flows in the forward direction and diode acts as a short circuit



Forward Characteristics

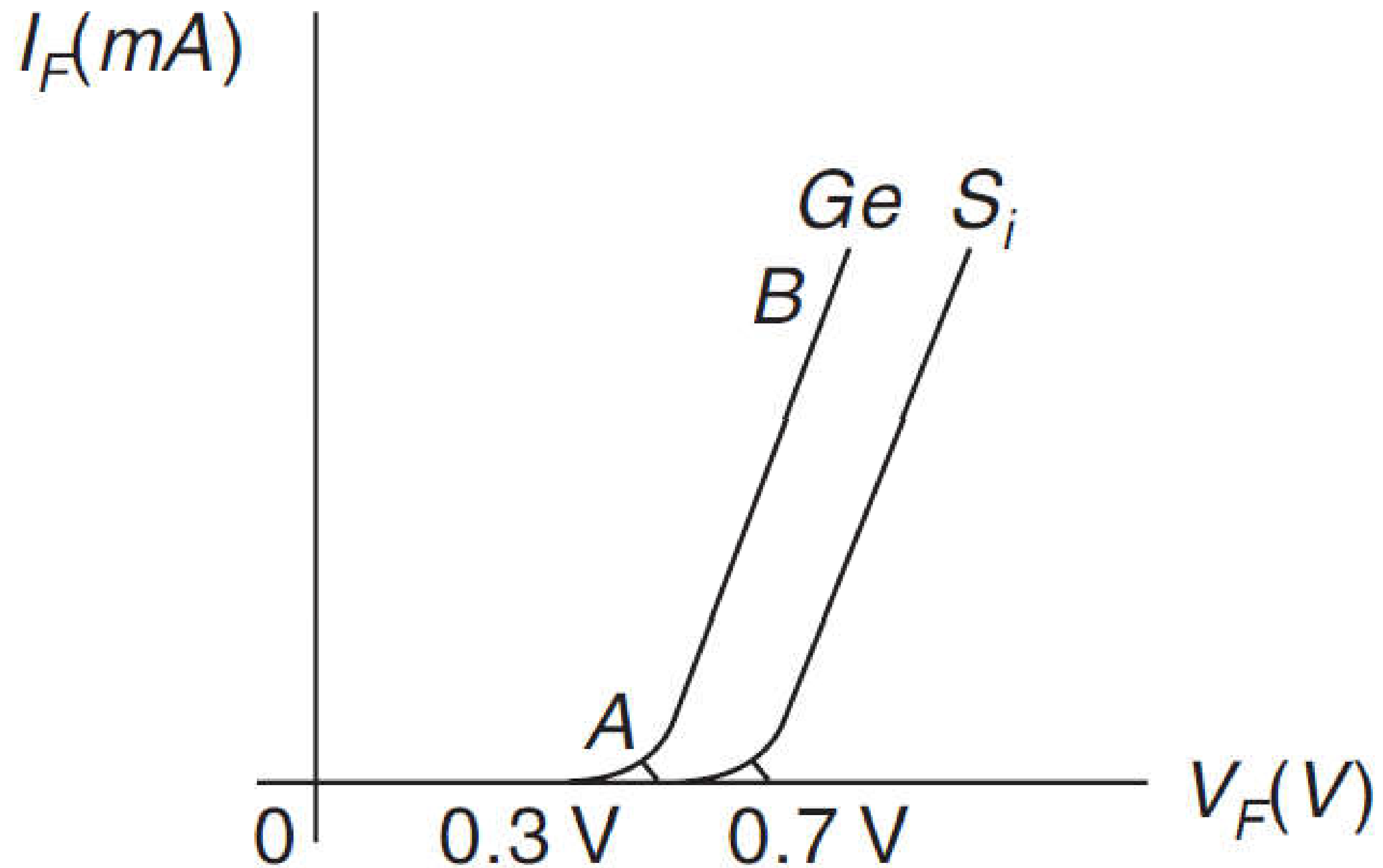

Diode Equation




$$I_D = I_s(e^{V_D/nV_T} - 1)$$

- ❑ I_s – Reverse Saturation Current
- ❑ V_d is the applied Forward Biased voltage
- ❑ n – Ideality Factor (if not mentioned, assume as 1)
- ❑ V_t – Thermal voltage (25 milli volts at room temperature: 27 degrees/300 degree K)


Reverse Bias



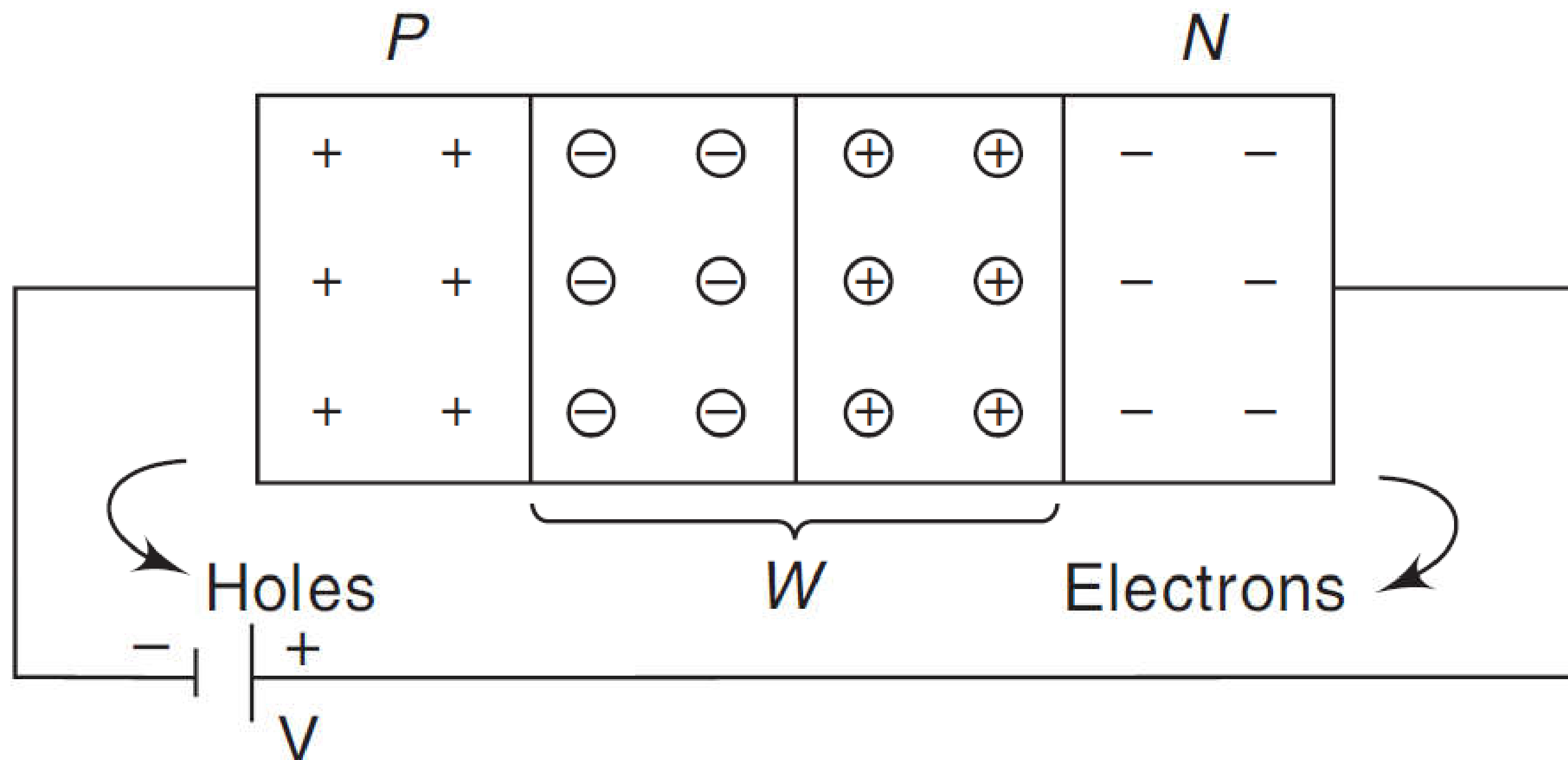- ❑ Positive terminal of the battery is connected to N – side and Negative terminal of the battery is connected to P – Side
- ❑ The free electrons and the free holes are attracted back towards both the battery terminals
- ❑ The charge carriers move away from the depletion layer
- ❑ Width of depletion layer increases
- ❑ No current flows and the diode acts as an open circuit




Breakdown Voltage

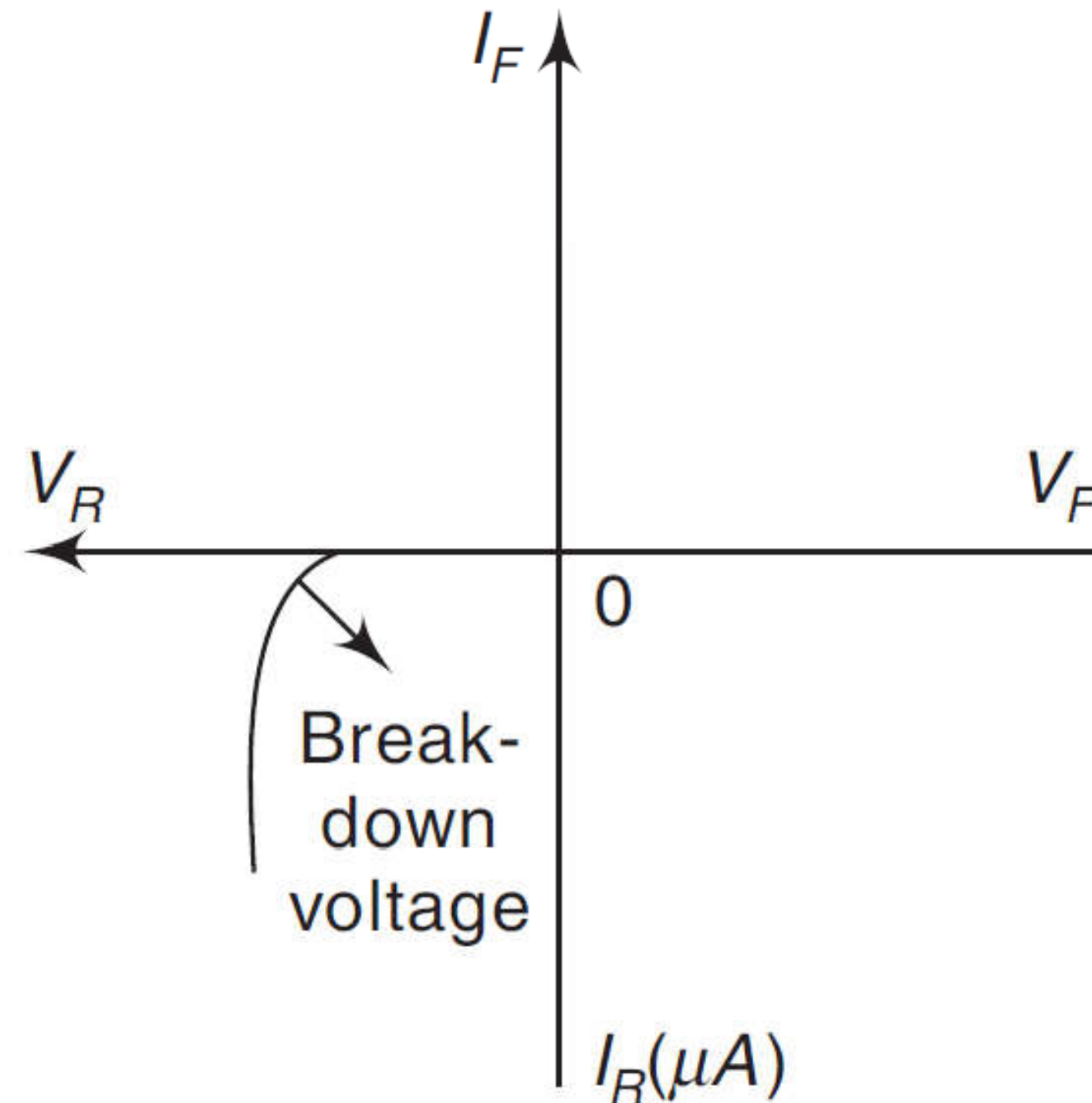

- ❑ Go on increasing the reverse bias. At certain voltage, The current increases at a very rapid rate in a direction opposite to that of the positive voltage region.
- ❑ The reverse-bias potential that results in this dramatic change in characteristics is called the **Breakdown Voltage**.

Diode Characteristics


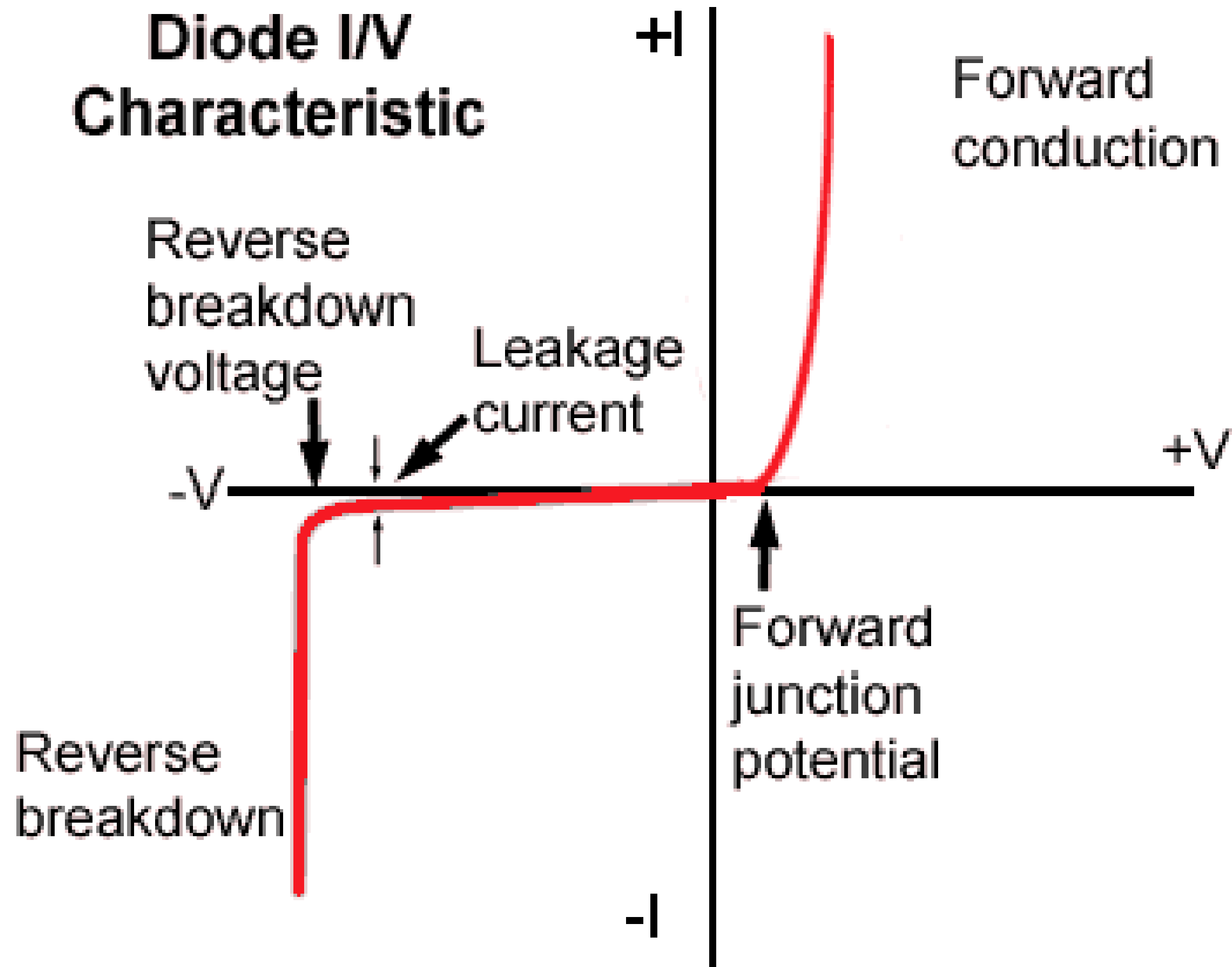





Equivalent Circuits



Ideal Diode

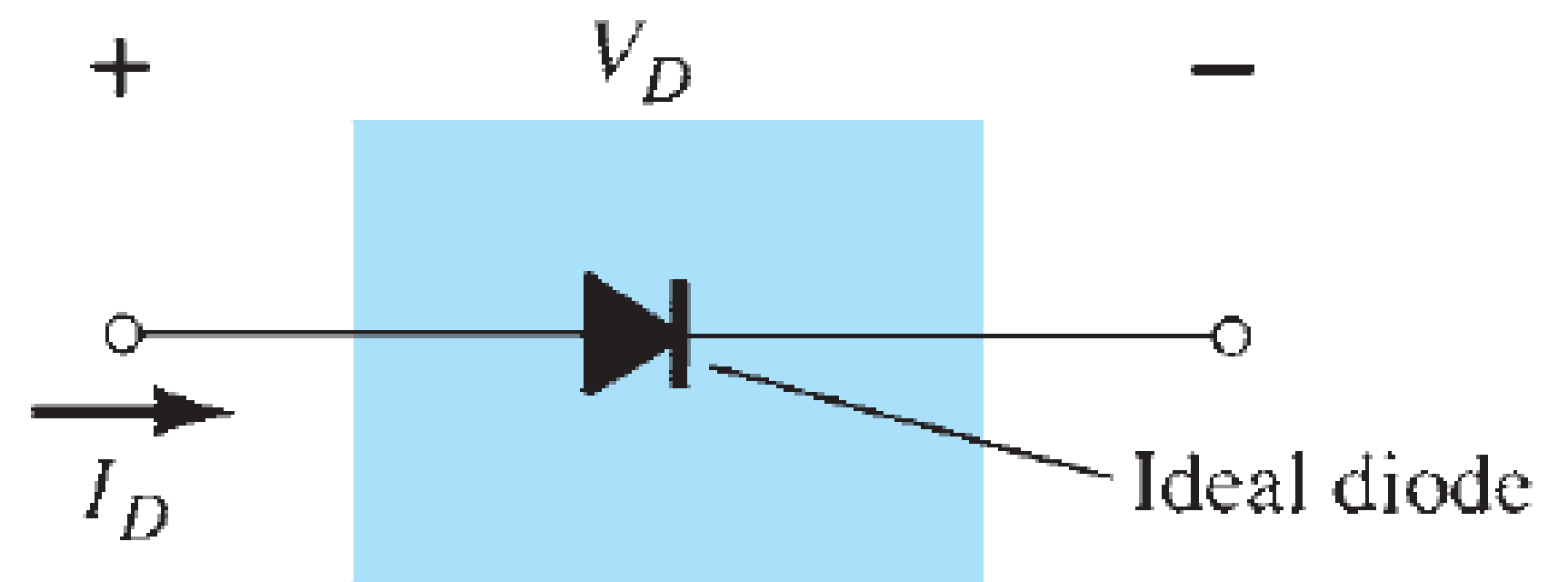 Diode will behave as short circuit as soon as the voltage across it becomes greater than zero





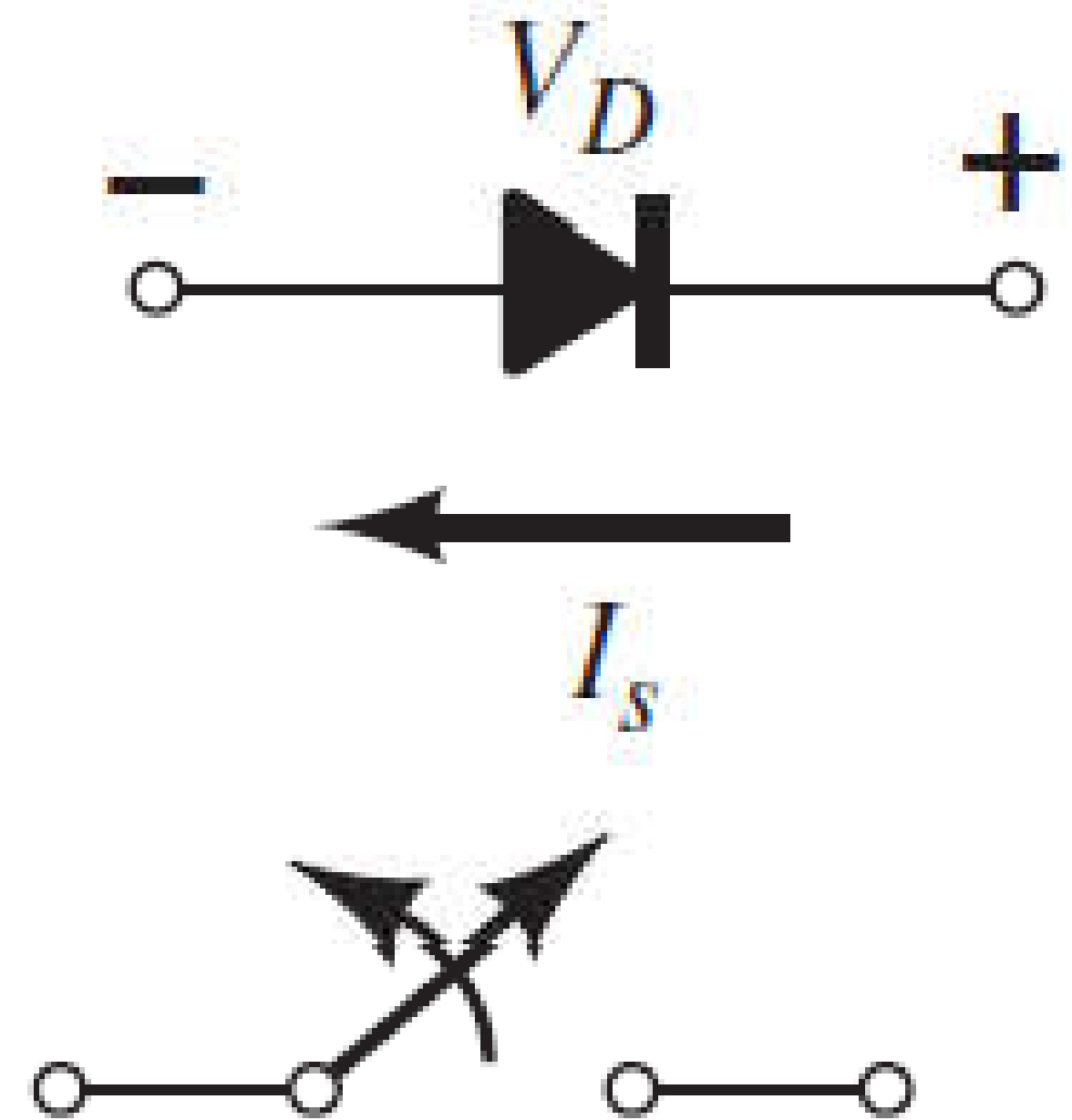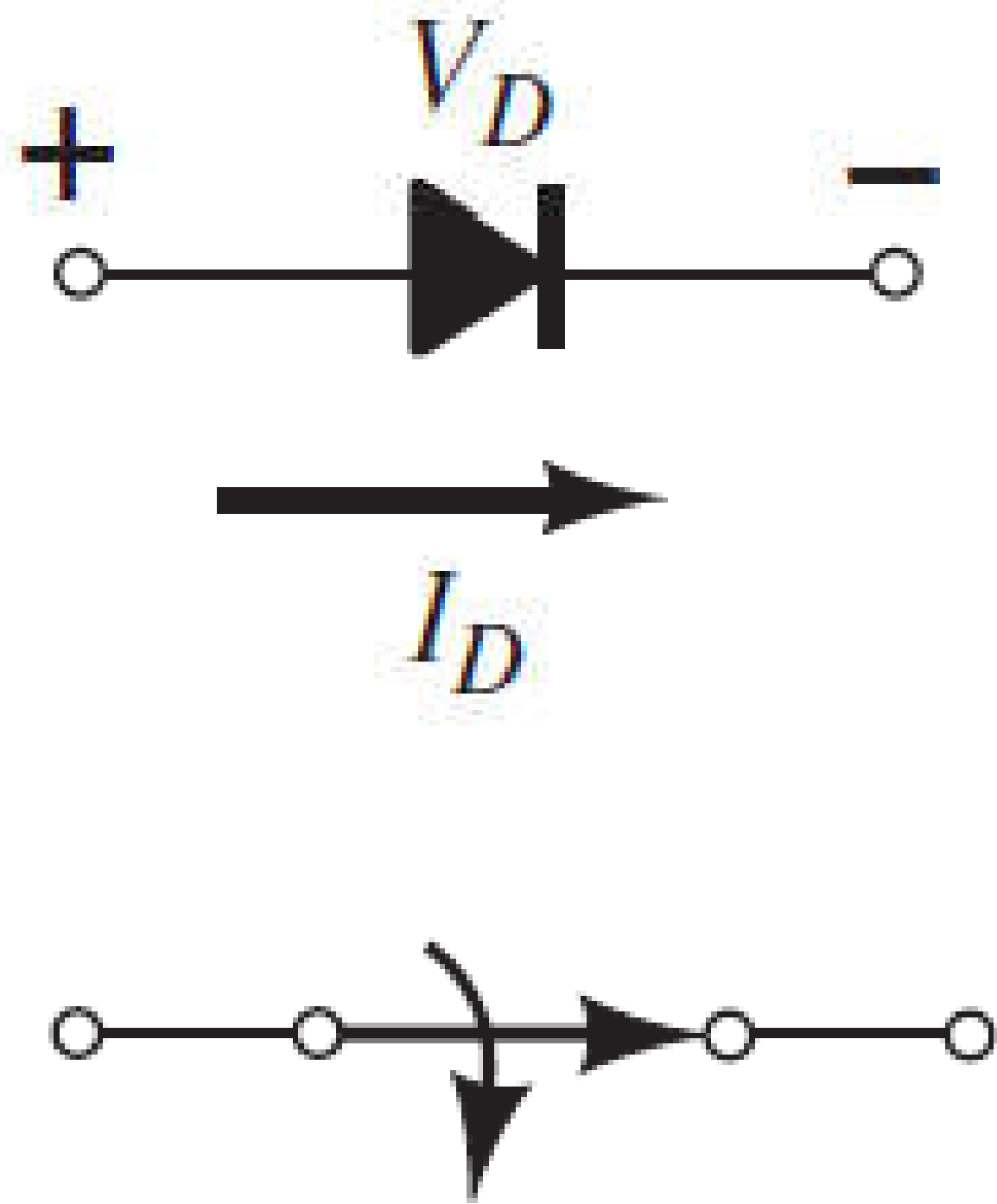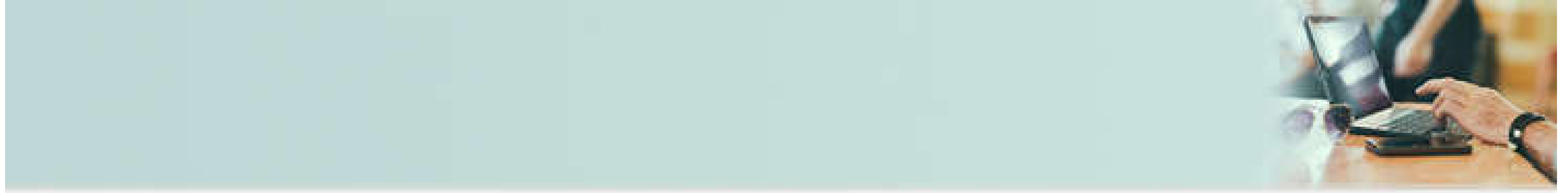


Practical Diode



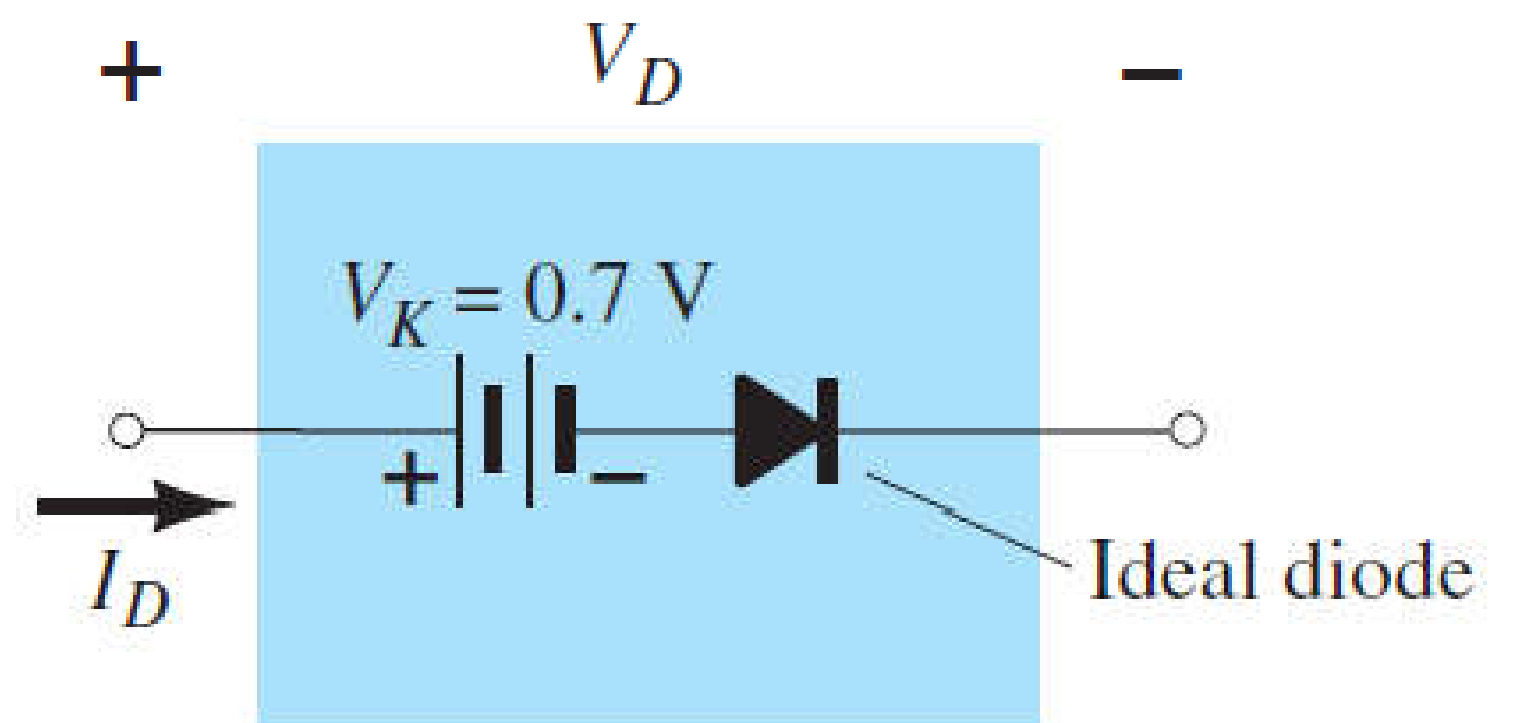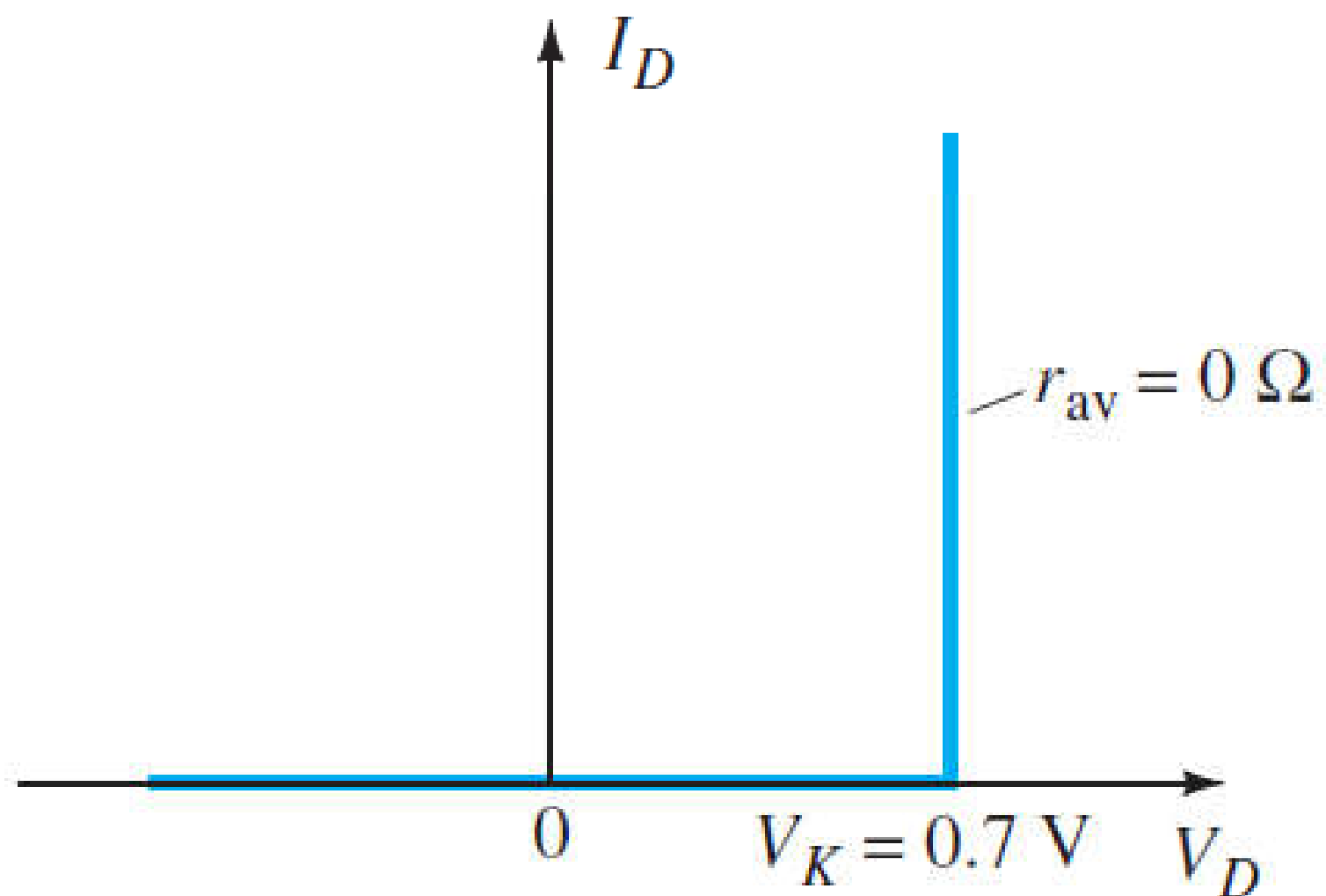We must overcome the potential barrier of 0.7 volts (silicon) for a diode to make it forward bias








Ideal vs. Actual Characteristics

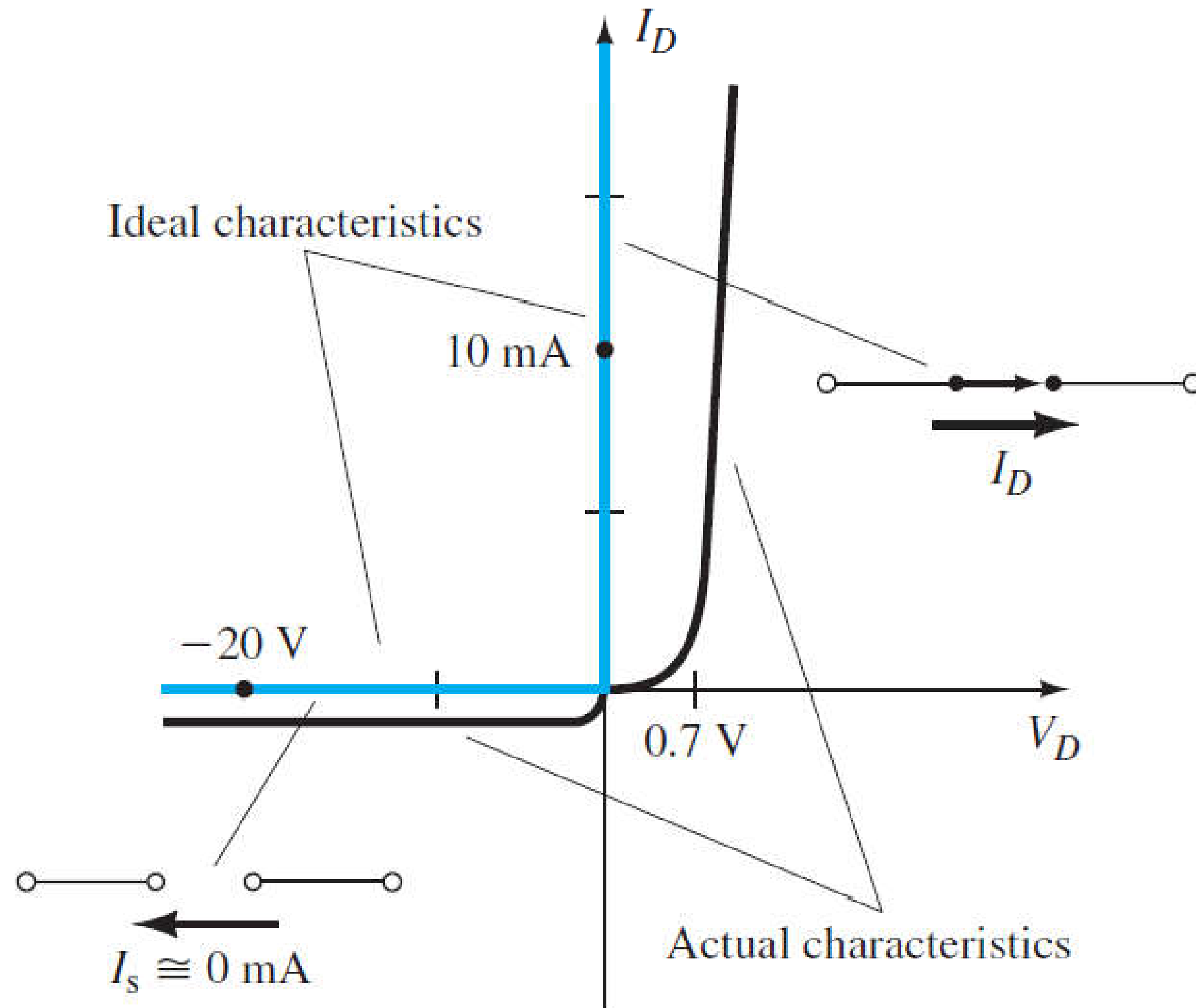

Diode as a Rectifier



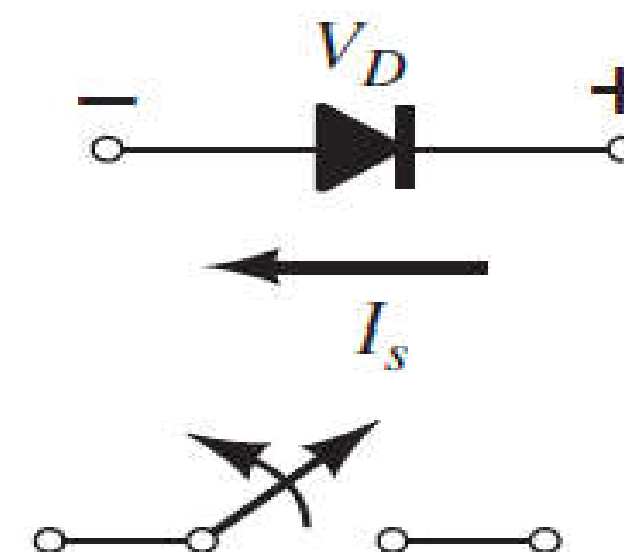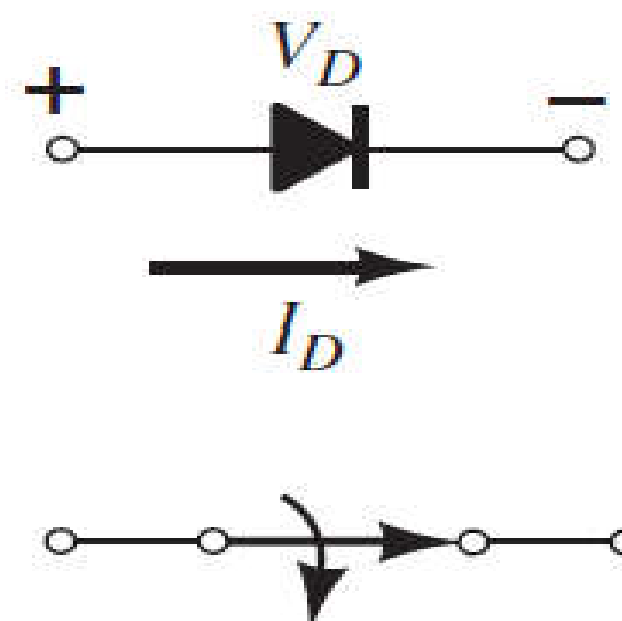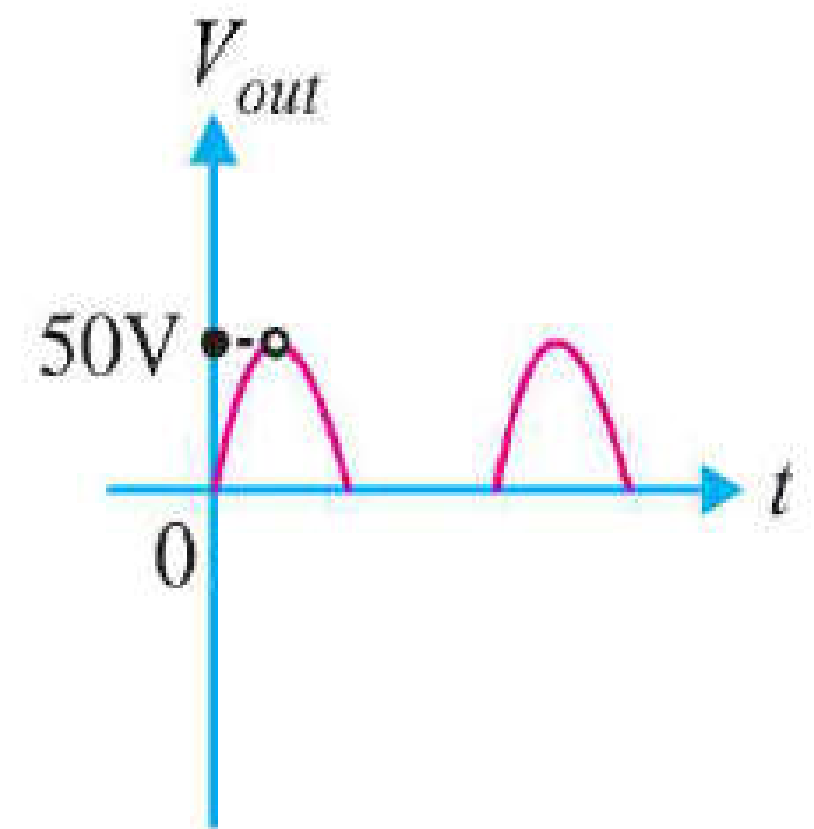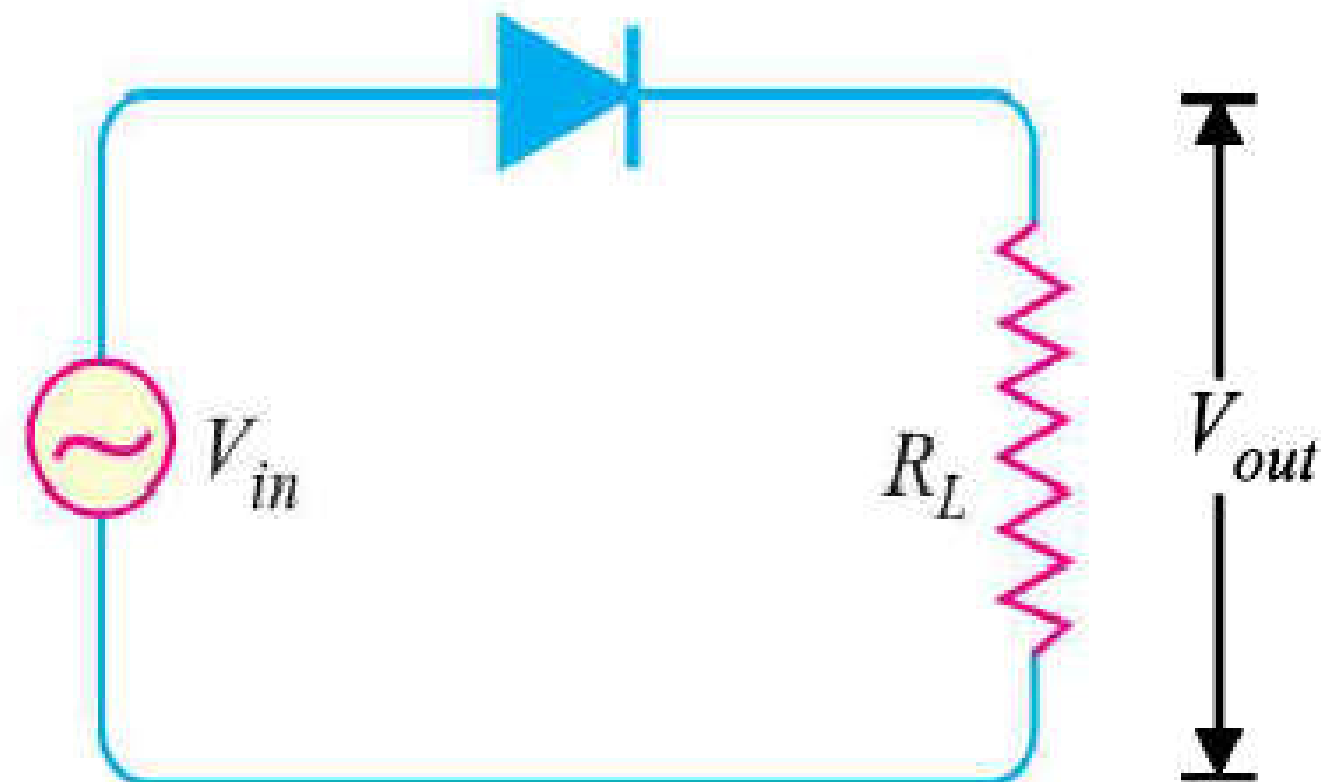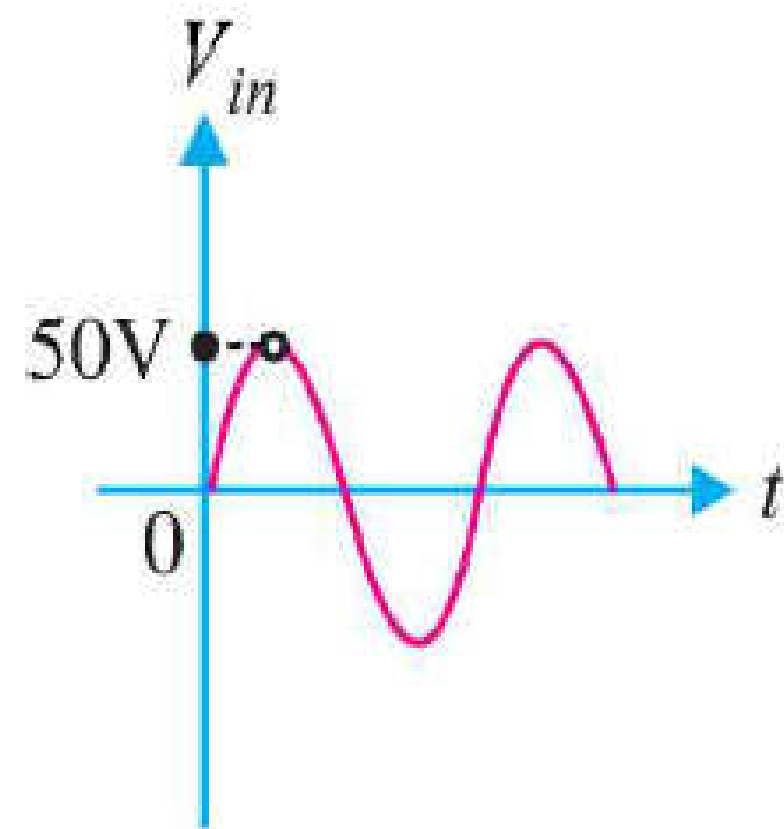
- ❑ Diode behaves as a switch
- ❑ Forward Biased – Closed Switch, connects AC Supply to load
- ❑ Reverse Biased – Open Switch, disconnects AC with load




Concept Check...



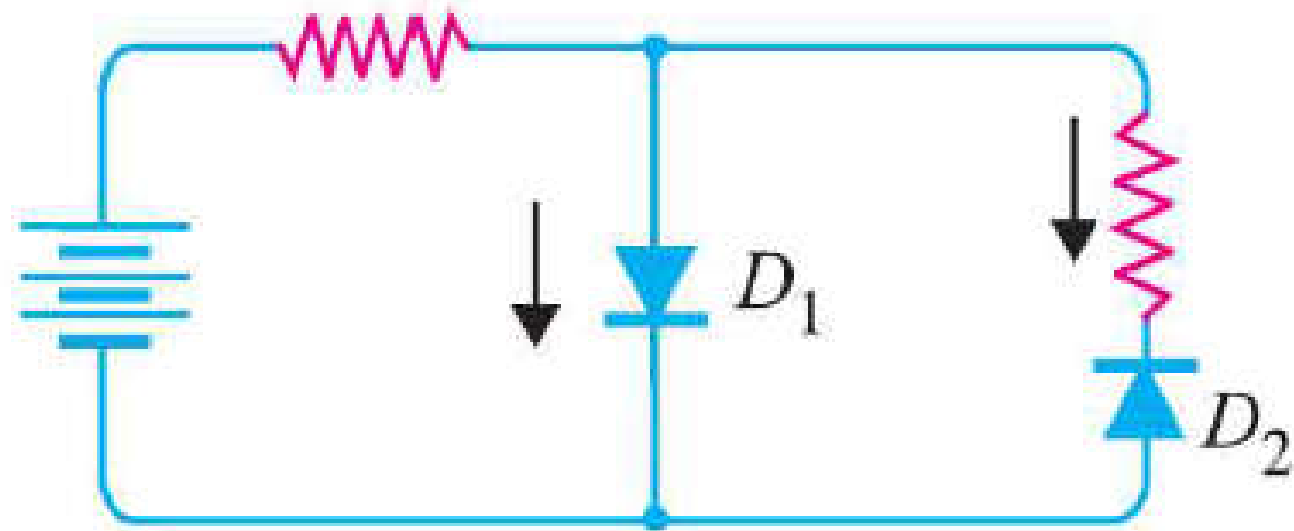
Identify whether the diode/diodes is/are forward or reverse biased?




(i)

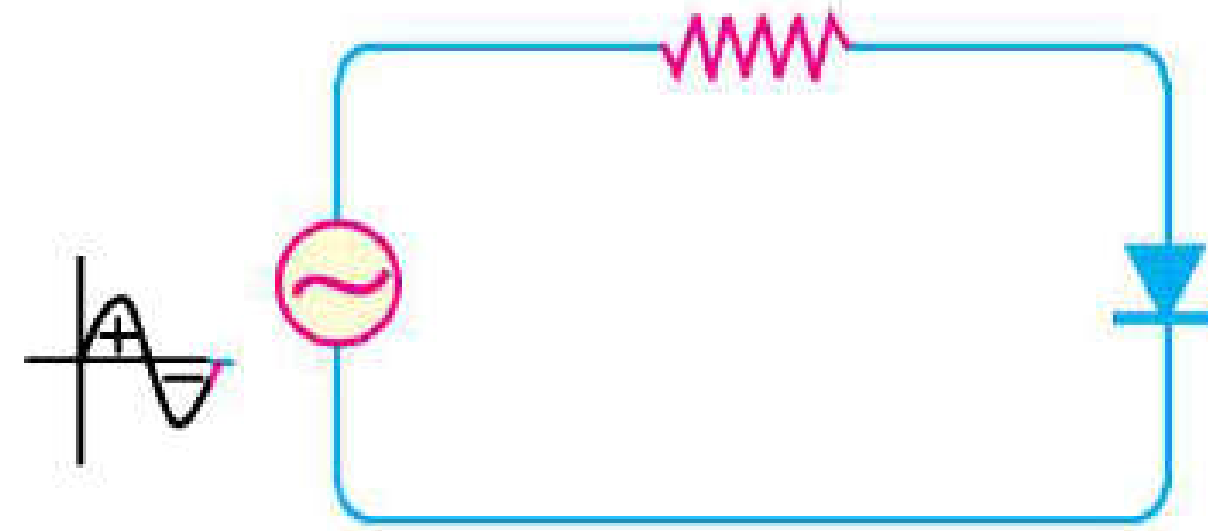

(ii)

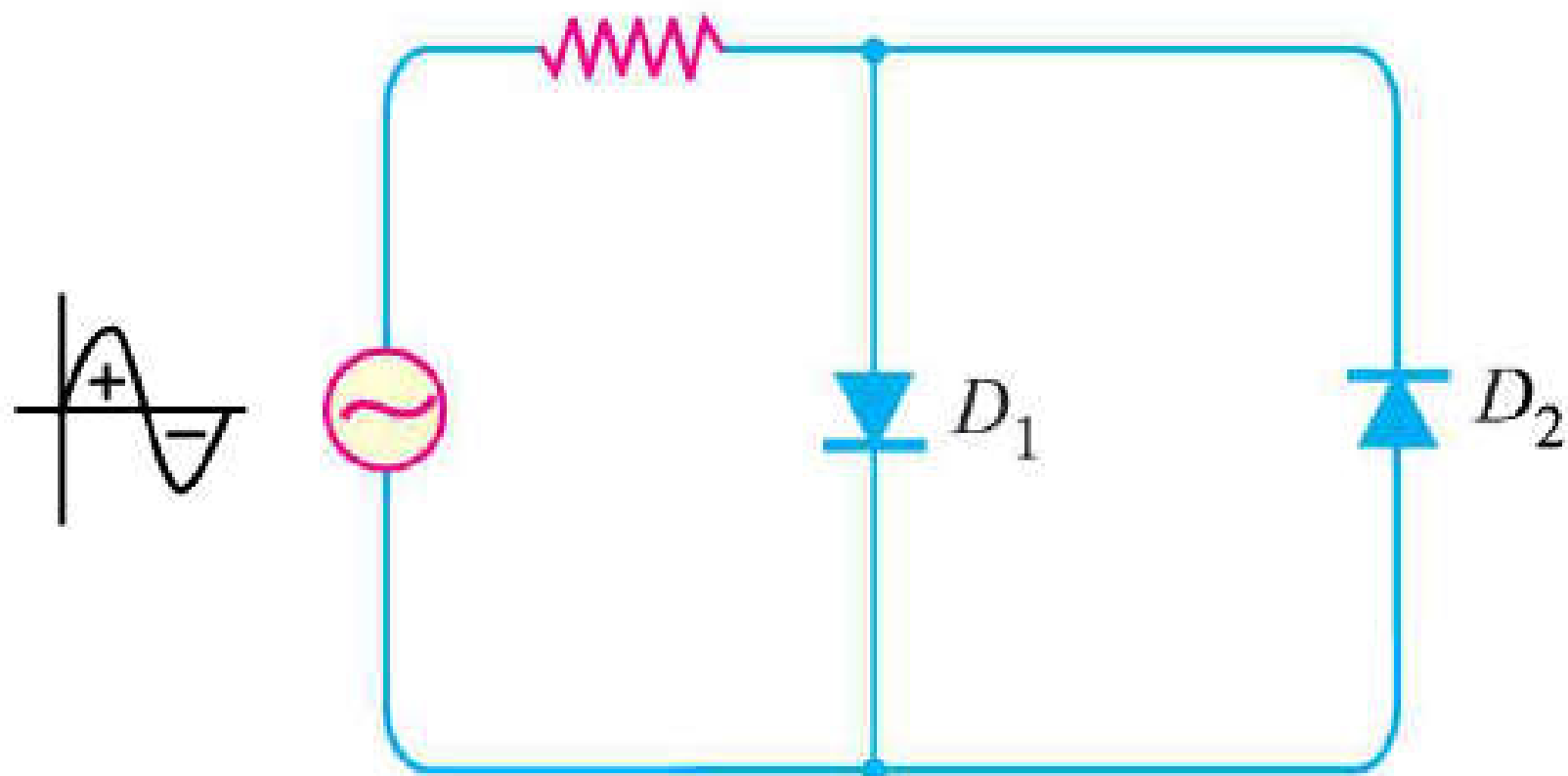

(iii)


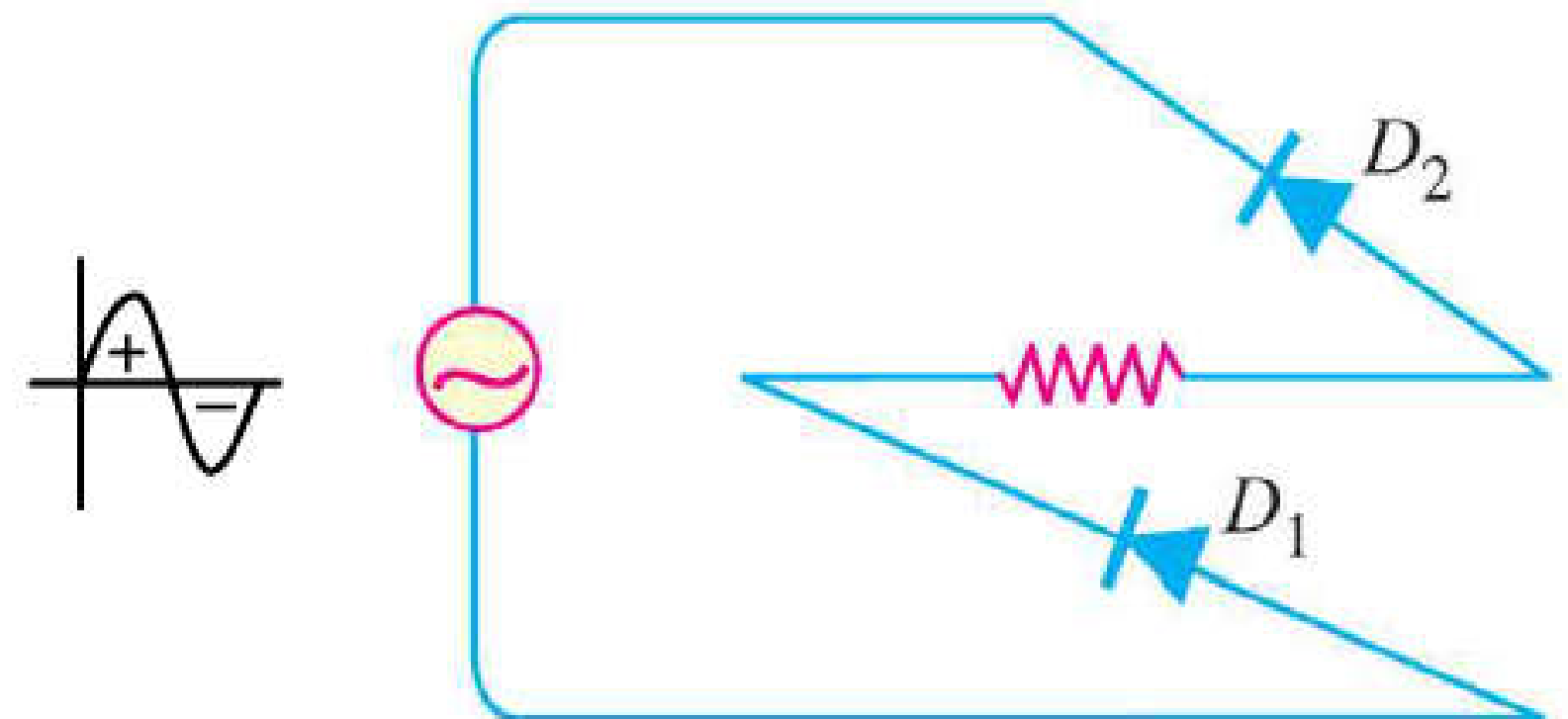


(iv)






Diode as a Clipper (Series)




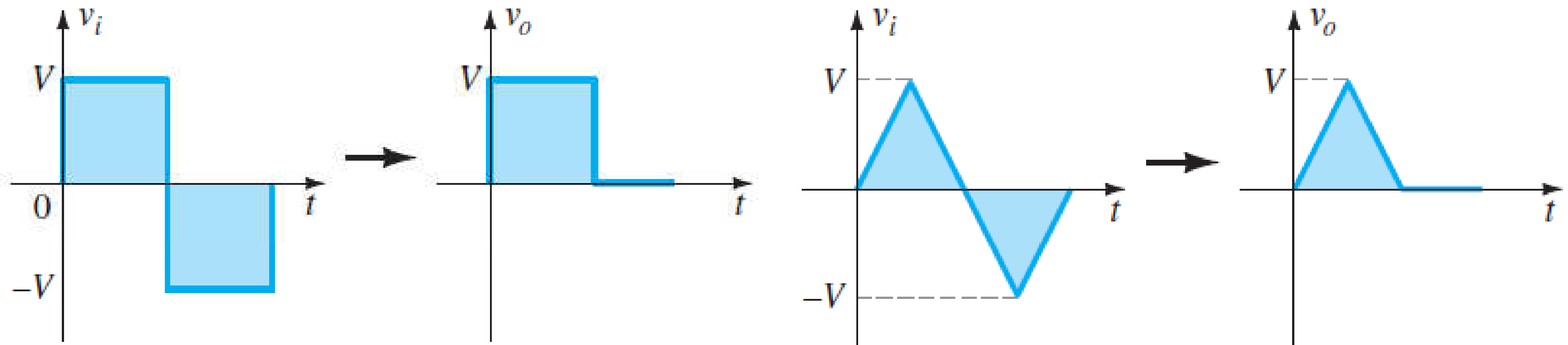
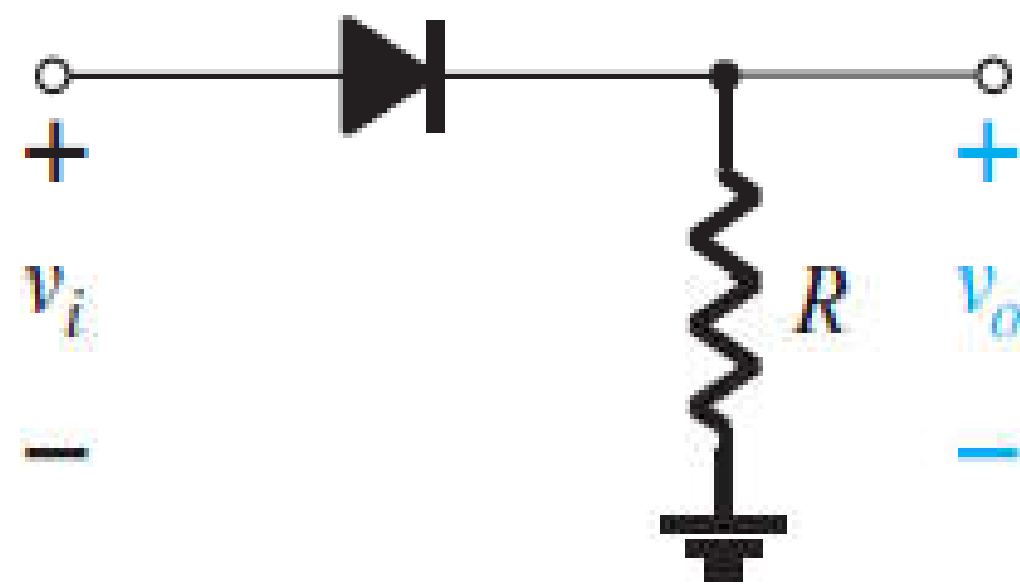
Clipping a portion of an input signal without distorting the remaining part of the waveform







Diode as a Clipper (Parallel)

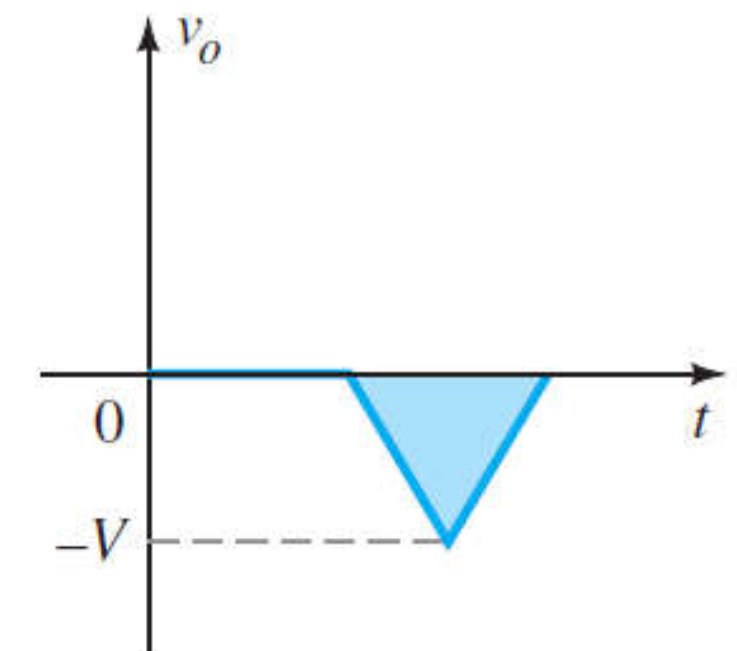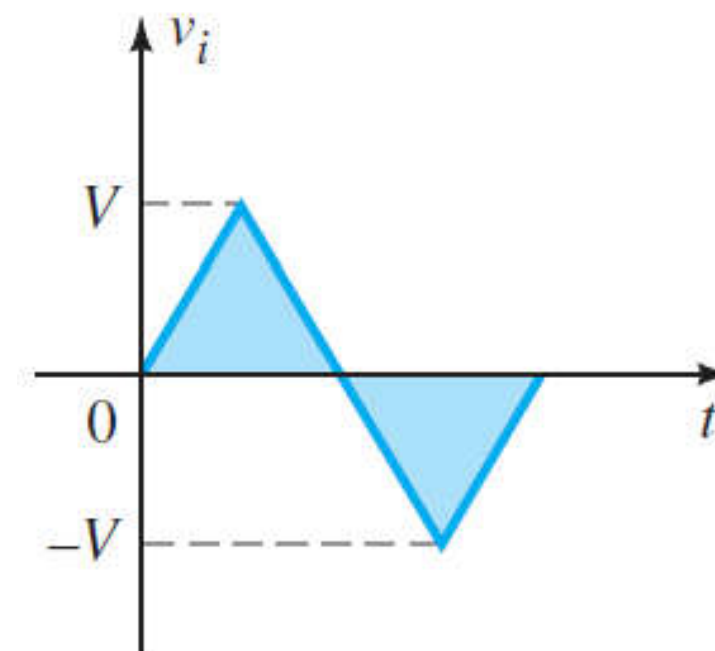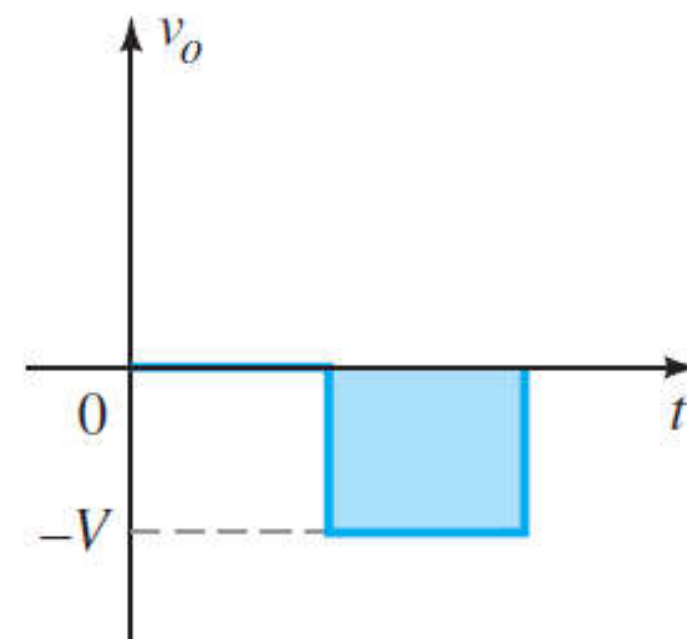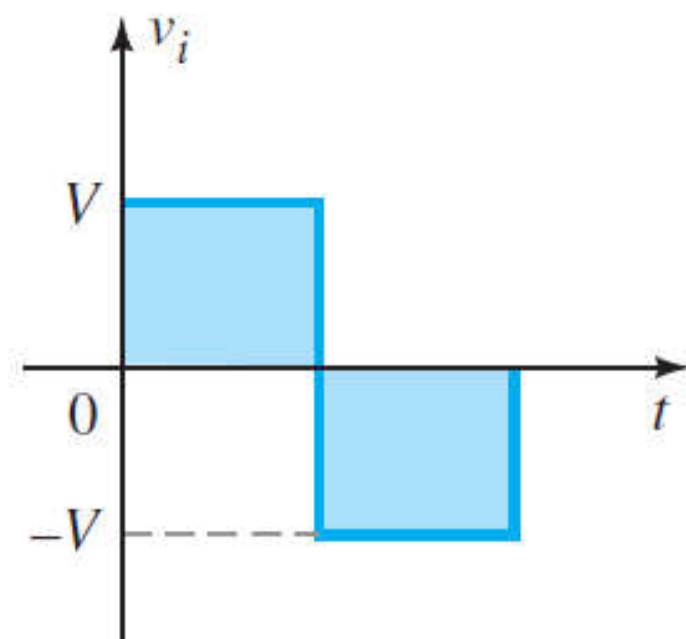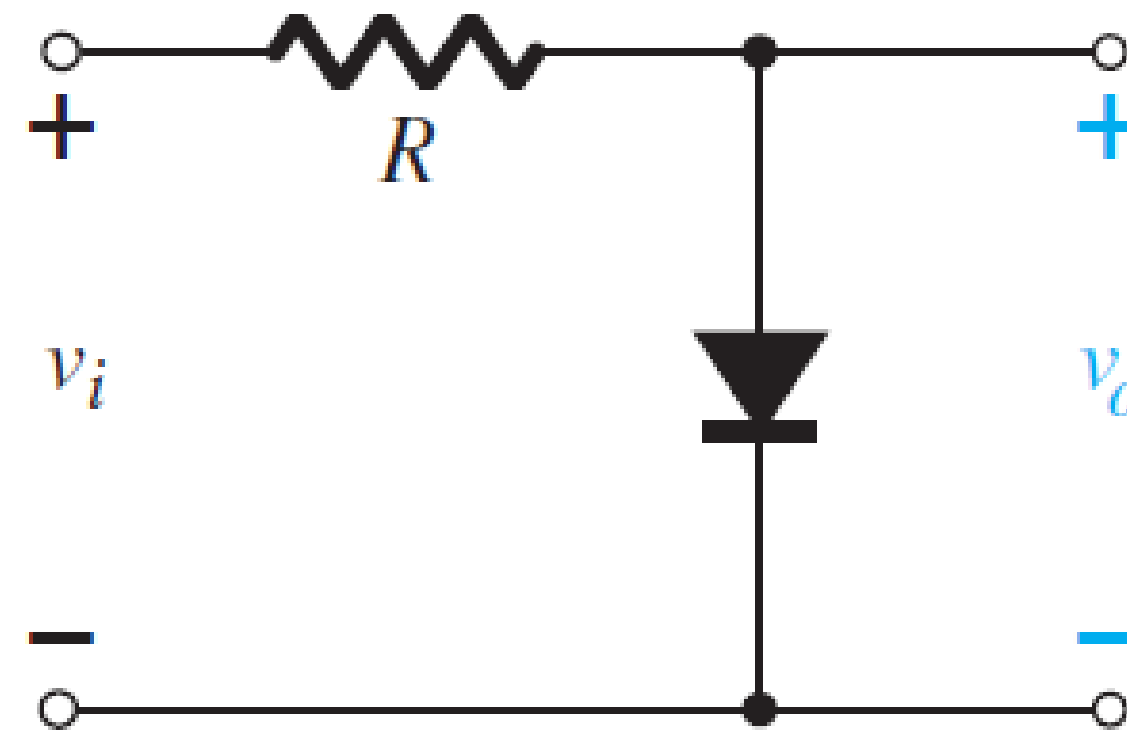

Concept Check...

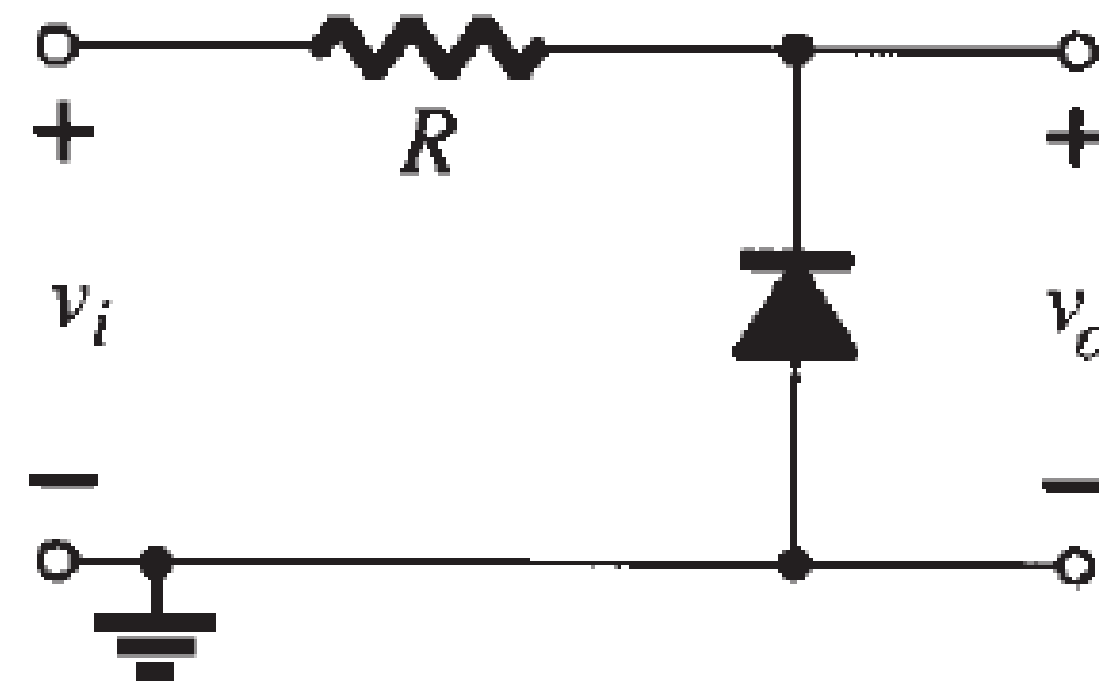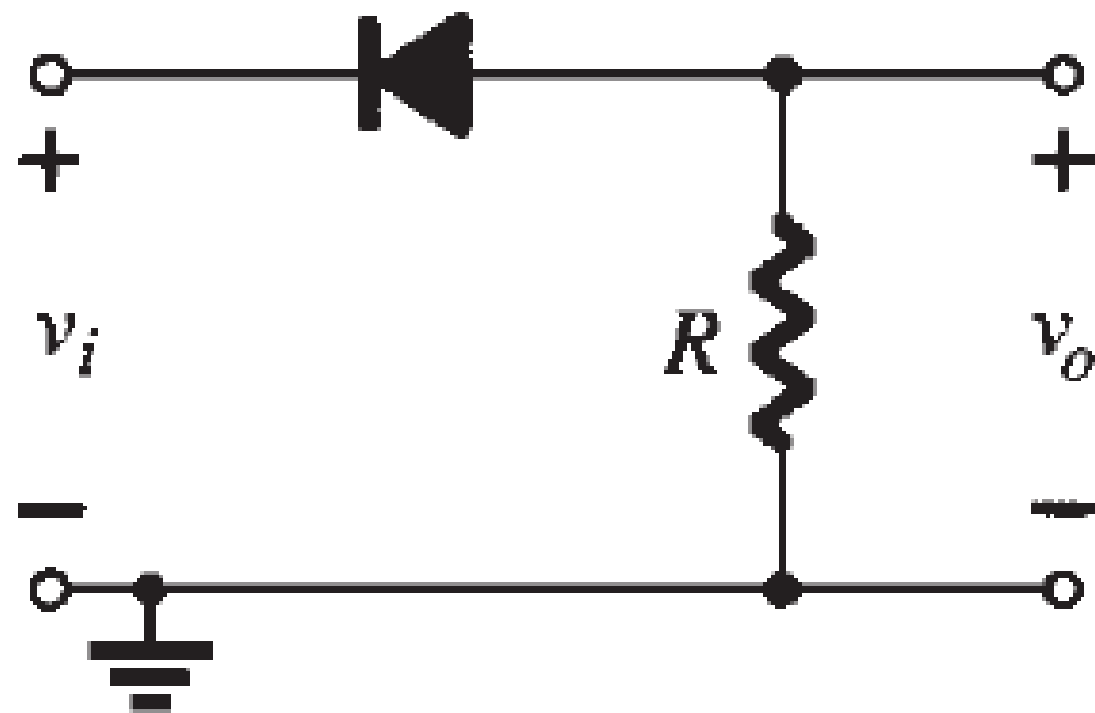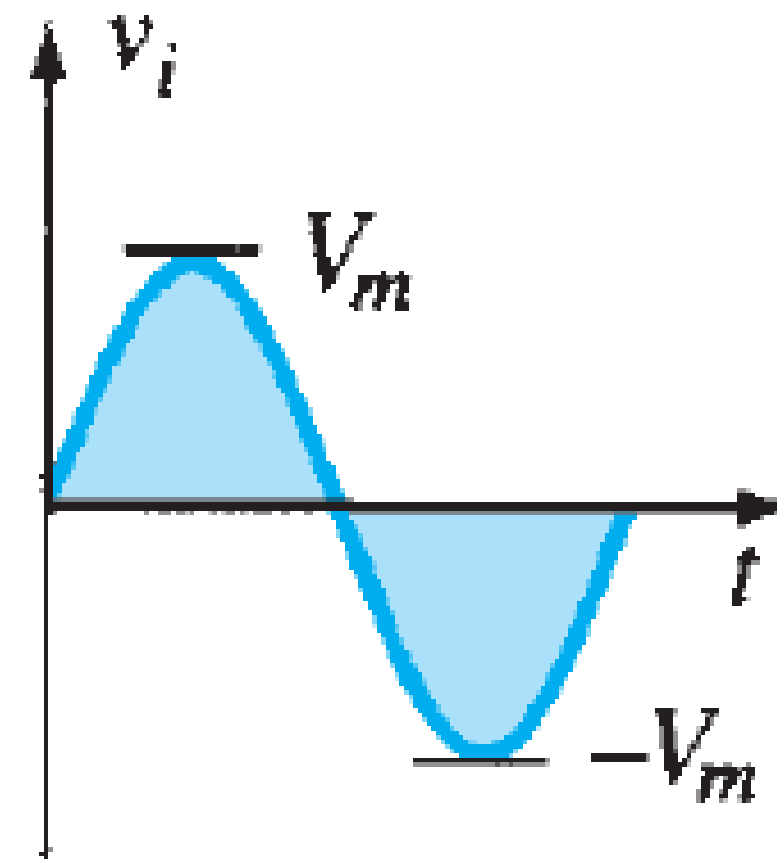

Solution

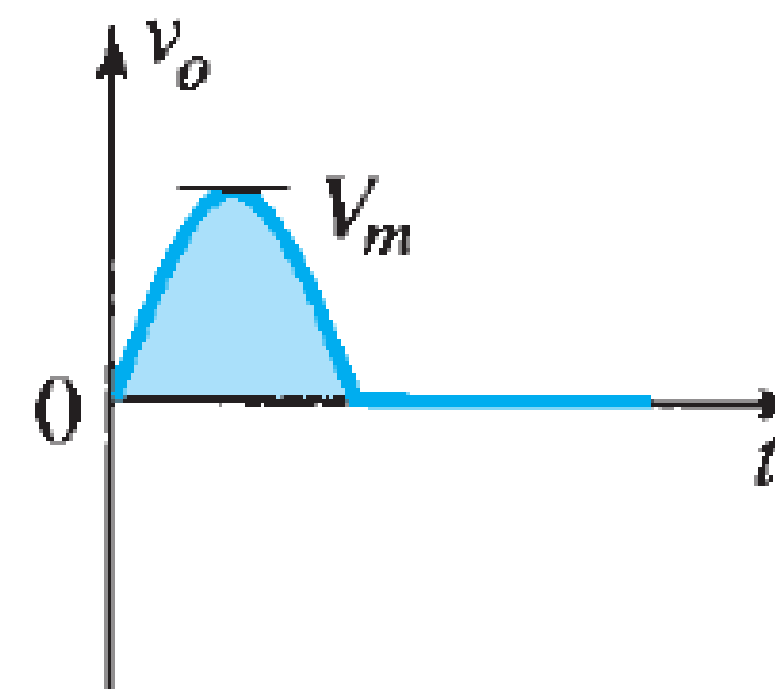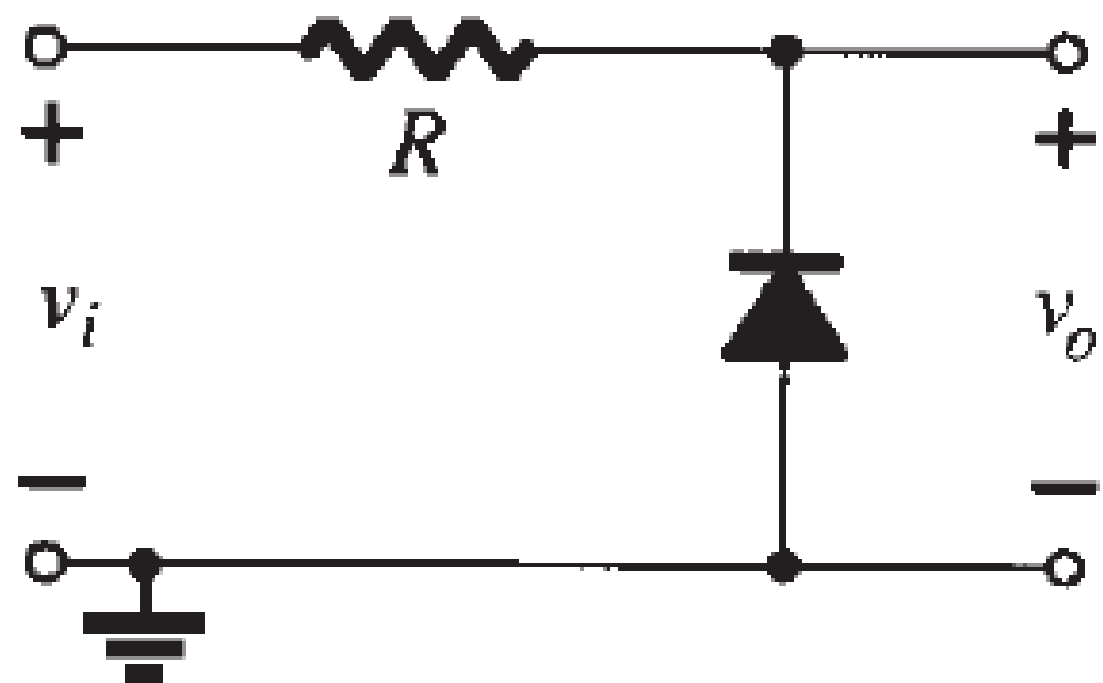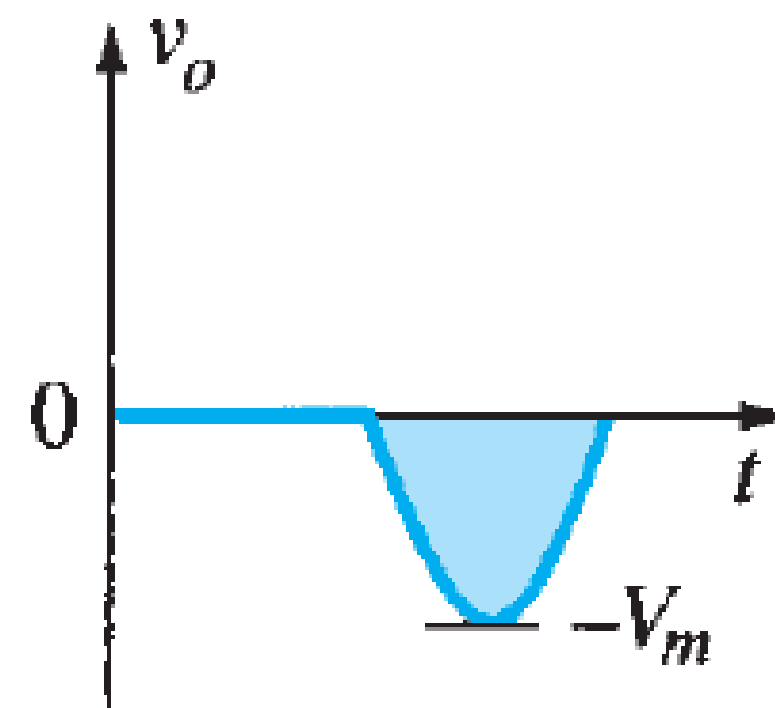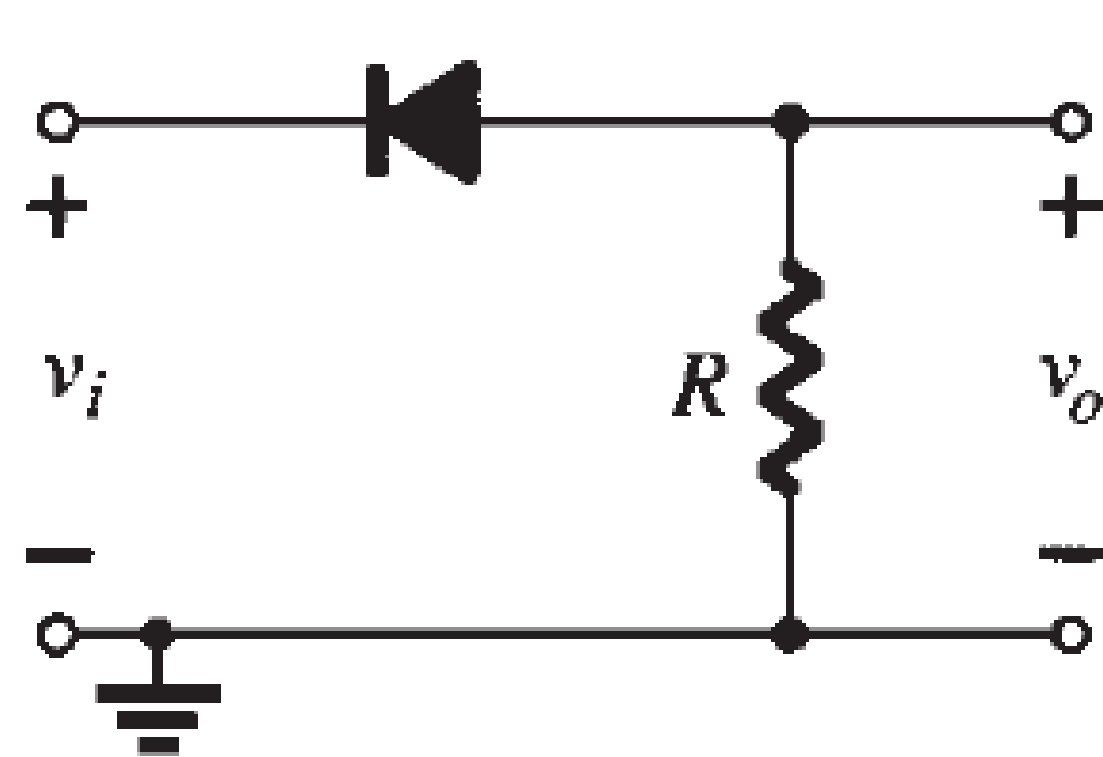

To Be Continued...