

DELD



Unit 4

Registers and Counters

Electronics Engineering Department

Registers







- ❑ An Array of Flip-Flops used to store binary information
- ❑ No. of Flip-Flops will be equal to the no of bits required to store the information
- ❑ Data can be entered serially or parallely
- ❑ It can also be used for Data movement
- ❑ Basically know as shift register, it shifts it output every clock pulse

Types





- ☐ Serial In Serial Out
 - ☐ Serial In Parallel Out
 - ☐ Parallel In Serial Out
 - ☐ Parallel In Parallel Out
-
- ☐ Shift Left
 - ☐ Shift Right


Types

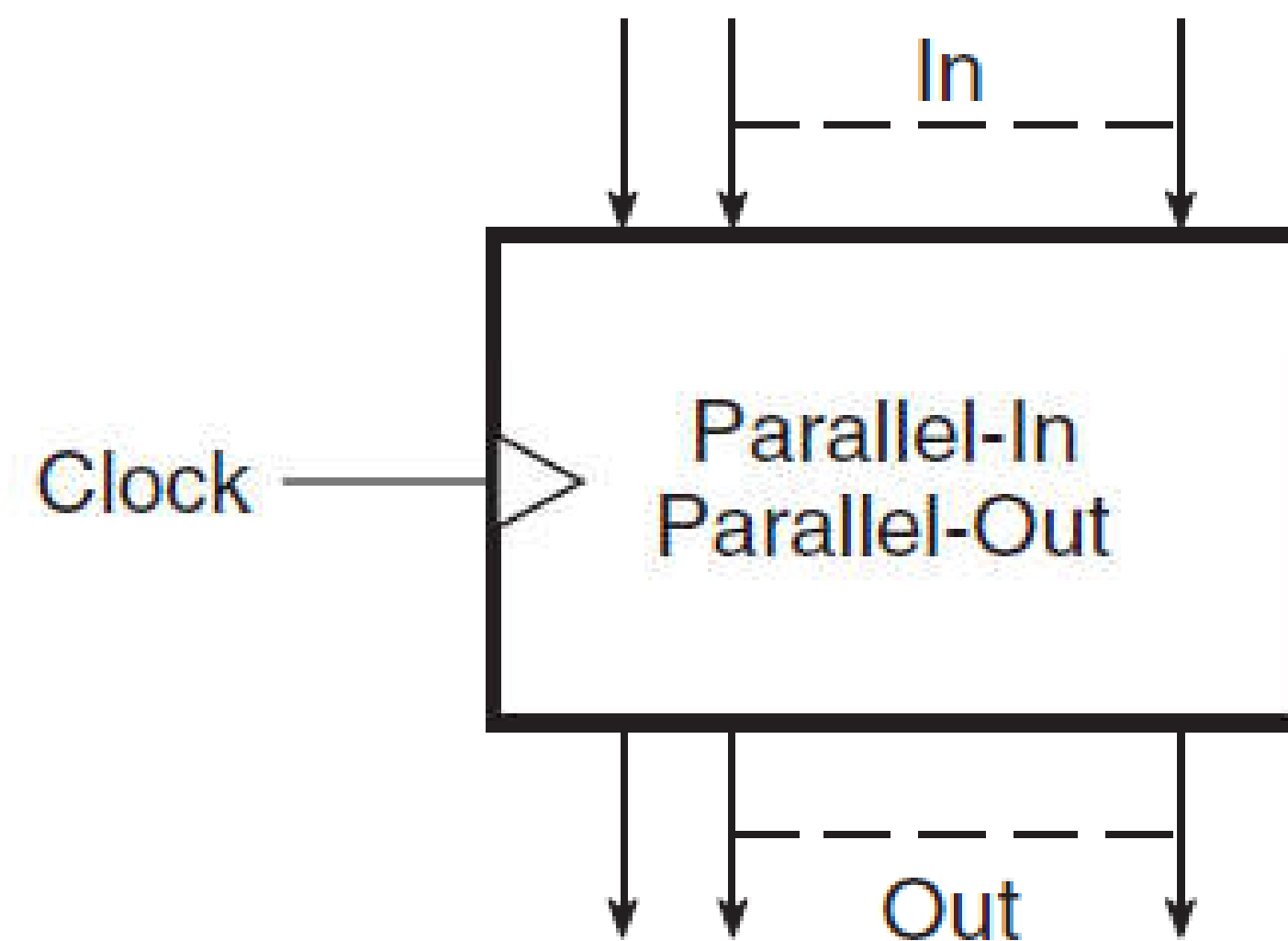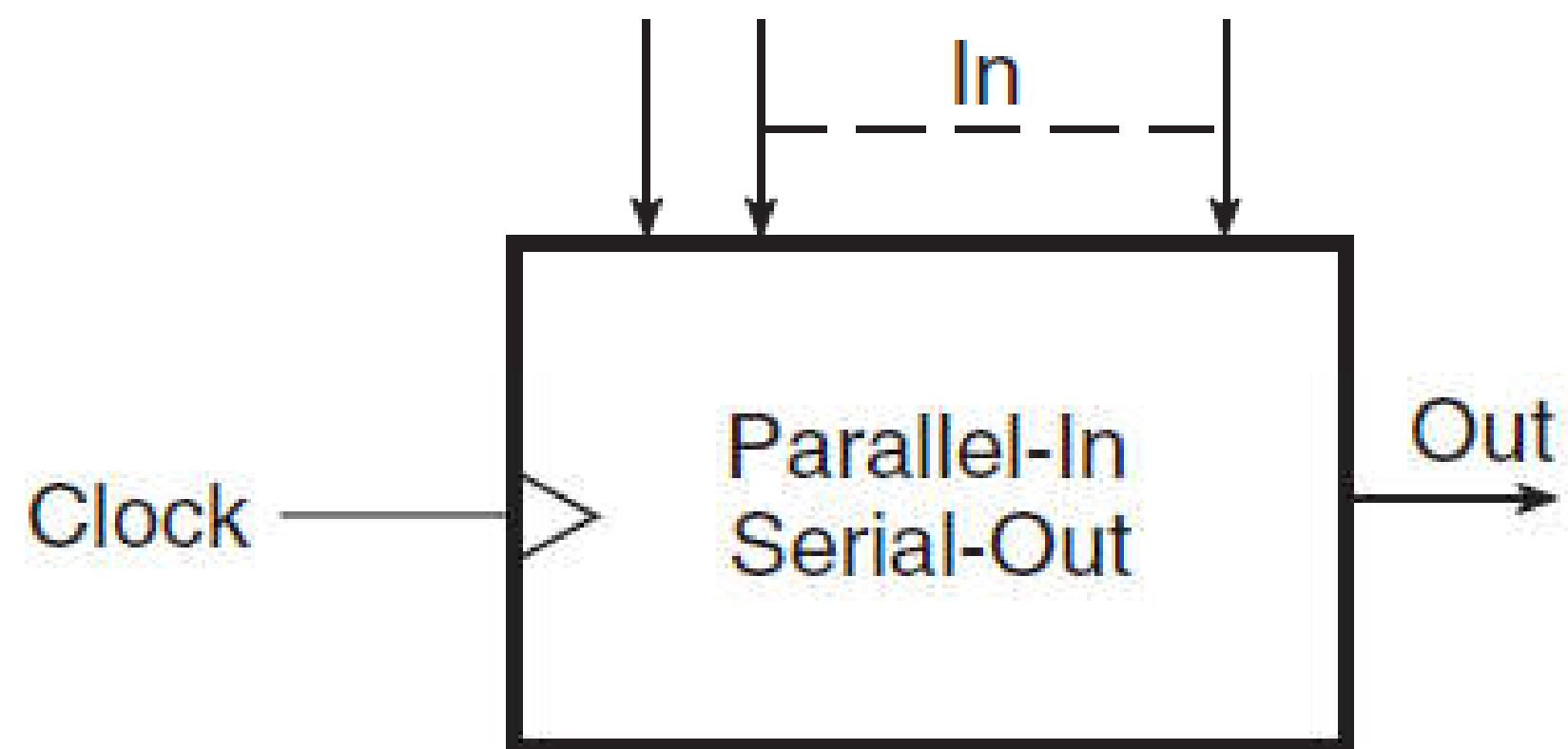
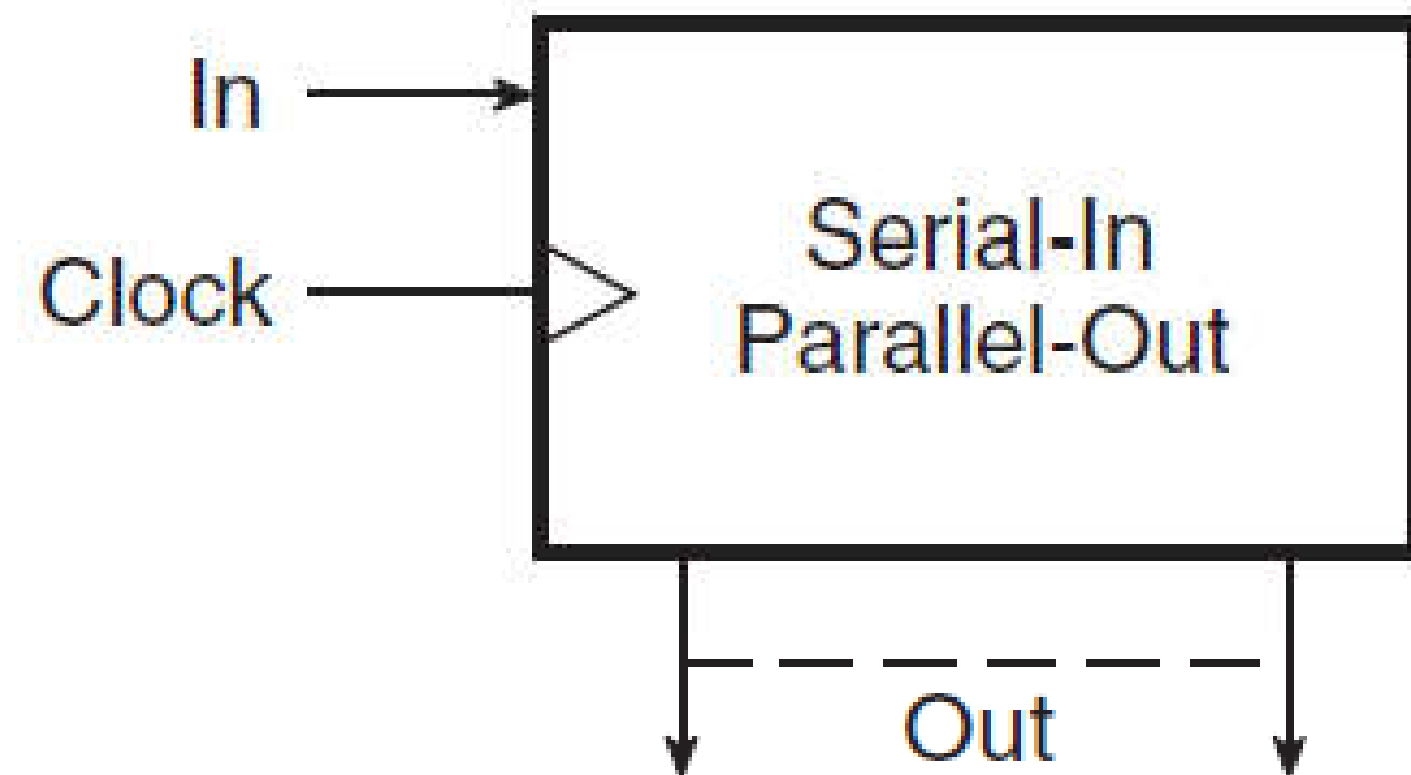
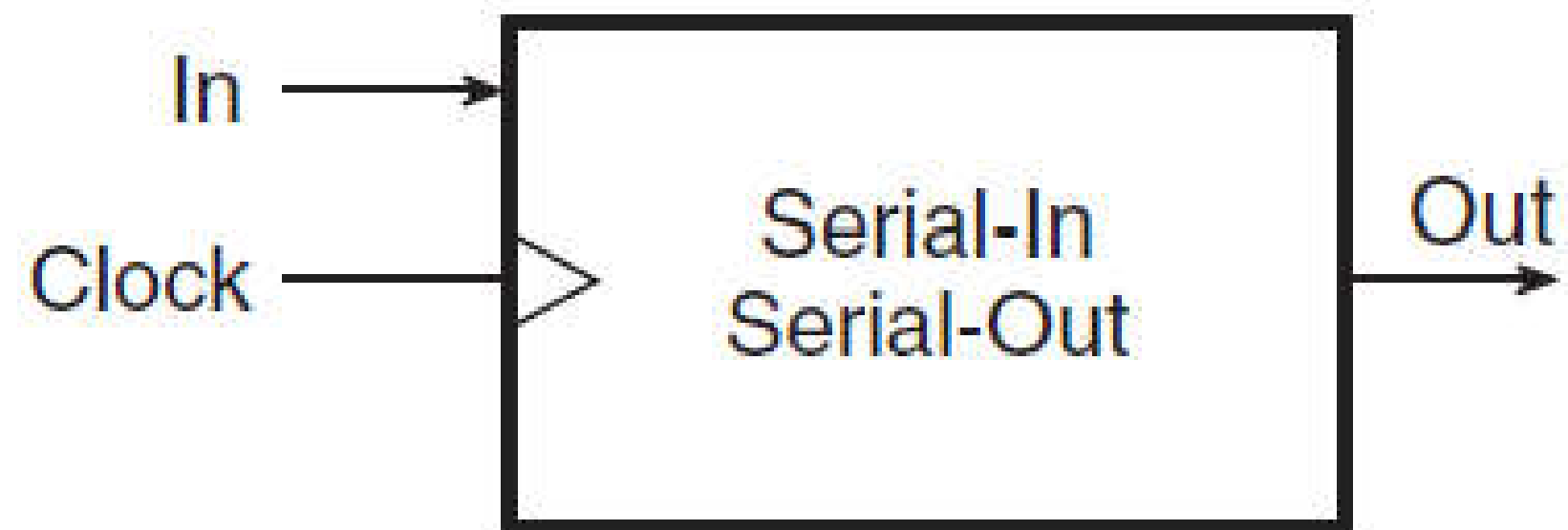






Working Concept

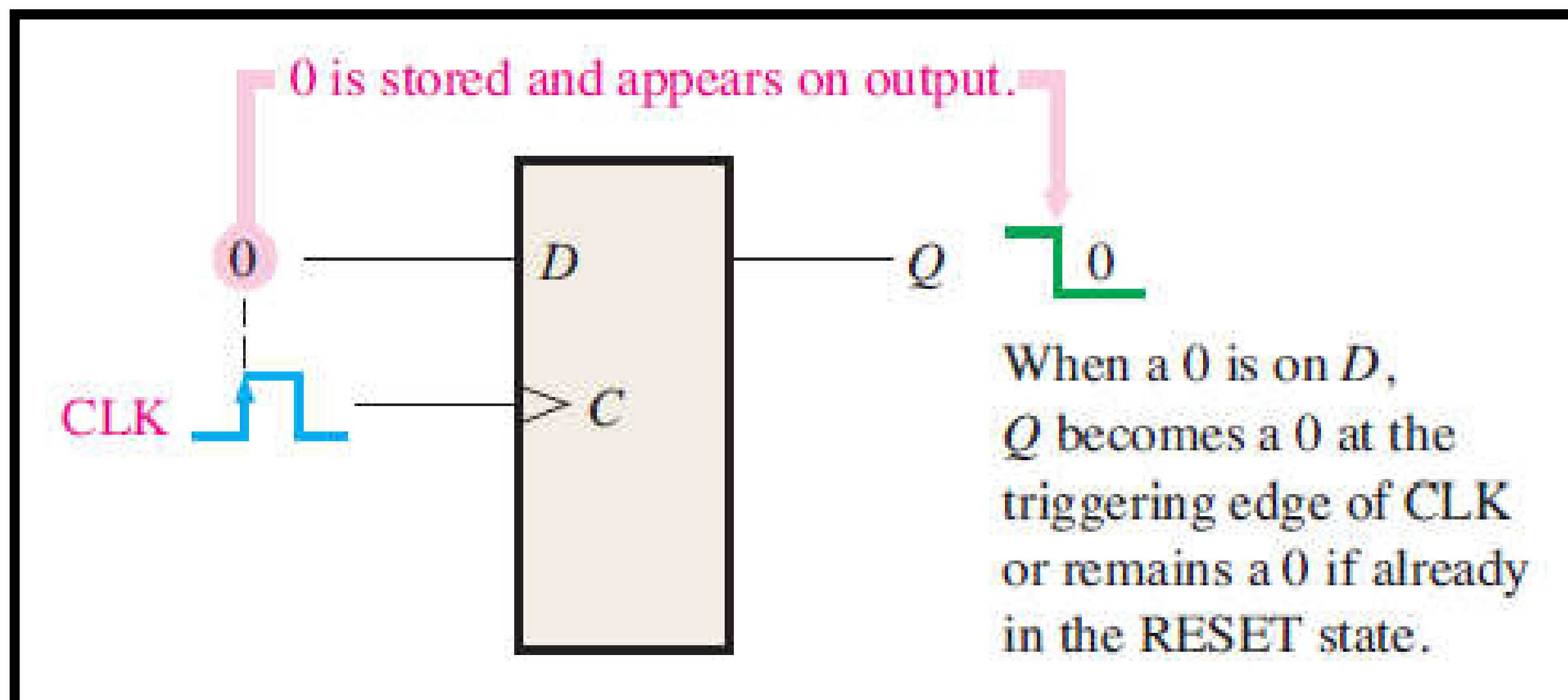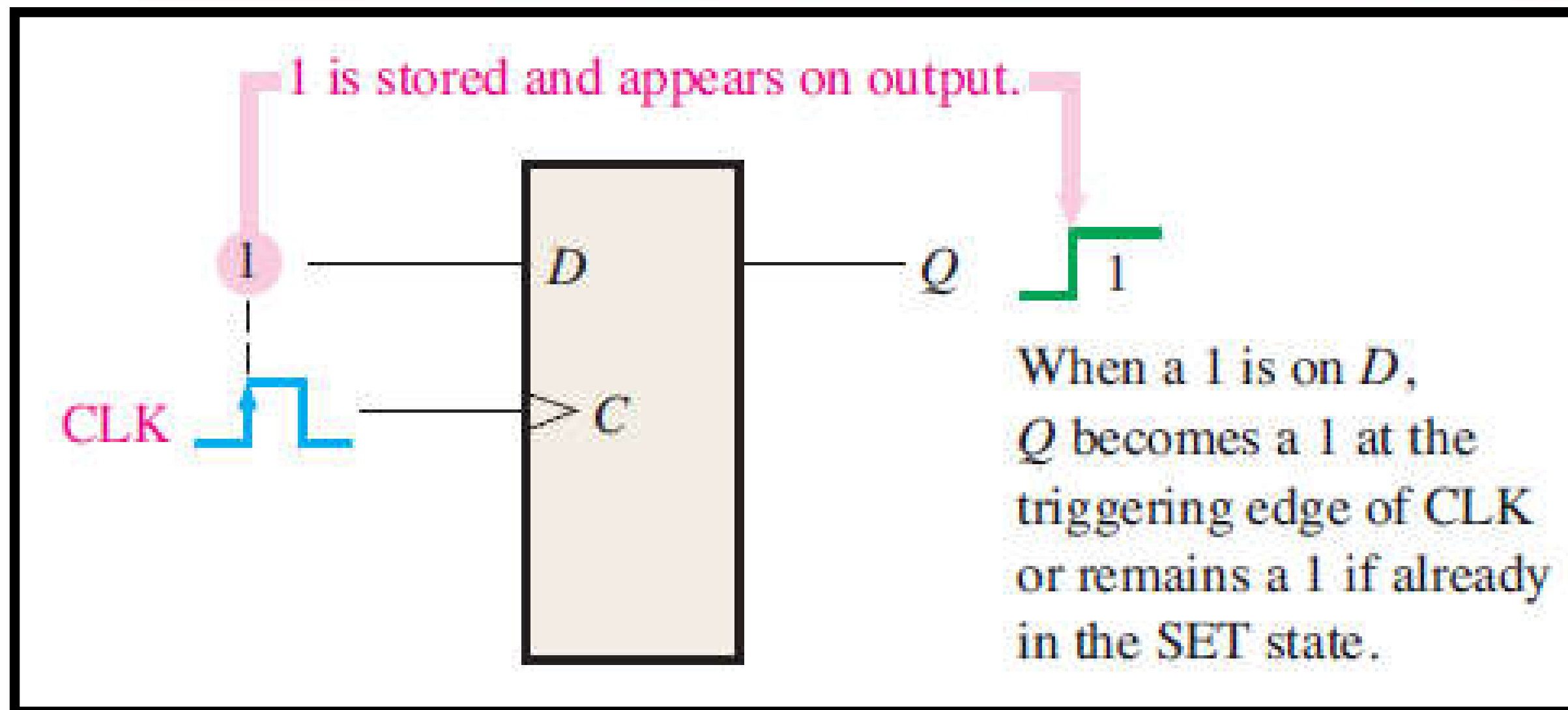


Another Perspective

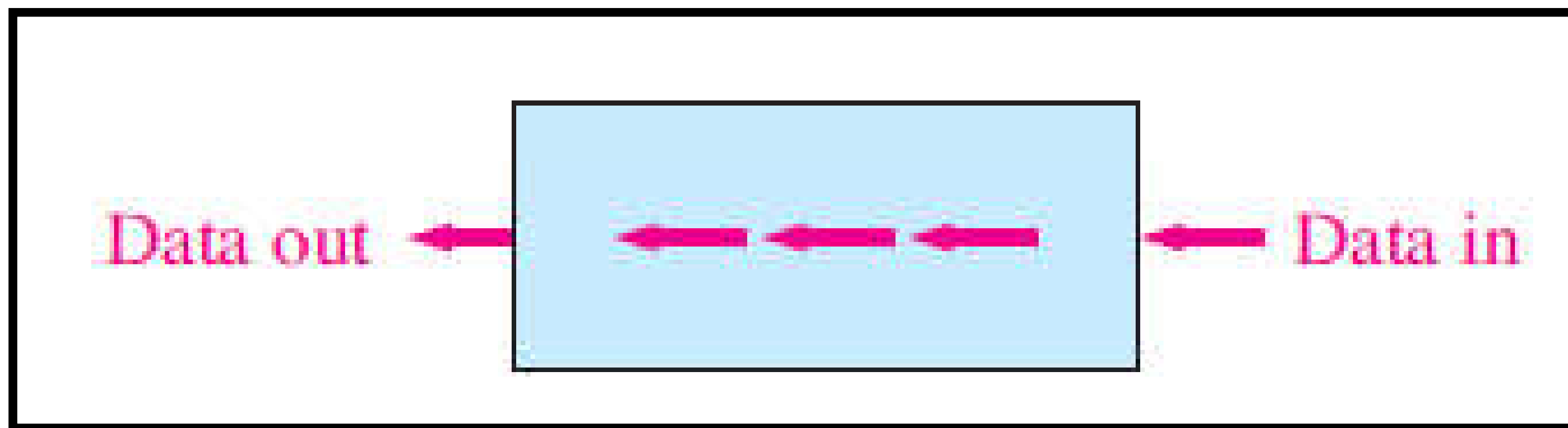

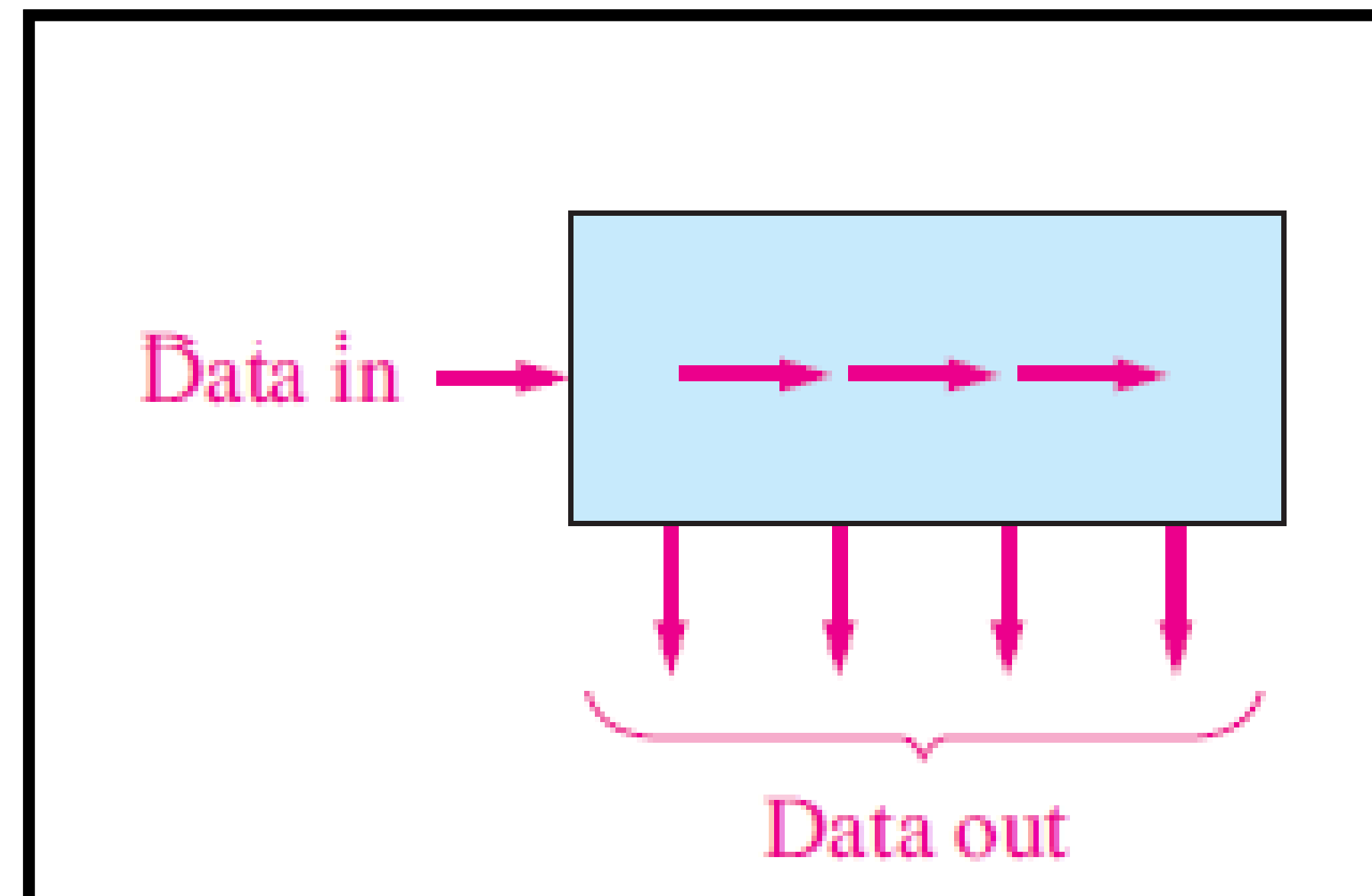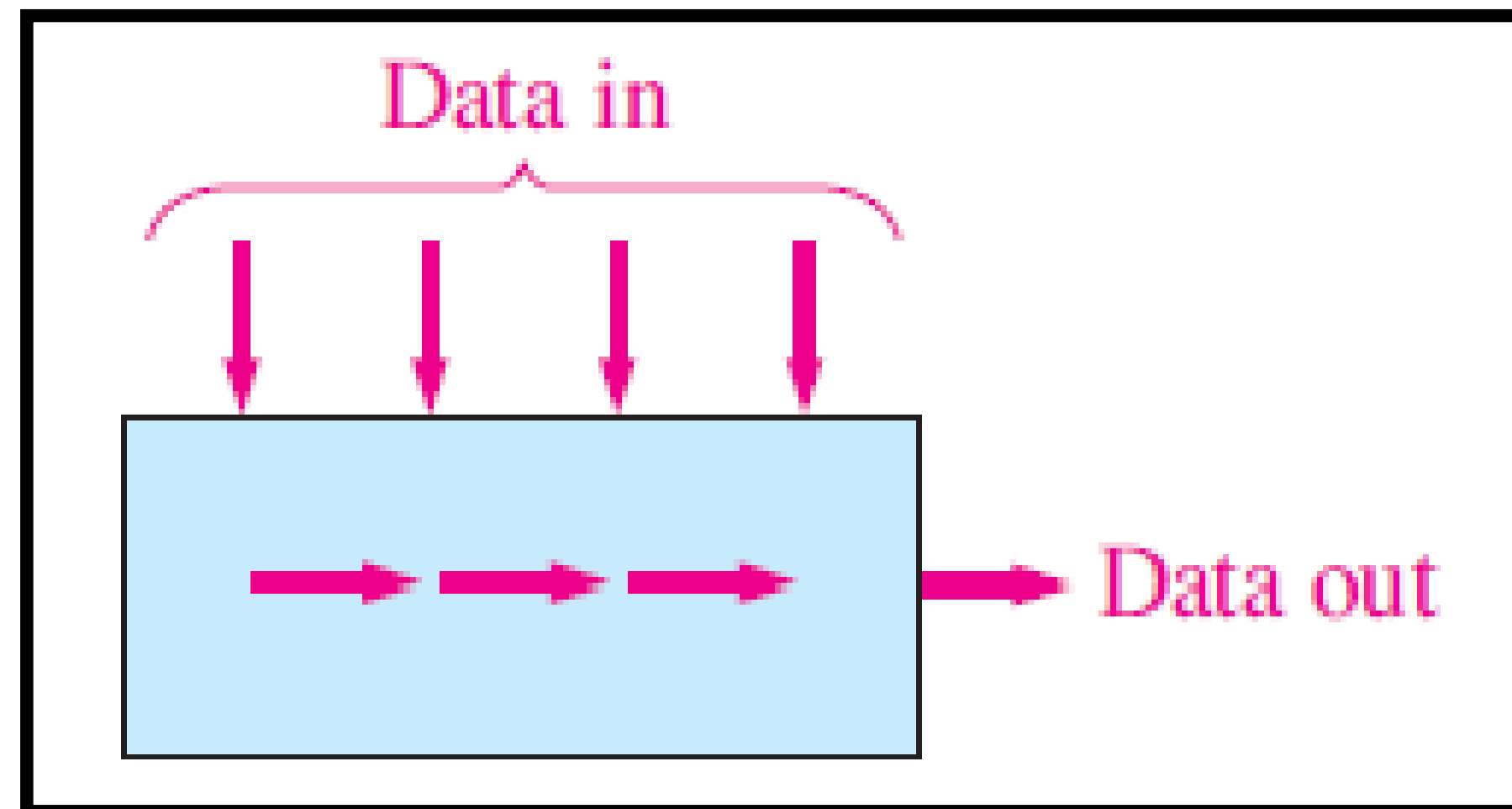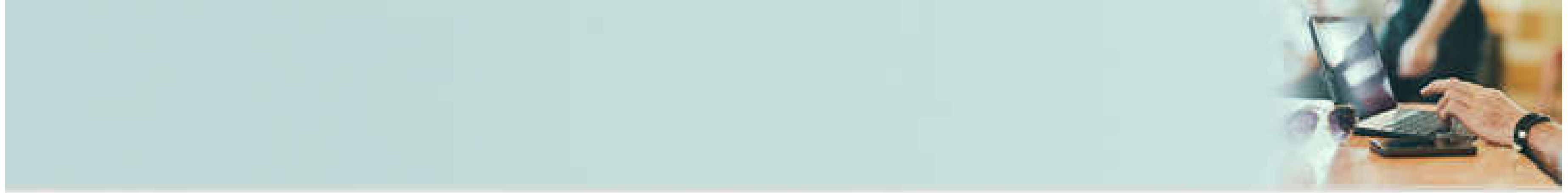

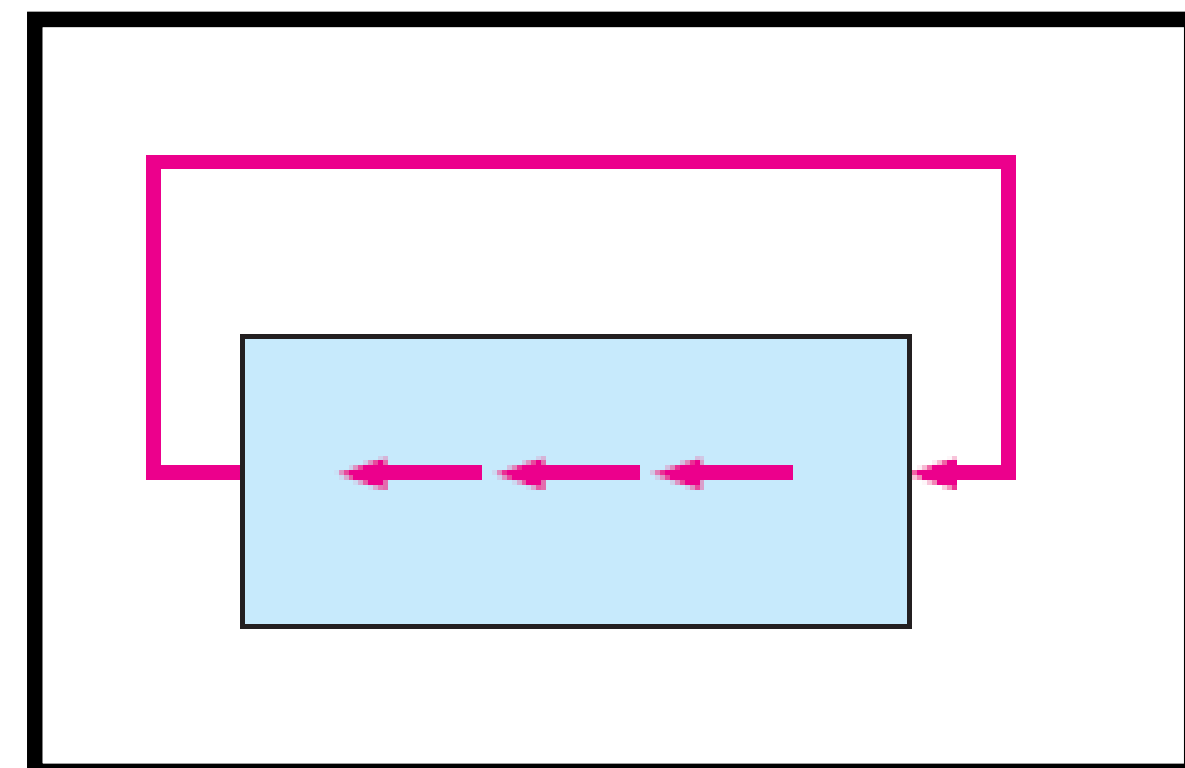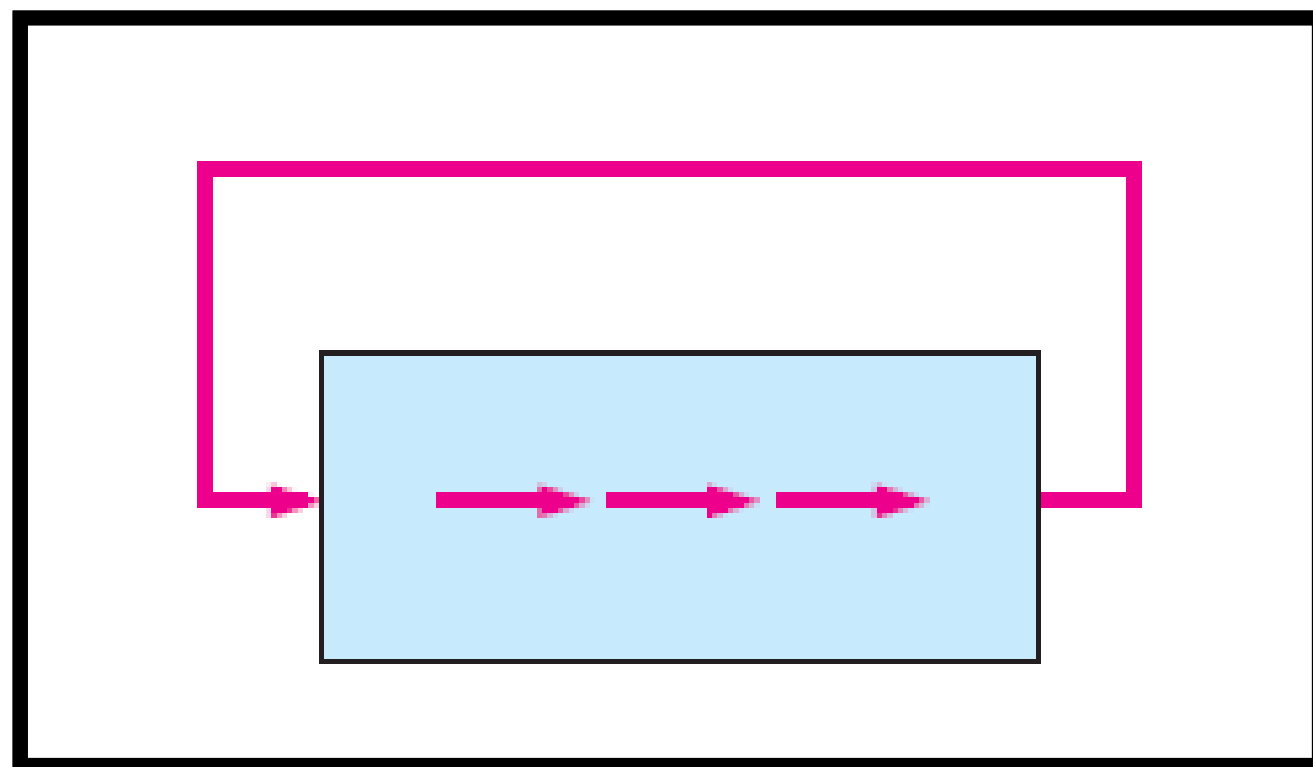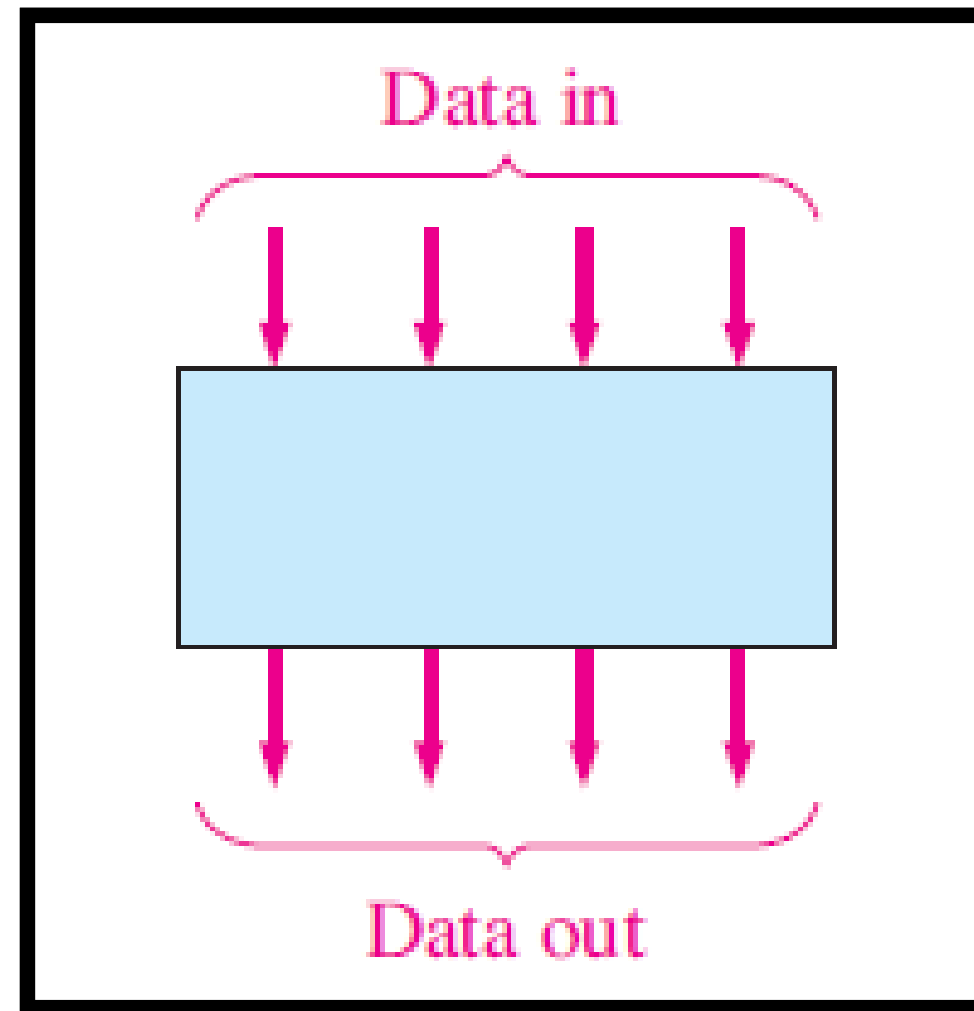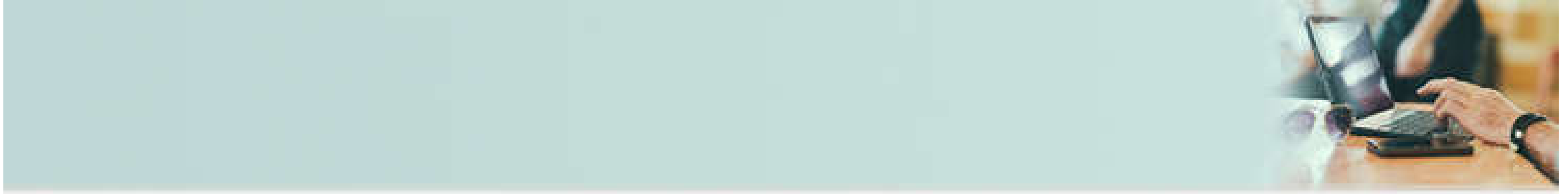

Serial In Serial Out

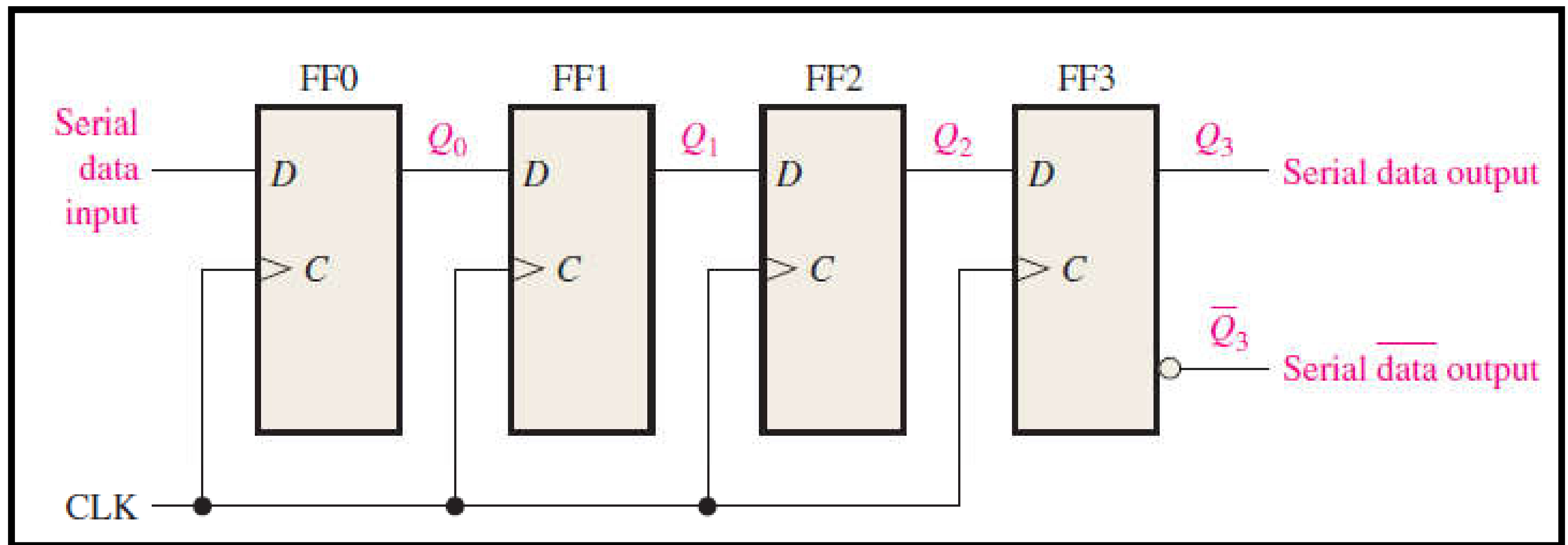

Bit Movement





CLK	FF0 (Q_0)	FF1 (Q_1)	FF2 (Q_2)	FF3 (Q_3)
Initial	0	0	0	0
1	0	0	0	0
2	1	0	0	0
3	0	1	0	0
4	1	0	1	0

Bit Movement Cont..




CLK	FF0 (Q_0)	FF1 (Q_1)	FF2 (Q_2)	FF3 (Q_3)
Initial	1	0	1	0
5	0	1	0	1
6	0	0	1	0
7	0	0	0	1
8	0	0	0	0


Concept Check

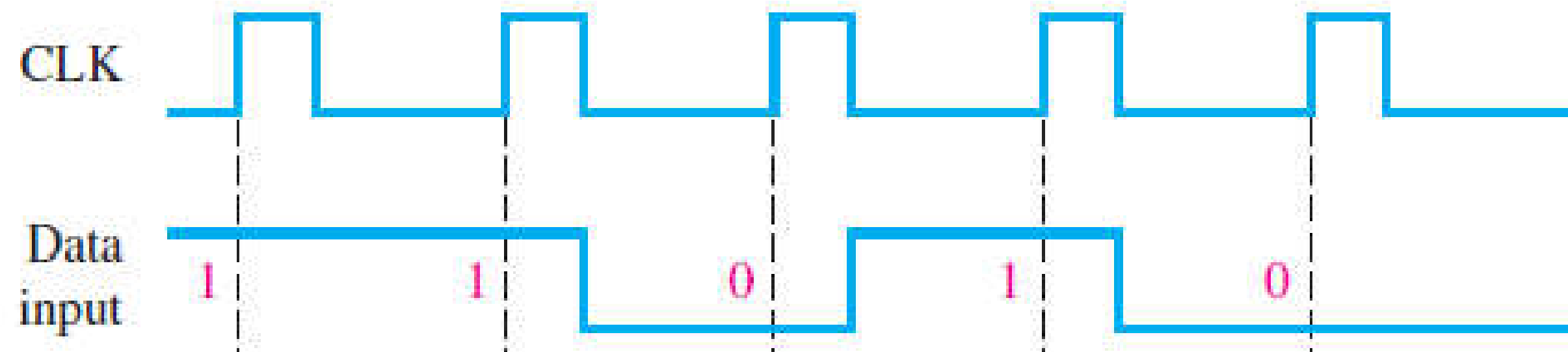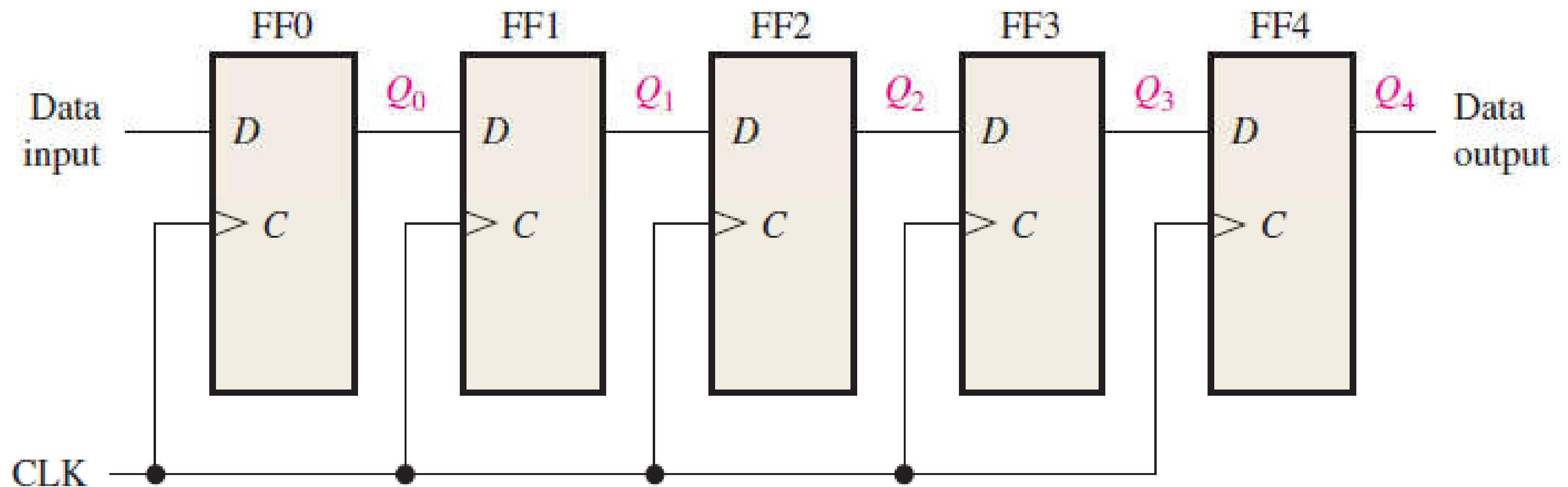


Solution

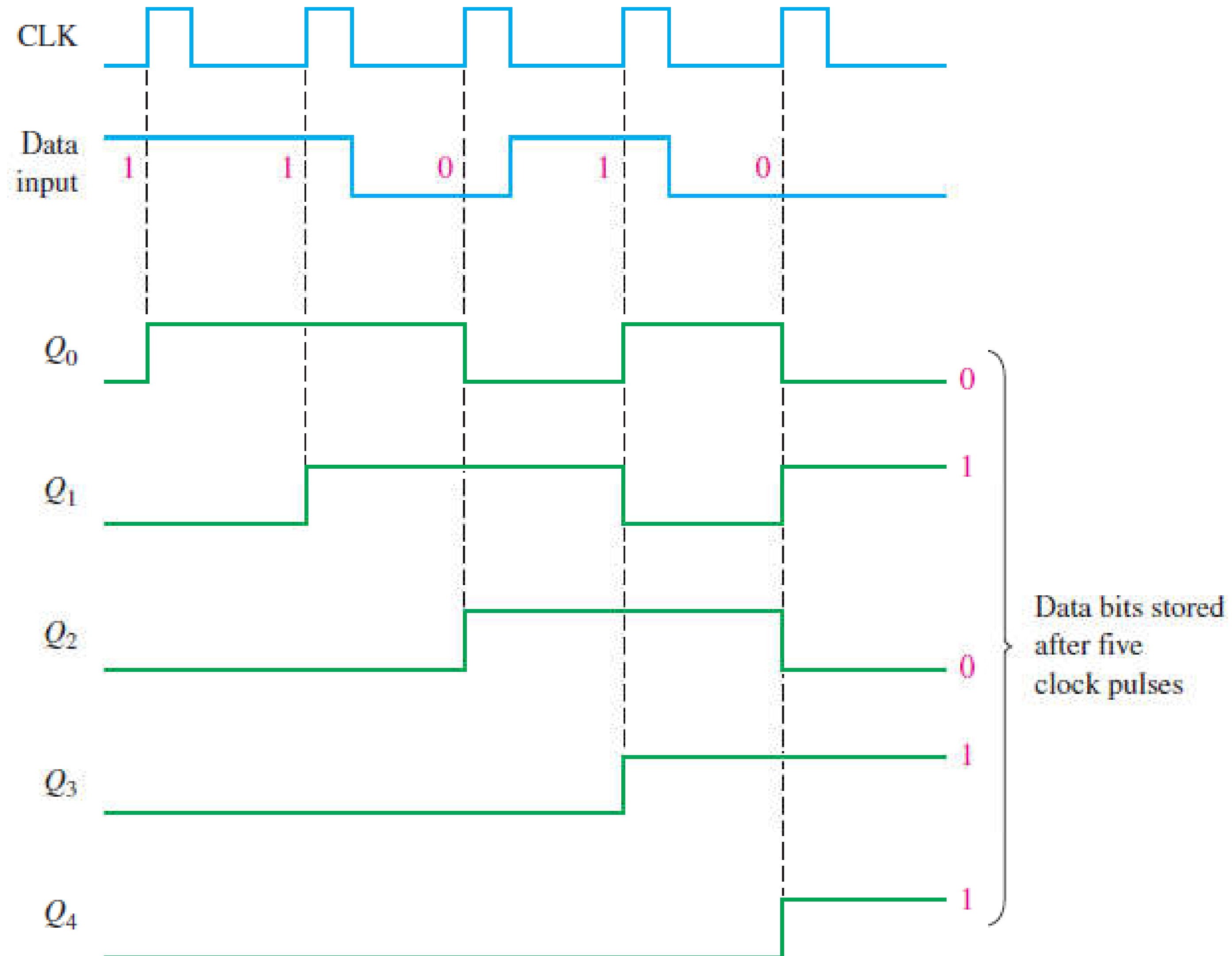


Serial In Parallel Out

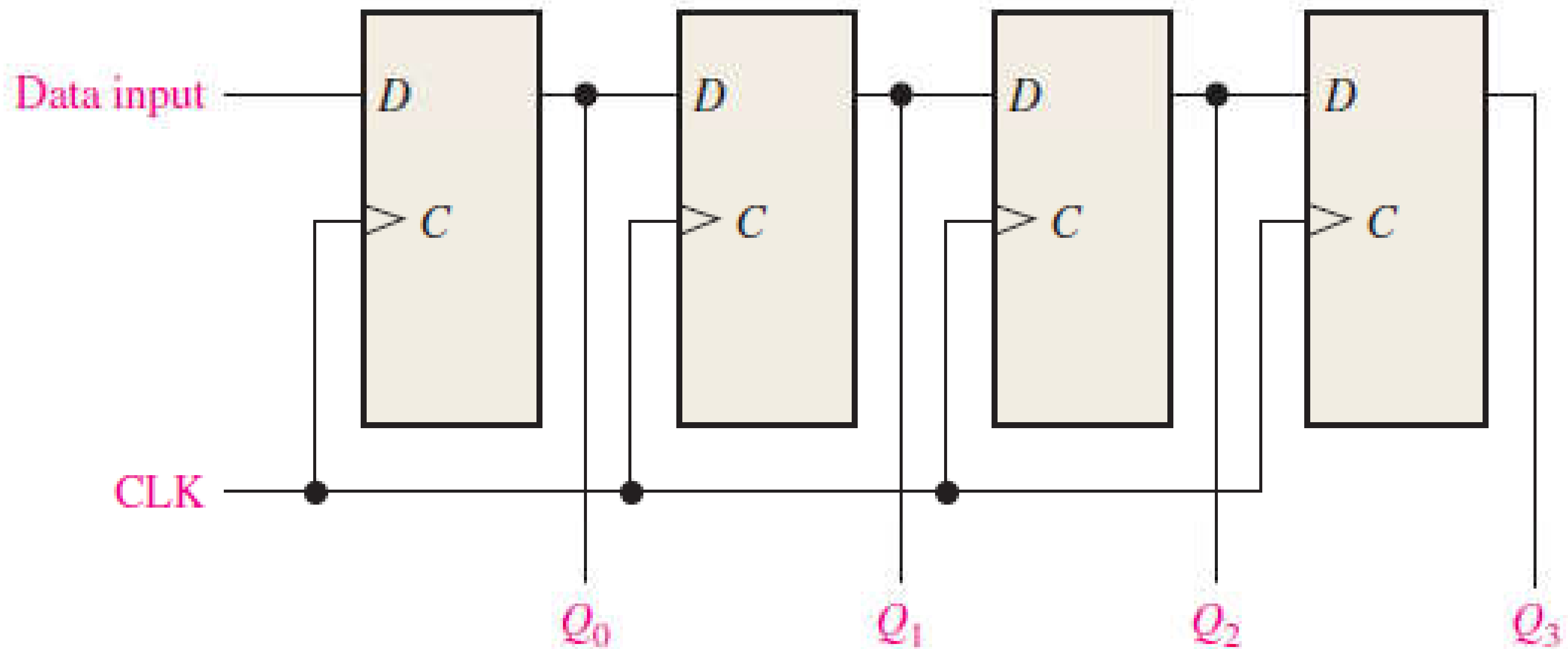


Concept Check

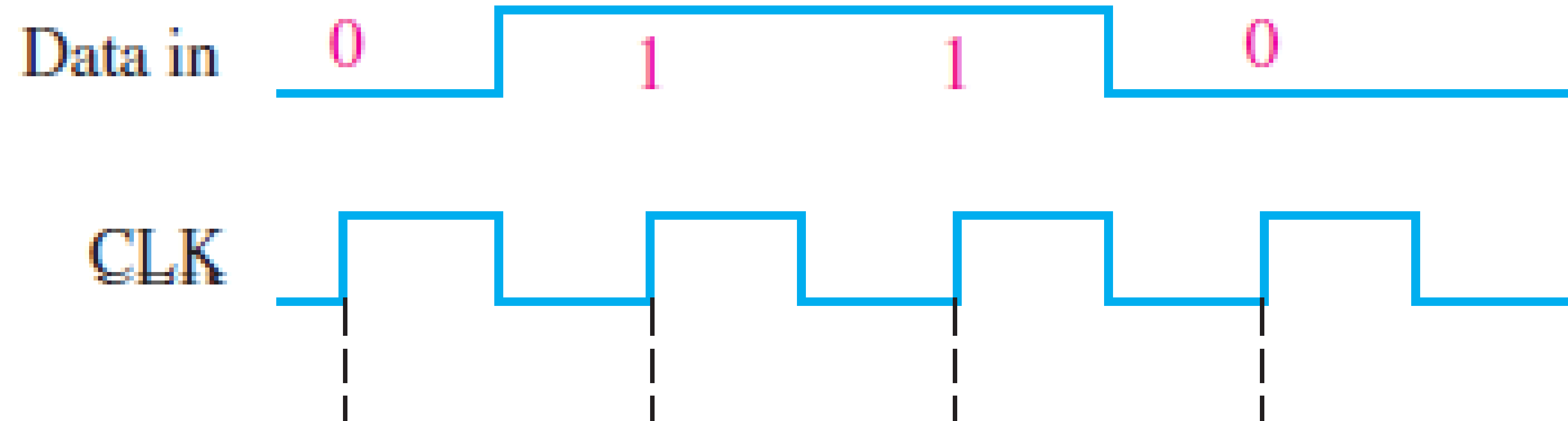

Solution

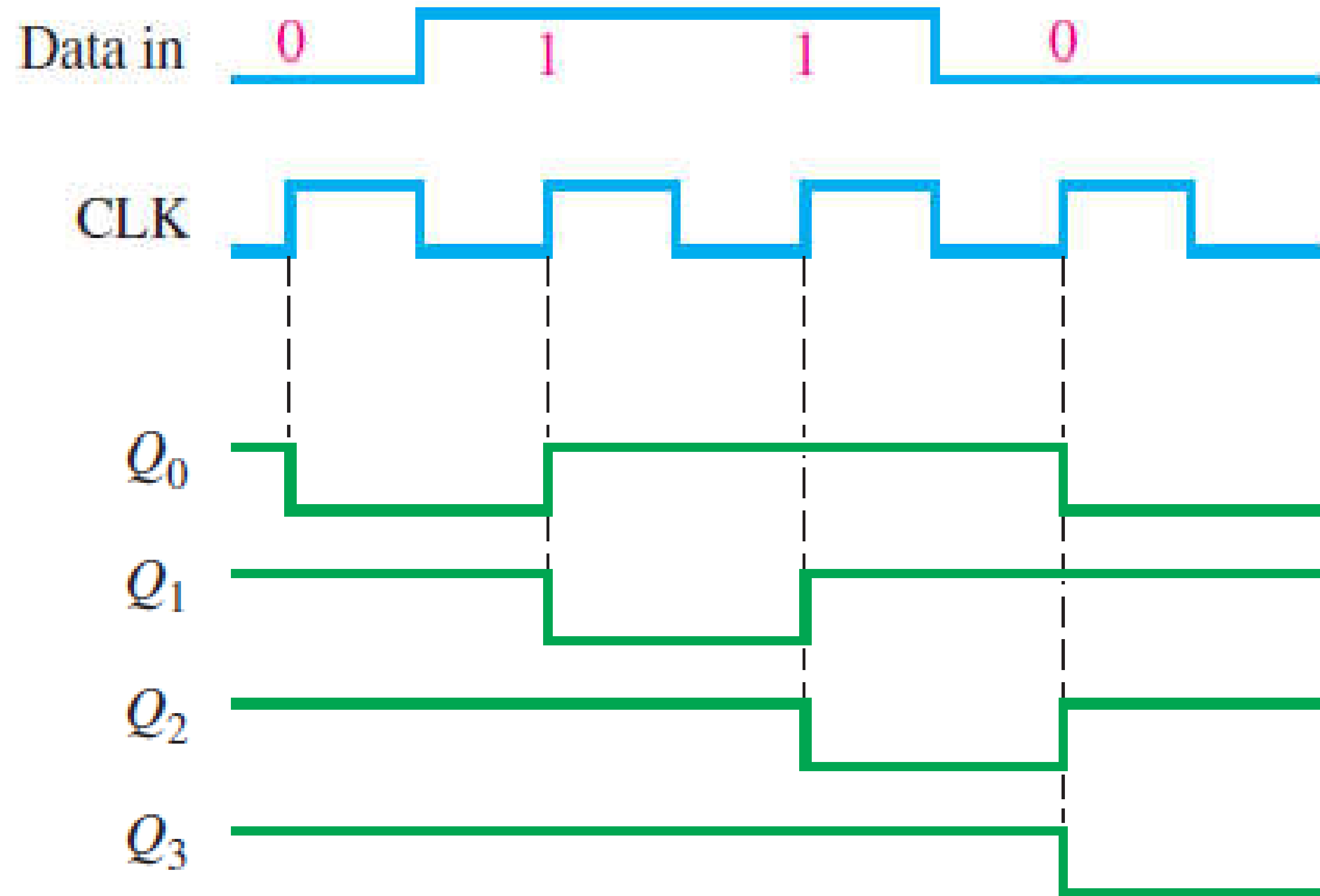

Parallel In Parallel Out

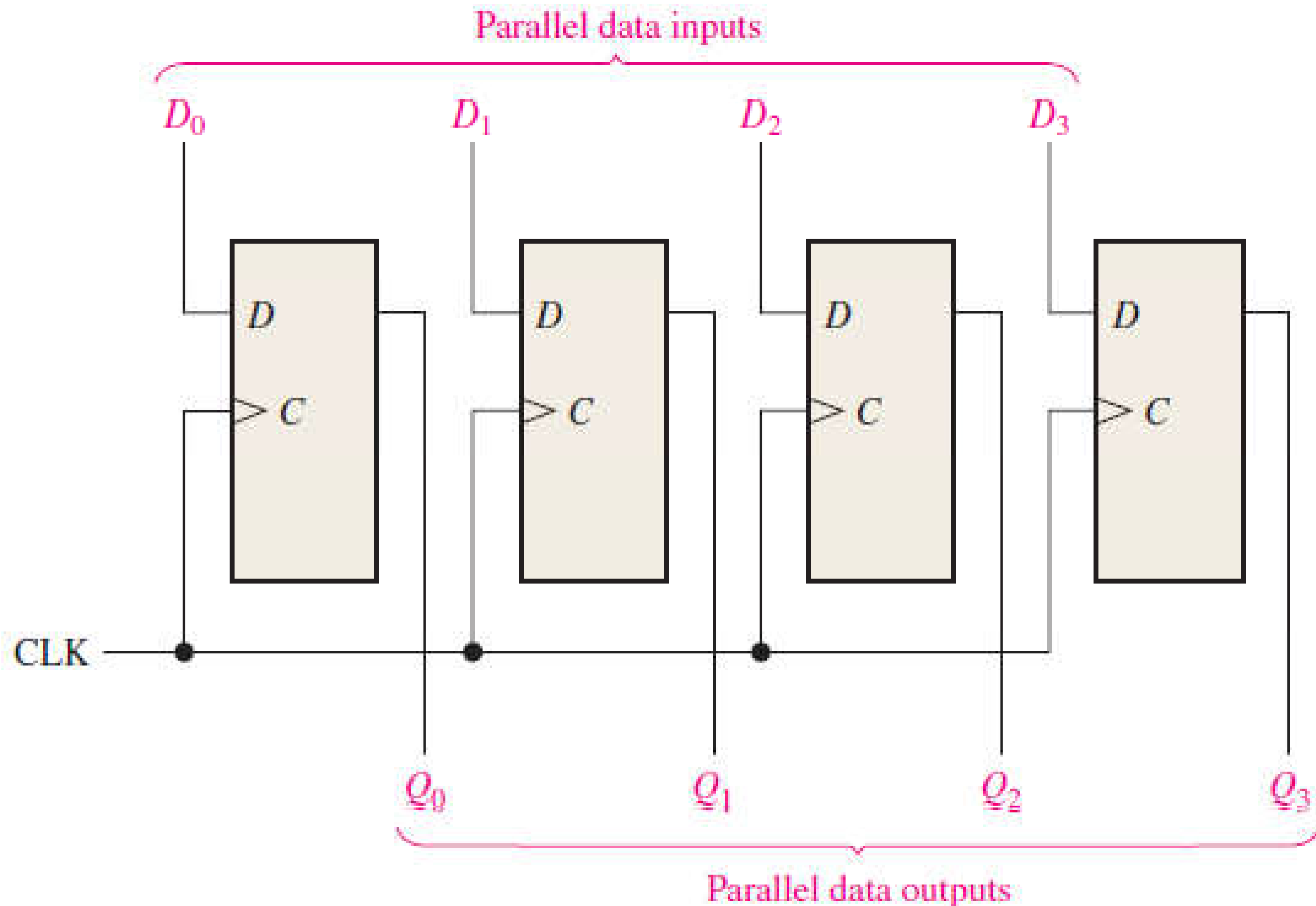

To B Continued...