




DELD – Tutorial 1



ECED SVNIT

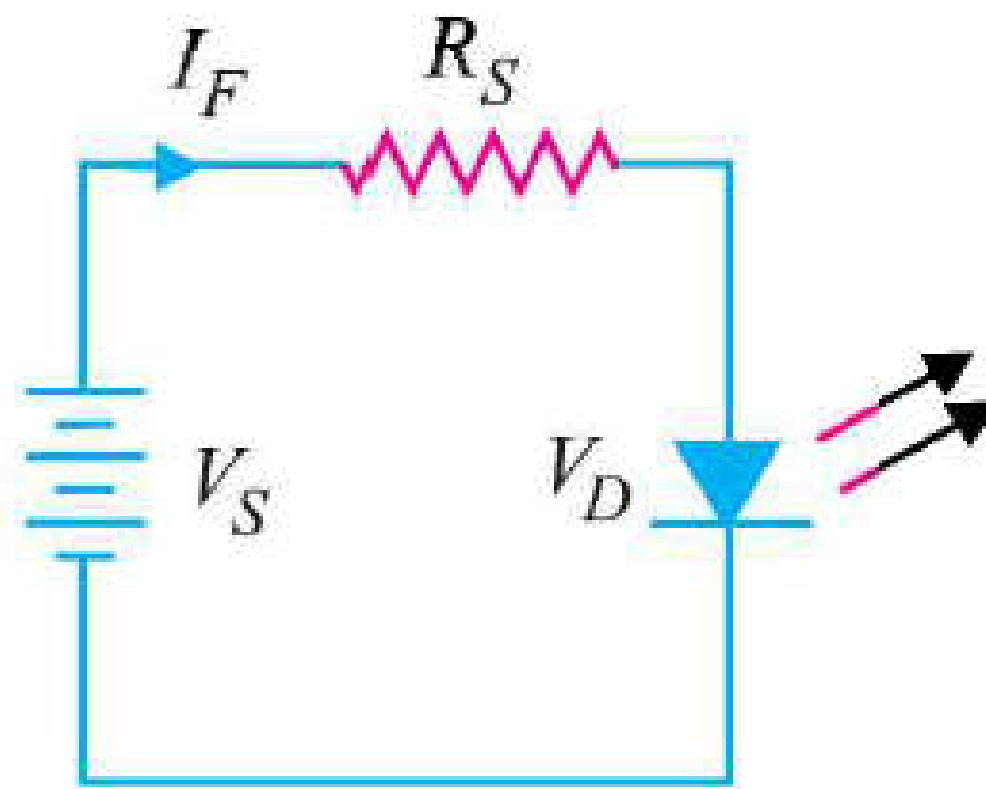Question

- What value of series resistor is required to limit the current through a LED to a 20 mA with a forward drop of 1.6 V when connected to a 10 V Supply?



Solution

$$V_S = 10 \text{ V}; \quad V_D = 1.6 \text{ V}; \quad I_F = 20 \text{ mA} = 20 \times 10^{-3} \text{ A}$$


$$R_S = \frac{V_S - V_D}{I_F}$$

$$R_S = \frac{10 - 1.6}{20 \times 10^{-3}} = \mathbf{420 \text{ } \Omega}$$




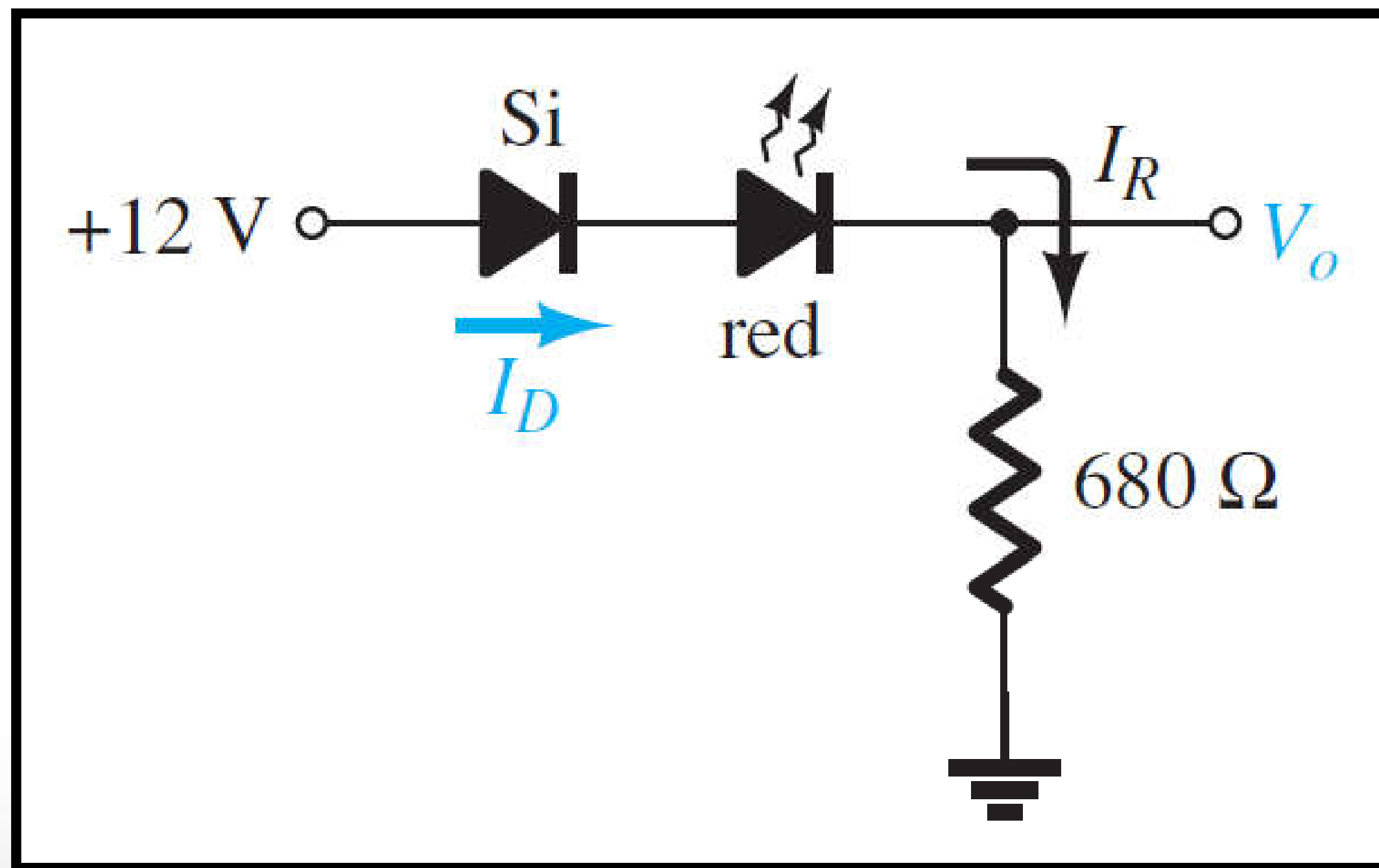Question

- Determine V_o and the series current/Diode current I_D . Assume the forward drop across LED to be 1.8 Volts.



Solution

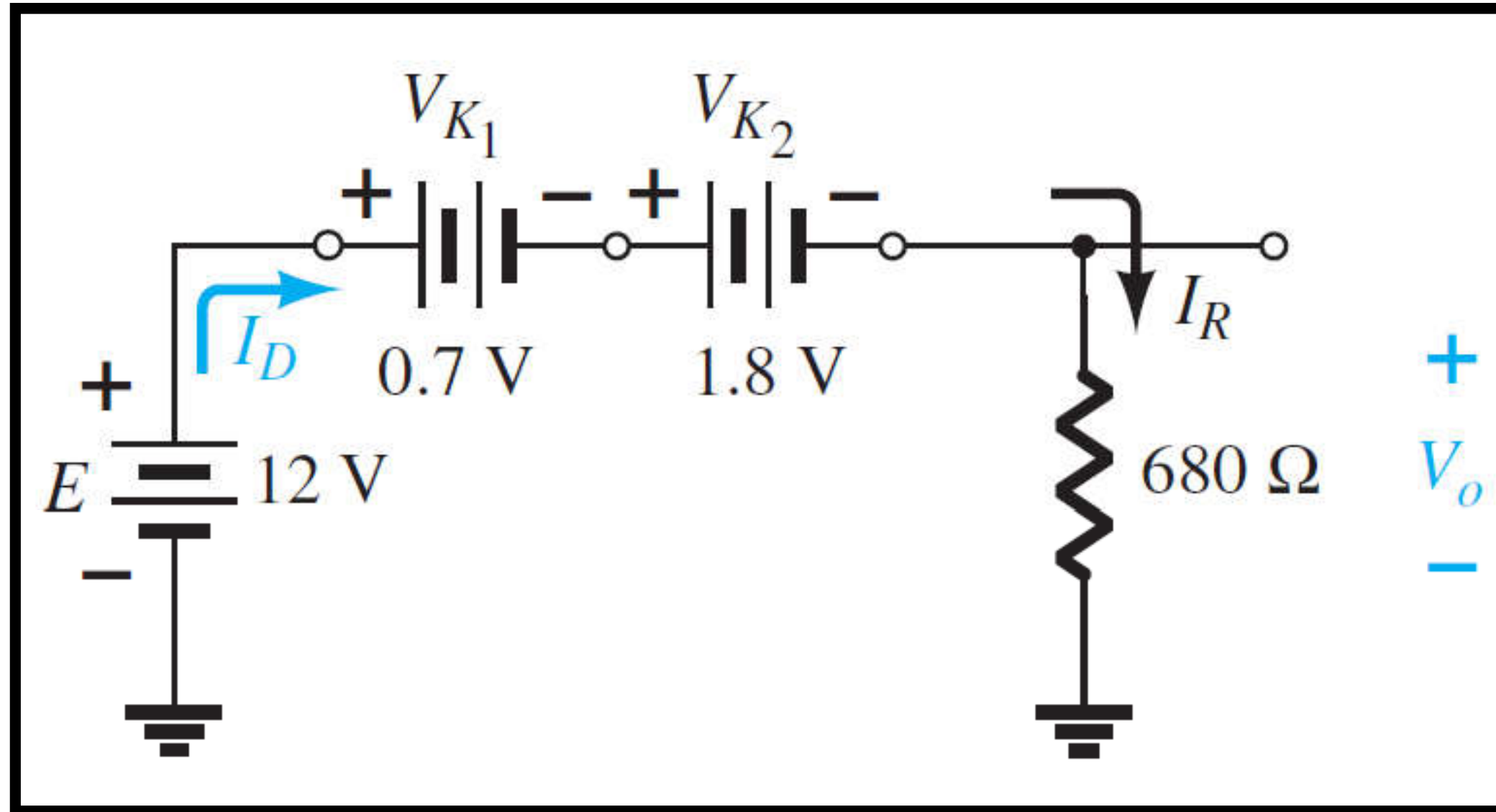


$$V_o = E - V_{K_1} - V_{K_2} = 12\text{ V} - 2.5\text{ V} = \mathbf{9.5\text{ V}}$$

$$I_D = I_R = \frac{V_R}{R} = \frac{V_o}{R} = \frac{9.5\text{ V}}{680\ \Omega} = \mathbf{13.97\text{ mA}}$$




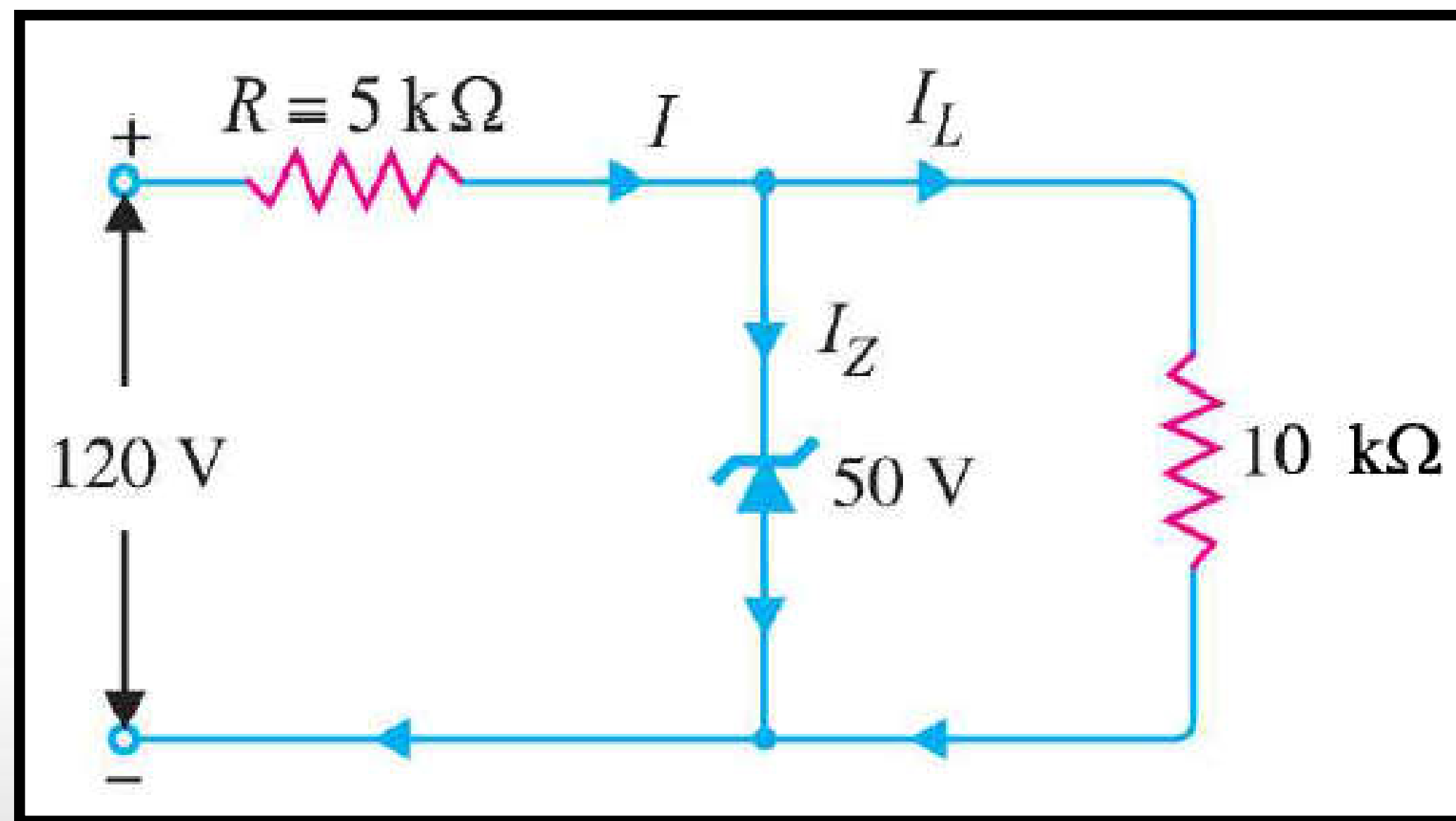Question

- Find 1) Output Voltage 2) Voltage drop across series resistance 3) The current through Zener Diode



Solution

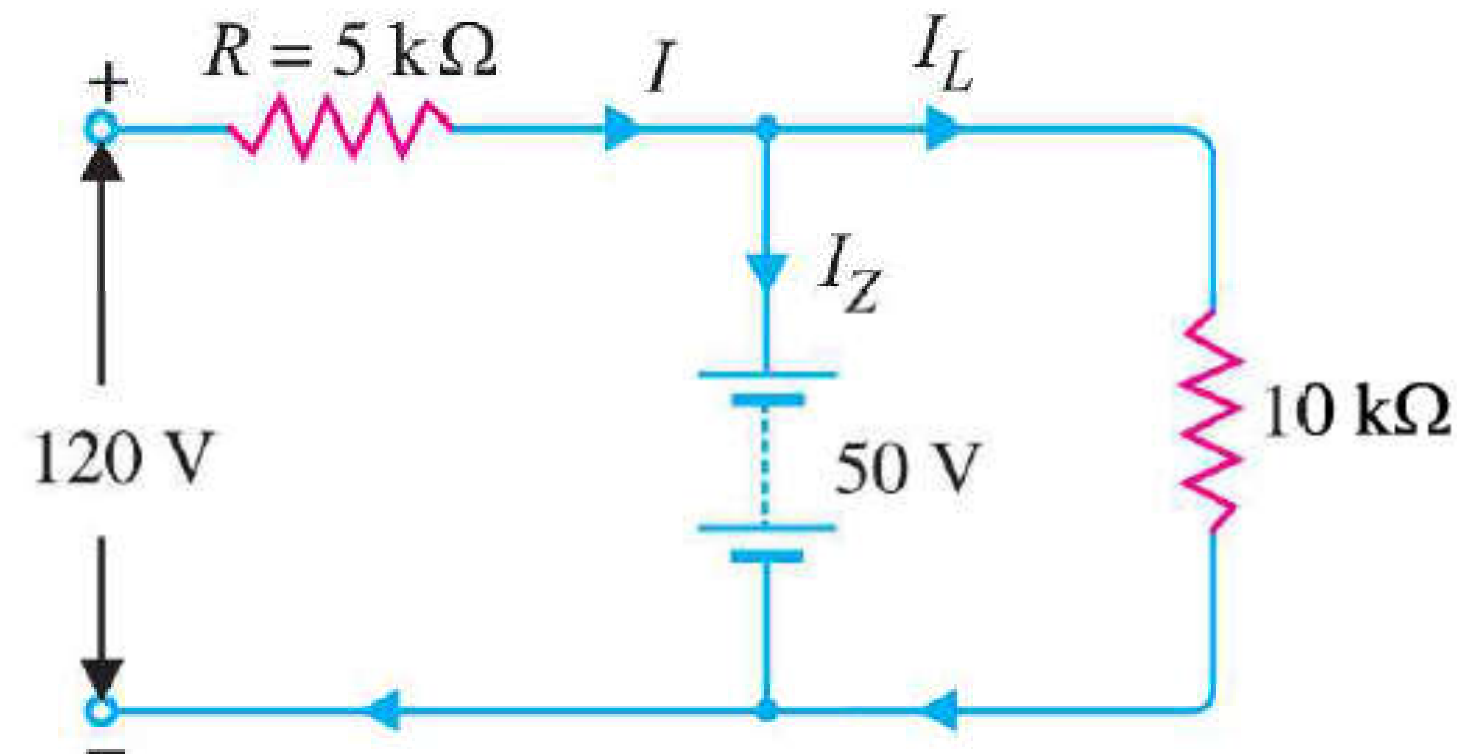

$$V = \frac{R_L E_i}{R + R_L} = \frac{10 \times 120}{5 + 10} = 80 \text{ V} \quad \text{Output voltage} = V_Z = \mathbf{50 \text{ V}}$$

$$\text{Voltage drop across } R = \text{Input voltage} - V_Z = 120 - 50 = \mathbf{70 \text{ V}}$$

$$\text{Load current, } I_L = V_Z / R_L = 50 \text{ V} / 10 \text{ k}\Omega = 5 \text{ mA}$$


$$\text{Current through } R, I = \frac{70 \text{ V}}{5 \text{ k}\Omega} = 14 \text{ mA}$$

Applying Kirchhoff's first law, $I = I_L + I_Z$


$$\therefore \quad \text{Zener current, } I_Z = I - I_L = 14 - 5 = \mathbf{9 \text{ mA}}$$



Concept of Rectification

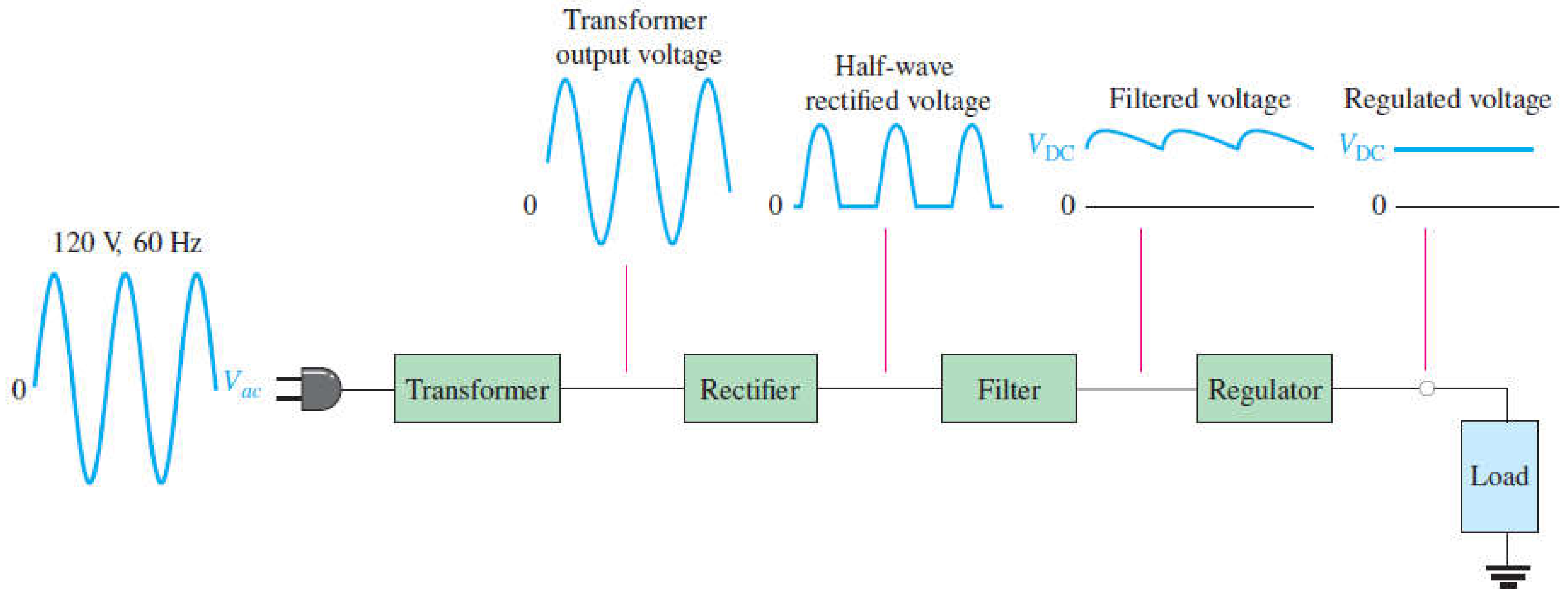

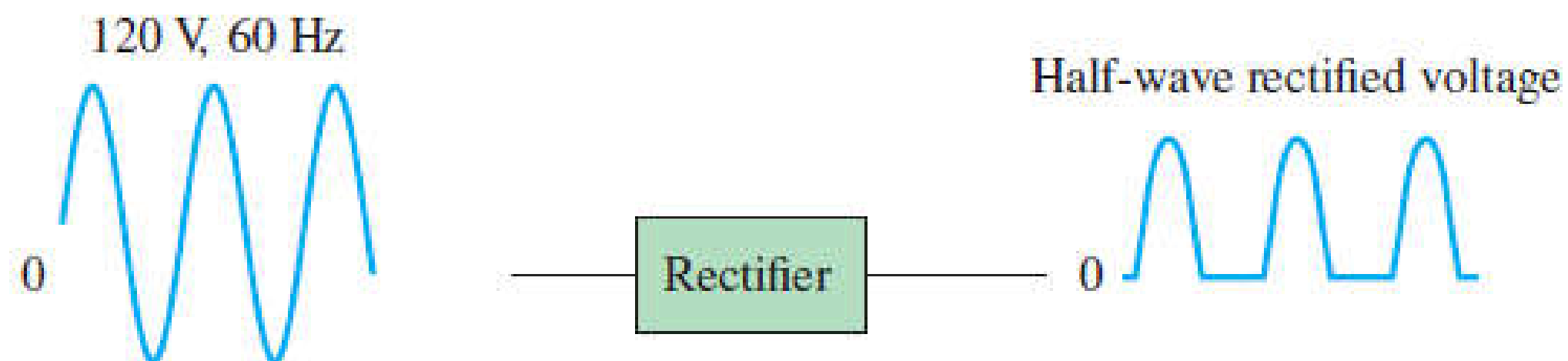
(a) Complete power supply with transformer, rectifier, filter, and regulator




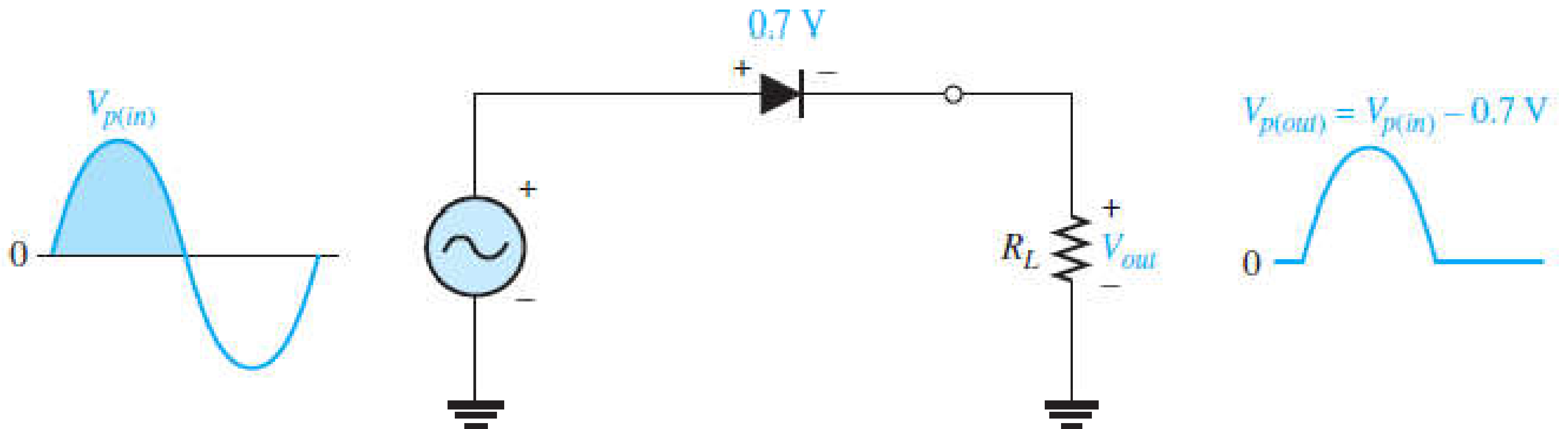
(b) Half-wave rectifier

Effect of Barrier Potential on HWR


$$V_{p(out)} = V_{p(in)} - 0.7 \text{ V}$$



Question

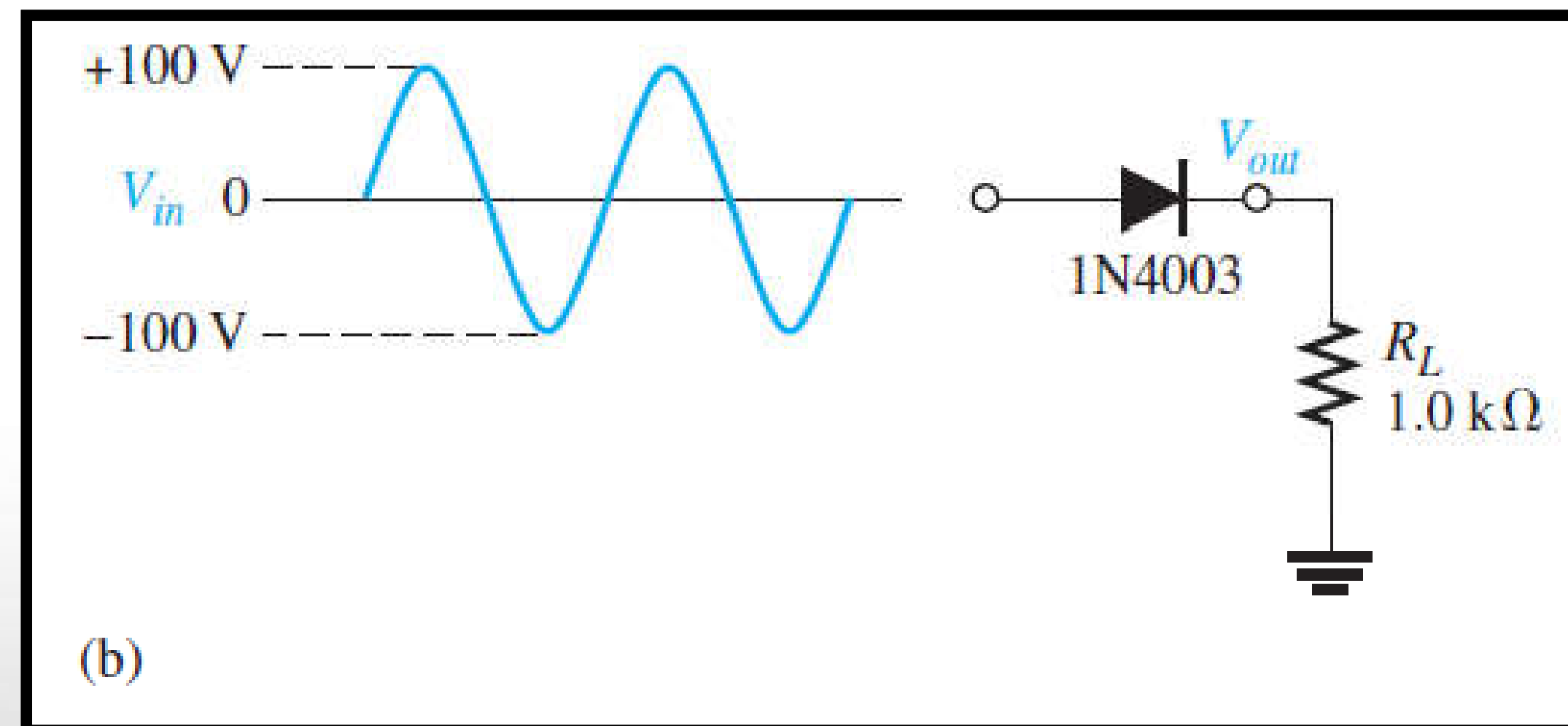
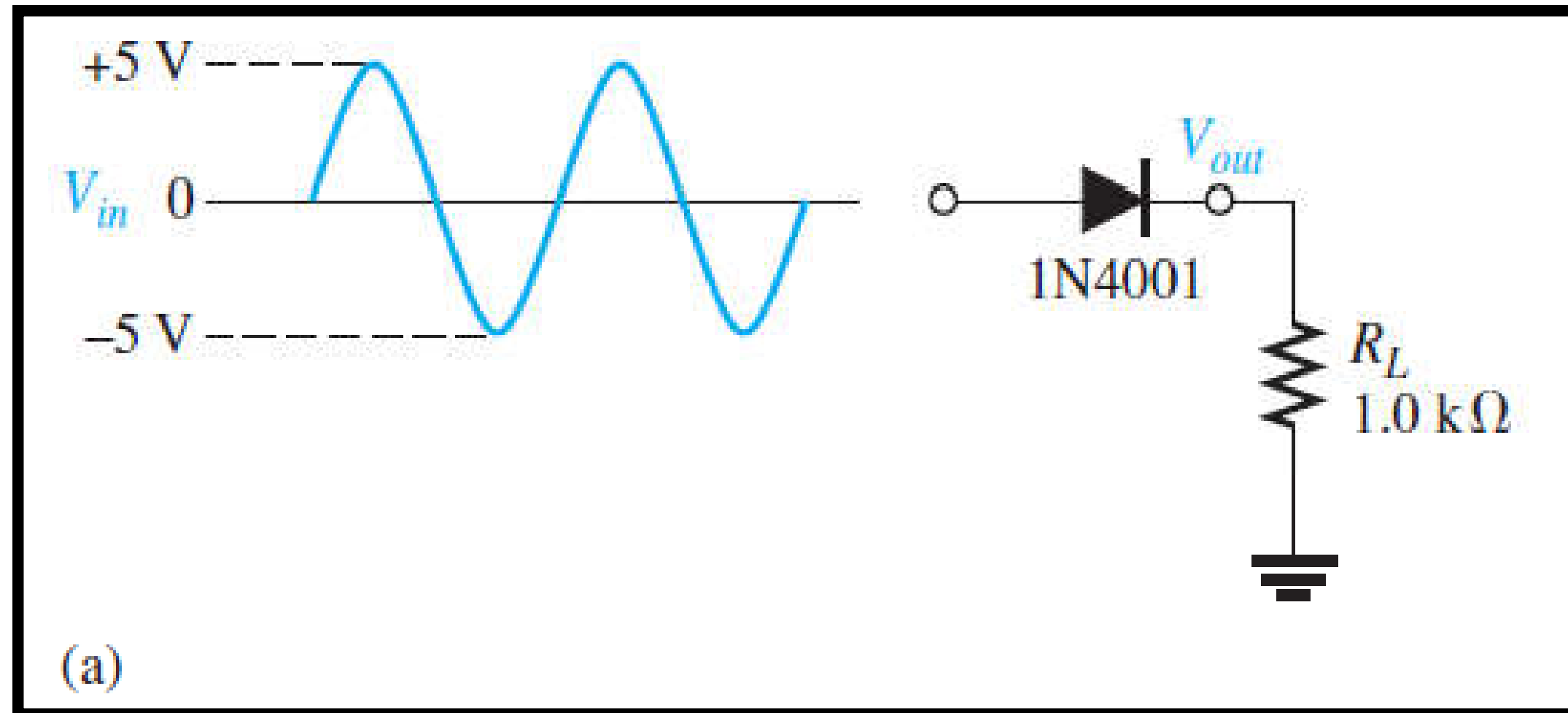


Solutions

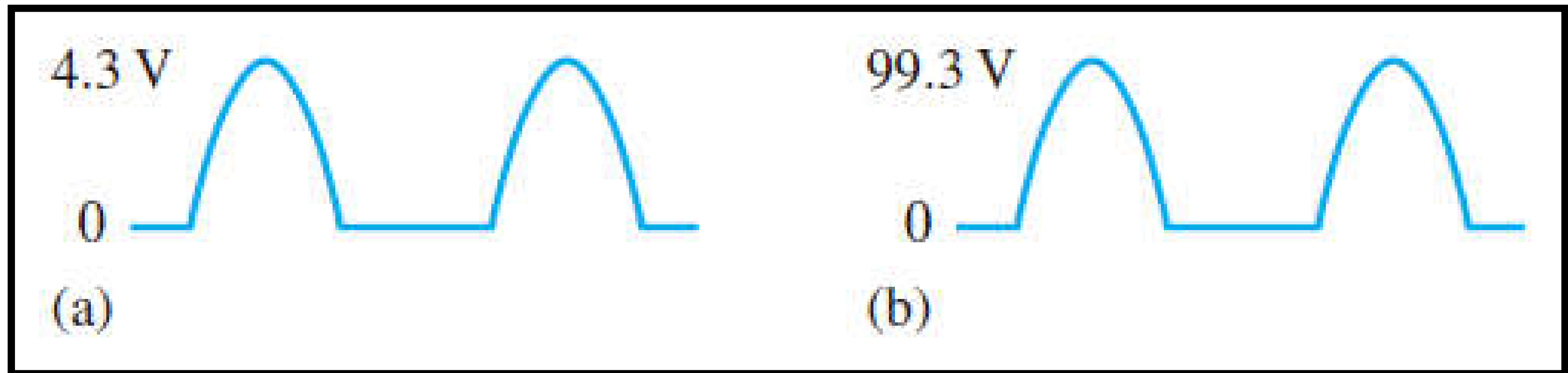

Clamper Circuits

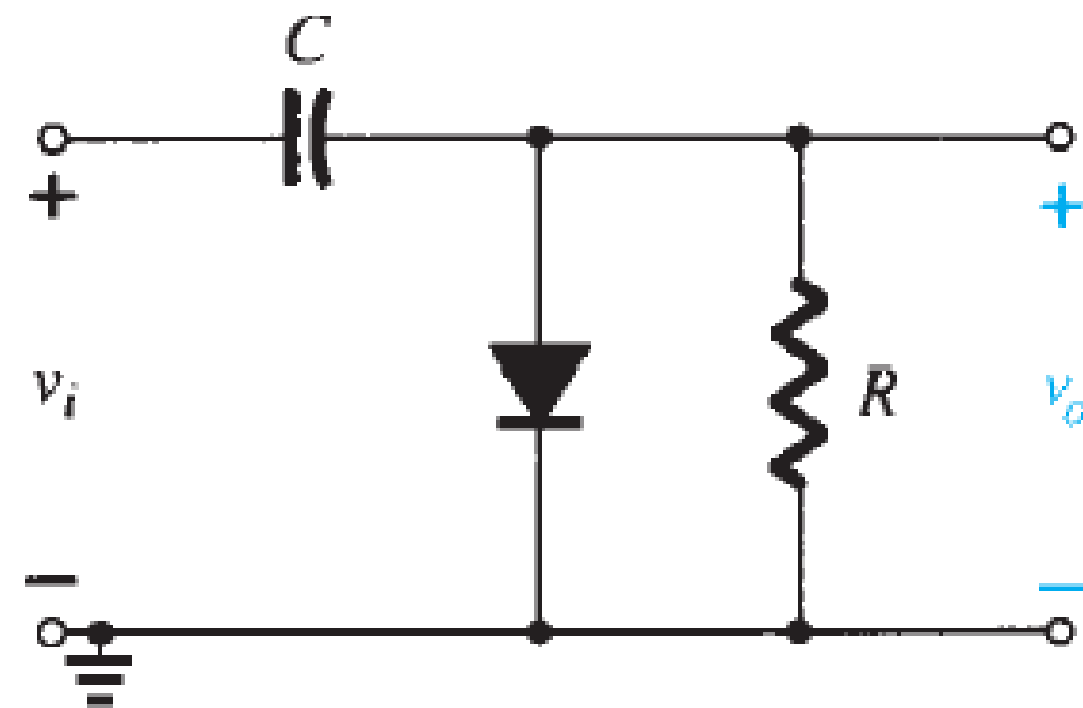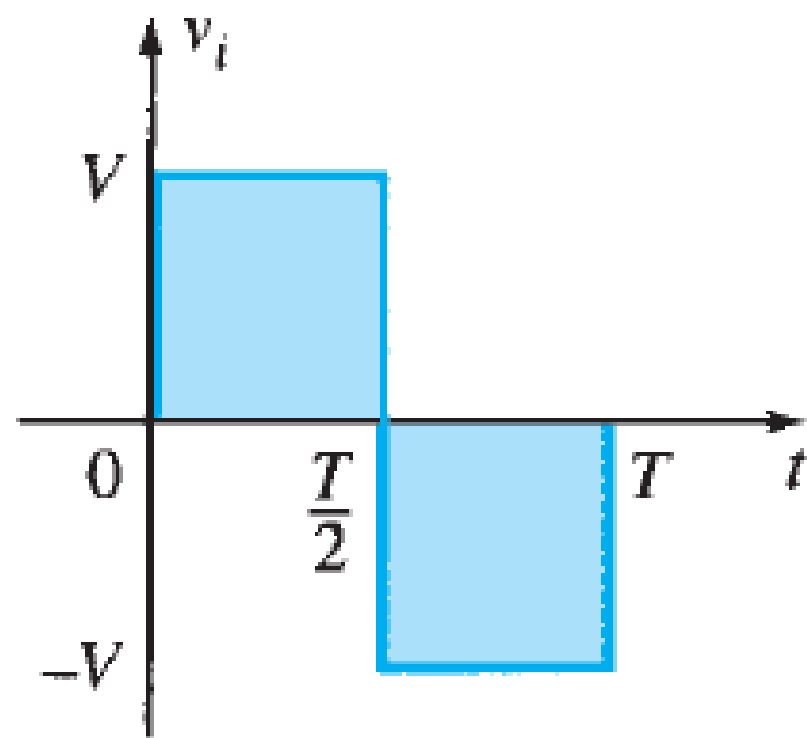- A clamper is a network constructed of a diode, a resistor, and a capacitor that shifts a waveform to a different dc level without changing the appearance of the applied signal.



Steps

Step 1: Start the analysis by examining the response of the portion of the input signal that will forward bias the diode.

Step 2: During the period that the diode is in the “on” state, assume that the capacitor will charge up instantaneously to a voltage level determined by the surrounding network.

Step 3: Assume that during the period when the diode is in the “off” state the capacitor holds on to its established voltage level.




Step 4: Throughout the analysis, maintain a continual awareness of the location and defined polarity for v_o to ensure that the proper levels are obtained.

Step 5: Check that the total swing of the output matches that of the input.



This is a property that applies for all clamping networks, giving an excellent check on the results obtained.






Clamper - Working

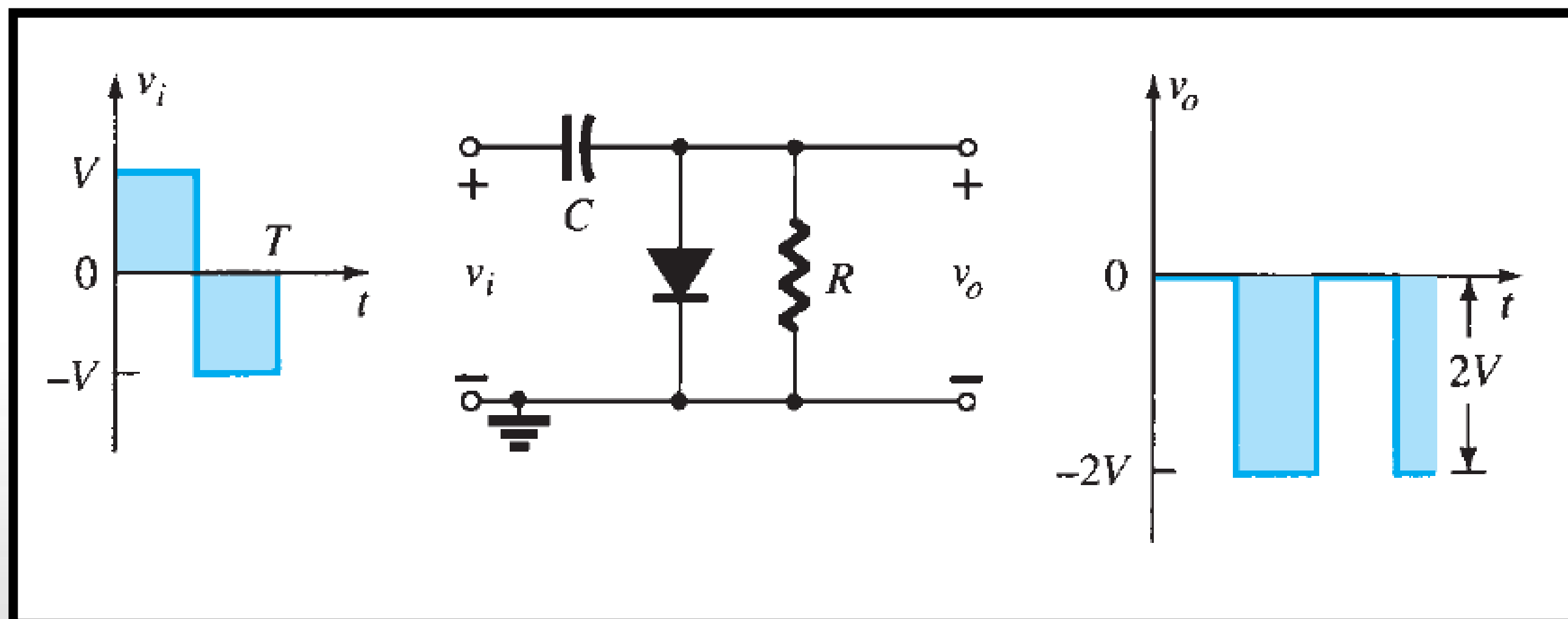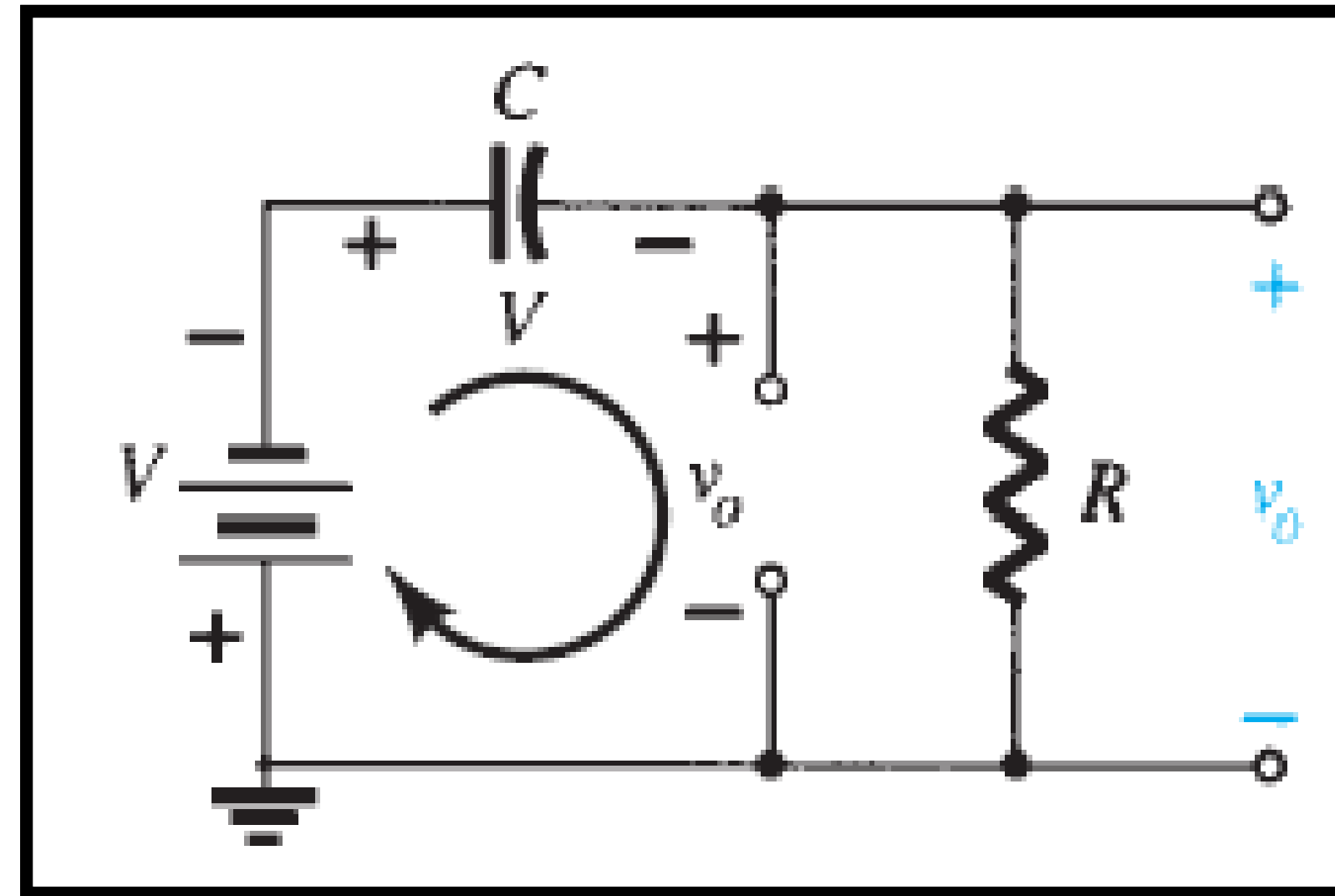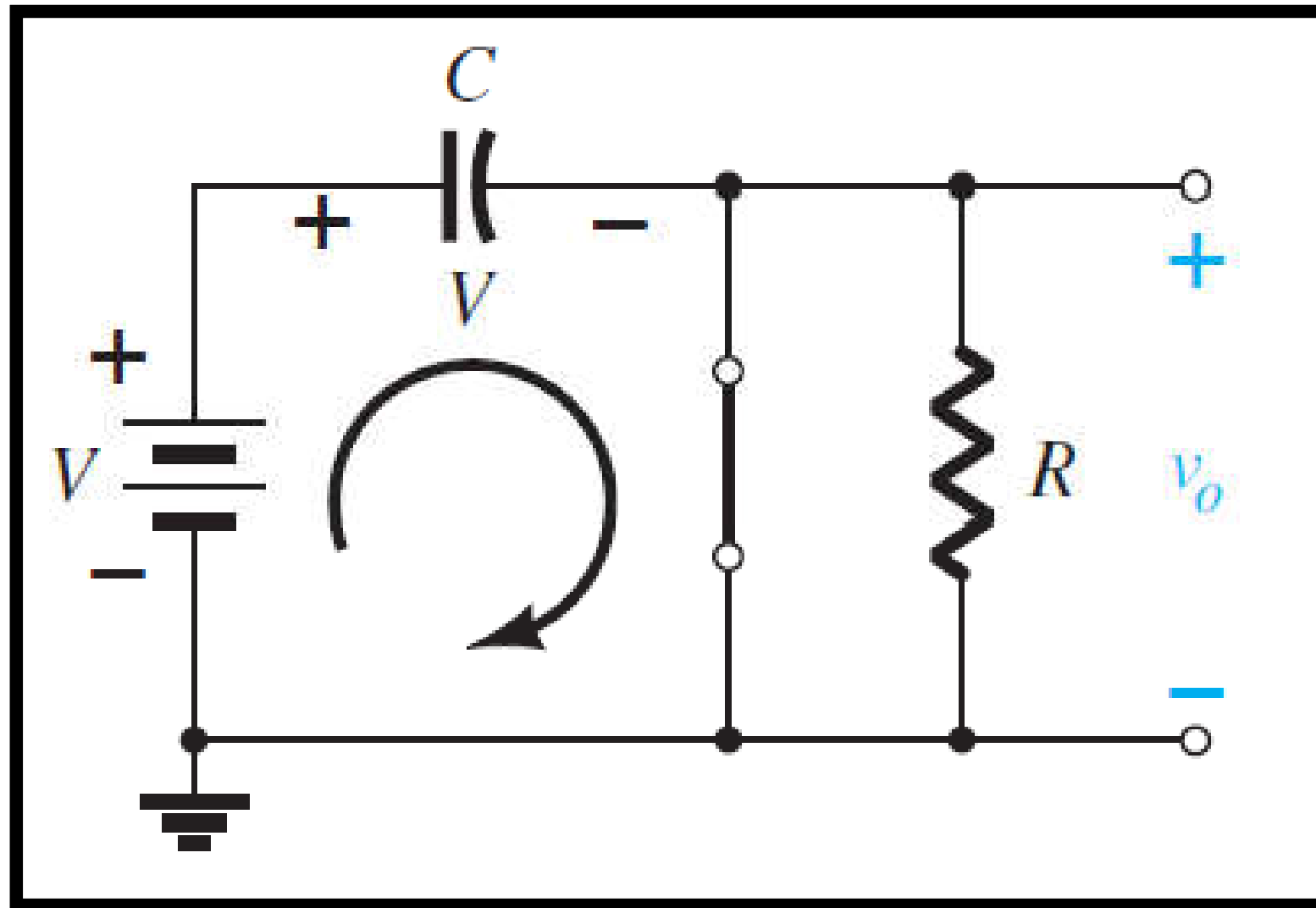


Clamper - Working

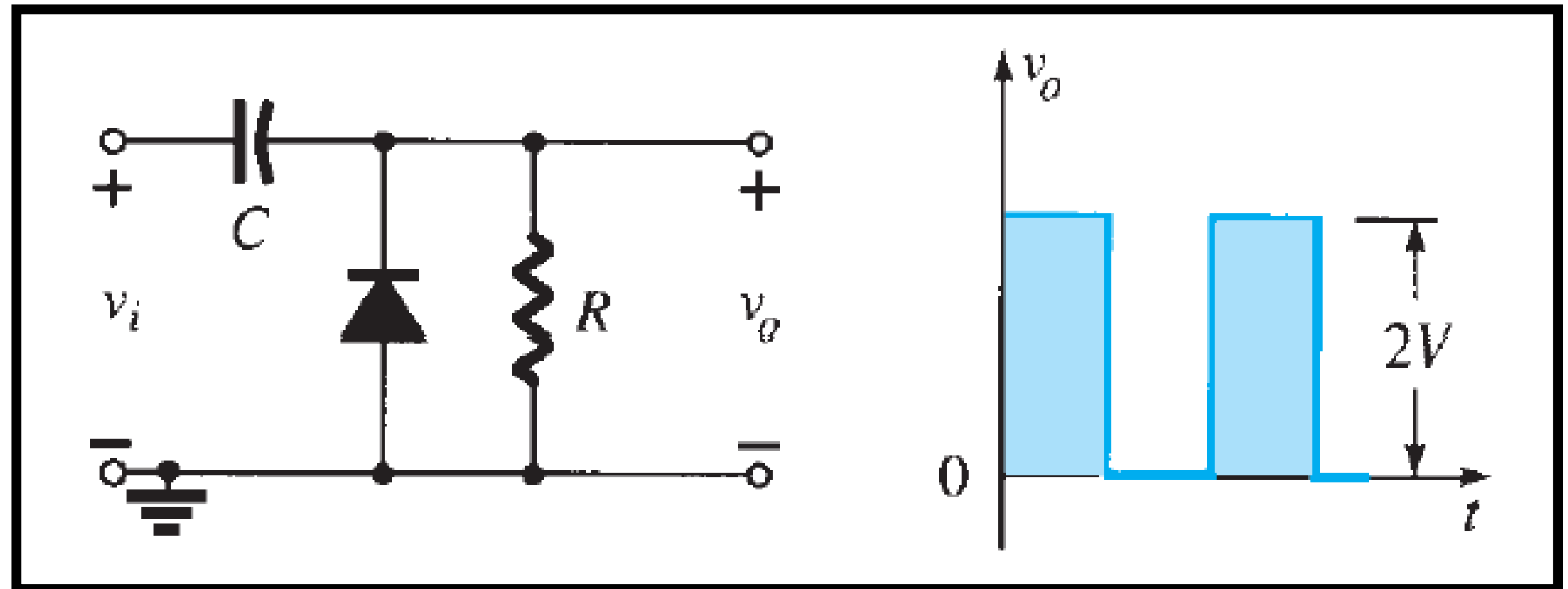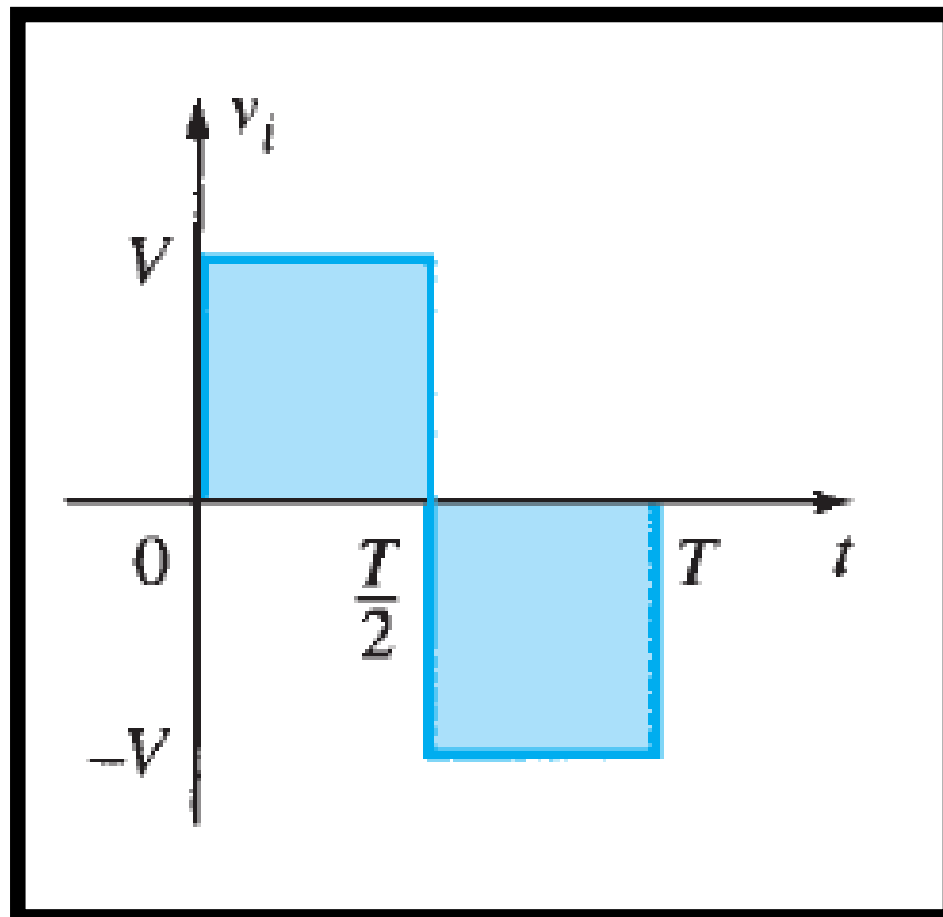



Concept Check

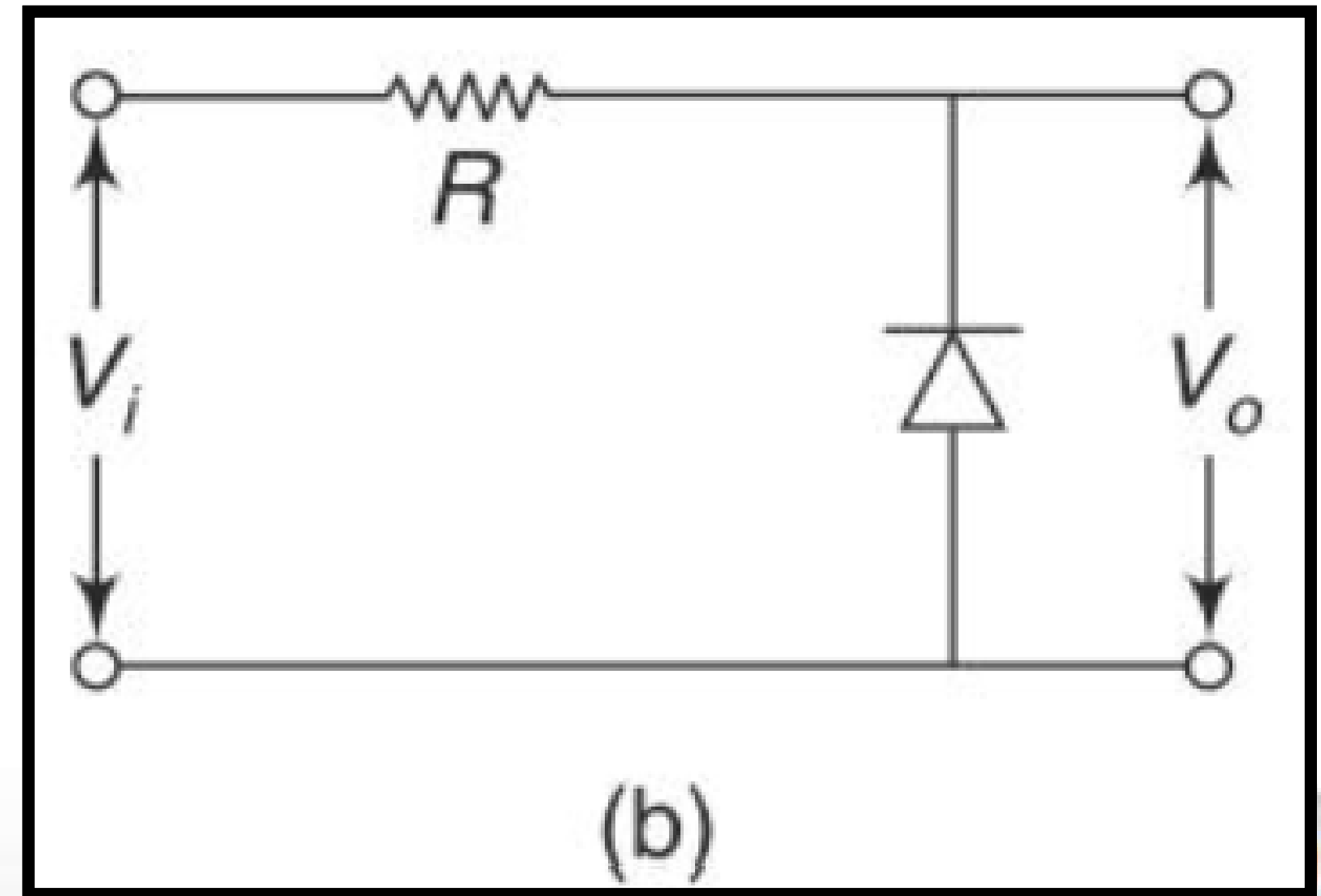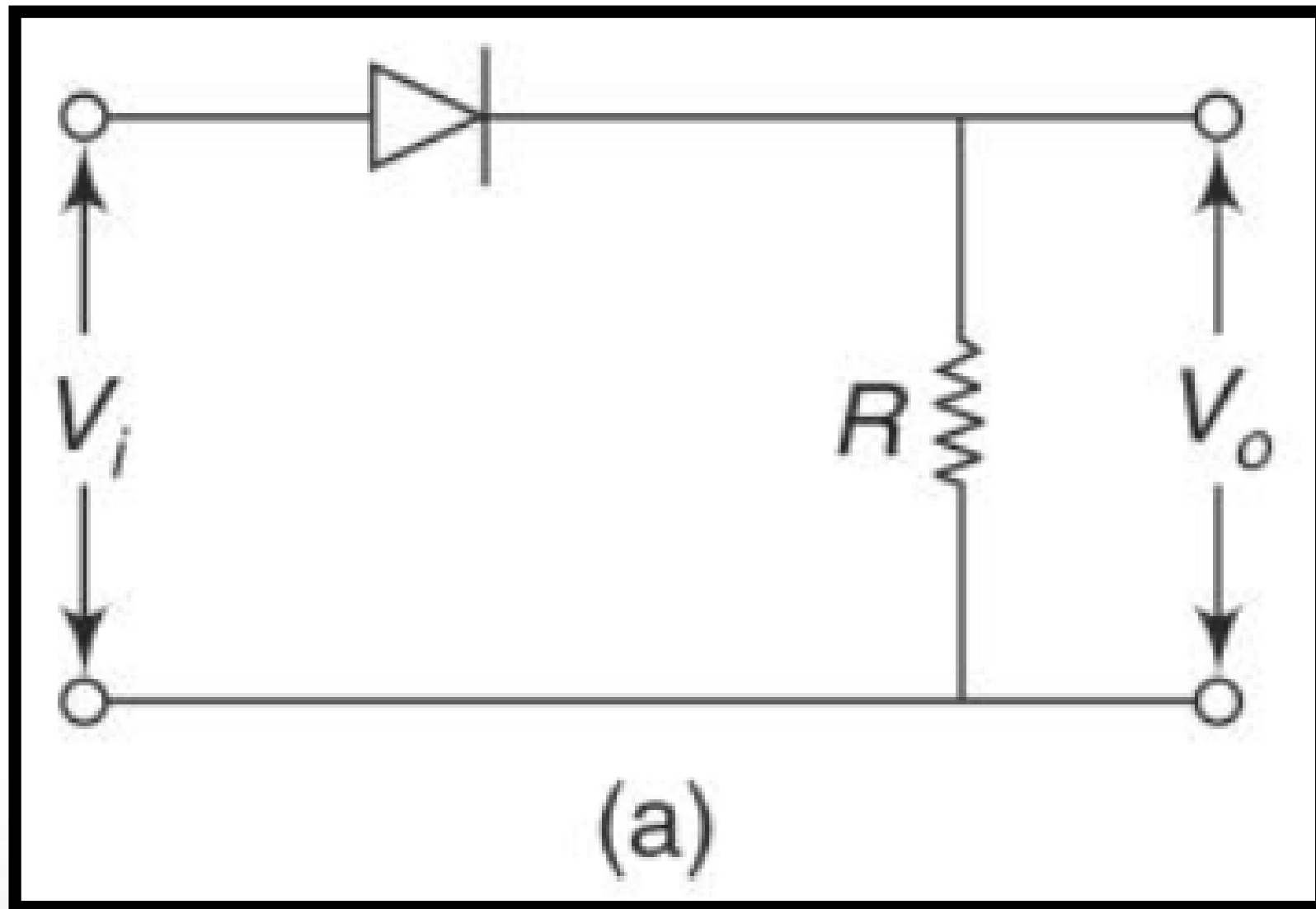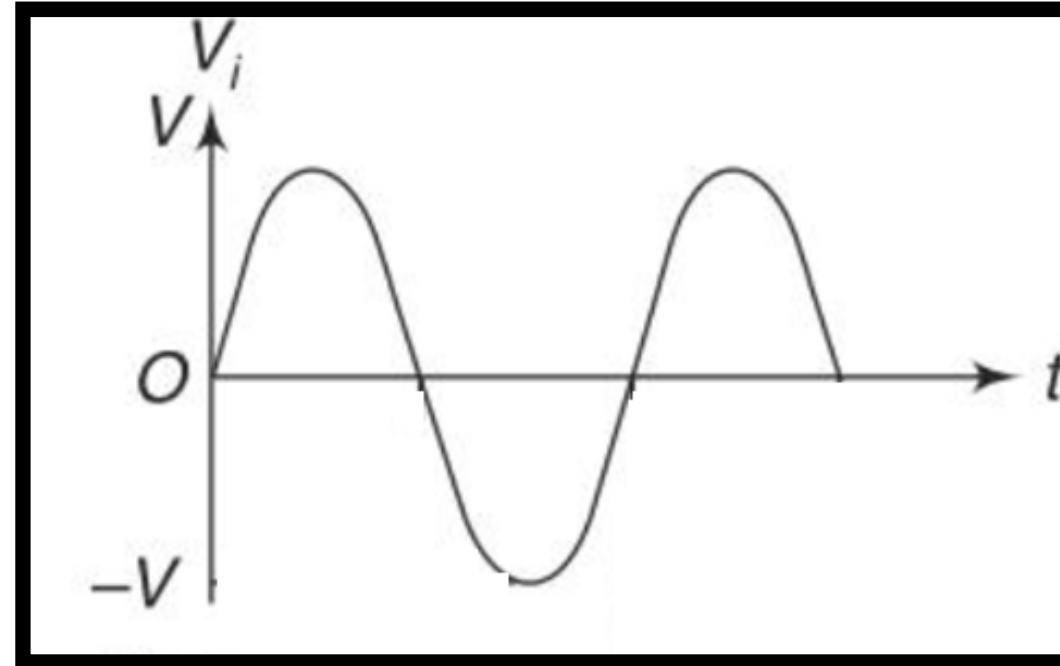



Solution

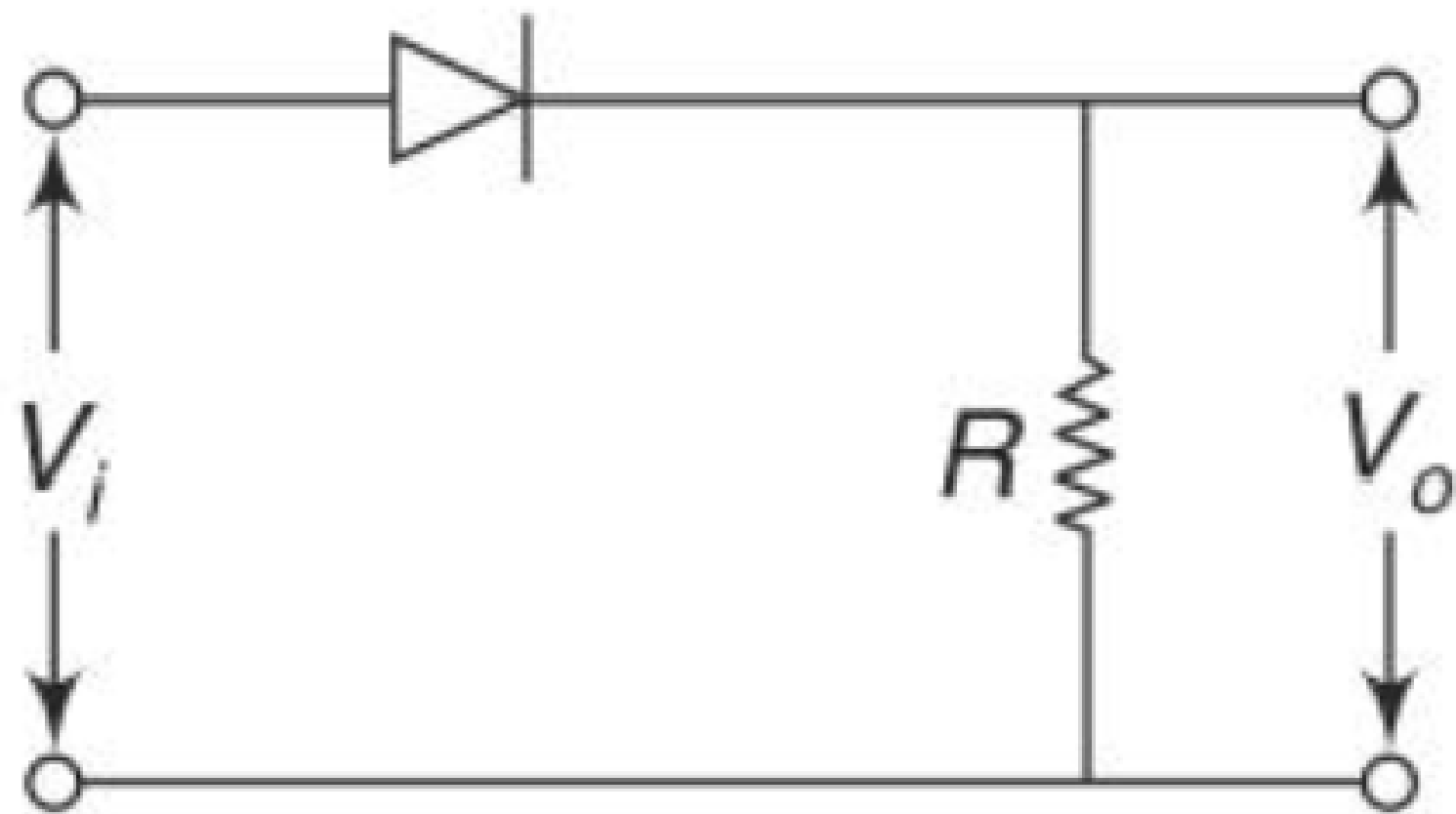


(a)

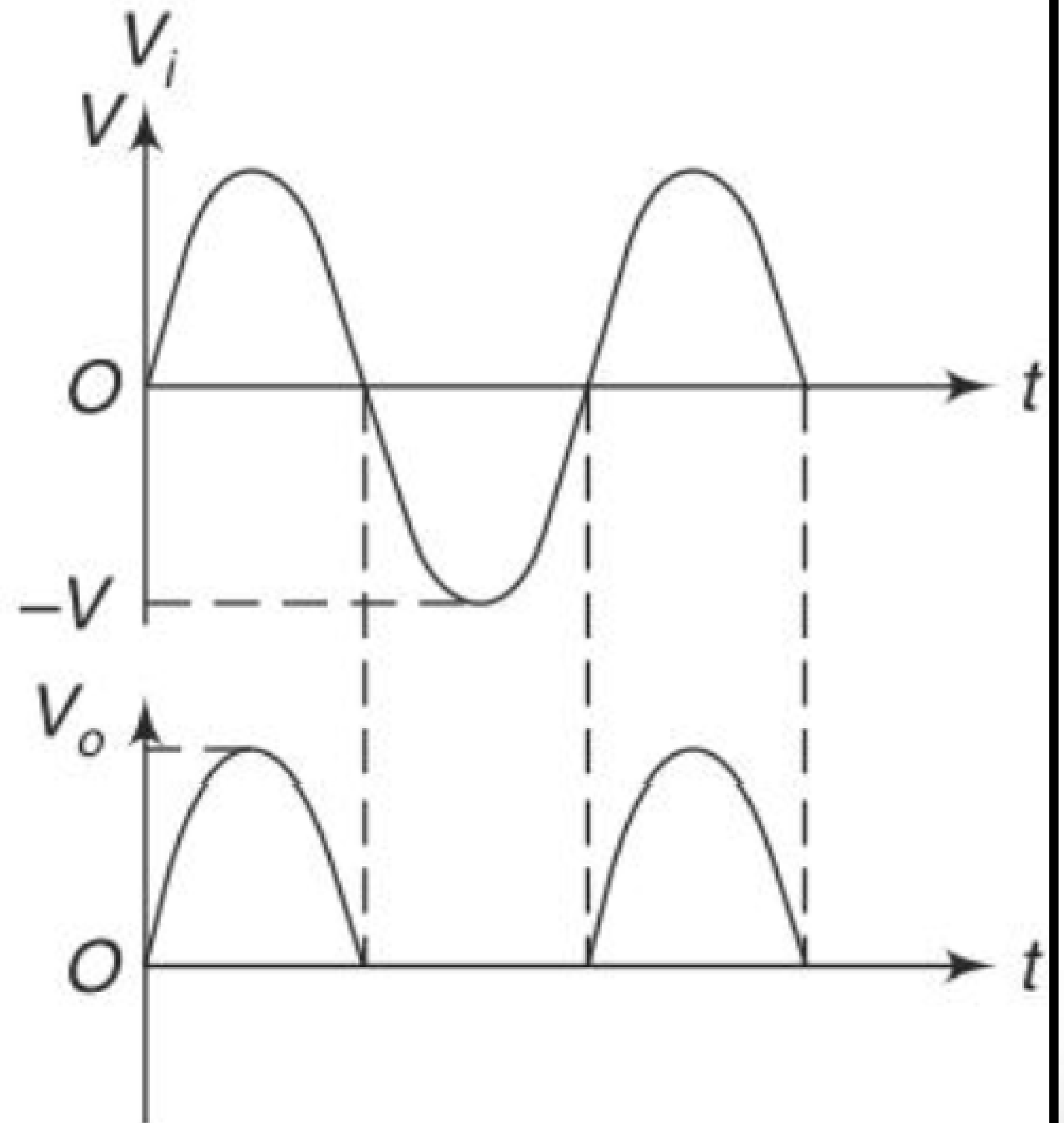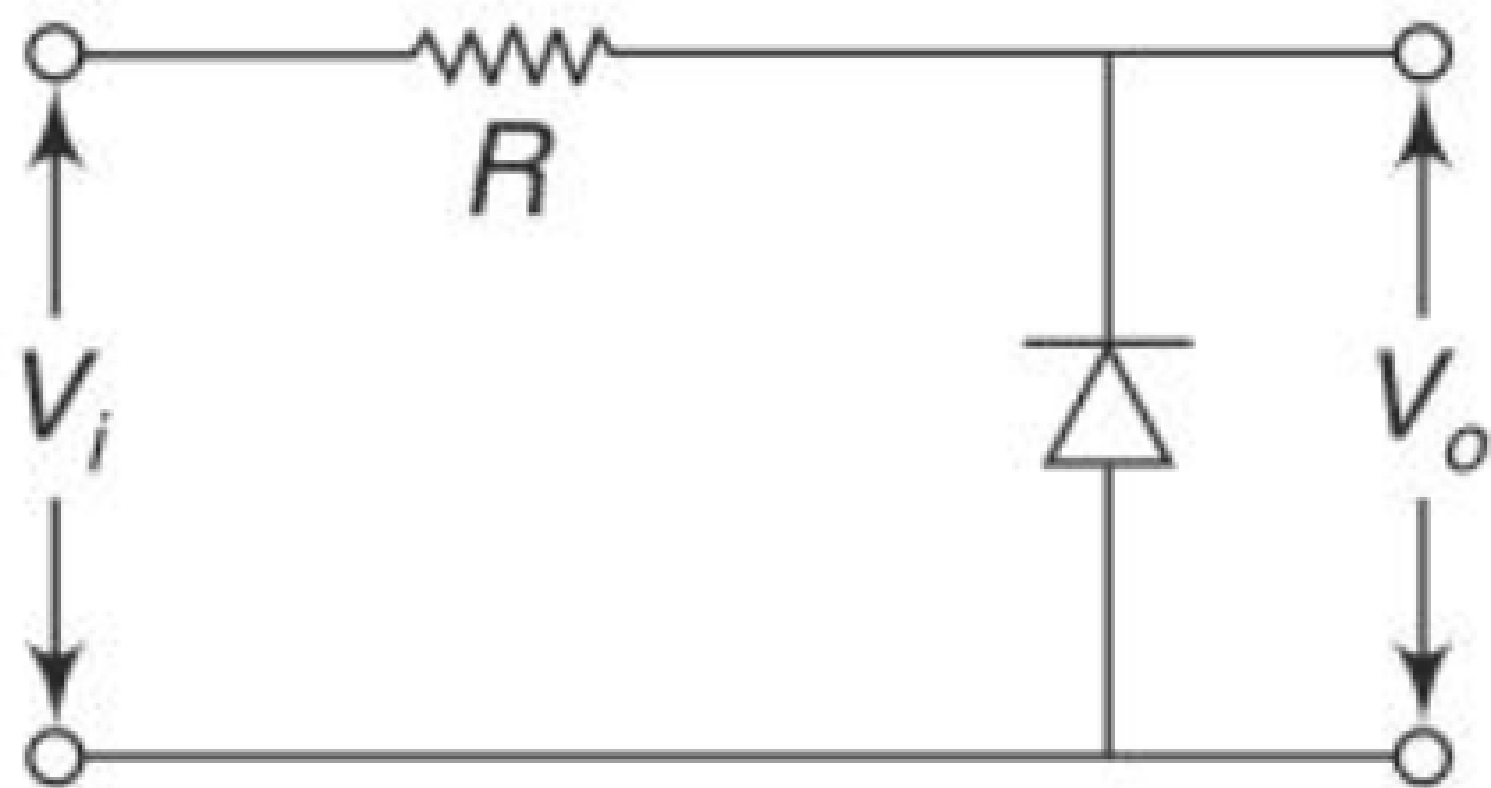



Concept Check

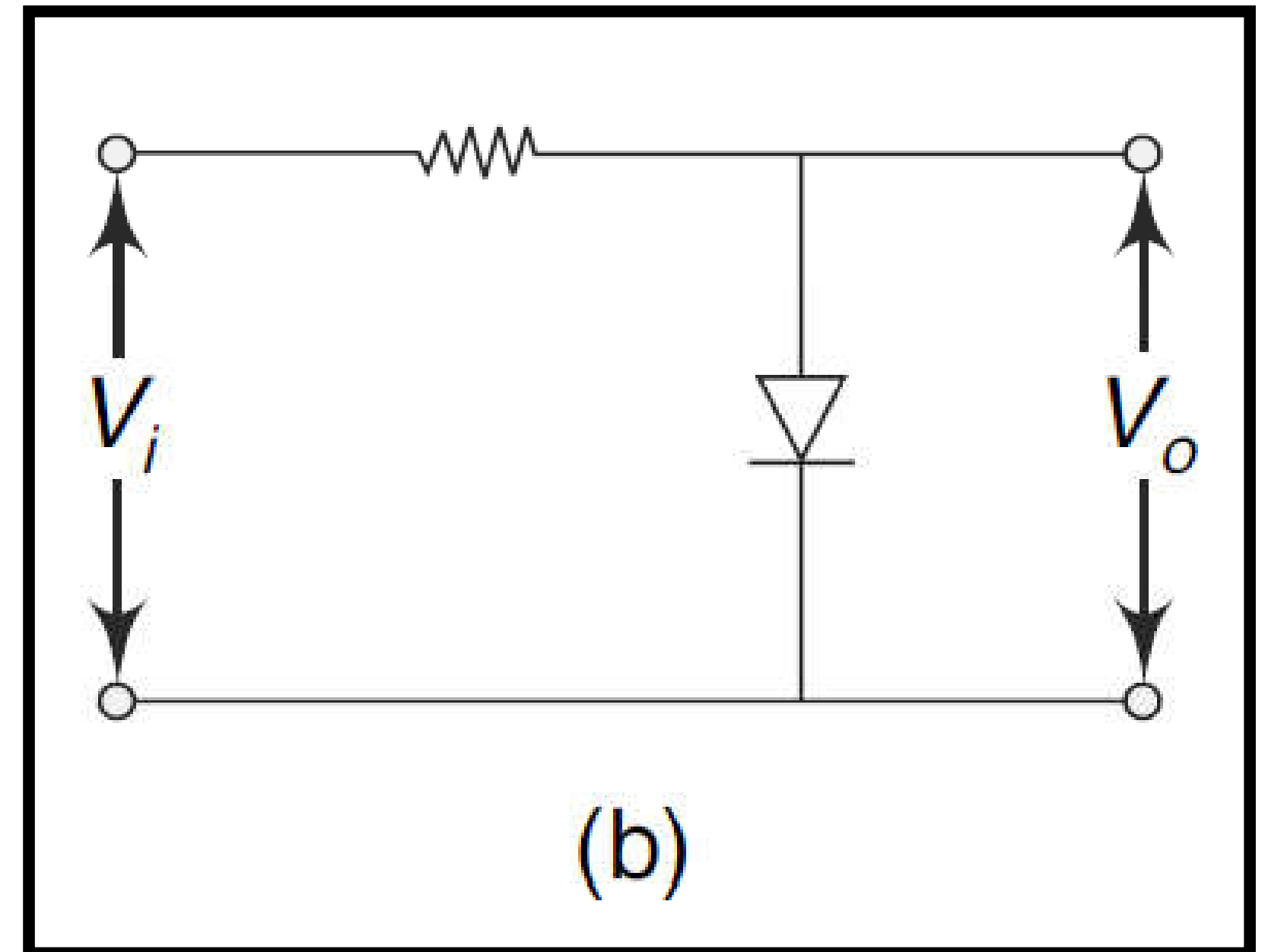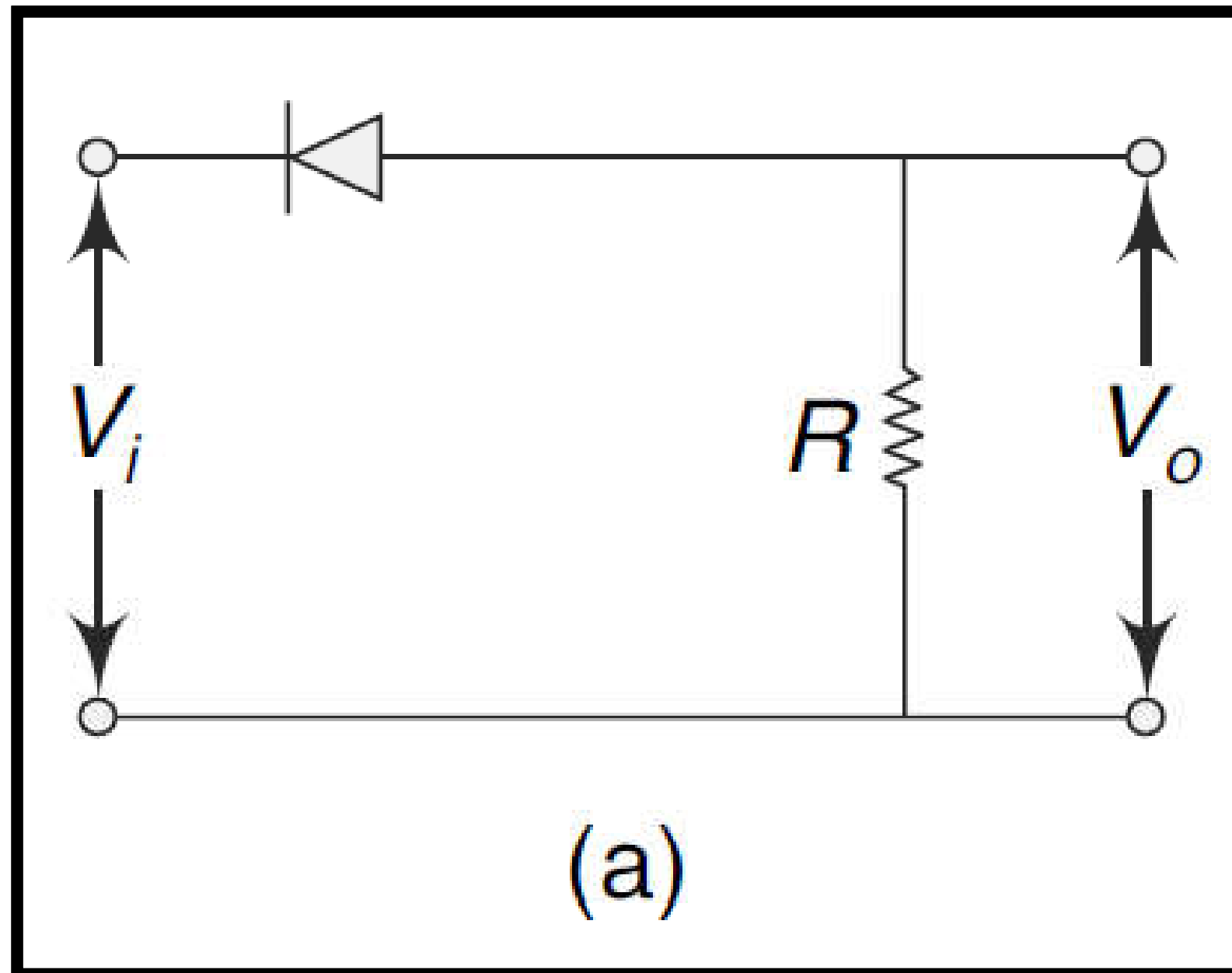



Solution

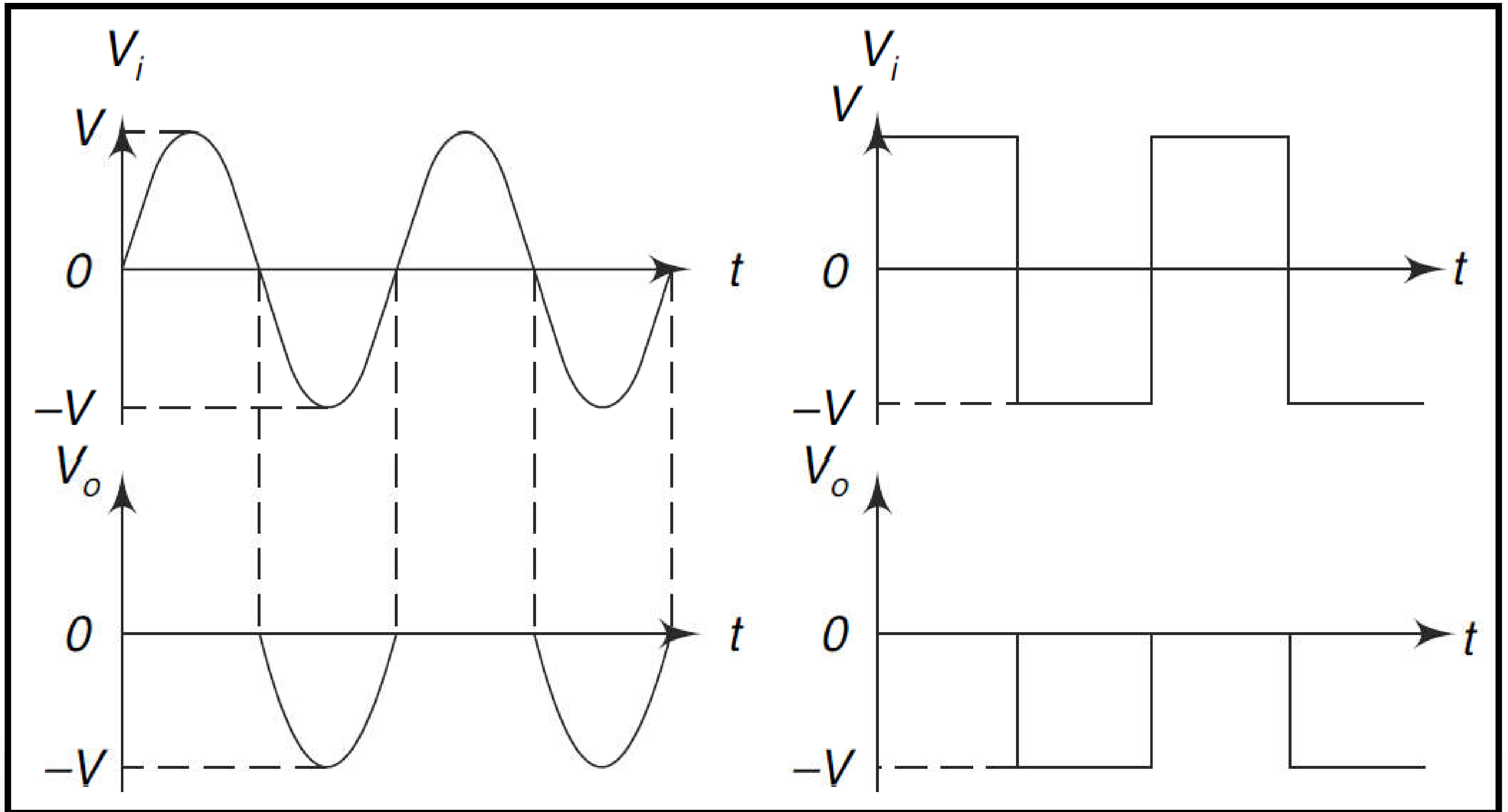



Question

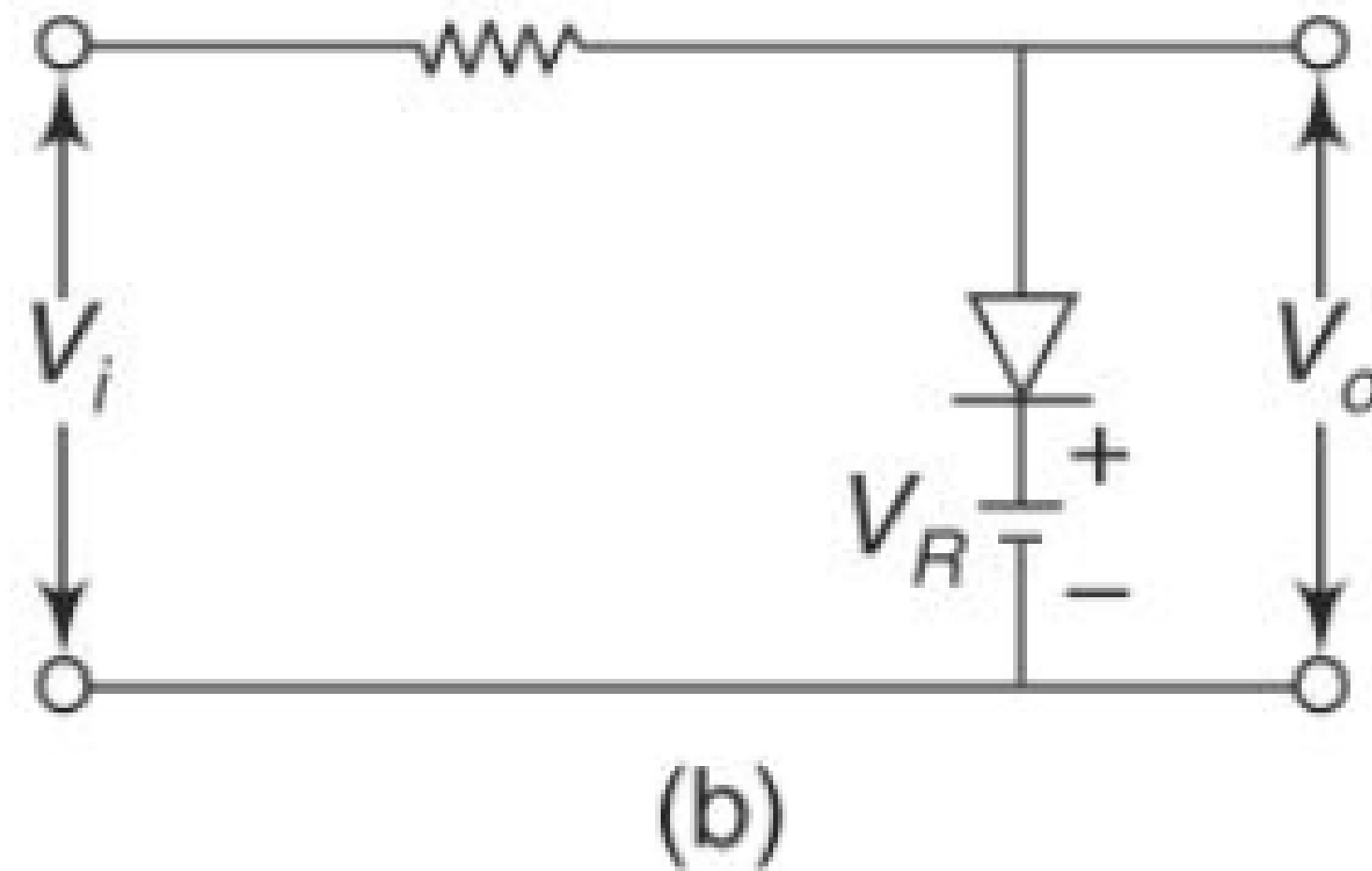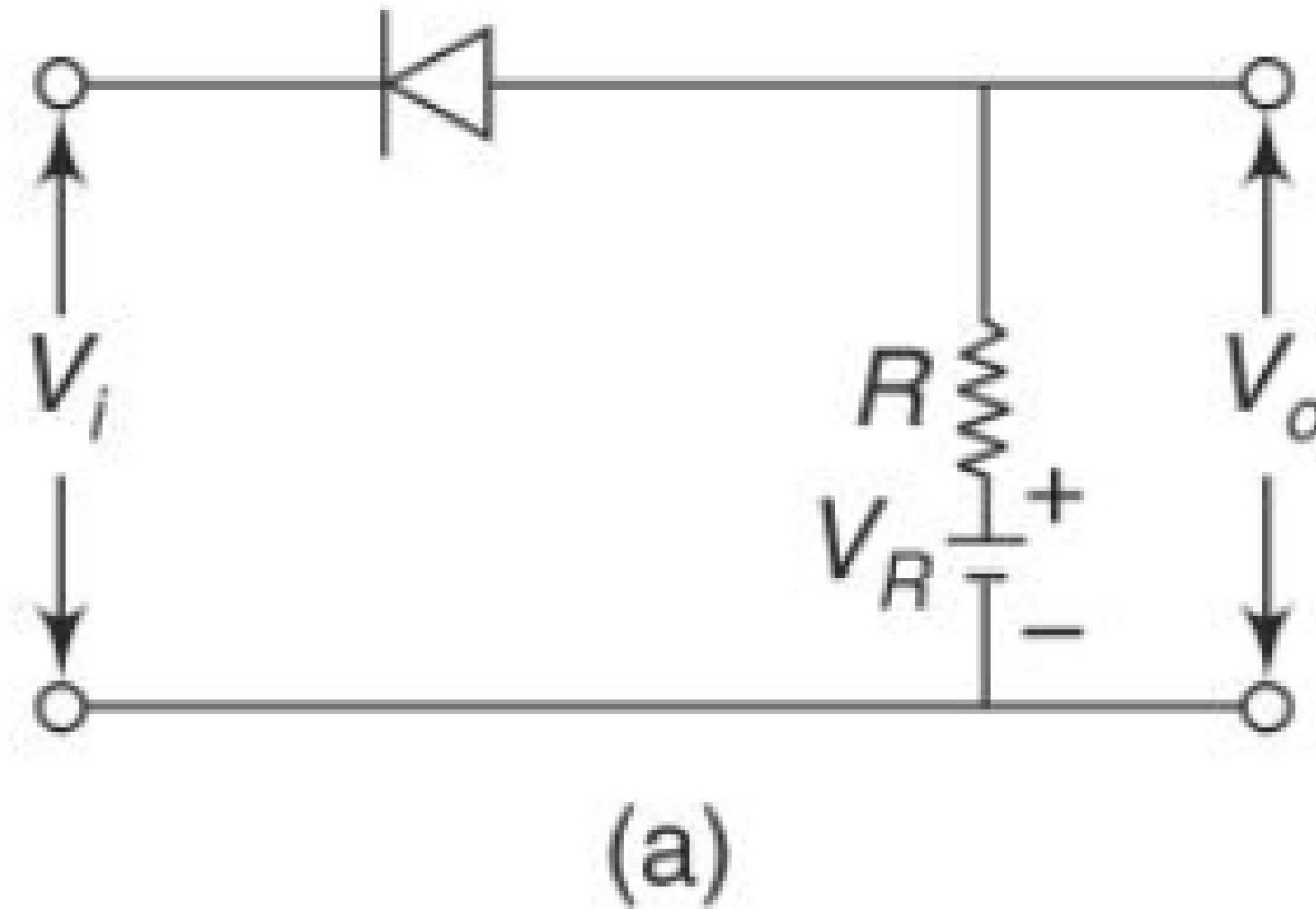




Solution

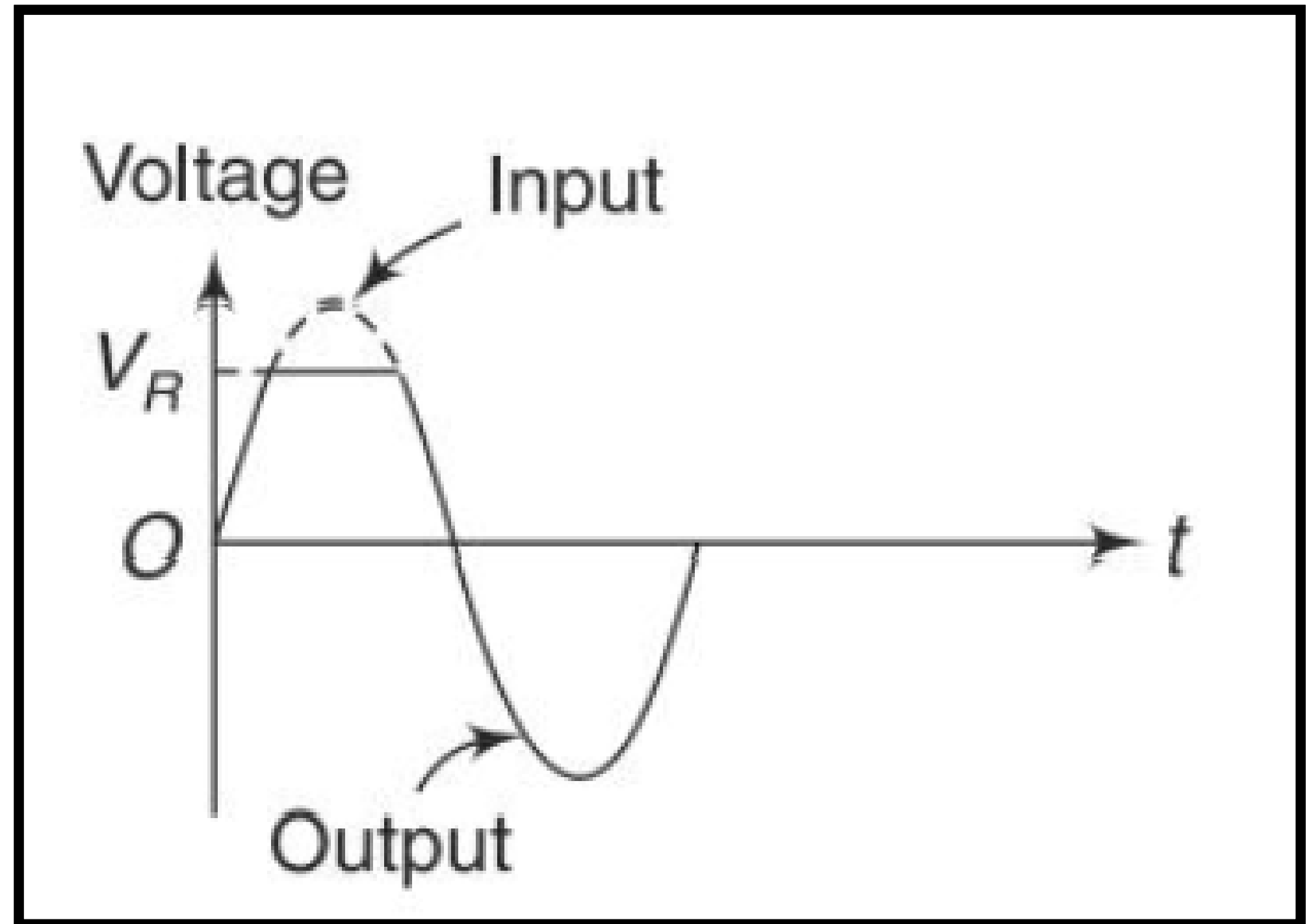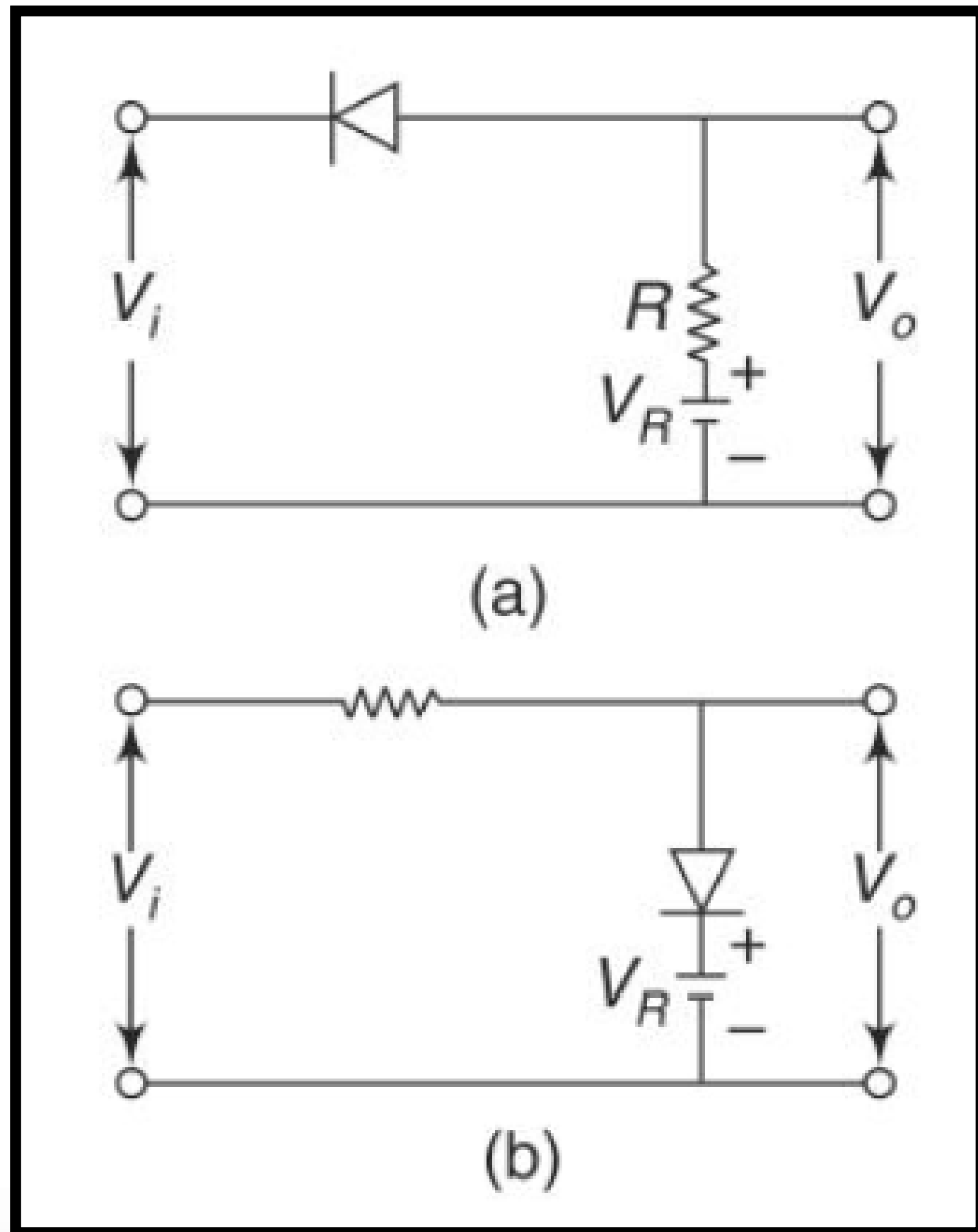



Question

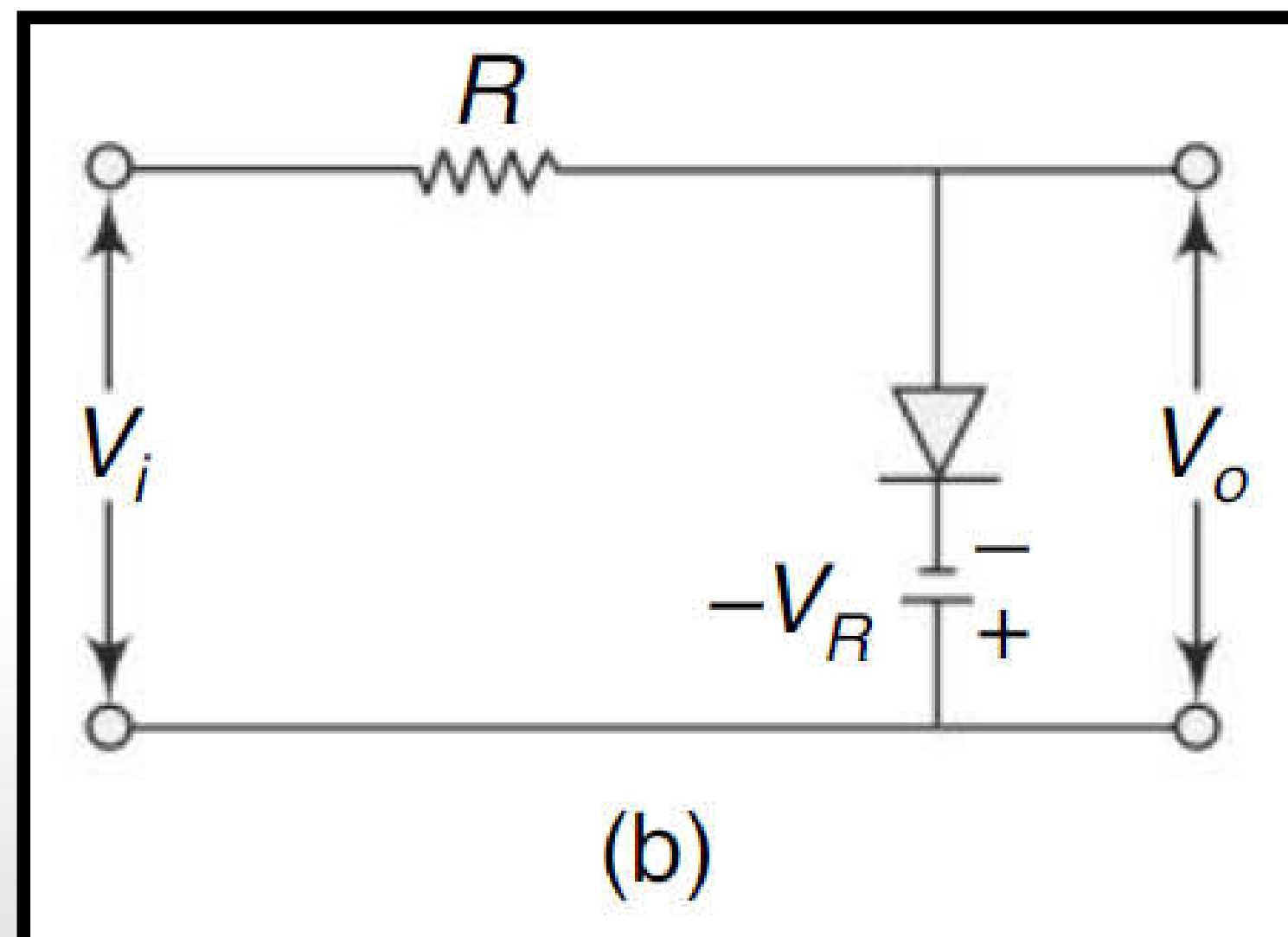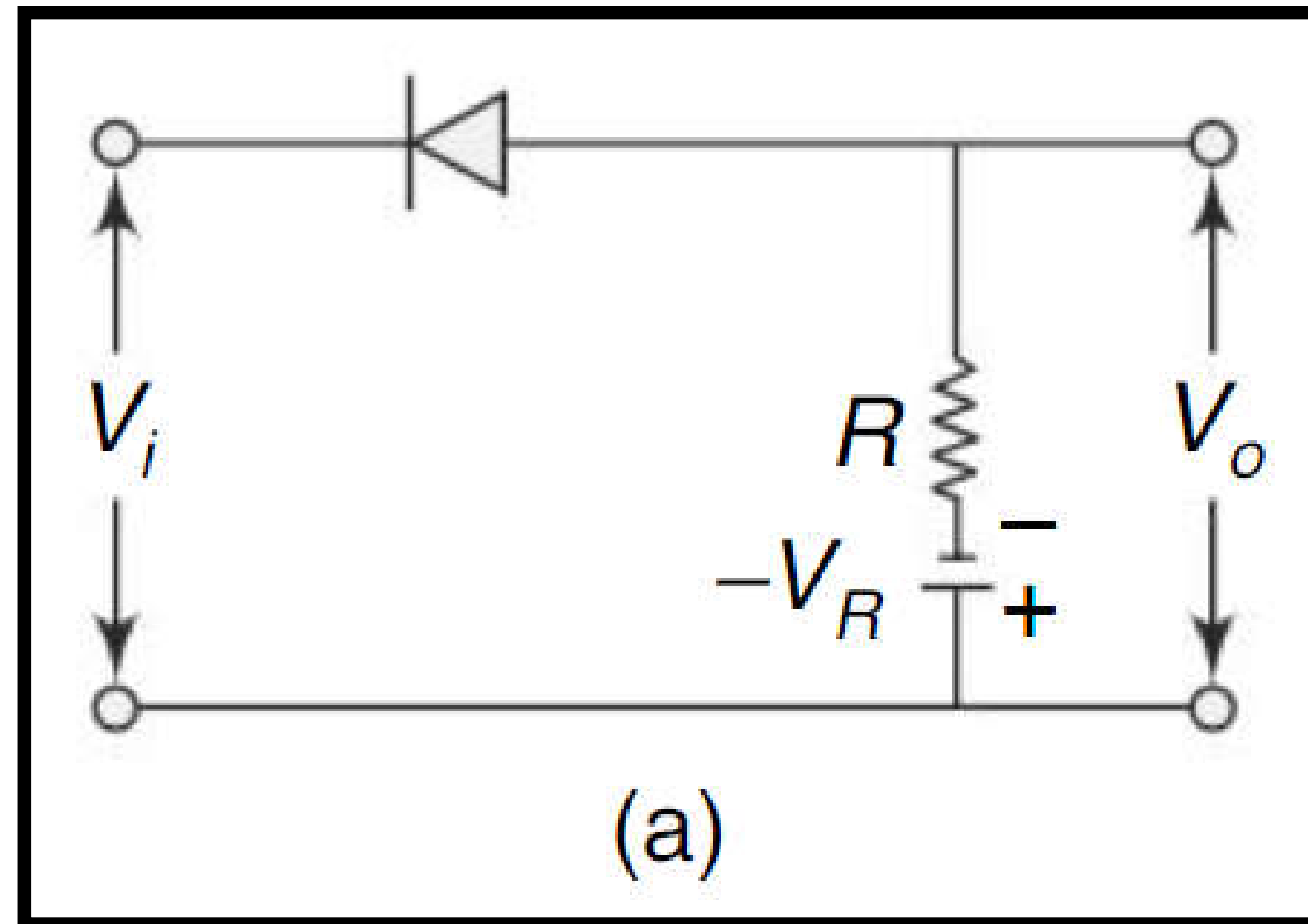




Solution

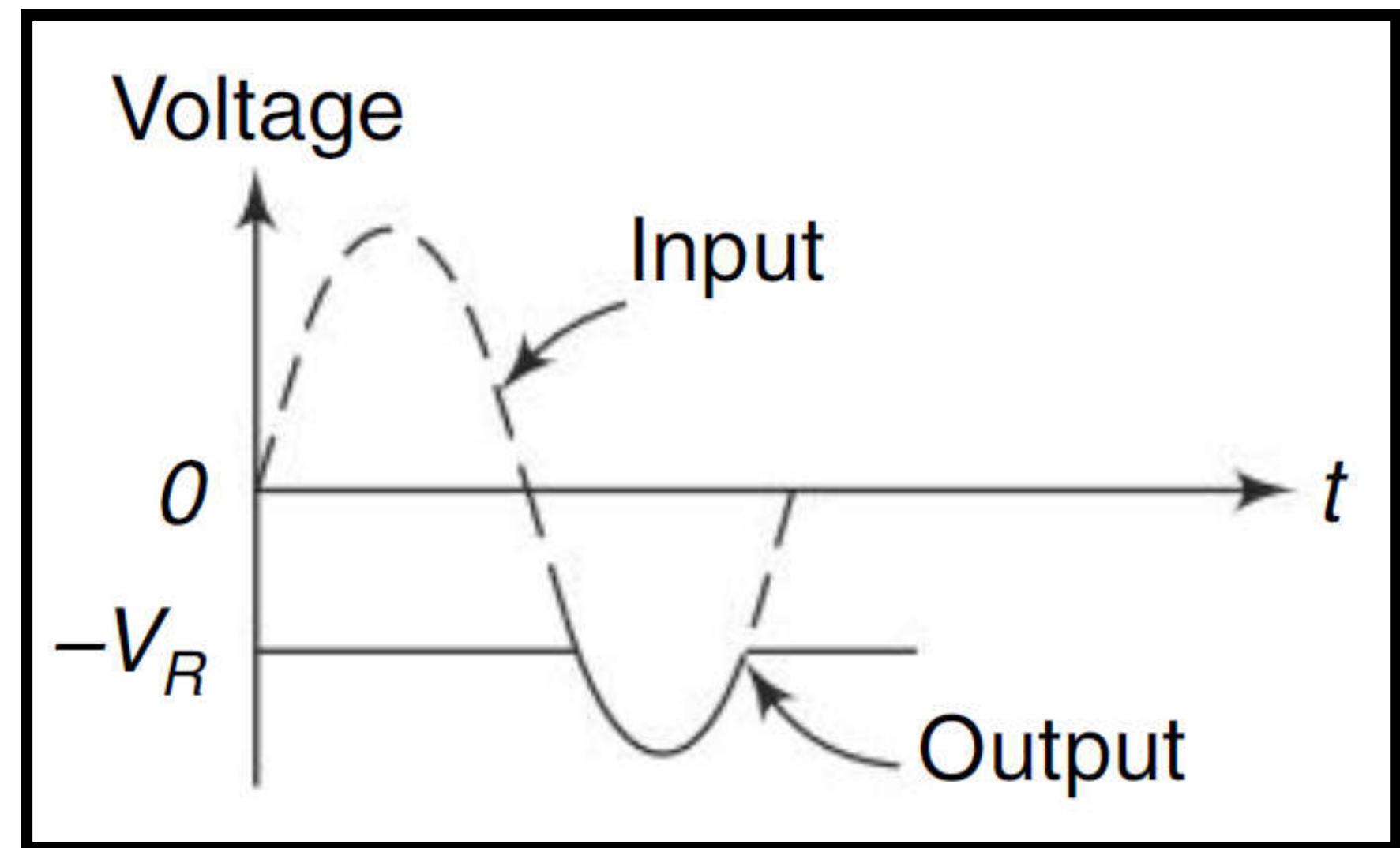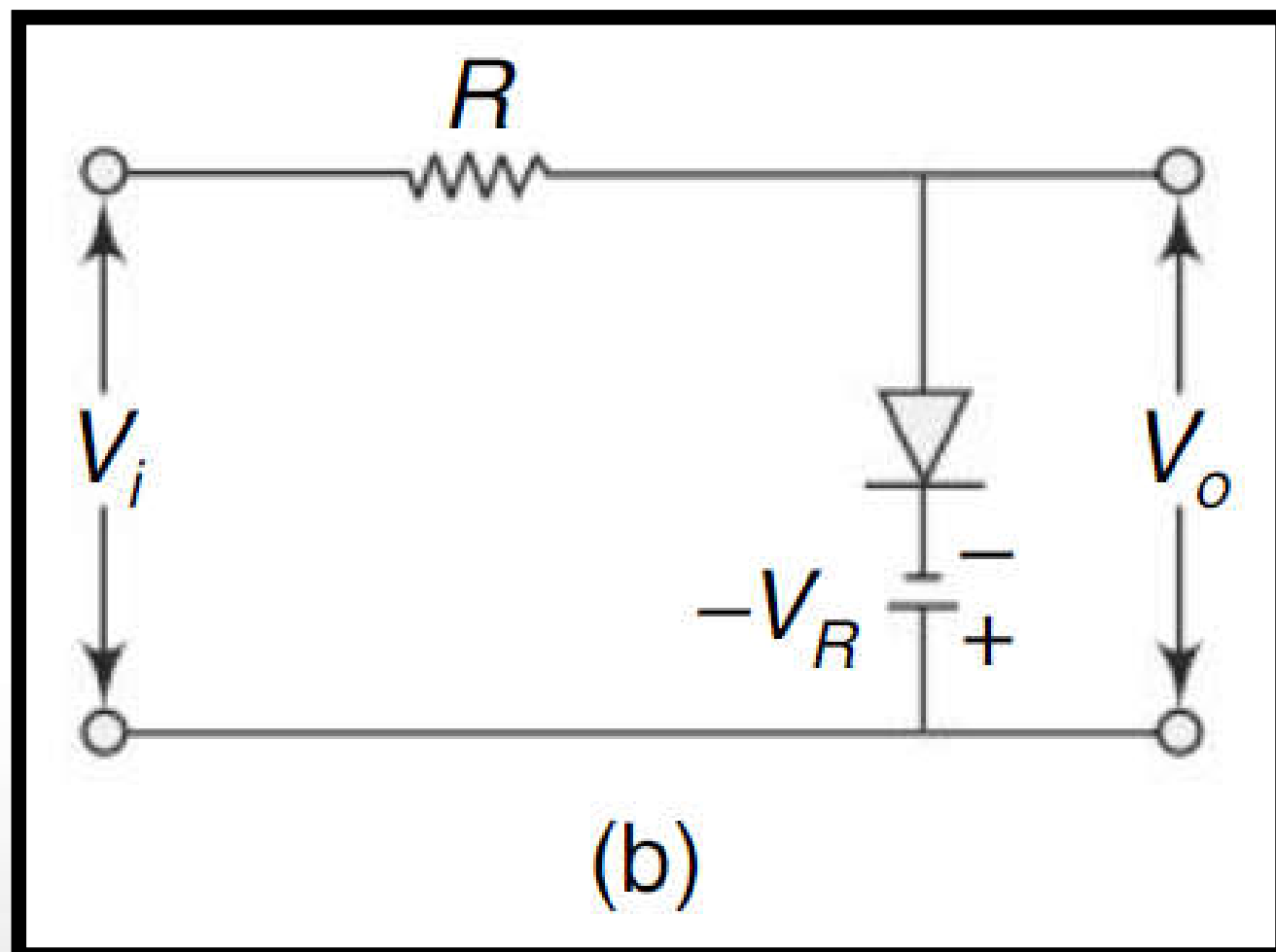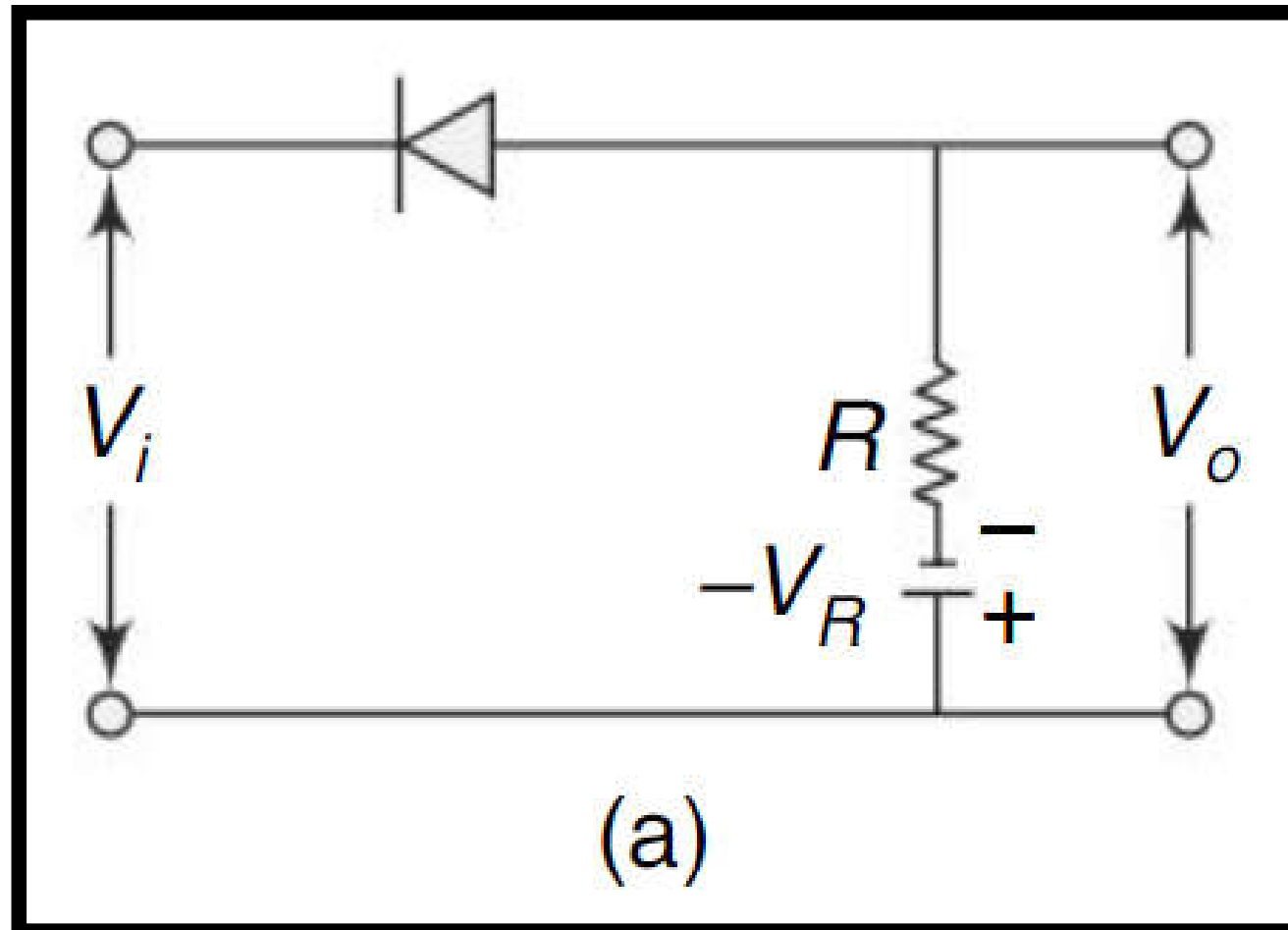



Question

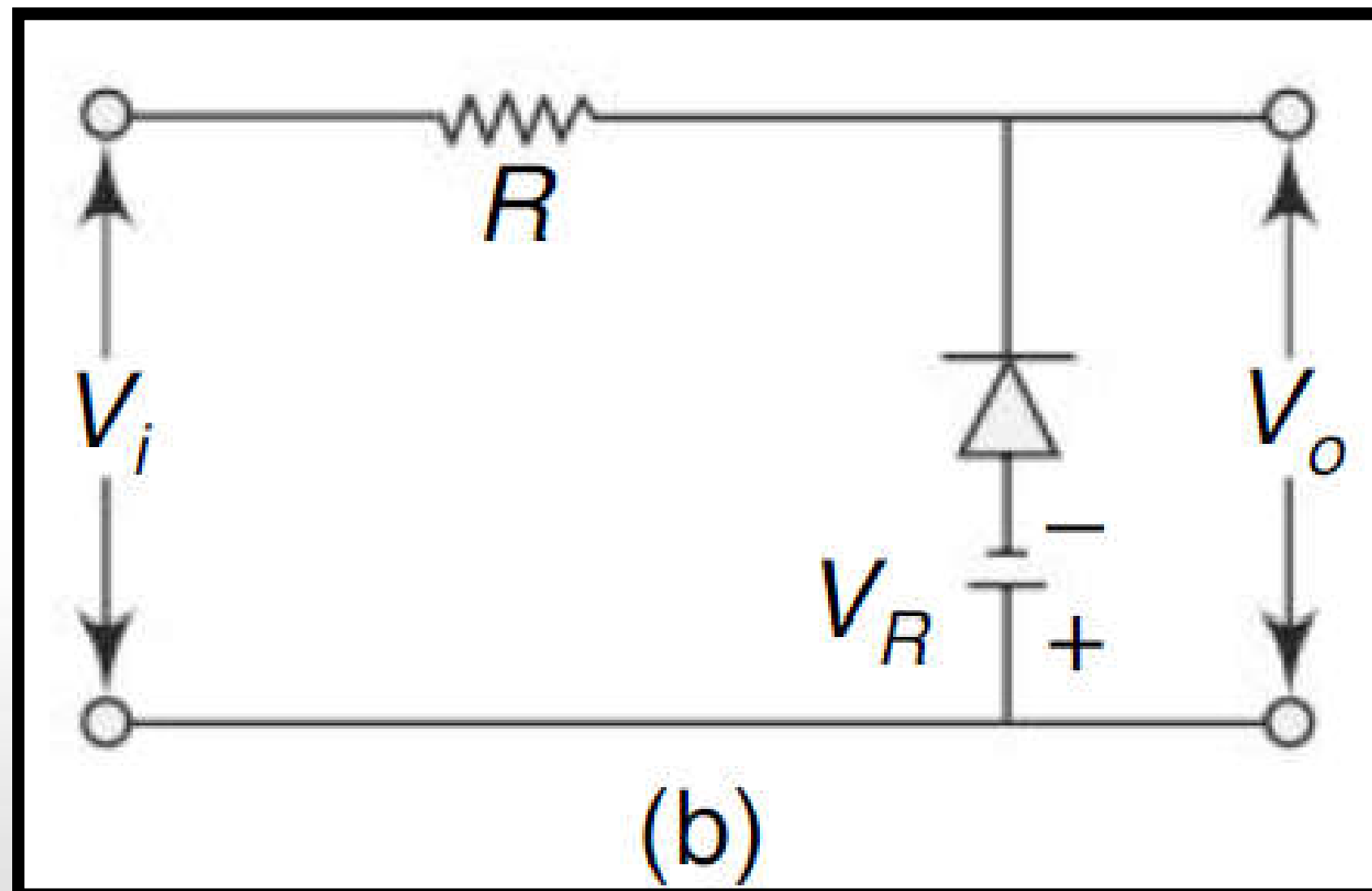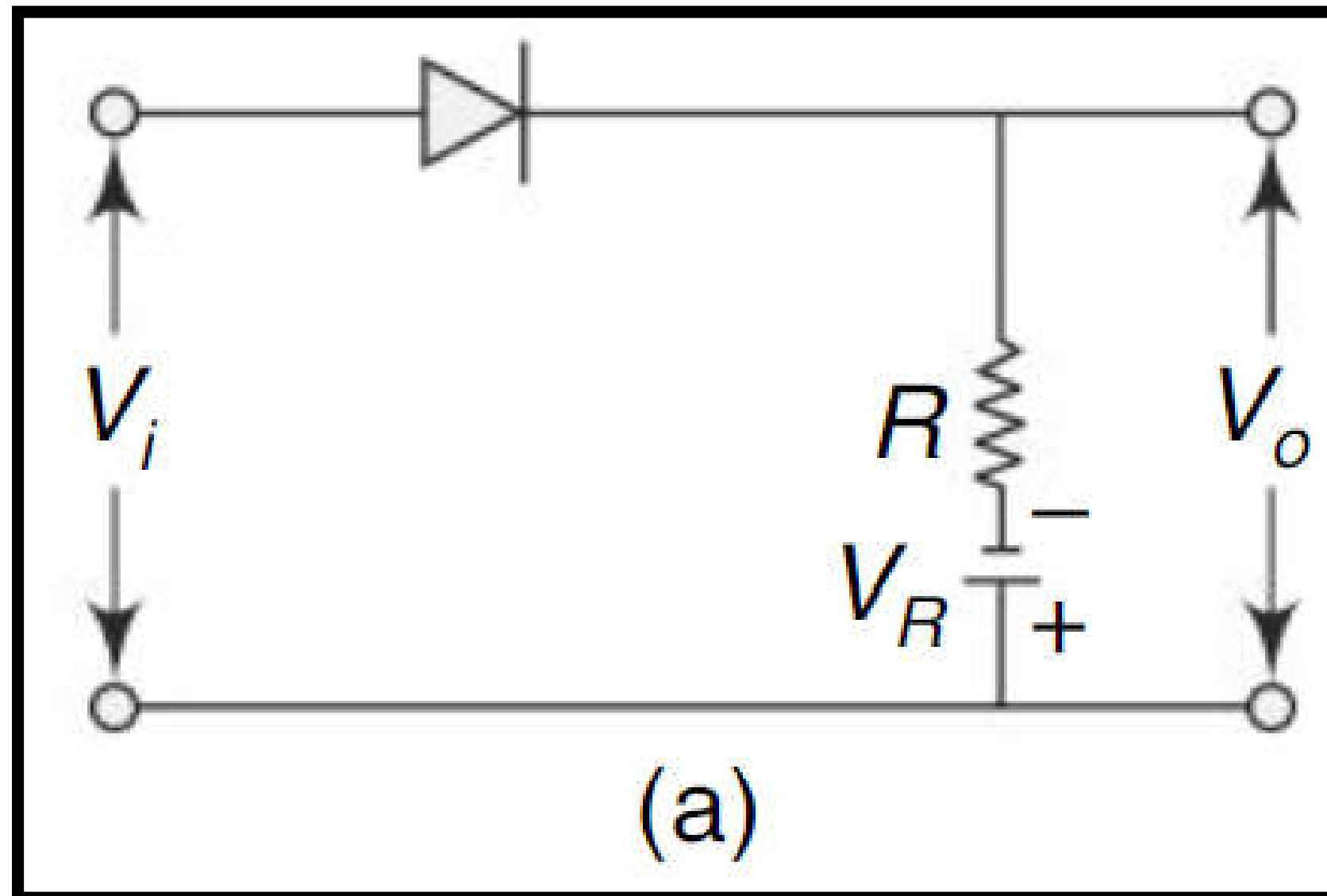


Solution

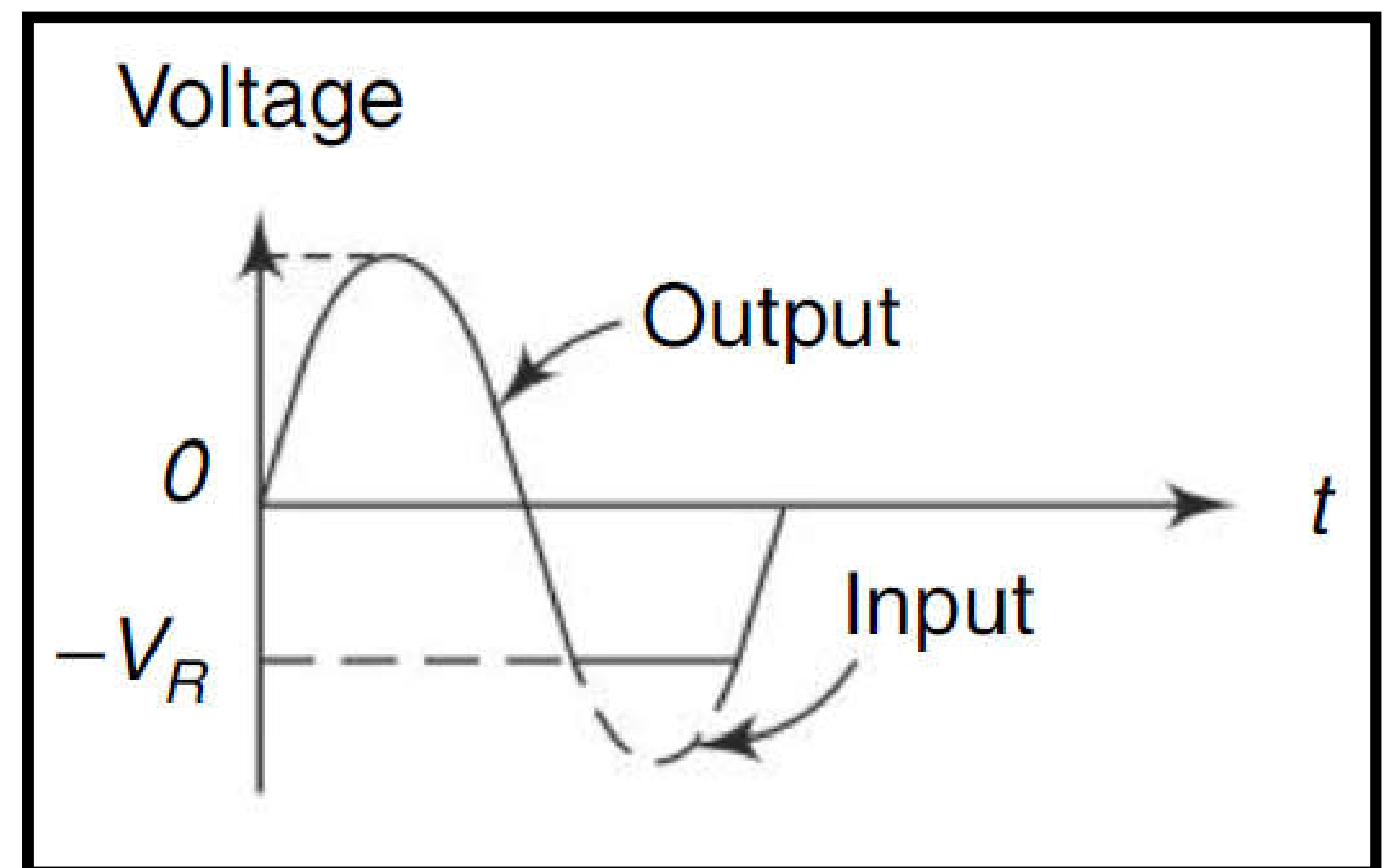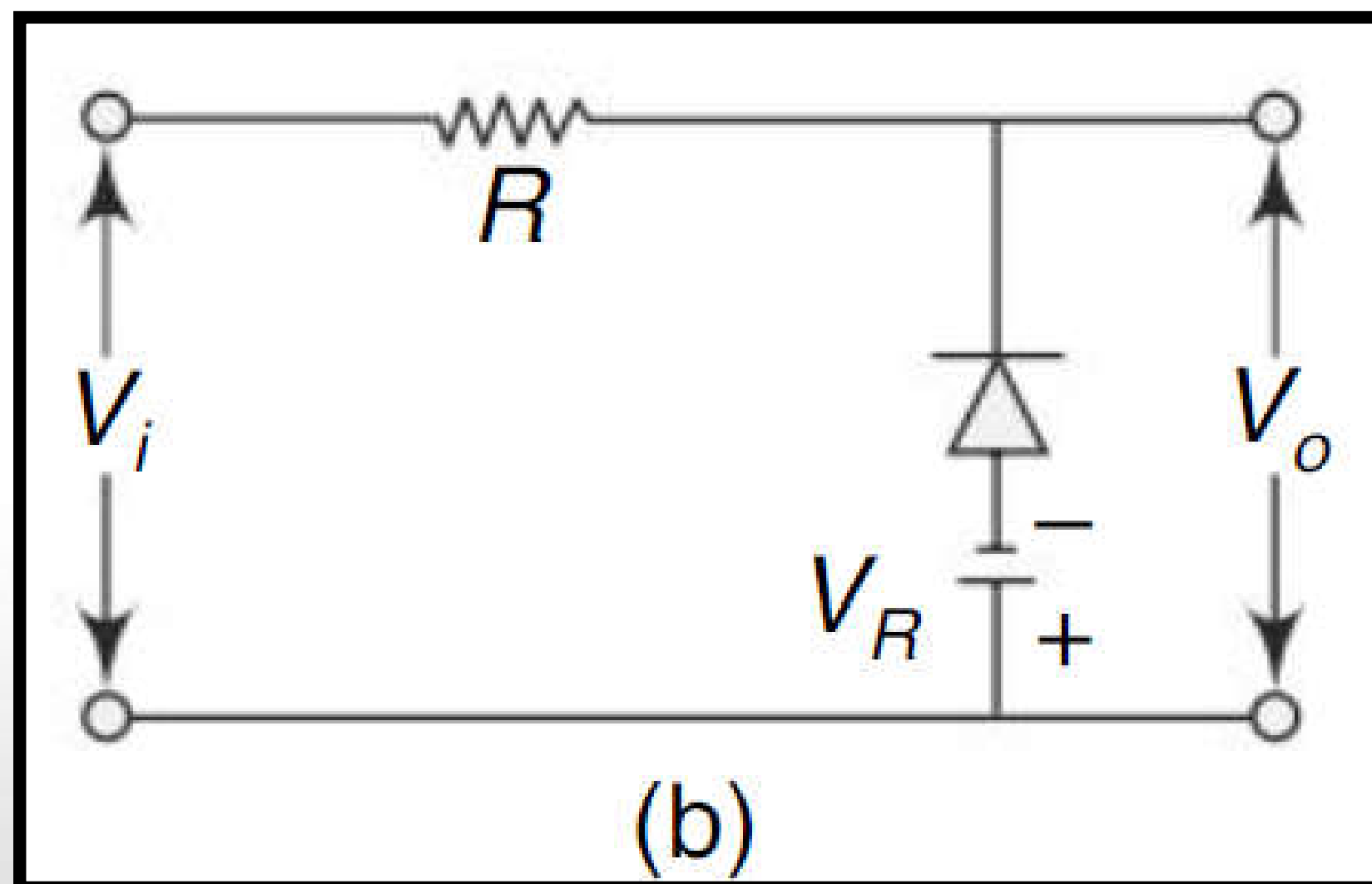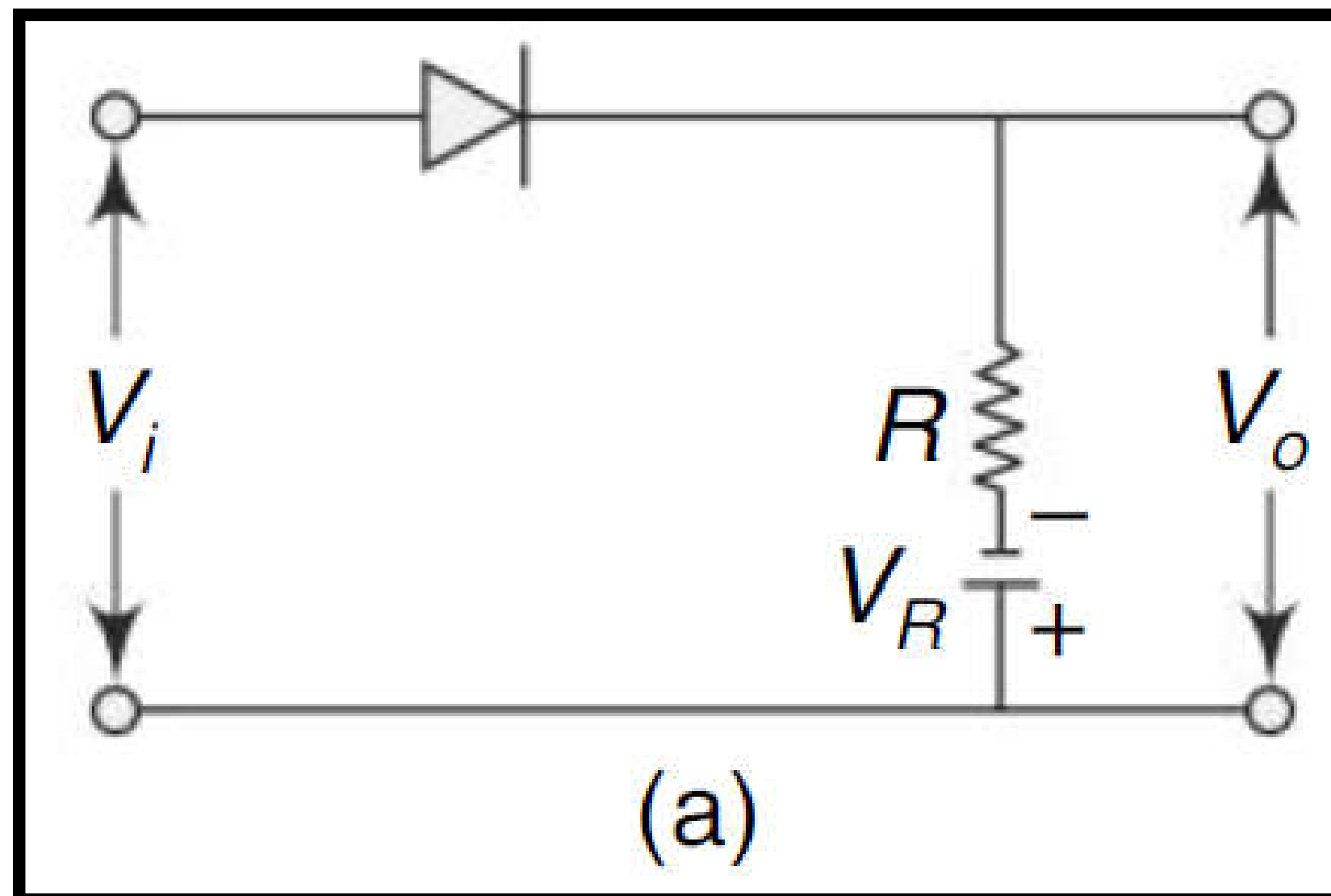


Question

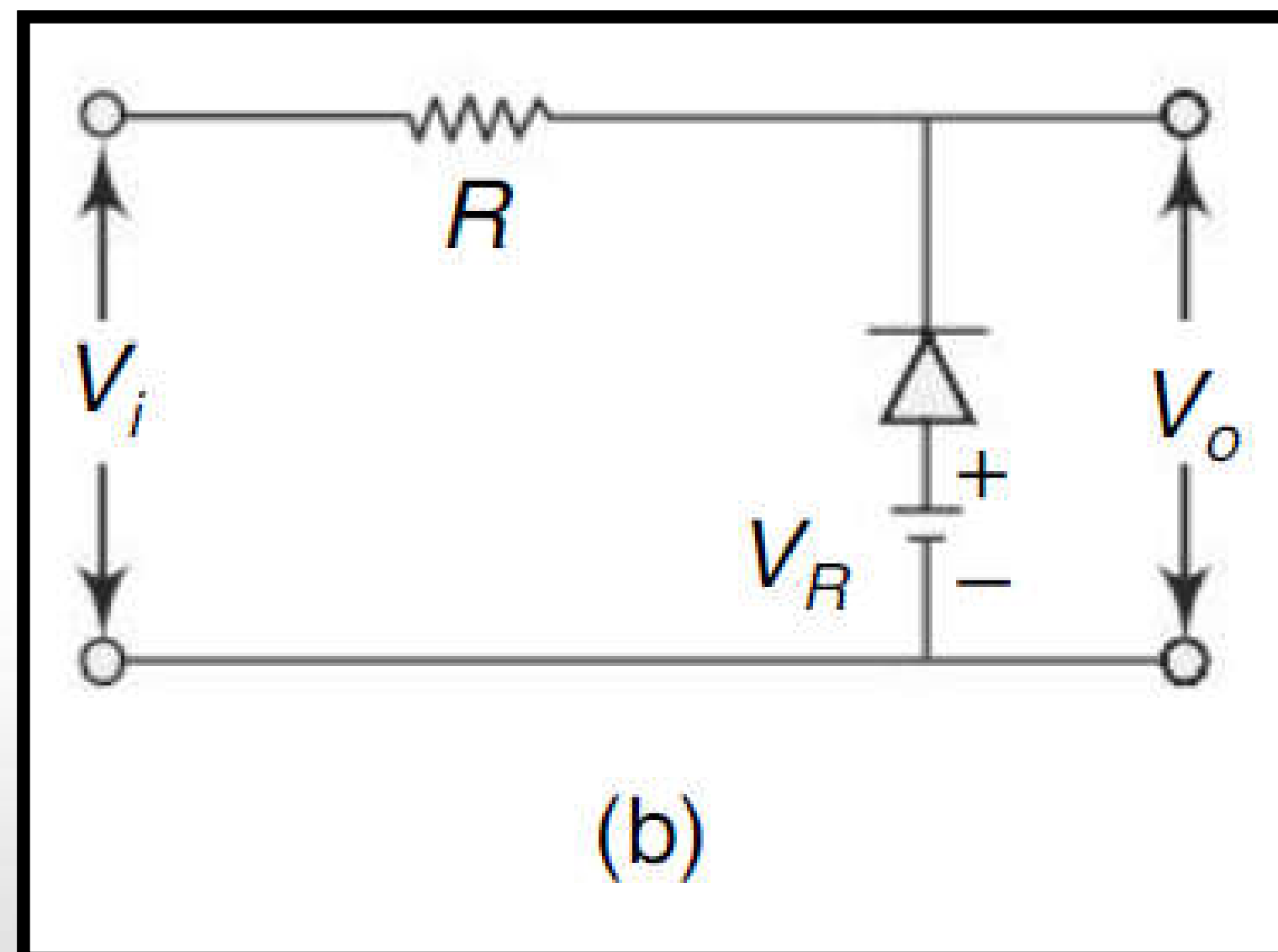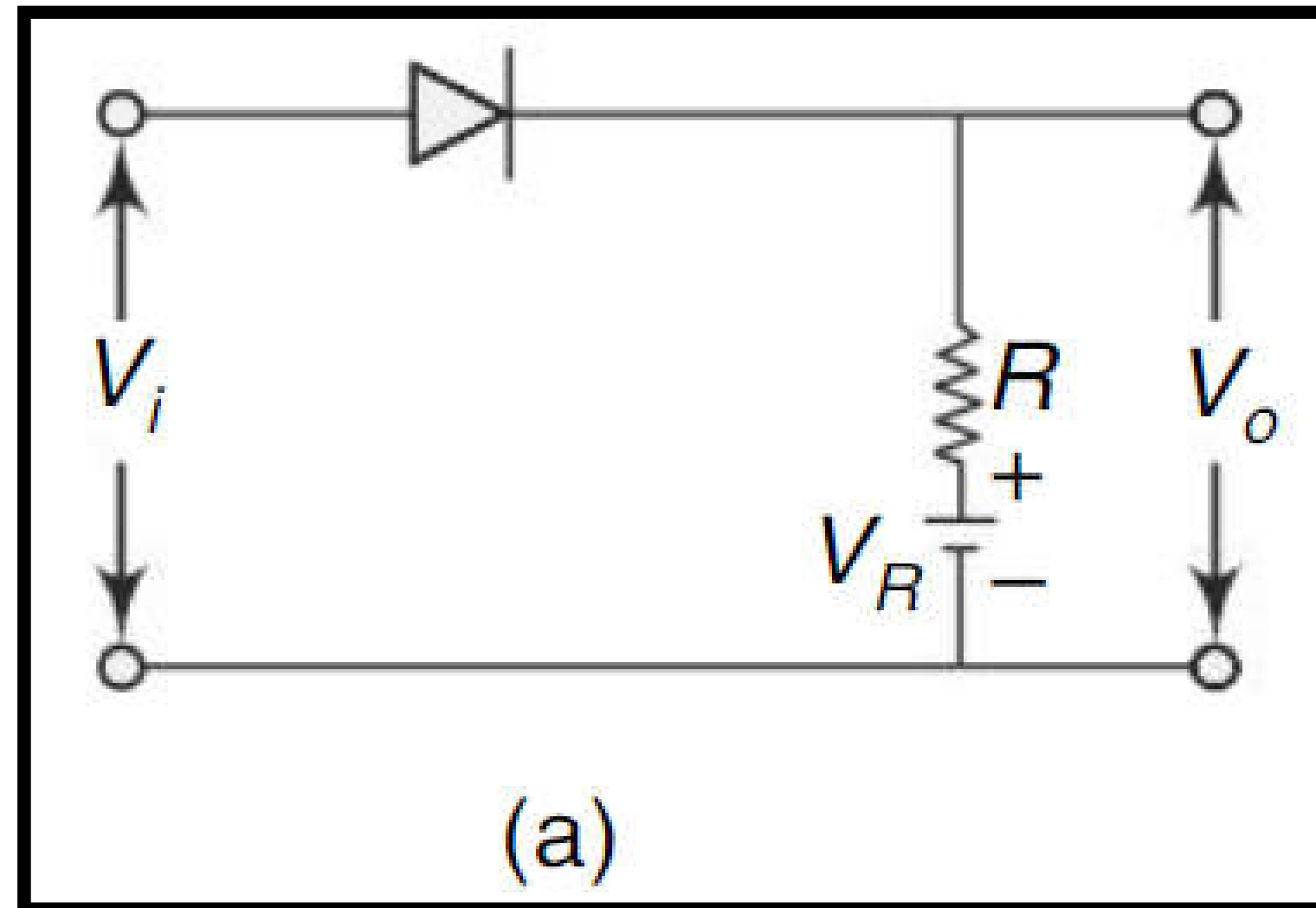


Solution

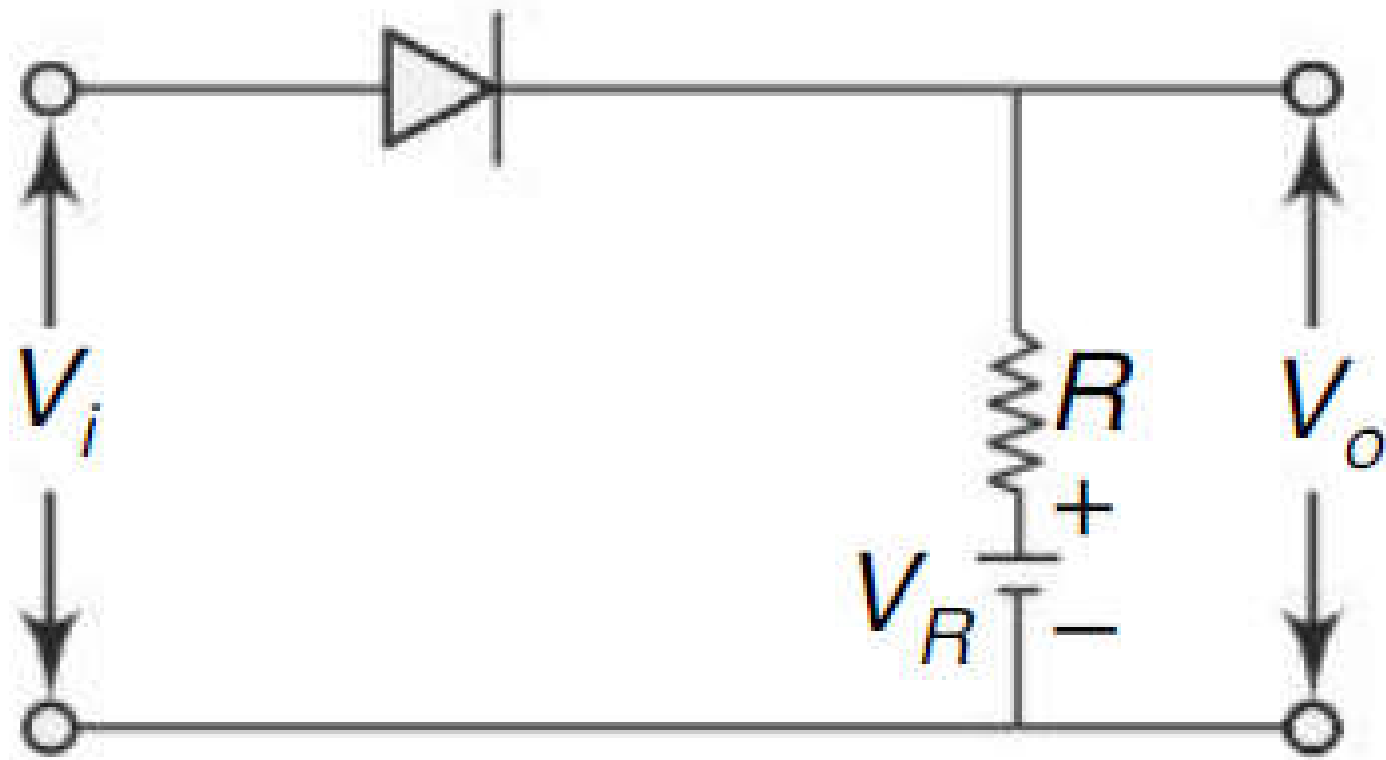


(a)

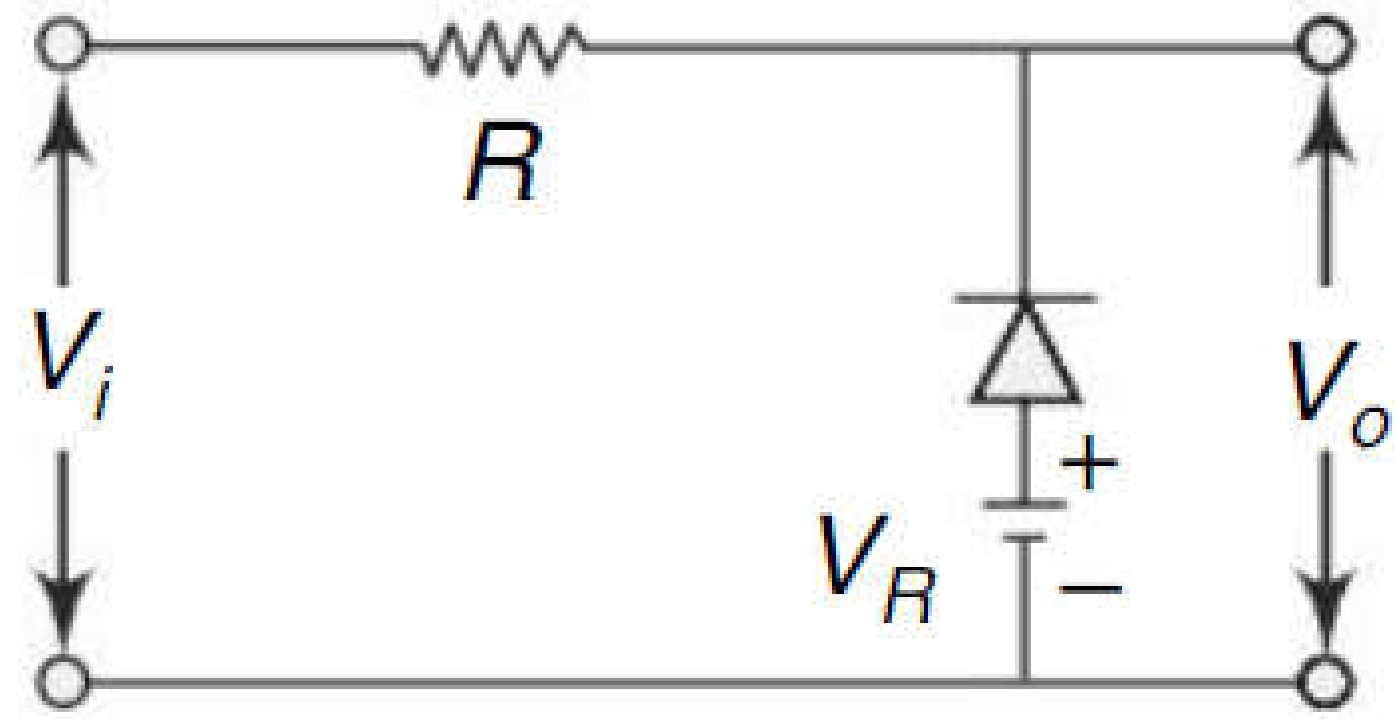


(b)

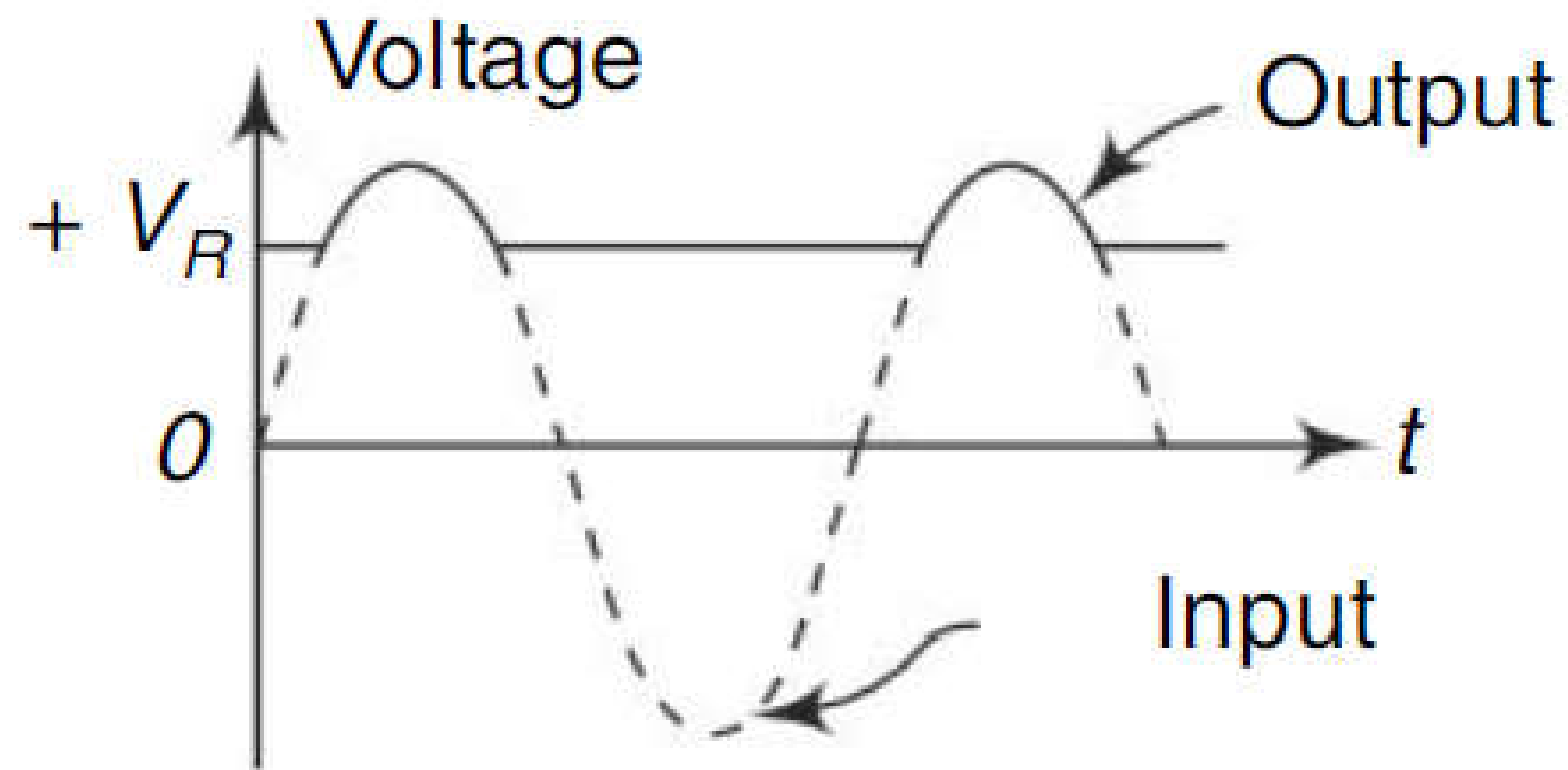



(c)

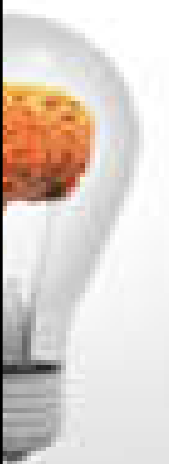


Two Level Clipper Circuit

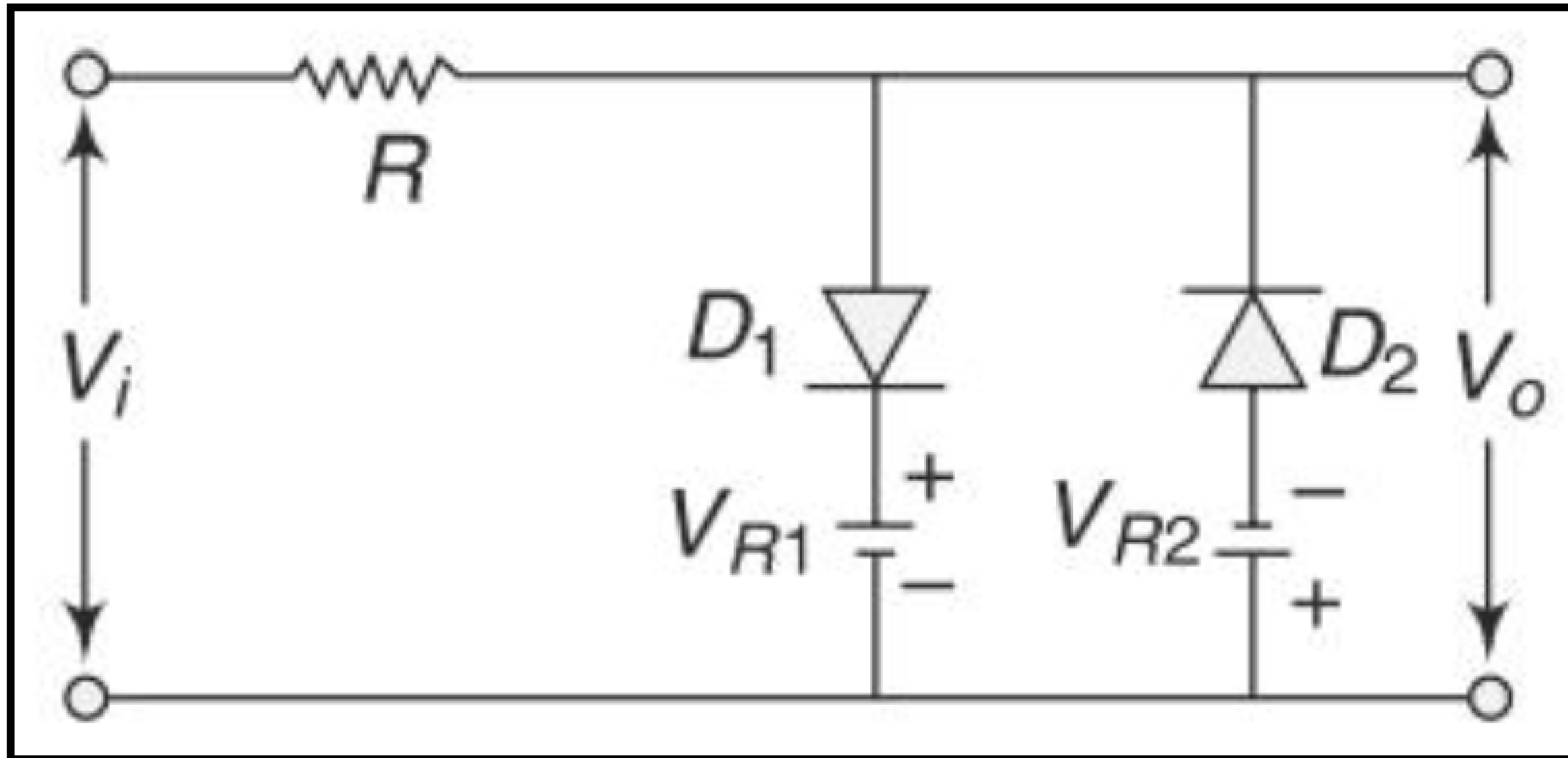



Solution

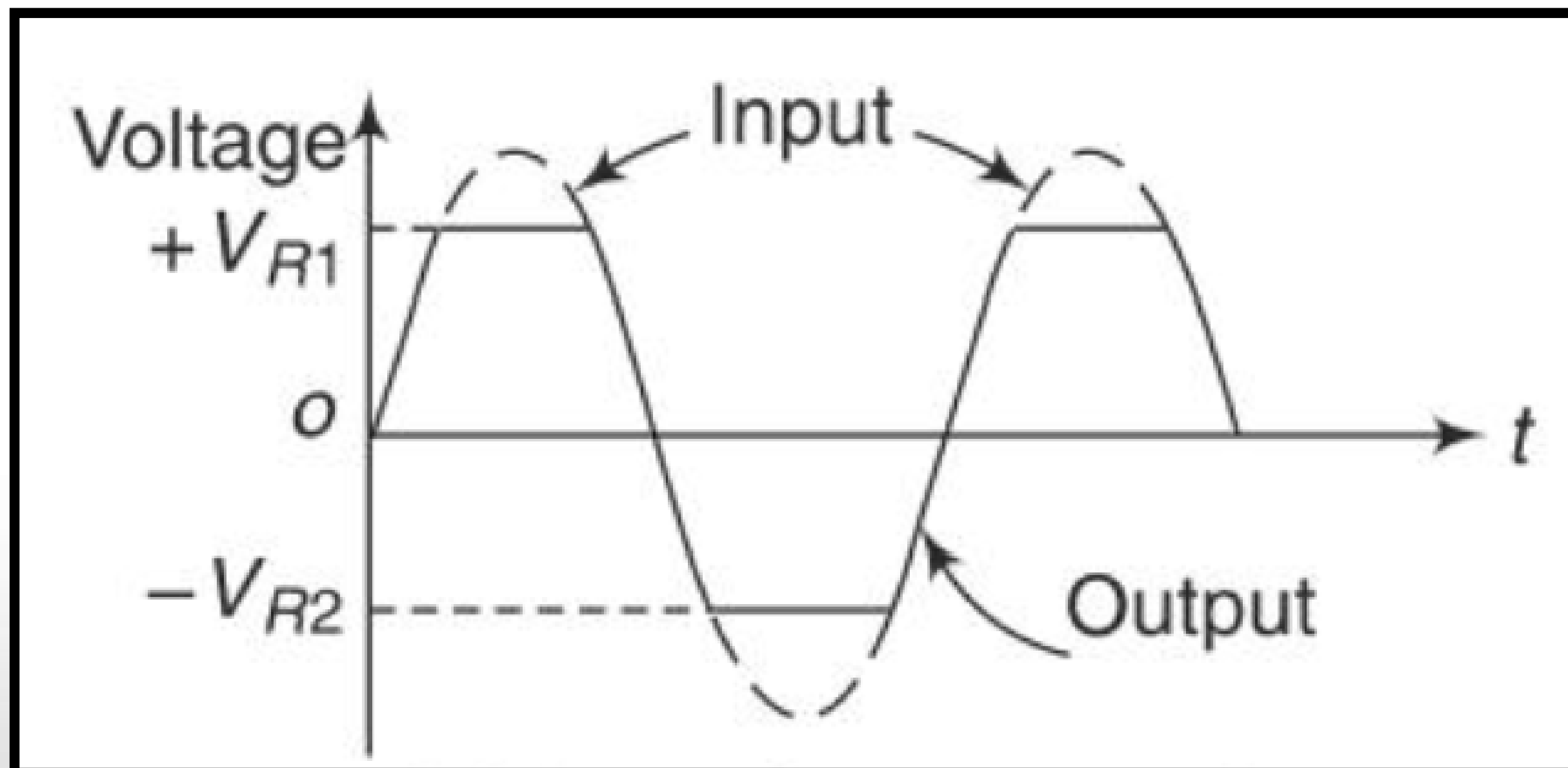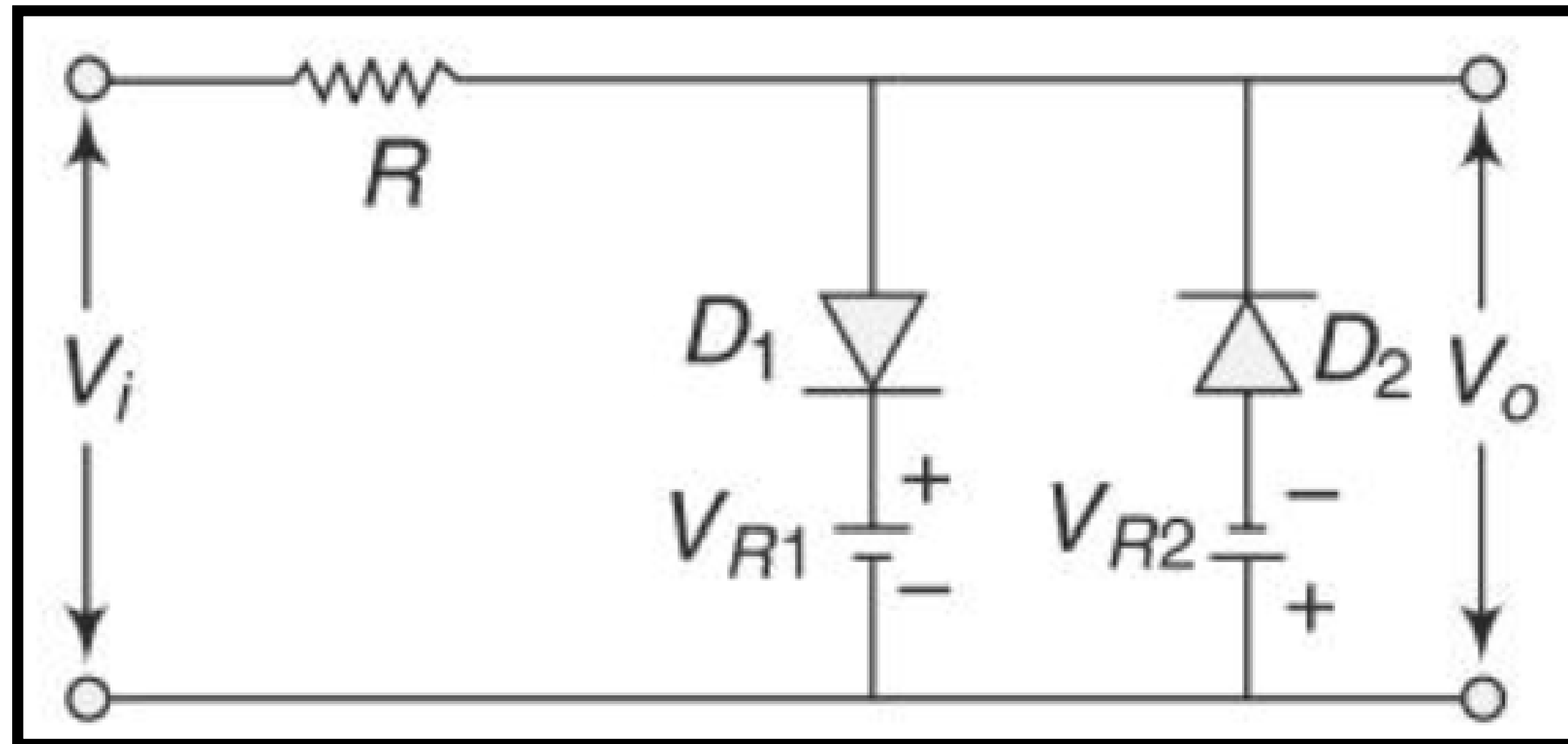


Question

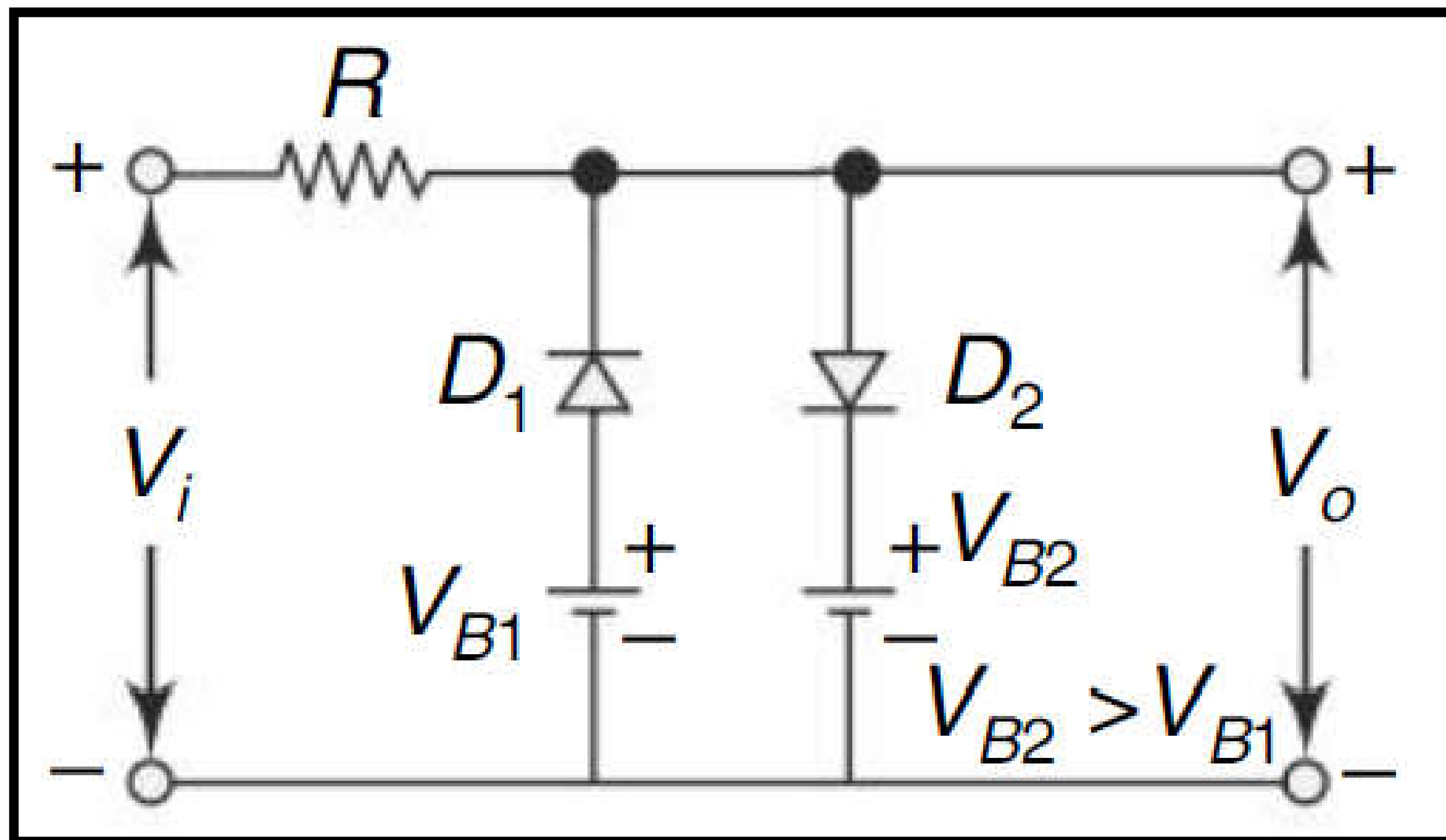


Solution

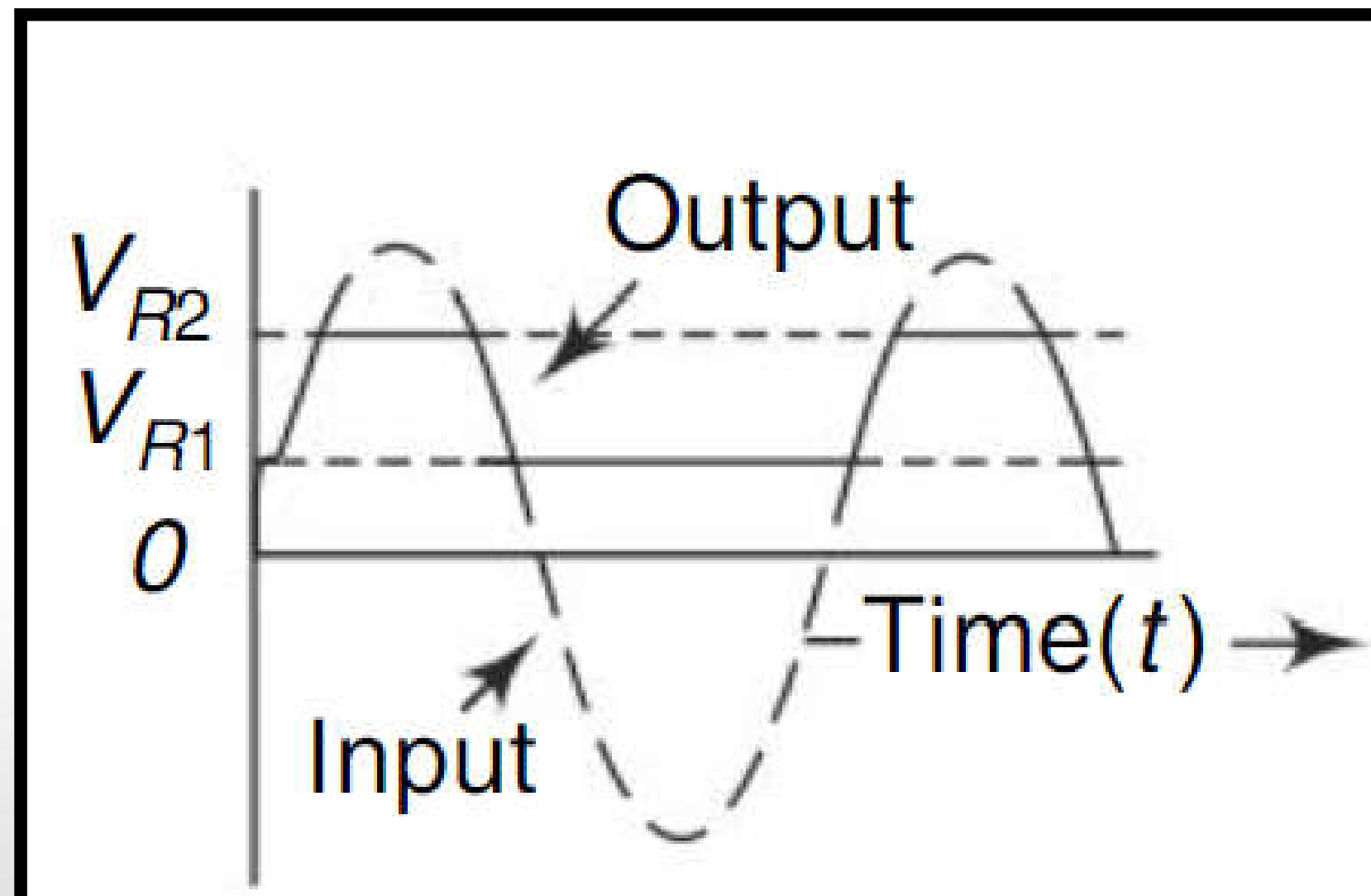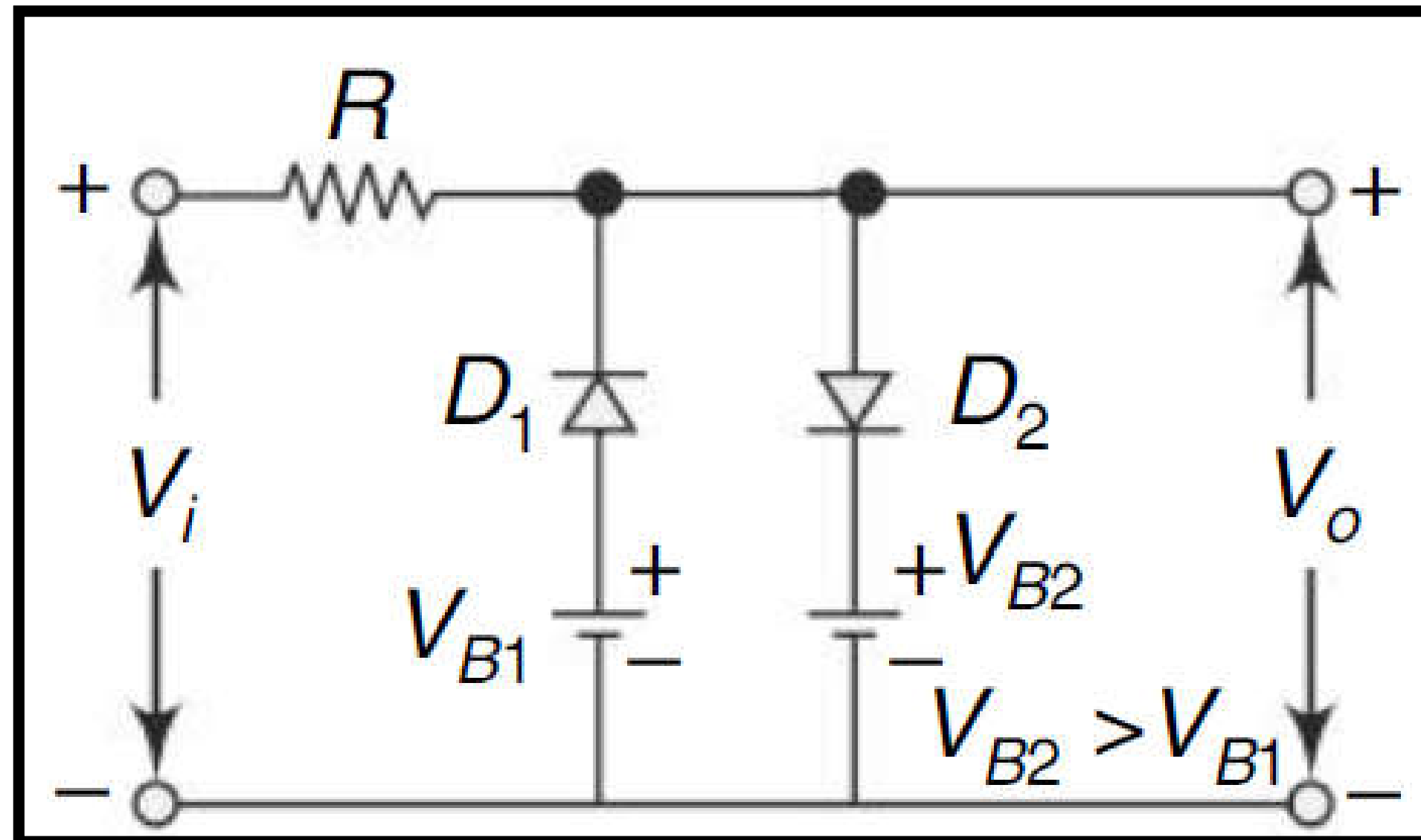

Determine Output assuming Ideal Diodes

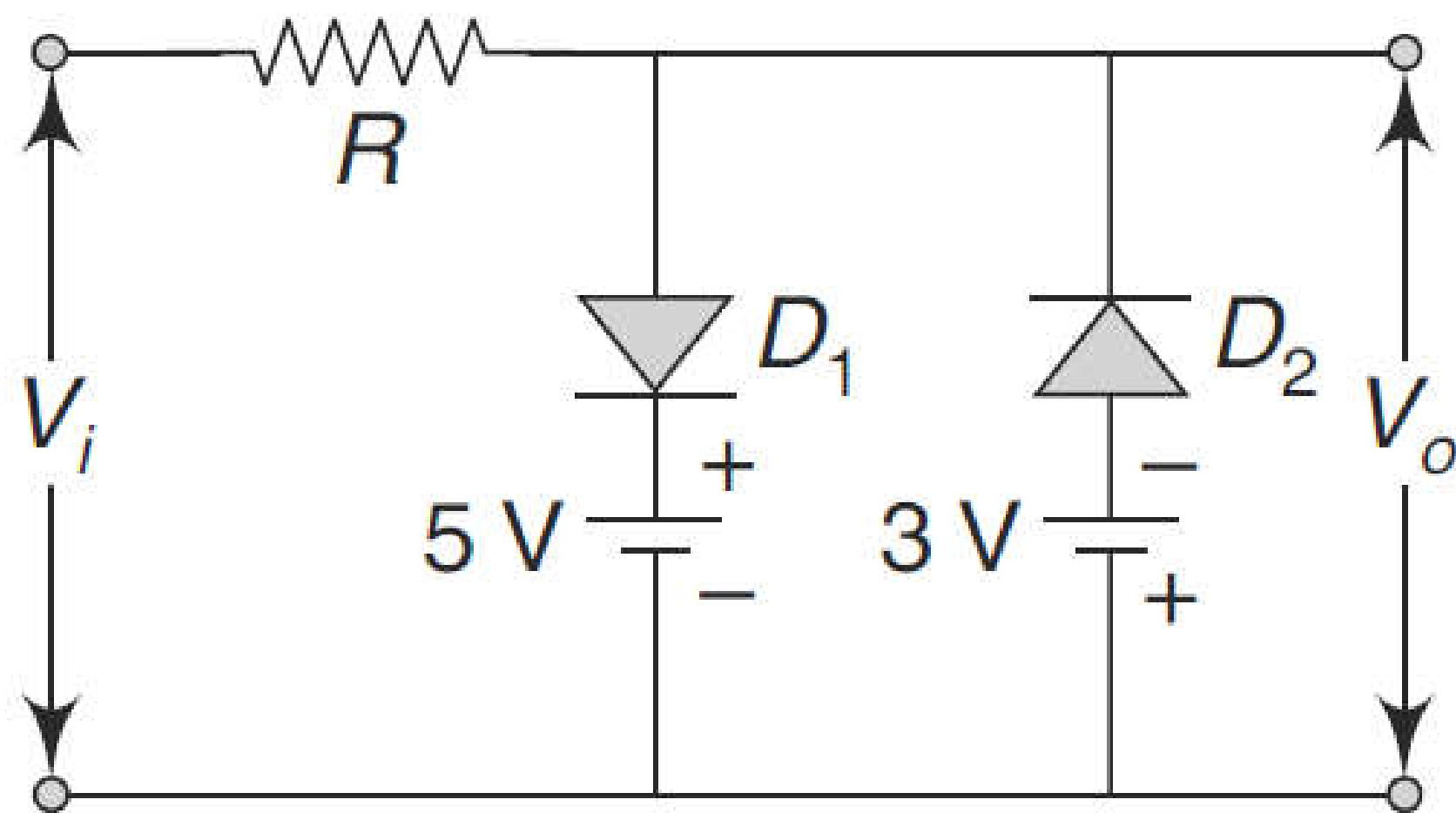


(a)

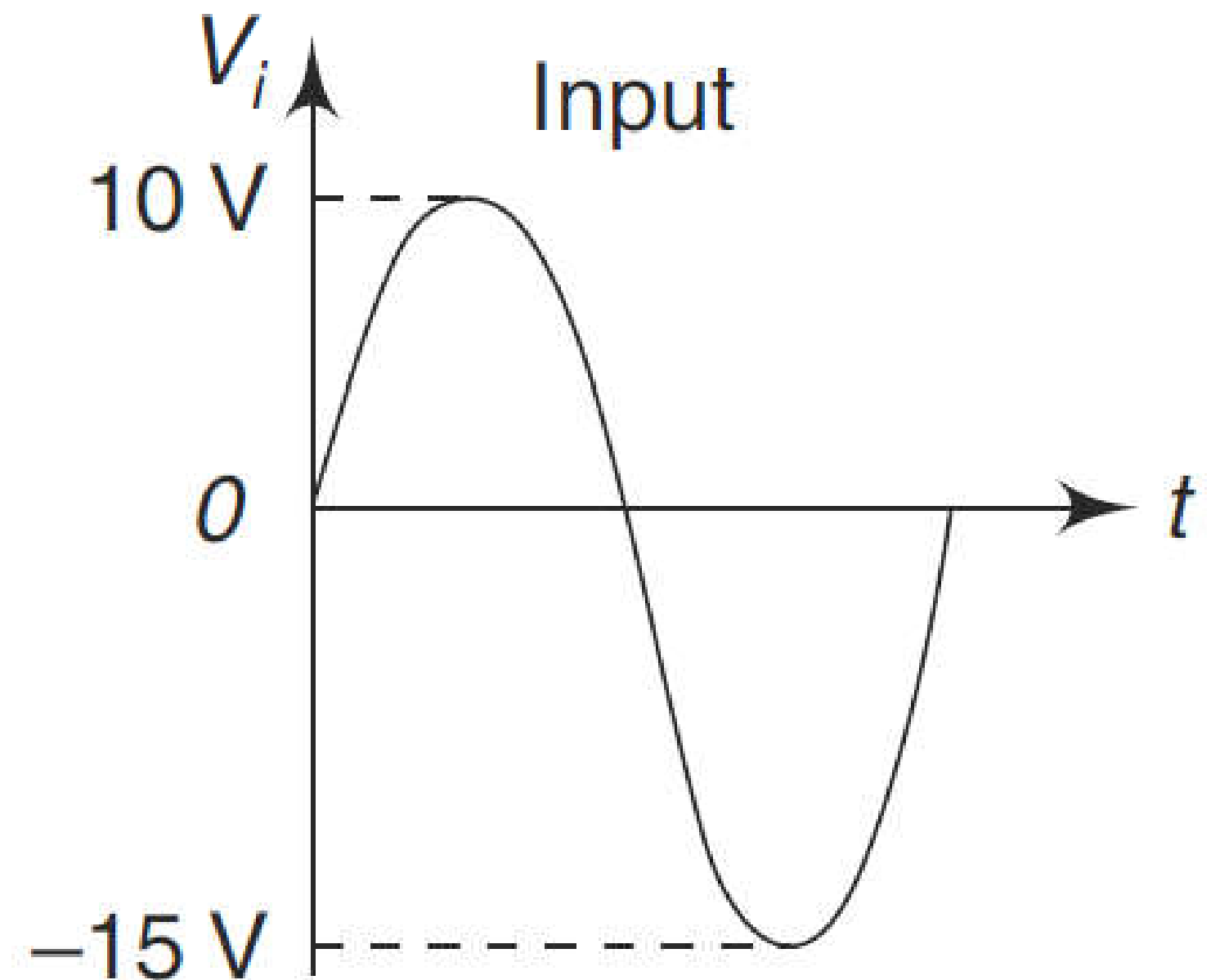


(b)




Solution

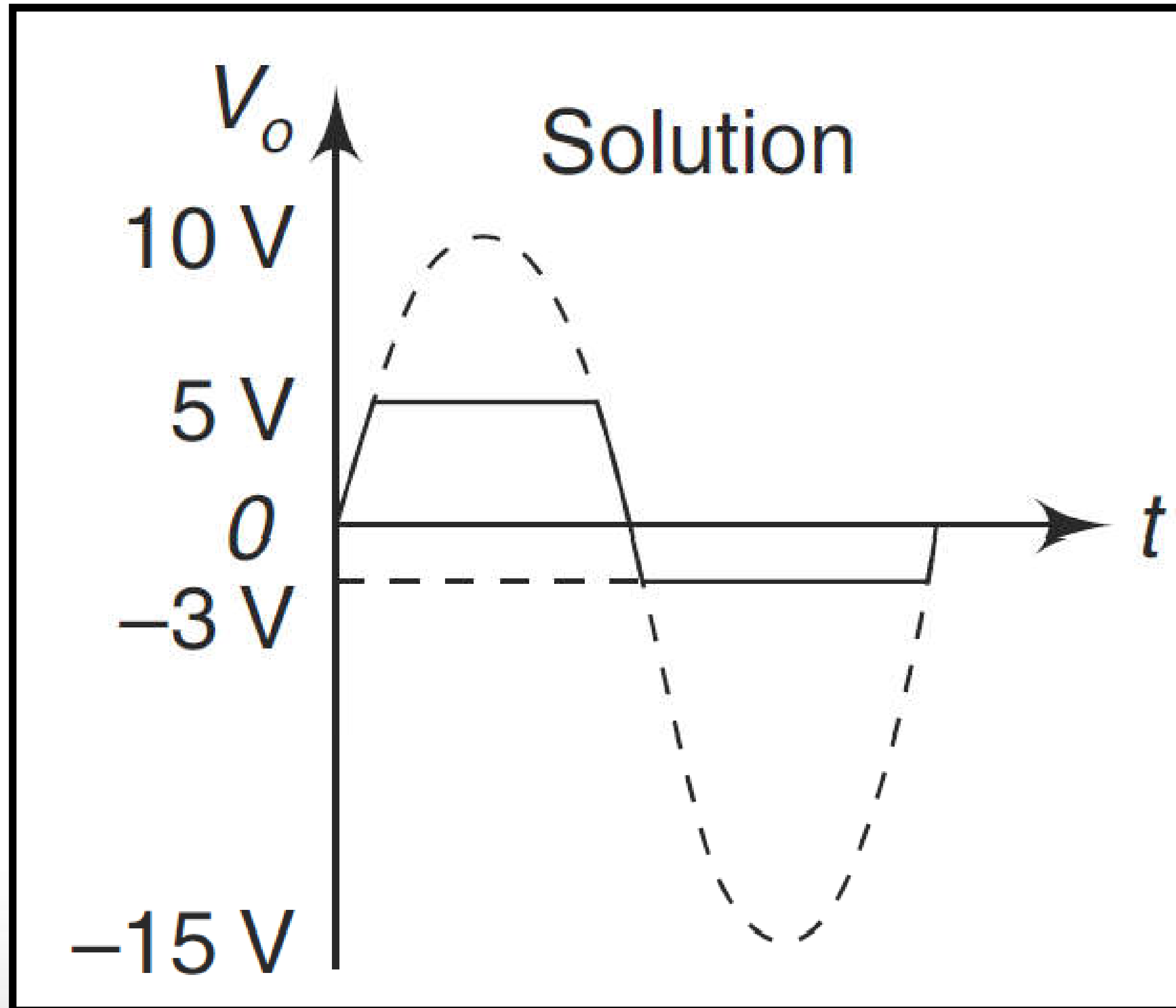

Zener Diode Clipper Circuits

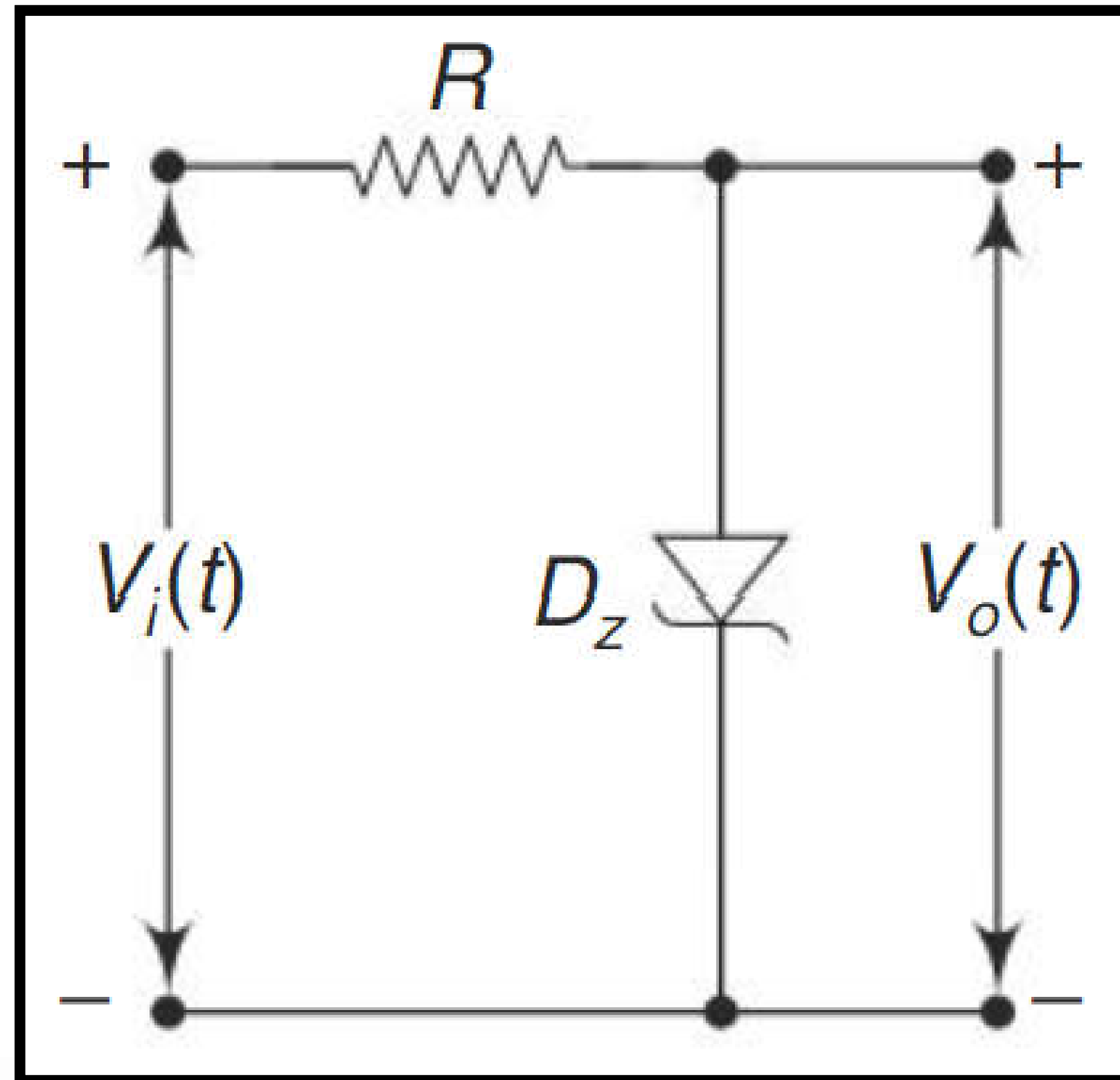

Solution

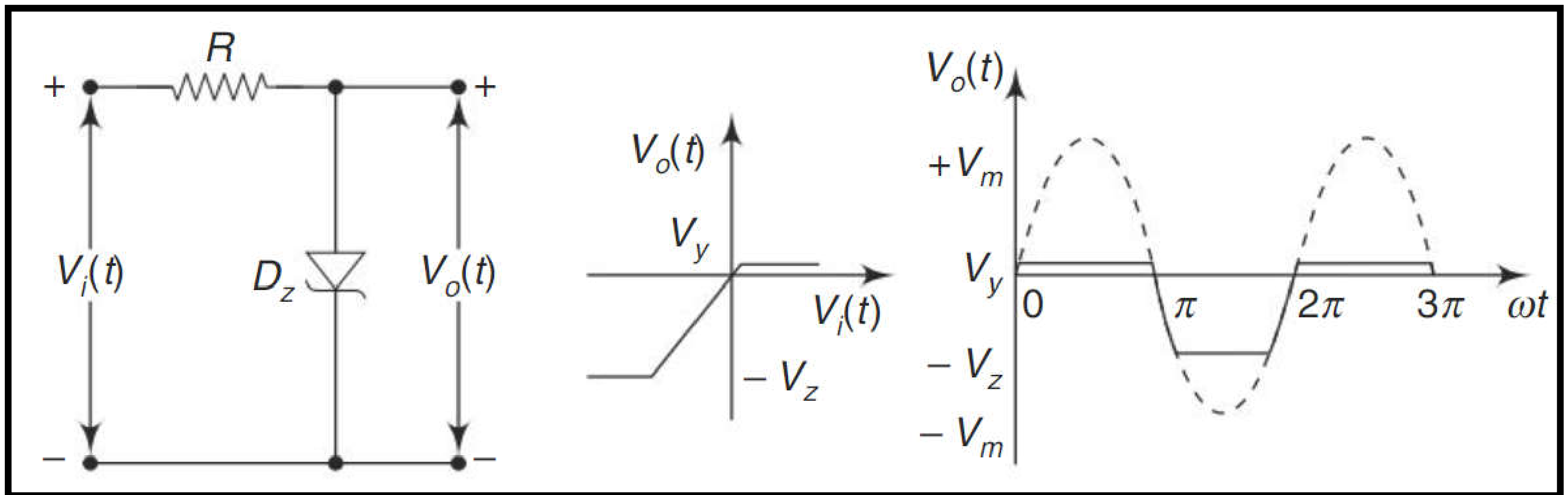

To Be Continued...

