



Expt. No: 9  
 Date: 22/10/2020

## Full Wave Rectifier


**AIM:** To study, design and implement Full Wave Rectifier Circuit.

**SOFTWARE TOOLS / OTHER REQUIREMENTS:**

1. Multisim Simulator/Circuit Simulator

 
**THEORY:**

The circuit diagram of the Bridge Rectifier along with inou-toutput waveforms is shown in figure below. The four diodes D1, D2, D3 and D4 are arranged in a bridge configuration and hence the name. The circuit contains a transformer that steps down the input ac magnitude depending on the requirement and provides the necessary isolation avoiding any risk of shocks.




Let  $V_i = V_m \sin \omega t$  be the input signal at the transformer secondary, it is a sinusoidal signal with maximum amplitude  $V_m$ . During the positive half-cycle of the input, the point A being positive with respect to the point B, the diodes D1 and D3 will be forward biased; however, the diodes D2 and D4 will be reverse biased. The pair of diodes D1 and D3 start conduction resulting in a current  $I_D$  flowing through the load resistor  $R_L$  in the direction marked for the entire positive half-cycle, i.e. from  $\omega t = 0$  to  $\pi$  and the diodes D2 and D4 will be in OFF condition. During the negative half-cycle of the input, the point B will be positive with respect to the point A and the diodes D2 and D4 will be forward biased, and the diodes D1 and D3 will be reverse biased. Diodes D2 and D4 start conduction resulting in a current  $I_D$  flowing through the load resistor  $R_L$  again in the same direction (as earlier) for the entire negative half-cycle, i.e.


from  $\omega t = \pi$  to  $2\pi$  and the diodes D1 and D3 will be in OFF condition. Thus, between  $\omega t = 0$  to  $\pi$ , D1 and D3 conduct and result in an output, between  $\omega t = \pi$  to  $2\pi$ , D2 and D4 conduct and result in an output  $V_o$  as indicated in Fig. (b). It can therefore be observed that for both cycles of input, there is a current flowing, hence the name full-wave rectifier.

 

(a) Positive half-cycle

 


(b) Negative half-cycle

 


(c) Diode waveforms

### CIRCUIT DIAGRAM (FROM MULTISIM)

 



**WAVEFORMS (FROM MULTISIM)**

 

**CONCLUSIONS**



- 1.) In this Experiment, We have studied about Full Wave Rectifier Circuit and its Working.
- 2.) We Verified the Theoretical Knowledge of Full Wave Rectifier Circuit by Performing Simulations of Full Wave Rectifier Circuit in Multisim.
- 3.) Hence, we have Successfully Designed, Plotted and Verified Full Wave Rectifier Circuit.



## ASSIGNMENT-9


U19CS012

  1. Calculate and Plot  $V_o$  for the following circuit.




A.) Multisim Calculations:

1.) Circuit Image:

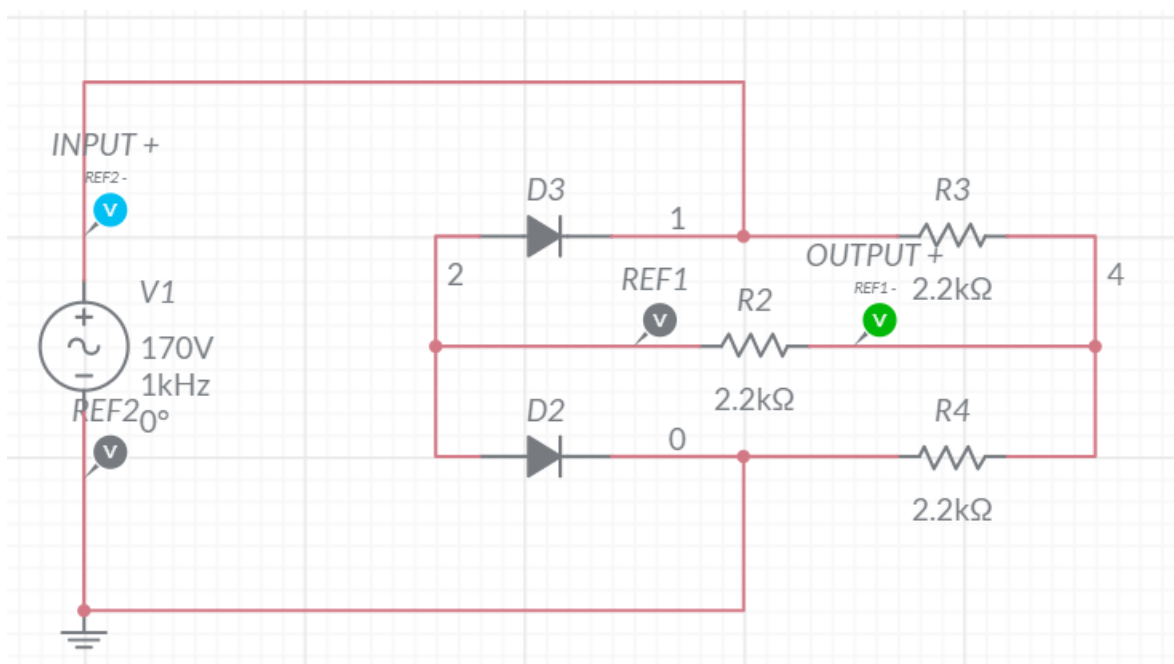



## 2.) Grapher Image:

 

## B.) Calculation Part




Page No.	
Date	

Q2.

170V

-170V



(U19C5012)

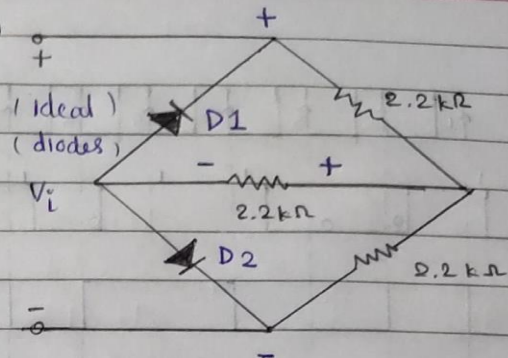

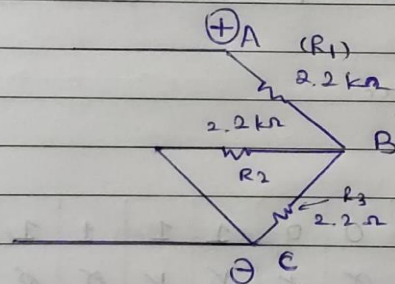 (A) During Positive half cycle

D1 will be Reverse biased

D2 will be short circuit  
(forward Biased)



$$R_{eq} = R_1 + (R_2 \parallel R_3)$$

$$= 2.2k\Omega + \frac{1}{\left(\frac{1}{2.2} + \frac{1}{2.2}\right)} = [3.3k\Omega]$$



$$i = \frac{V}{R_{eq}} = \frac{170}{(3.3k\Omega)}$$

Ans:  $V_{R_2} = (V) \times \frac{(1.1)k\Omega}{(1.1+2.2)k\Omega} = 170 \times \frac{1}{3} = \frac{170V}{3}$

(B) During Negative half cycle

D1 will be forward biased

D2 will be reverse biased

  

$$R_{eq} = R_3 + (R_1 \parallel R_2) = (2.2 + 1.1)k\Omega = 3.3k\Omega$$

$$V_{R_2} = (V) \times \frac{(R_1 \parallel R_2)}{(R_3 + (R_1 \parallel R_2))} = 170 \times \frac{1.1}{(1.1+2.2)}$$

Ans:  $V_{R_2} = \frac{170V}{3}$