

# DIGITAL ELECTRONICS & LOGIC DESIGN LAB


---

LAB 1: ASSIGNMENT 1 & 2


Submitted By: U19CS012 (D-12)  
BHAGYA VINOD RANA | C.S.E., SVNIT
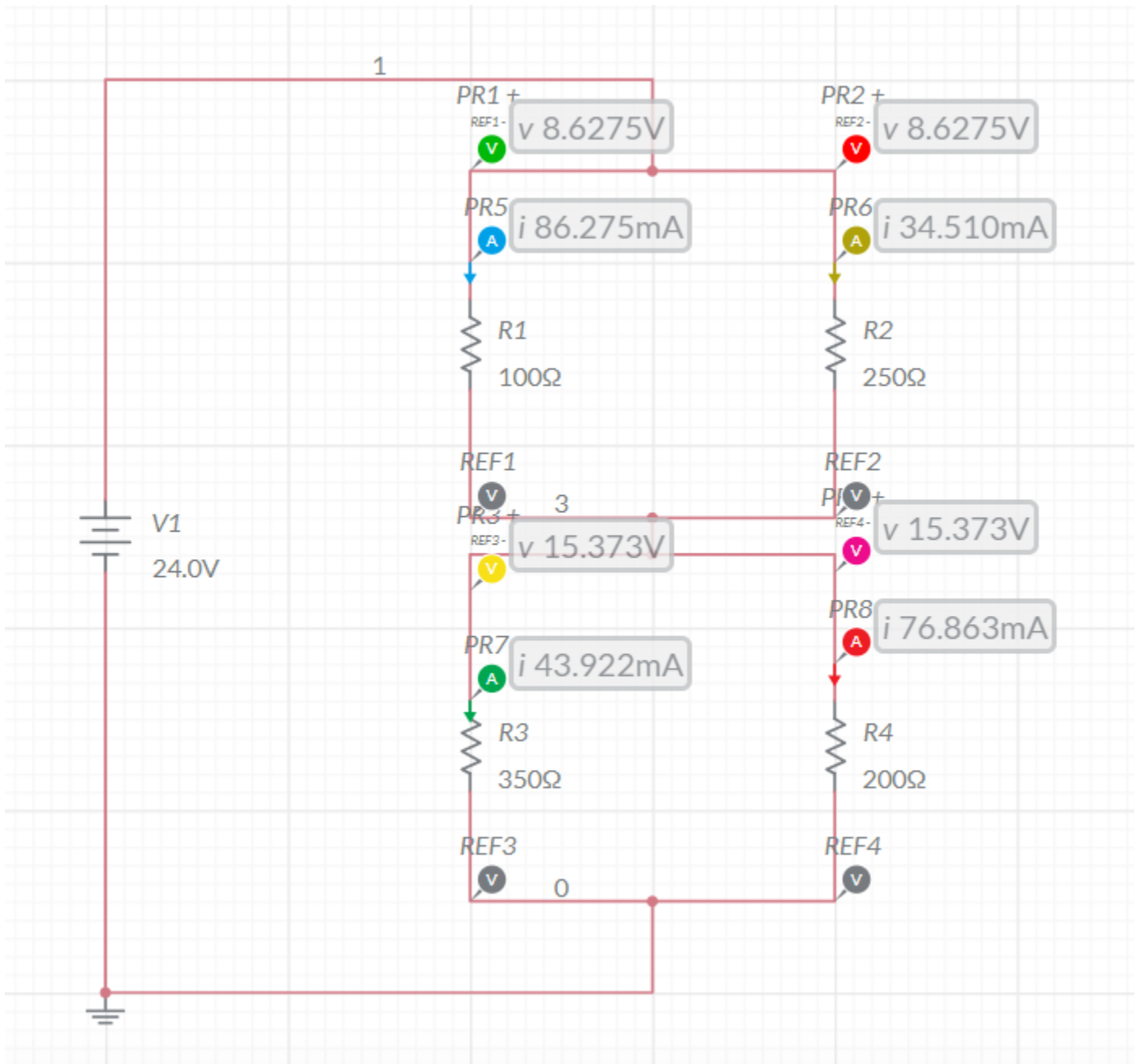
# Assignment -1

a.) Implement the circuit as shown in Figure in Multisim online.



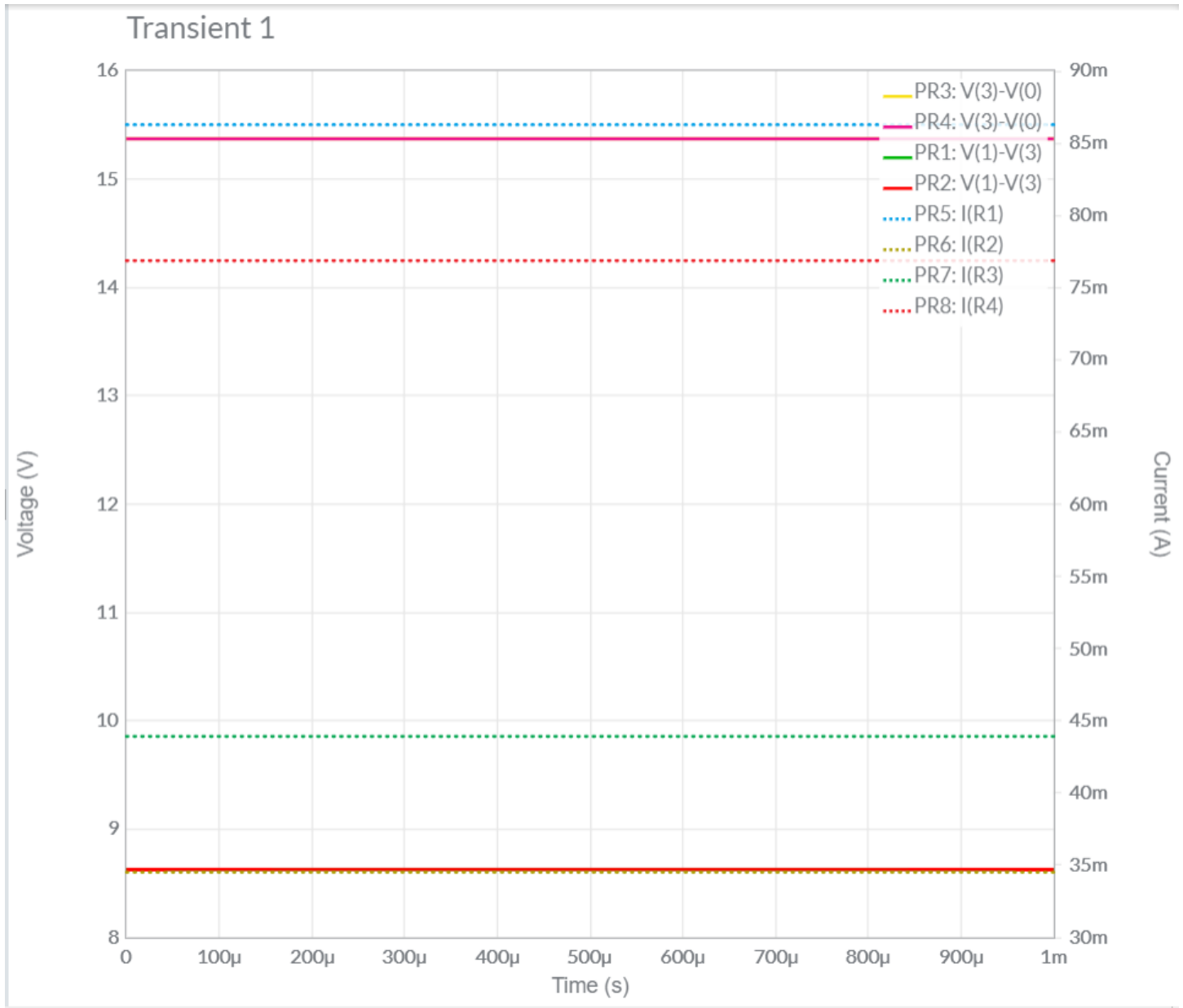b.) Evaluate the current and voltage across each resistor using simulator.



### DC OP 1


Signal	Value
PR3: V(3)-V(0)	15.373V
PR4: V(3)-V(0)	15.373V
PR1: V(1)-V(3)	8.6275V
PR2: V(1)-V(3)	8.6275V
PR5: I(R1)	86.275mA
PR6: I(R2)	34.510mA
PR7: I(R3)	43.922mA
PR8: I(R4)	76.863mA

c.) Compare with theoretical values.

# ASSIGNMENT - 1

(UI9CS012)

①

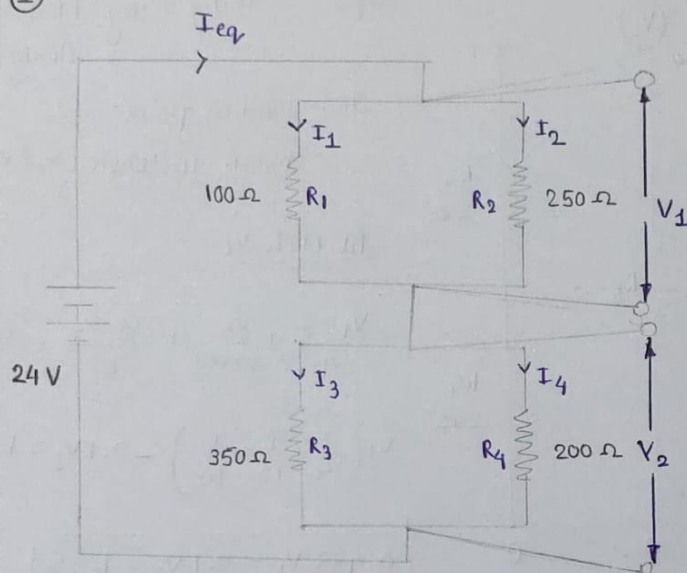

$$\text{Step 1: } R_{eq} = \left( \frac{R_1 \times R_2}{R_1 + R_2} \right) + \left( \frac{R_3 \times R_4}{R_3 + R_4} \right) \Omega$$

$$R_{eq} = \left( \frac{250 \times 100}{350} + \frac{350 \times 200}{550} \right) \Omega$$

$$= 71.4286 + 127.27 \Omega$$

$$= 198.7013 \Omega$$

$$\approx 198.7 \Omega$$

$$\text{Step 2: } I_{eq} = \frac{V}{R_{eq}} = \frac{24V}{198.7 \Omega}$$

$$= 0.120785 A$$

$$= 120.785 mA$$

Step 3: Parallel

$$V_1 = I_1 R_1 \text{ --- (i) } \quad V_1 = I_2 R_2 \text{ --- (ii) }$$

$$\Rightarrow I_1 R_1 = I_2 R_2 \text{ --- (1) }$$

$$I_1 + I_2 = I_{eq} \text{ --- (2) }$$

Derivation (Just for info)

$$I_1 = I_{eq} - \left( \frac{I_1 R_1}{R_2} \right) \Rightarrow I_1 \left( 1 + \frac{R_1}{R_2} \right) = I_{eq} \Rightarrow \left[ I_1 = \frac{I_{eq} (R_2)}{R_1 + R_2} \right]$$

$$\text{Similarly } \left[ I_2 = \frac{I_{eq} (R_1)}{R_1 + R_2} \right]$$

$$I_1 = \frac{(I_{eq}) R_2}{(R_1 + R_2)} = \frac{(120.785) mA \times (250)}{(350)} = 86.275 mA$$

$$I_2 = \frac{(I_{eq}) R_1}{(R_1 + R_2)} = \frac{(120.785) mA \times (100)}{(350)} = 34.51 mA$$

$$V_1 = I_1 R_1 = (86.275 \times 10^{-3} A) \times (100 \Omega) = 8.6275 V$$

Similarly;

$$I_3 = \frac{(I_{eq}) R_4}{(R_3 + R_4)} = \frac{(120.785) mA \times (200)}{(550)} = 43.9218 mA \approx 43.922 mA$$

$$I_4 = \frac{(I_{eq}) R_3}{(R_3 + R_4)} = \frac{(120.785) mA \times (350)}{(550)} = 76.8632 mA$$

$$V_2 = I_3 \times R_3 = (43.922 \times 10^{-3} A) \times 350 \Omega = 15.3727 V \approx 15.373 V$$

#### *d.) Final Result and Conclusion*

Resistor	Voltage (V)		Current (mA)	
	Multism	Theoretical	Multism	Theoretical
R1	8.6275	8.6275	86.275	86.275
R2	8.6275	8.6275	34.51	34.51
R3	15.373	15.373	43.922	43.922
R4	15.373	15.373	76.863	76.8632


#### *Conclusion:*

We can observe from Above Table, Both the *Theoretical* and *Multisim* Values of Current and Voltage are **Equal**.


Hence, Experiment is Performed Successfully (without any Error).
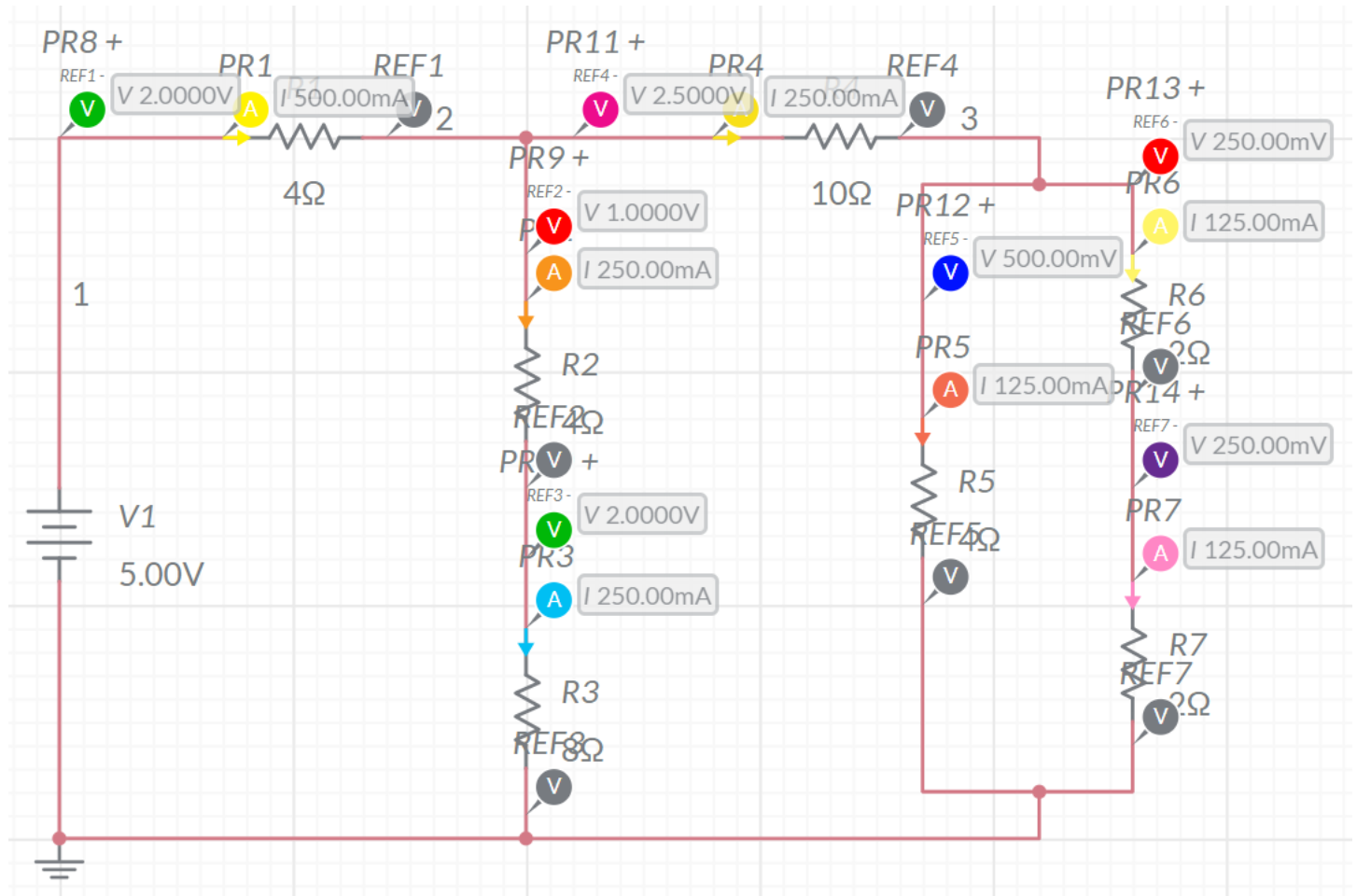
## Assignment -2

a.) Implement the circuit as shown in Figure in Multisim online.



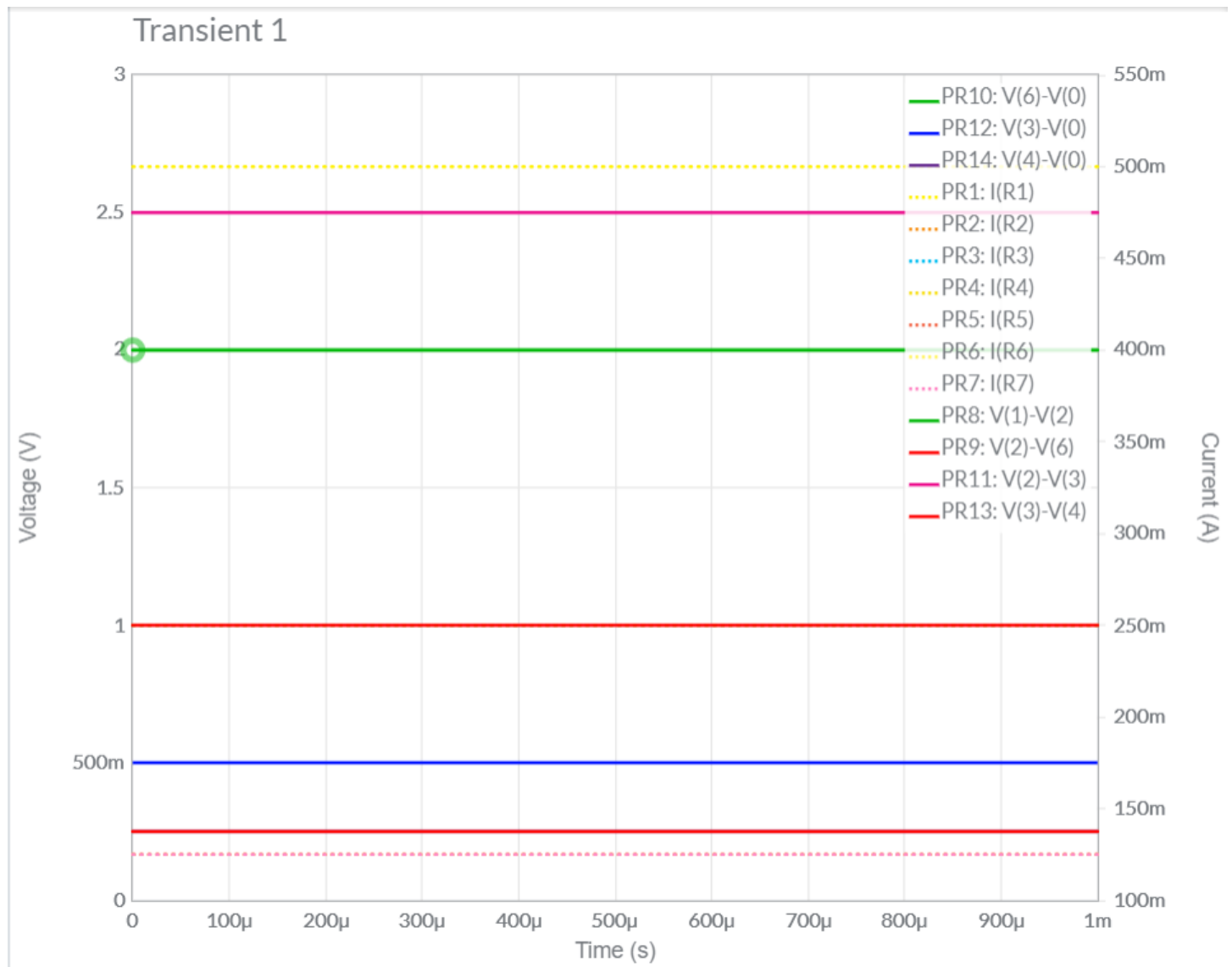b.) Evaluate the current and voltage across each resistor using simulator.



### DC OP 1


Signal	Value
PR10: V(6)-V(0)	2.0000V
PR12: V(3)-V(0)	500.00mV
PR14: V(4)-V(0)	250.00mV
PR1: I(R1)	500.00mA
PR2: I(R2)	250.00mA
PR3: I(R3)	250.00mA
PR4: I(R4)	250.00mA
PR5: I(R5)	125.00mA
PR6: I(R6)	125.00mA
PR7: I(R7)	125.00mA
PR8: V(1)-V(2)	2.0000V
PR9: V(2)-V(6)	1.0000V
PR11: V(2)-V(3)	2.5000V
PR13: V(3)-V(4)	250.00mV



c.) Compare with theoretical values.

## ASSIGNMENT - 2

(U19CS012)

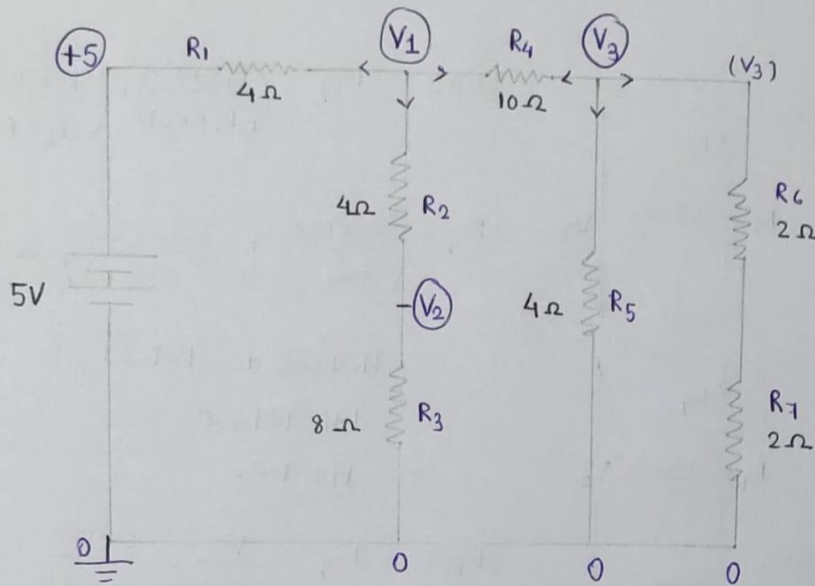

Step 1: Solving using Node Analysis

Two Junction points as shown in figure ( $V_1$  &  $V_3$ )

At Node  $V_1$

$$\frac{V_1 - 5}{4} + \frac{V_1}{4+8} + \frac{V_1 - V_3}{10} = 0$$

$$V_1 \left( \frac{1}{4} + \frac{1}{12} + \frac{1}{10} \right) - 0.1 V_3 = 1.25$$

$$0.433 V_1 - 0.1 V_3 = 1.25 \quad \text{Eqn (1)}$$

Step 2: At Node  $V_3$ :

$$\frac{V_3 - V_1}{10} + \frac{V_3}{4} + \frac{V_3}{2+2} = 0$$

$$V_3 (0.6) - 0.1 V_1 = 0$$

$$V_1 = 6 V_3 \quad \rightarrow \text{Eqn (2)}$$

$$V_3 (0.433 \times 6 - 0.1) = 1.25$$

$$V_3 = 0.5004 \text{ V}$$

$$V_3 \approx 0.5 \text{ V}$$

$$V_1 = 3 \text{ V}$$

Across Resistor	Voltage (volt)	Current
$R_1$	$5 - V_1 = \boxed{2 \text{ V}}$	$I_{R_1} = \frac{V_{R_1}}{(R_1)} = \frac{2 \text{ V}}{4 \Omega} = 0.5 \text{ A} = \boxed{500 \text{ mA}}$
$R_2$	$V_{R_2} = I_{R_2} \times R_2 = (0.25 \text{ A}) \times 4 \Omega = \boxed{1 \text{ V}}$	$I_{R_2} = \frac{V_1}{(R_2 + R_3)} = \frac{3}{12} = 0.25 \text{ A} = \boxed{250 \text{ mA}}$
$R_3$	$V_{R_3} = I_{R_3} \times R_3 = 0.25 \times 8 \Omega = \boxed{2 \text{ V}}$	$I_{R_3} = I_{R_2} = 0.25 \text{ A} = \boxed{250 \text{ mA}}$
$R_4$	$V_{R_4} = V_1 - V_3 = \boxed{2.5 \text{ V}}$	$I_{R_4} = \frac{V_{R_4}}{R_4} = \frac{2.5 \text{ V}}{10 \Omega} = \boxed{250 \text{ mA}} = 0.25 \text{ A}$
$R_5$	$V_{R_5} = V_3 = \boxed{0.5 \text{ V}}$	$I_{R_5} = \frac{V_{R_5}}{R_5} = \frac{0.5}{4} = 0.125 \text{ A} = \boxed{125 \text{ mA}}$
$R_6$	$V_{R_6} = I_{R_6} \times R_6 = \boxed{0.25 \text{ V}}$	$I_{R_6} = \frac{V_3}{(R_6 + R_7)} = \frac{0.5}{4} = \boxed{125 \text{ mA}}$
$R_7$	$V_{R_7} = I_{R_7} \times R_7 = \boxed{0.25 \text{ V}}$	$I_{R_7} = I_{R_6} = \boxed{125 \text{ mA}}$



#### *d.) Final Result and Conclusion*

Resistor	Voltage (V)		Current (mA)	
	Multism	Theoretical	Multism	Theoretical
R1	2	2	500	500
R2	1	1	250	250
R3	2	2	250	250
R4	2.5	2.5	250	250
R5	0.5	0.5	125	125
R6	0.25	0.25	125	125
R7	0.25	0.25	125	125

#### *Conclusion:*

We can observe from Above Table, Both the *Theoretical* and *Multisim* Values of Current and Voltage are **Equal**.

Hence, Experiment is Performed Successfully (without any Error).

Submitted By:  
Roll Number: U19CS012 (D-12)  
Name: Bhagya Rana