
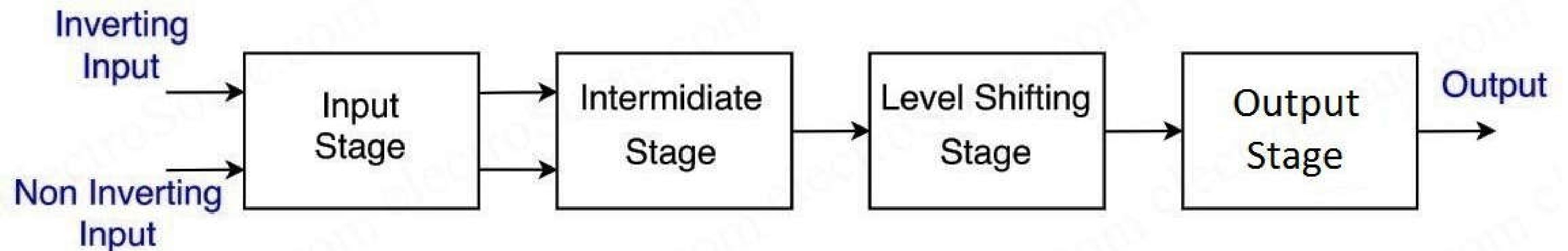


Opamp



Opamp Block Diagram

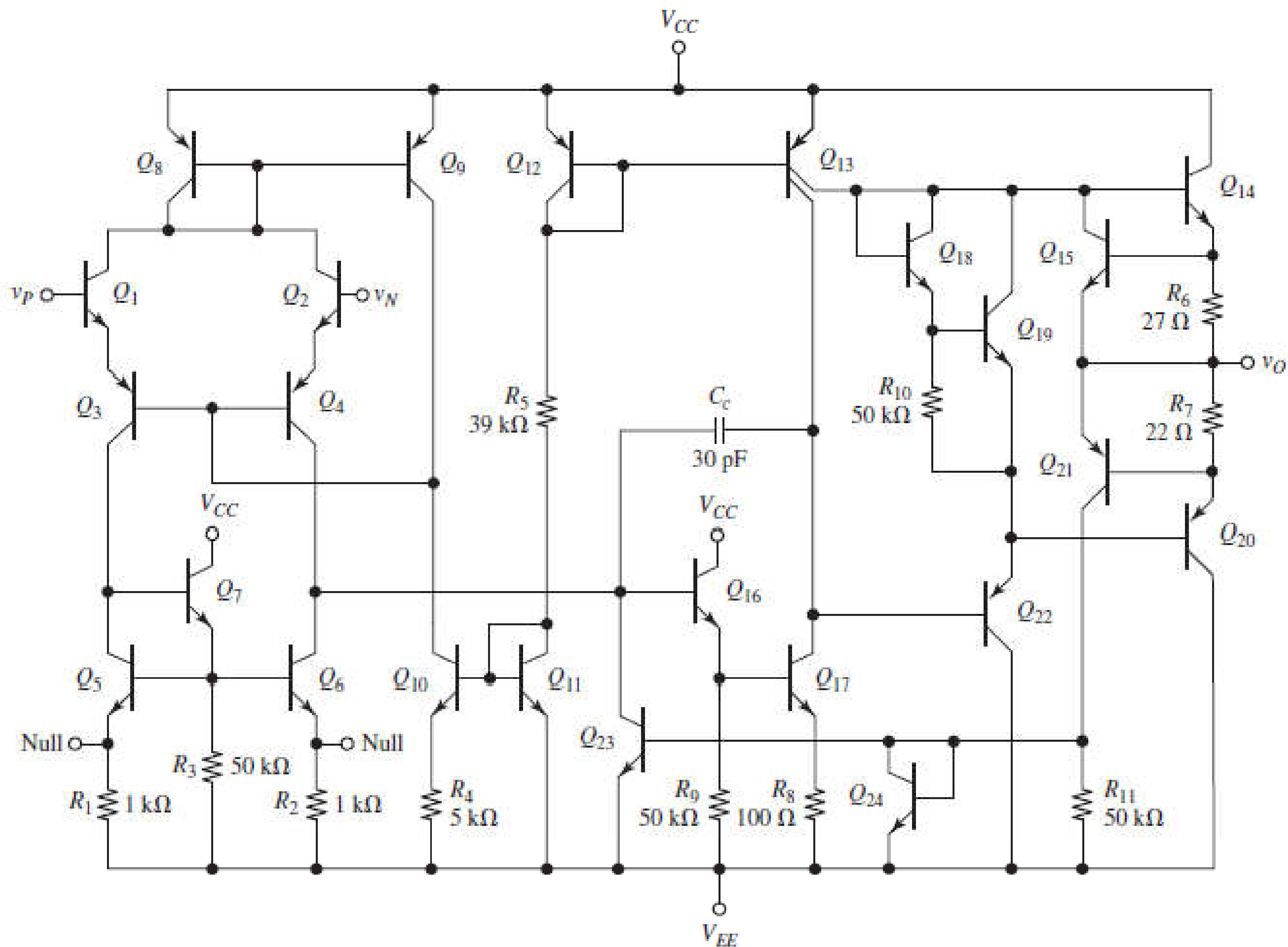


- An op amp is an active circuit element designed to perform mathematical operations of addition, subtraction, multiplication, division, differentiation, and integration, etc.



741 Package and Pin Details

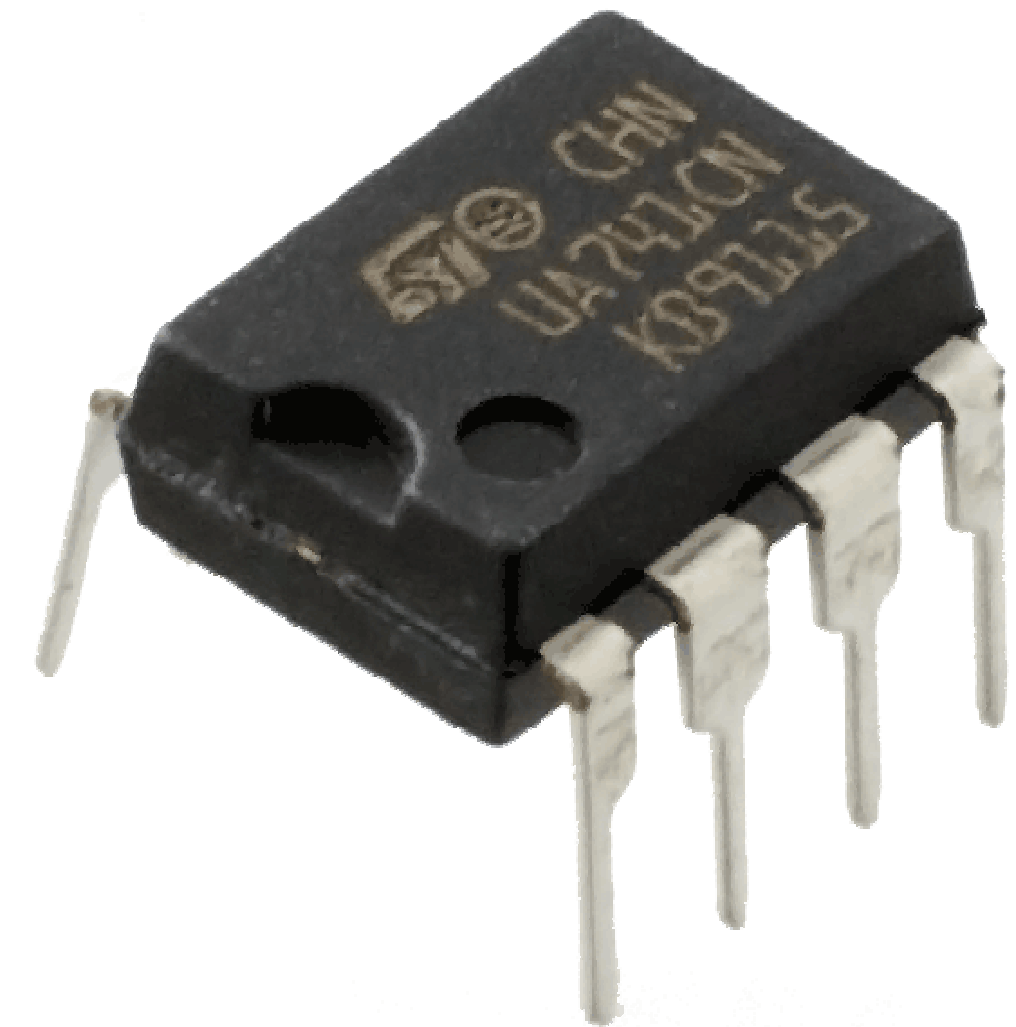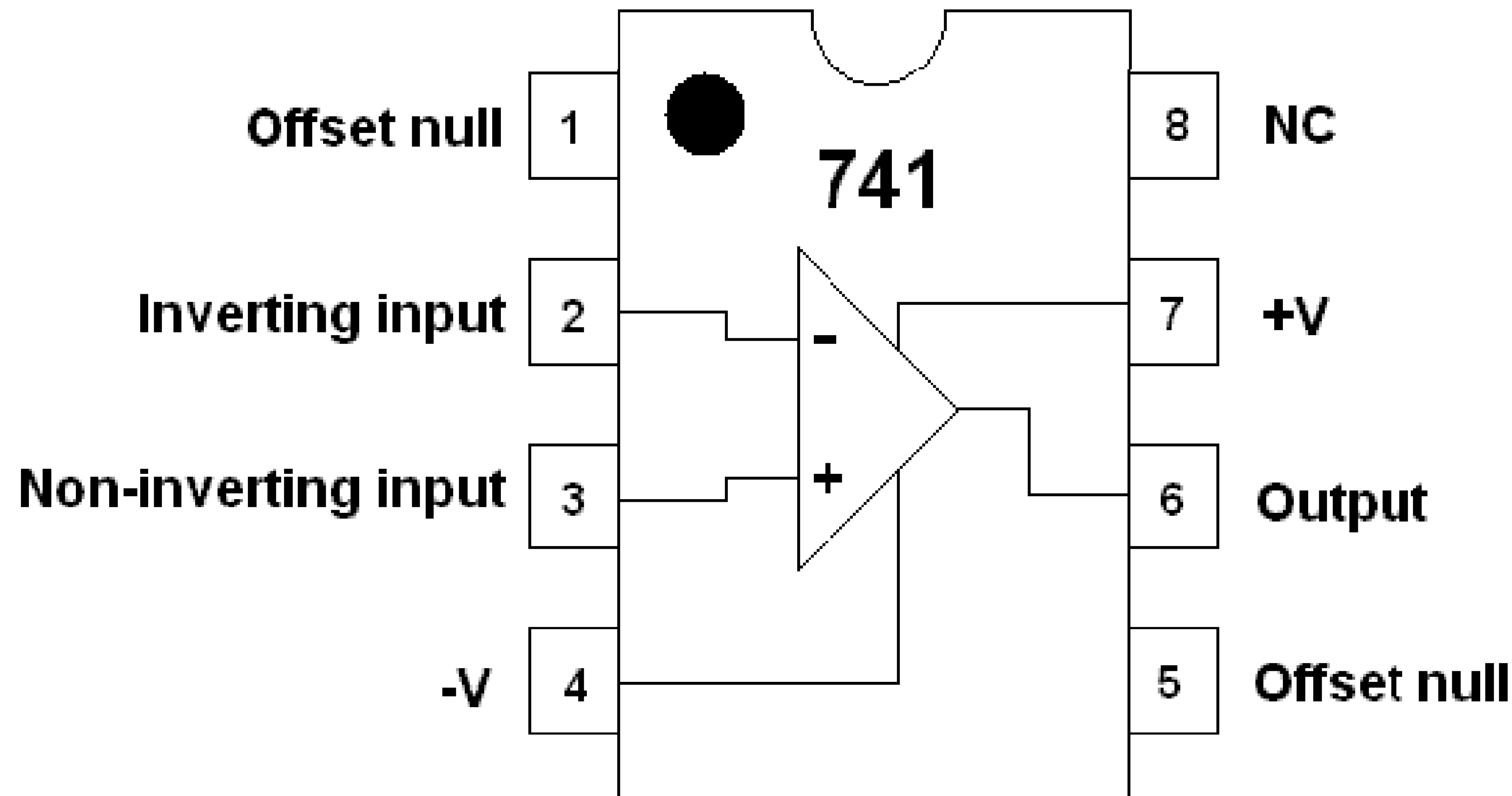

Schematic Symbol

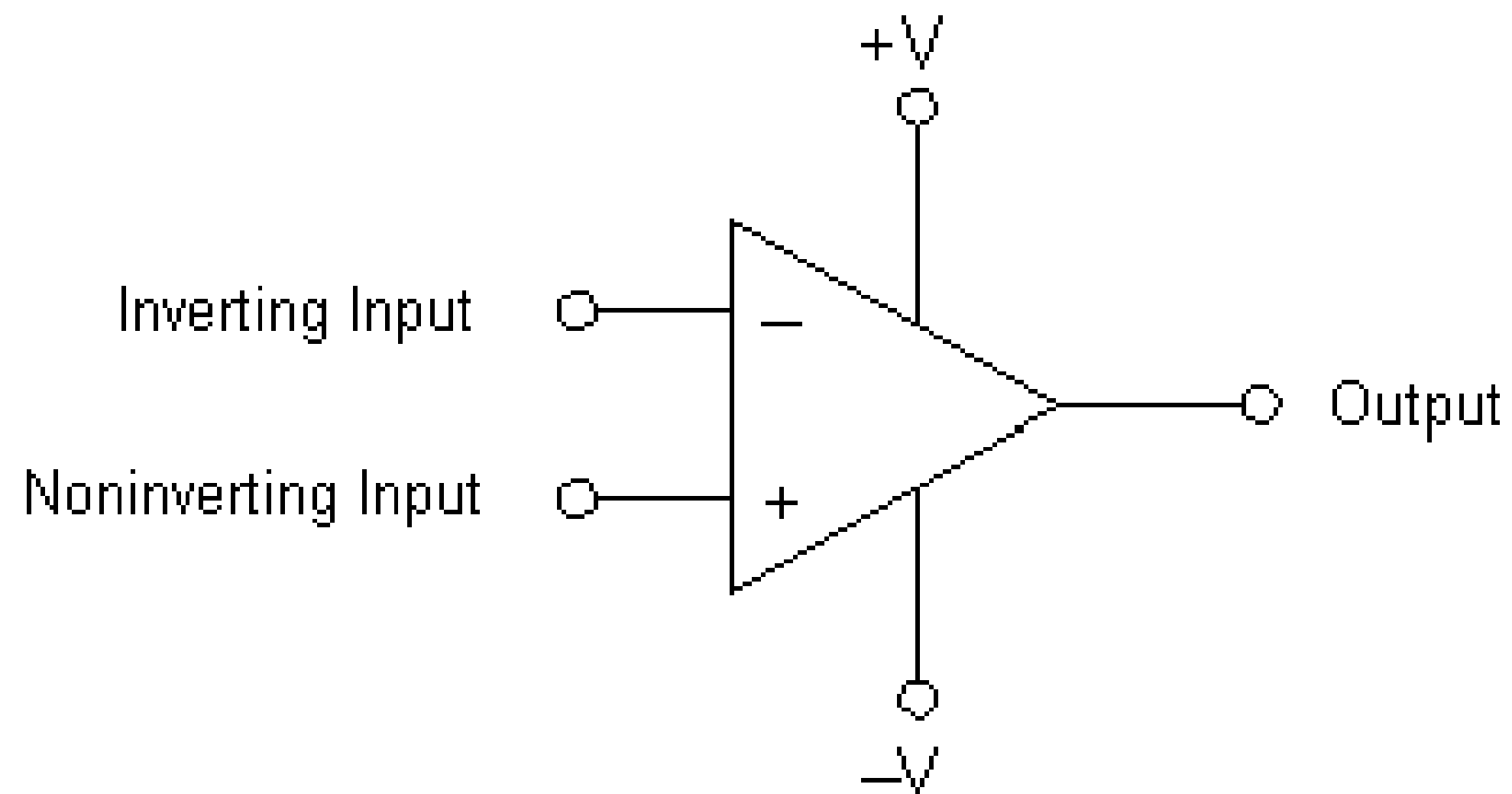


An Ideal Op-Amp

- Infinite open loop gain
- Infinite input impedance
- Zero output impedance
- Infinite bandwidth
- Infinite CMRR

Ideal versus Real Op-Amp

Parameter	Ideal Op-Amp	Real Op-Amp
Differential Voltage Gain	∞	$10^5 - 10^9$
Gain Bandwidth Product (Hz)	∞	1-20 MHz
Input Resistance (R)	∞	$10^6 - 10^{12} \Omega$
Output Resistance (R)	0	100 - 1000 Ω

Equivalent Circuit Non – Ideal Opamp

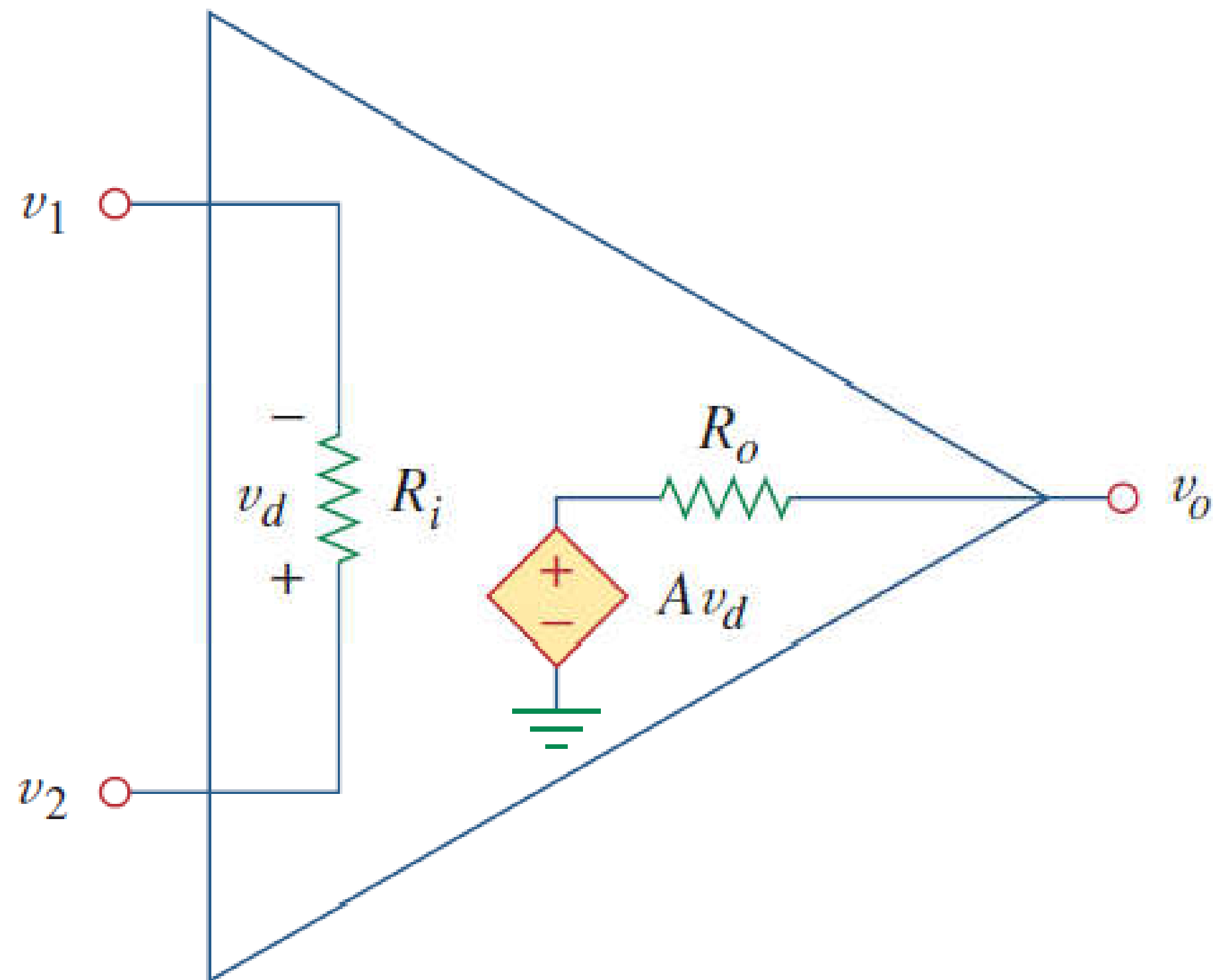

Basics of an Op-Amp Circuit


- An op-amp amplifies the difference of the inputs V_+ and V_- (known as the differential input voltage)
- This is the equation for an *open loop* gain amplifier:

$$V_{\text{out}} = A(V_+ - V_-)$$


- K is typically very large – at around 10,000 or more for IC Op-Amps
- This equation is the basis for all the types of amps we will be discussing

Open Loop vs Closed Loop

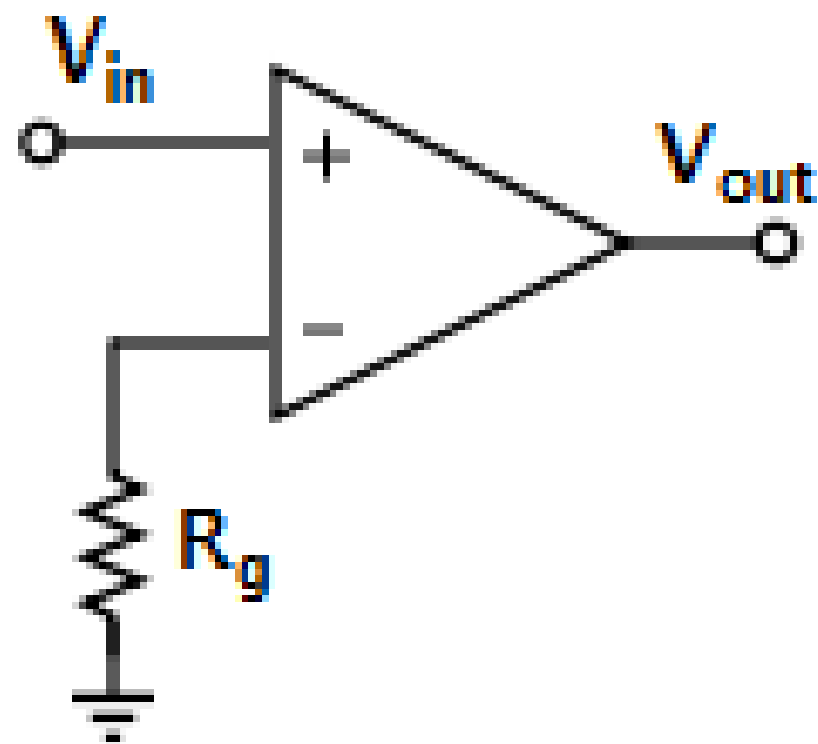- A closed loop op-amp has feedback from the output to the input, an open loop op-amp does not



Open Loop

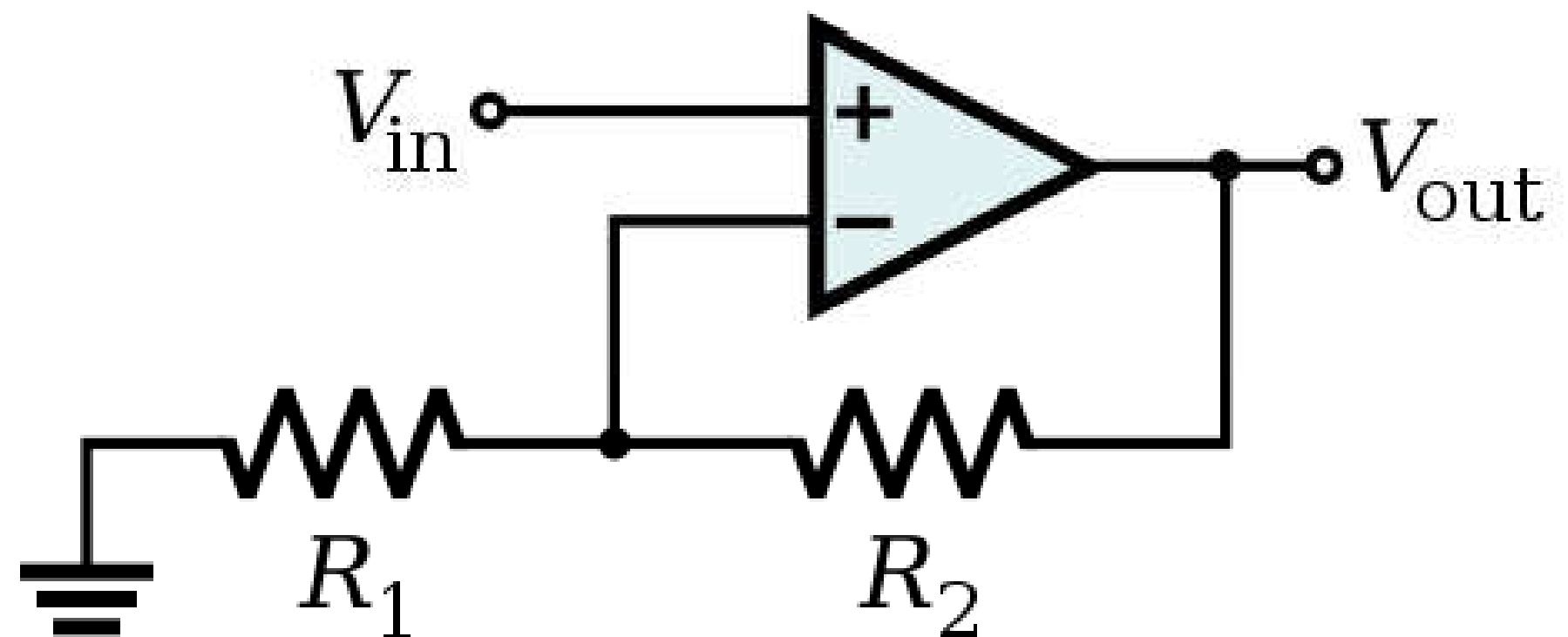


Closed Loop

Analysis Steps

- **Ideal Opamp**


- Opamp does not accept any input current
- Voltage at inverting Terminal = Voltage at non-inverting terminal.
- Apply KCL at the input nodes.
- No KCL at the output nodes (Reason ?)

KCL

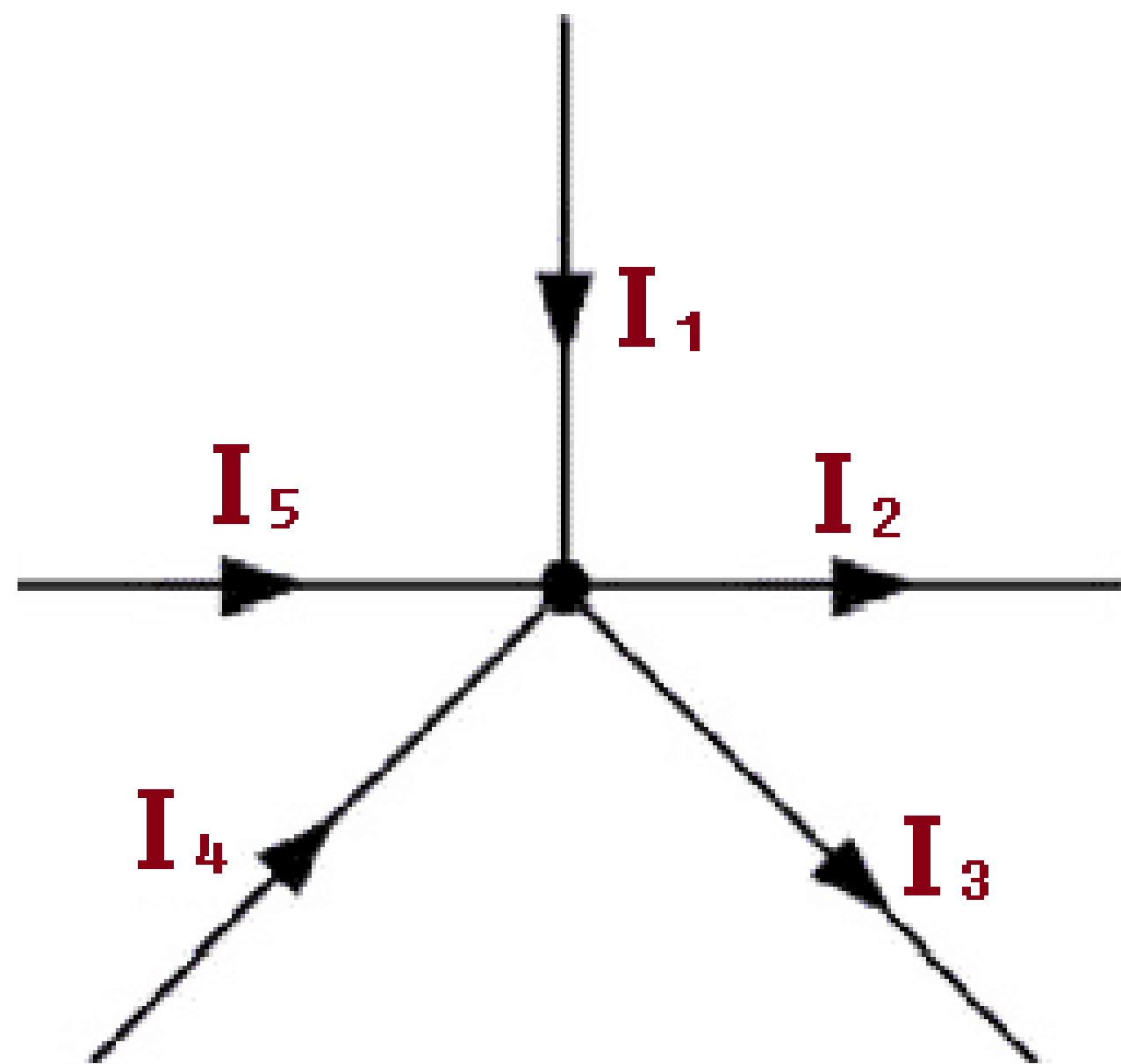

$$I_1 - I_2 - I_3 + I_4 + I_5 = 0$$

(a)

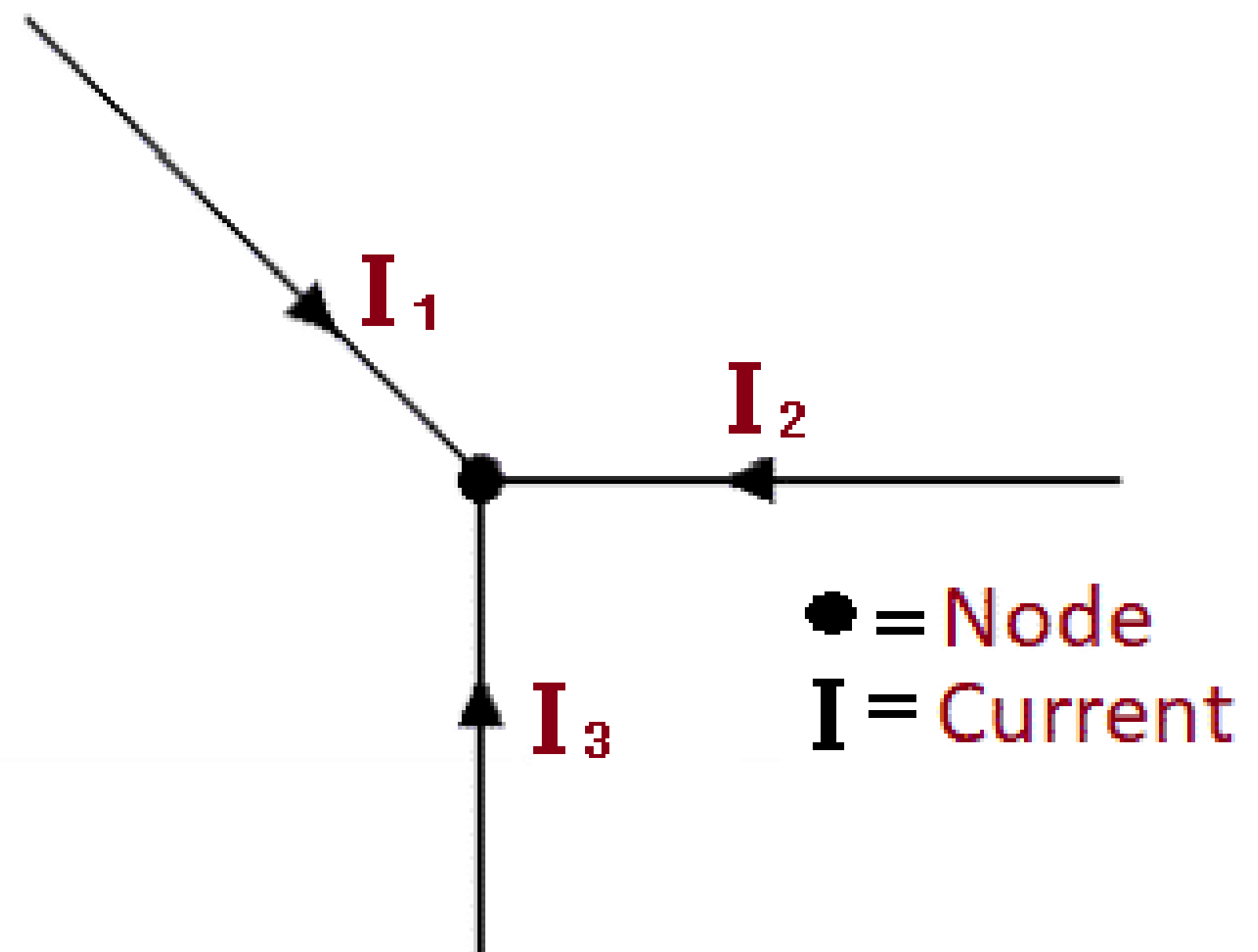


● = Node
 I = Current

$$I_1 + I_2 + I_3 = 0$$


(b)

KVL

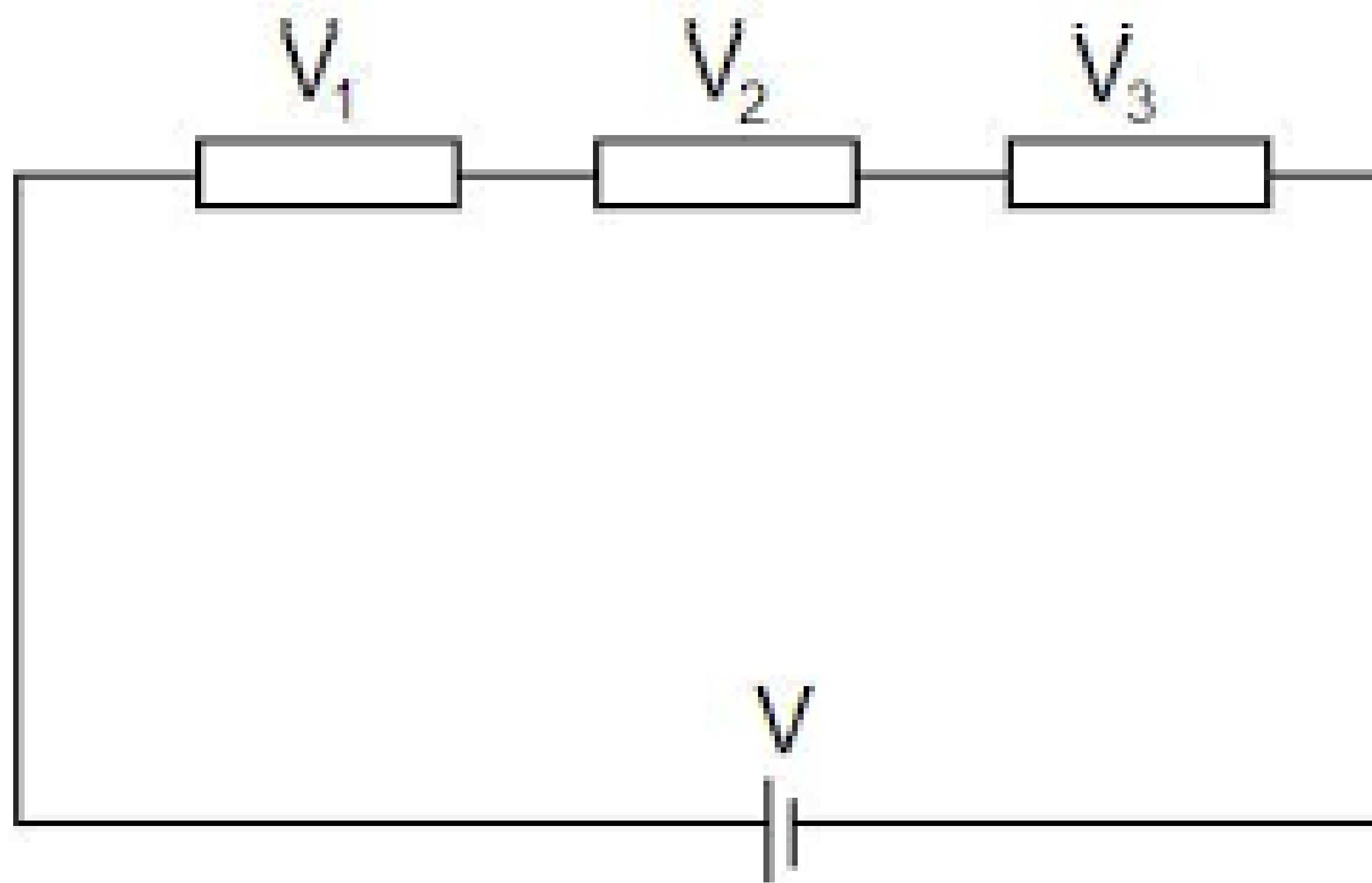


$$V = V_1 + V_2 + V_3$$

Current Division & Voltage Division

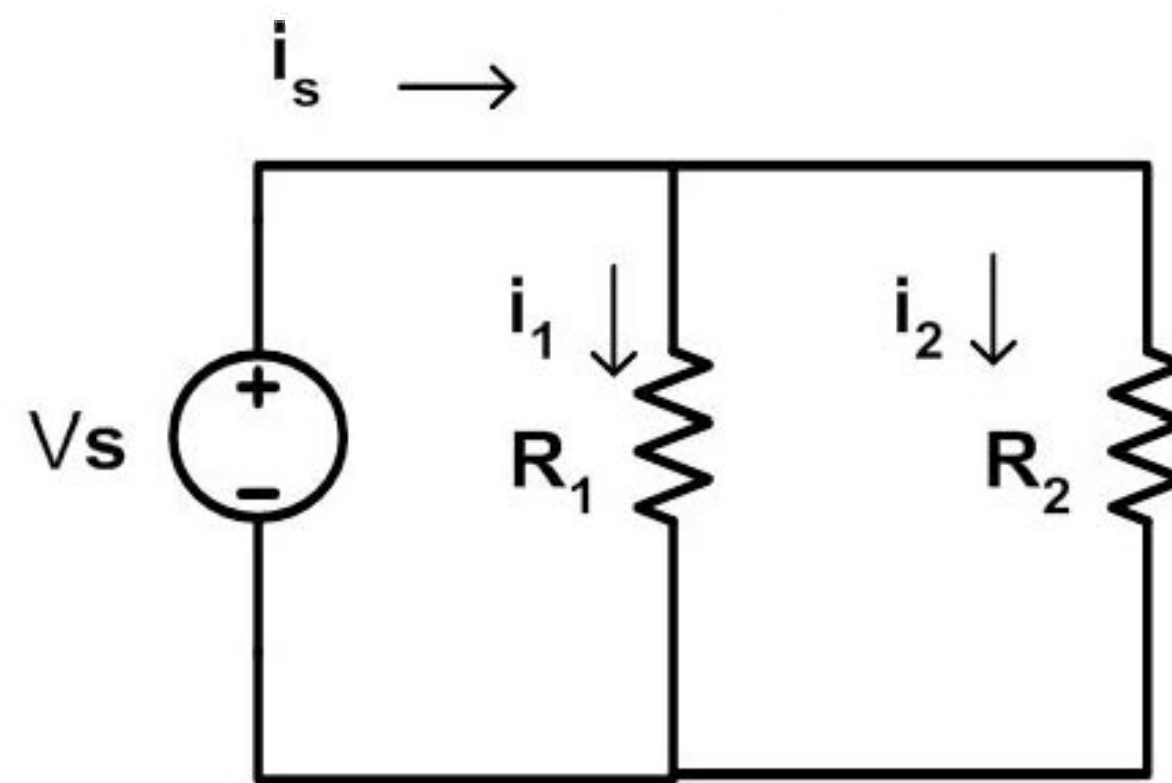

$$i_1 = \frac{R_2}{R_1 + R_2} i_s$$


$$i_2 = \frac{R_1}{R_1 + R_2} i_s$$

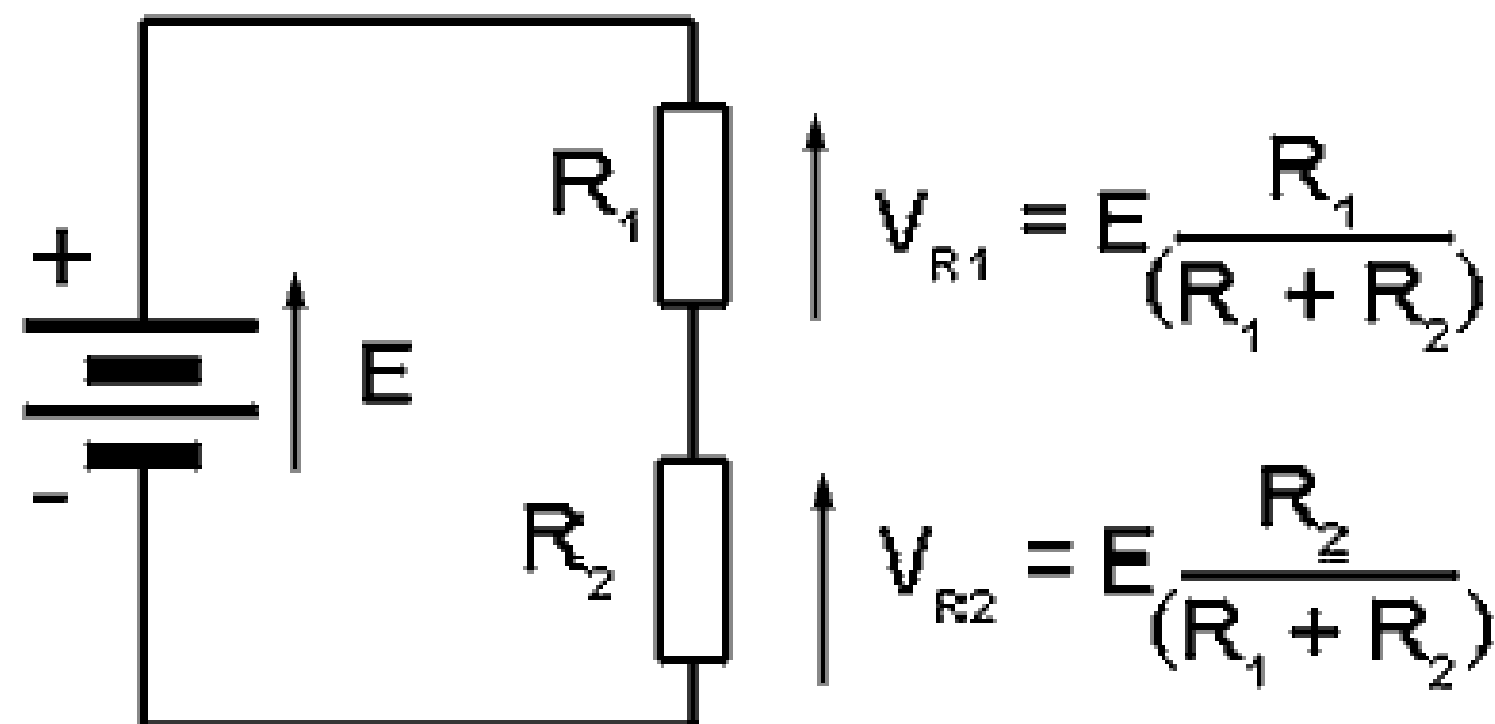

$$V_{R1} = E \frac{R_1}{R_1 + R_2}$$

$$V_{R2} = E \frac{R_2}{R_1 + R_2}$$

Inverting Amplifier

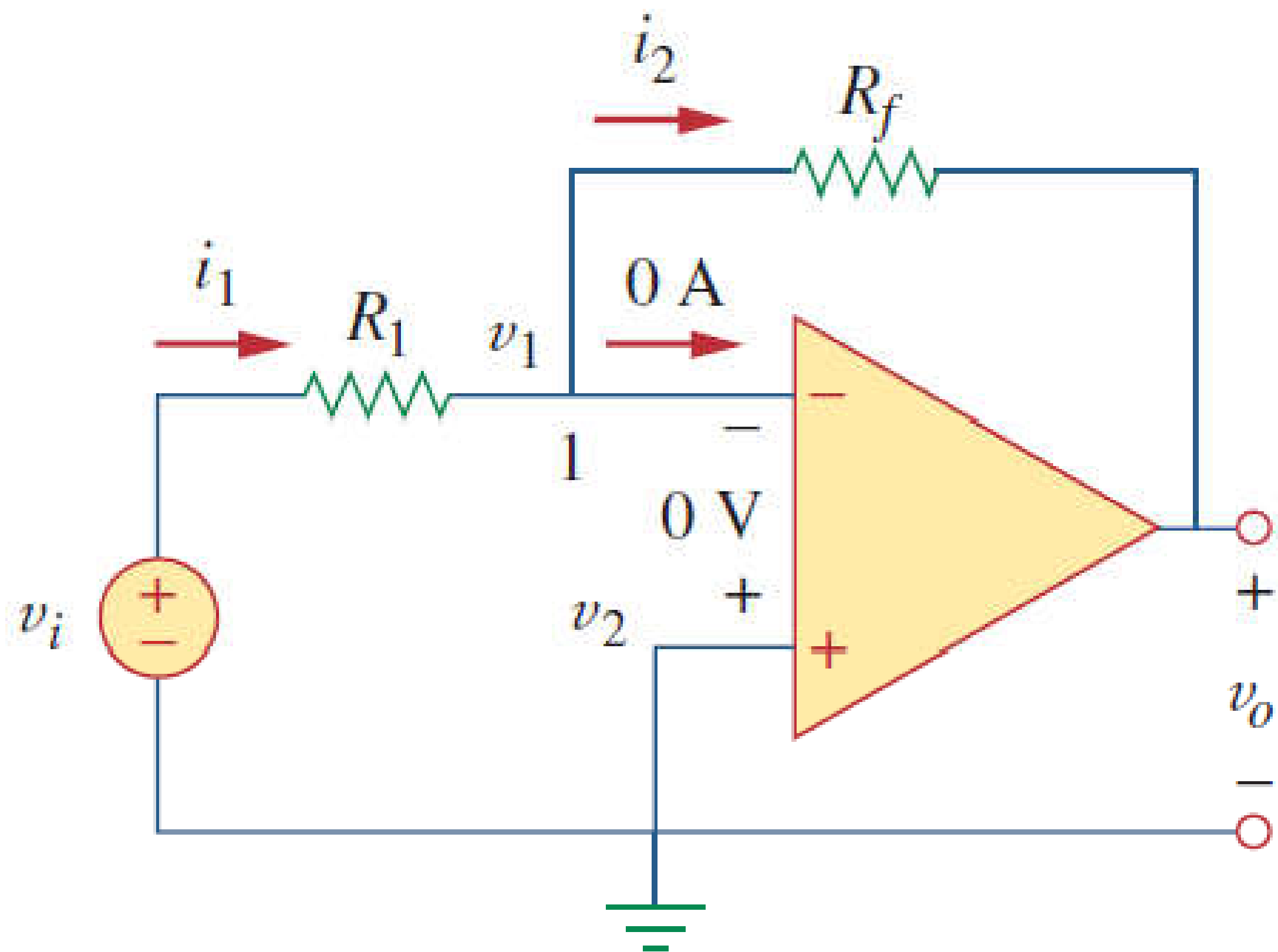

Gain Equation

$$i_1 = i_2 \Rightarrow \frac{v_i - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$

$$v_o = -\frac{R_f}{R_1} v_i$$



To Be Continued...